ALTERNATING CURRENT

Ш.

1. AC AND DC CURRENT :

A current that changes its direction periodically is called alternating current (AC). If a current maintains its direction constant it is called direct current (DC).



If a function suppose current, varies with time as $i = I_m sin (\omega t + \varphi)$, it is called sinusoidally varying function. Here I_m is the peak current or maximum current and i is the instantaneous current. The factor ($\omega t + \varphi$) is called phase. ω is called the angular frequency, its unit rad/s. Also $\omega = 2\pi f$ where f is called the frequency, its unit s⁻¹ or Hz. Also frequency f = 1/T where T is called the time period.

2. AVERAGE VALUE :

Average value of a function, from t₁ to t₂, is defined as $<f> = \frac{t_1}{t_2 - t_1}$. We can find the value of t_1 graphically if the graph is simple. It is the area of f-t graph from t₁ to t₂.

fdt

Example 1. Find the average value of current shown graphically, from t = 0 to t = 2 sec.



Solution : From the i – t graph, area from t = 0 to t = 2 sec = $2 \times 2 \times 10 = 10$ Amp. sec. $\frac{10}{2}$

Average Current = 2 = 5 Amp.

2π

Example 2. Find the average value of current from t = 0 to $t = \omega$ if the current varies as $i = I_m \sin \omega t$.



Example 3. Show graphically that the average of sinusoidally varying current in half cycle may or may not be zero.



Alternating Current,

$$= \sqrt{4+4+2\times 2\times 2\left(-\right)}$$

1 2

= 2, so effective value or rms value = $2/\sqrt{2} = \sqrt{2}$ A

H-

4.

AC SINUSOIDAL SOURCE :

Figure shows a coil rotating in a magnetic field. The flux in the coil changes as ϕ = NBA cos (ω t + ϕ).

-dφ

Emf induced in the coil, from Faraday's law is $dt = N B A \omega \sin(\omega t + \phi)$. Thus the emf between the points A and B will vary as $E = E_0 \sin(\omega t + \phi)$. The potential difference between the points A and B will also vary as $V = V_0 \sin(\omega t + \phi)$. The symbolic notation of the above arrangement is $A = B^{-1} \otimes B^{-1}$. We do not put any + or – sign on the AC source.



5. POWER CONSUMED OR SUPPLIED IN AN AC CIRCUIT:

Consider an electrical device which may be a source, a capacitor, a resistor, an inductor or any combination of these. Let the potential difference be $V = V_A - V_B = V_m \sin \omega t$. Let the current through it be $i = I_m \sin(\omega t + \varphi)$. Instantaneous power P consumed by the device = V i = (V_m sin ωt) ($I_m sin(\omega t + \varphi)$)

$$A \stackrel{i}{\longrightarrow} B$$

$$\frac{2\pi}{\overset{\circ}{\oplus}} Pdt$$

$$\frac{2\pi}{\overset{\circ}{\oplus}} = V_m I_m \cos \phi = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \cdot \cos \phi = V_{rms} I_{rms} \cos \phi.$$

Average power consumed in a cycle = $\omega = V_m I_m \cos \phi = \sqrt{2}$. $\sqrt{2}$. $\cos \phi = V_{rms} I_{rms}$. Here $\cos \phi$ is called **power factor**.

Note : $Isin\phi$ is called "wattless current".

$$\begin{array}{c}
Icos\phi \\
\downarrow \phi \\
Isin\phi
\end{array}$$

5.1 POWER FACTOR

so

:.

• The factor $\cos \phi$ present in the relation for average power of an ac circuit is called power factor

$$\cos \phi = \frac{P_{ac}}{E_{rms}I_{rms}} = \frac{P_{av}}{P_{v}}$$

Thus, ratio of average power and virtual power in the circuit is equal to power factor.

Power factor is also equal to the ratio of the resistance and the impedance of the ac circuit.

Thus, $\cos \phi = \frac{R}{Z}$

- Power factor depends upon the nature of the components used in the circuit.
- If a pure resistor is connected in the ac circuit then

$$\phi = 0, \cos \phi = 1$$

$$P_{av} = \frac{E_0 I_0}{2} = \frac{E_0^2}{2R} = E_{rms} I_{rms}$$

Alternating Current

Thus the power loss is maximum and electrical energy is converted in the form of heat.

• If a pure inductor or a capacitor are connected in the ac circuit, then

 $\phi = \pm 90^{\circ}, \cos \phi = 0$

 \therefore P_{av} = 0 (minimum)

Thus there is no loss of power.

If a resistor and an inductor or a capacitor are connected in an ac circuit, then $\phi \neq 0$ or $\pm 90^{\circ}$

Thus ϕ is in between 0 & 90°.

• If the components L, C and R are connected in series in an ac circuit, then

$$\tan\phi = \frac{X}{R} = \frac{(\omega L - 1/\omega C)}{R}$$

and
$$\cos \phi = \frac{R}{Z} = \frac{R^2 + (\omega L - 1/\omega C)^2}{[R^2 + (\omega L - 1/\omega C)^2]^{1/2}}$$

- \therefore Power factor $\cos \phi = \overline{Z}$
- Power factor is a unitless quantity .
- If there is only inductance coil in the circuit, there will be no loss of power and energy will be stored in the magnetic field.
- If a capacitor is only connected in the crcuit, even then there will be no loss of power and energy will be stored in the electrostatic field.
- In reality an inductor and a capacitor do have some resistance, so there is always some loss of power.
- In the state of resonance the power factor is one.

Example 8. When a voltage $v_s = 200\sqrt{2} \sin(\omega t + 15^\circ)$ is applied to an AC circuit the current in the circuit is found to be i = 2 sin ($\omega t + \pi/4$) then average power consumed in the circuit is

(A) 200 watt (B) $400\sqrt{2}$ watt (C) $100\sqrt{6}$ watt (D) $200\sqrt{2}$ watt Solution : $P_{av} = v_{rms} I_{rms} \cos \phi = \frac{200\sqrt{2}}{\sqrt{2}} \cdot \frac{2}{\sqrt{2}} \cos (30^{\circ}) = 100\sqrt{6}$ watt

6. SOME DEFINITIONS :

The factor $\cos \phi$ is called Power factor. I_m sin ϕ is called wattless current.

$$\frac{V_m}{V_m}$$

Impedance Z is defined as $Z = I_m = I_{rms}$

 ωL is called inductive reactance and is denoted by X_L ${}^{ \omega C}$ is called capacitive reactance and is denoted by $X_C.$

7. PHASOR DIAGRAM

It is a diagram in which AC voltages and current are represented by rotating vectors. The phasor represented by a vector of magnitude proportional to the peak value rotate counter clockwise with an angular frequency ω about the origin. The projection of the phasor on vertical axis gives the instantaneous value of the alternating quantity involved. For fig.



$$\begin{split} \mathsf{E} &= \mathsf{E}_0 \sin \, \omega t \\ \mathsf{I} &= \mathsf{I}_0 \sin \, (\omega t - \pi/2) \\ &= -\mathsf{I}_0 \cos \omega t \end{split}$$

9.

8. PURELY RESISTIVE CIRCUIT:

Writing KVL along the circuit, $= V_m \sin \omega t$ $V_s - iR = 0$ $V_s = V_m \sin \omega t$ i = R = R = Im sin ωt or R We see that the phase difference between potential difference across resistance, V_R and i_R is 0. ⇒ V_{rms}^{2} V_{rms} V_m R R R ; $\langle P \rangle = V_{rms} I_{rms} \cos \varphi =$ $I_m =$ Irms = Graphical and vector representations of E and I are shown below : Е or E I **PURELY CAPACITIVE CIRCUIT:** V_s = V_m sin ωt Writing KVL along the circuit, V_s – C = 0 $d(CV_m \sin \omega t)$ dq d(CV) or i = dt =dt _ dt = $CV_m\omega \cos \omega t = \frac{\sqrt{m}}{1/\omega C} \cos \omega t = \frac{\sqrt{m}}{X_C} \cos \omega t = I_m \cos \omega t.$ 1 $X_{C} = \omega C$ and is called capacitive reactance. Its unit is ohm Ω . From the graph of current versus time and voltage versus time Т $\overline{4}$, it is clear that current attains its peak value at a time before the time at which voltage attains its peak value. Corresponding

to $\overline{4}$ the phase difference

 $= \omega \Delta t = \frac{2\pi}{T} \frac{T}{4} = \frac{2\pi}{4} = \frac{\pi}{2}$, ic leads vc by $\pi/2$ Diagrammatically (phasor diagram) it is represented as V_m

Since $\phi = 90^{\circ}$, $< P > = V_{rms} I_{rms} \cos \phi = 0$.

The graphical and vector representations of E and I are shown in the following figures :



Solved Examples-

Example 9. An alternating voltage $E = 200\sqrt{2}$ sin (100 t) V is connected to a 1µF capacitor through an ac ammeter (it reads rms value). What will be the reading of the ammeter?

Solution : Comparing E = $200\sqrt{2}$ sin (100 t) with E = E₀ sin ω t we find that,

$$E_0 = 200 \sqrt{2} V$$
 and $\omega = 100$ (rad/s)
 $X_c = \frac{1}{100} = \frac{1}{100 \times 10^{-6}} = 10^4 \Omega$

$$S_{0}$$
, we not see the second second second the second s

And as ac instruments reads rms value, the reading of ammeter will be,

$$I_{rms} = \frac{E_{rms}}{X_c} = \frac{E_0}{\sqrt{2}X_c} \left[as \quad E_{rms} = \frac{E_0}{\sqrt{2}} \right] \quad i.e., \quad I_{rms} = \frac{200\sqrt{2}}{\sqrt{2} \times 10^4} = 20 \text{mA}$$

\square

10. PURELY INDUCTIVE CIRCUIT:

Writing KVL along the circuit,

$$V_{s} - L \frac{di}{dt} = 0 \qquad \Rightarrow L = \frac{di}{dt} V_{m} \sin \omega t$$

$$\int L di = \int V_{m} \sin \omega t \, dt \Rightarrow i = -\frac{V_{m}}{\omega L} \cos \omega t + C$$

$$< i > = 0 \qquad C = 0$$

$$\therefore i = -\frac{V_{m}}{\omega L} \cos \omega t \Rightarrow I_{m} = \frac{V_{m}}{X_{L}}$$





From the graph of current versus time and voltage versus time $\,\,4\,$, it is clear that voltage attains its peak value at a time $\,$ before the time at

which current attains its peak value. Corresponding to $\,4\,$ the phase

difference = $\omega\Delta t = \frac{2\pi}{T} \frac{T}{4} = \frac{2\pi}{4} = \frac{\pi}{2}$.

Diagrammatically (phasor diagram) it is represented as $\downarrow I_{m}$. iL lags behind vL by $\pi/2$. Since $\phi = 90^{\circ}$, $< P > = V_{rms}I_{rms}cos \phi = 0$

Graphical and vector representations of E and I are shown in the following figures :





Summary :

Alternating Current

AC source connected with			Z	Phasor Diagram
Pure Resistor	0	V _R is in same phase with i _R	R	$\xrightarrow{\bigvee_m} I_n$
Pure Inductor	□/2	V_L leads i_L	XL	V [™] ↓ I [™]
Pure Capacitor	□/2	$V_{\rm C}$ lags i _C	Xc	↓ Vm

11. **RC SERIES CIRCUIT WITH AN AC SOURCE :**

Let $i = I_m \sin(\omega t + \phi)$ \Rightarrow V_R=iR= I_mR sin (ω t+ φ) $V_{C}=(I_{m} X_{C})sin(\omega t + \phi - \overline{2}) \Rightarrow V_{S}=V_{R} + V_{C}$ or $V_m \sin (\omega t + \phi) = I_m R \sin (\omega t + \phi) + I_m X_C \sin (\omega t + \phi - \frac{1}{2})$ $V_{m} = \sqrt{(I_{m}R)^{2} + (I_{m}X_{c})^{2} + 2(I_{m}R)(I_{m}X_{c})\cos\frac{\pi}{2}}$ $I_{m} = \frac{V_{m}}{\sqrt{R^{2} + Xc^{2}}} \Rightarrow Z = \sqrt{R^{2} + Xc^{2}}$ OR Using phasor diagram also we can find the above result. $\tan \phi = \frac{\frac{I_m X_c}{I_m R}}{\frac{I_m R}{R}} = \frac{X_c}{R} , \qquad X_c = \frac{1}{\omega c} .$ Solved Examples. In an RC series circuit, the rms voltage of source is 200V and its Example 10. 100 frequency is 50 Hz.If R =100 Ω and C= π μ F, find (i) Impedance of the circuit (ii) Power factor angle (iii) Power factor (iv) Current (v) Maximum current (vi) voltage across R (vii) voltage across C (viii) max voltage across R (ix) max voltage across C (x) < P > $(xi) < P_R >$ $(xii) < P_C >$ 10⁶ $X_{C} = \frac{100}{\pi} (2\pi 50)$ =100 Ω Solution : (i) $Z = \sqrt{R^2 + Xc^2} = \sqrt{100^2 + (100)^2} = 100\sqrt{2} \text{ or}$ (ii) $\tan \phi = \frac{R}{R} = 1$ $\therefore \phi = 45^{\circ 2}$ (iii) Power factor= $\cos \phi = \sqrt{2}$







1

7

(iv) Current I_{rms} = $\frac{V_{rms}}{Z} = \frac{200}{100\sqrt{2}} = \sqrt{2} A$ (v) Maximum current = $I_{rms}\sqrt{2}$ =2A (vi) voltage across R=V_{R,rms}=I_{rms}R= $\sqrt{2}$ ×100 Volt (vii) voltage across C=V_{C,rms}=I_{rms}X_C= $\sqrt{2}$ ×100 Volt (viii) max voltage across $R = \sqrt{2} V_{R rms} = 200$ Volt (ix) max voltage across $C = \sqrt{2} V_{C,rms} = 200 Volt$ (x) $\langle P \rangle = V_{rms} I_{rms} \cos \phi = 200 \times \sqrt{2} \times \sqrt{2} = 200 \text{ Watt}$ (xi) $\langle P_R \rangle = I_{rms}^2 R = 200 W$ $(x) < P_{C} > = 0$ In the above question if $v_s(t) = 200 \sqrt{2} \sin (2\pi 50 t)$, find (a) i (t), (b) $v_R(t)$ and (c) $v_C(t)$ Example 11. $= 2 \sin (2\pi 50 t + 45^{\circ})$ Solution : (a) $i(t) = I_m \sin(\omega t + \phi)$ (b) $V_R(t) = i_R \cdot R = i(t) R$ $= 2 \times 100 \sin (100 \pi t + 45^{\circ})$ (c) vc (t) = icXc (with a phase lag of 90°) = 2 ×100 sin (100 π t + 45 – 90) \square 12. LR SERIES CIRCUIT WITH AN AC SOURCE : $v_s = V \sin \omega t$ $V = \sqrt{(IR)^{2} + (IXL)^{2}} = I\sqrt{(R)^{2} + (XL)^{2}} = IZ \implies \tan \phi = \frac{IXL}{IR} = \frac{XL}{R}$ From the phasor diagram Solved Examples A 100π H inductor and a 12 ohm resistance are connected in series to a 225 V, 50 Hz ac source. Example 12. Calculate the current in the circuit and the phase angle between the current and the source voltage. 9 Here $X_L = \omega L = 2\pi f L = 2\pi \times 50 \times 100\pi = 9 \Omega$ Solution : So. Z = $\sqrt{R^2 + X_L^2} = \sqrt{12^2 + 9^2} = 15 \Omega$ So (a) I = $\frac{1}{Z} = \frac{15}{15} = 15 \text{ A}$ Ans. and (b) $\phi = \tan^{-1} \left(\frac{X_L}{R} \right) = \tan^{-1} \left(\frac{9}{12} \right) = \tan^{-1} 3/4 = 37^{\circ}$ i.e., the current will lag the applied voltage by 37° in phase. Ans. Example 13. When an inductor coil is connected to an ideal battery of emf 10 V, a constant current 2.5 A flows. When the same inductor coil is connected to an AC source of 10 V and 50 Hz then the current is 2A. Find out inductance of the coil . Solution : When the coil is connected to dc source, the final current is decided by the resistance of the coil 10 **r** = $\overline{2.5} = 4 \Omega$ ÷ When the coil is connected to ac source, the final current is decided by the impedance of the coil.

$$\therefore$$
 $Z = \frac{10}{2} = 5_{\Omega}$

But Z = $\sqrt{(r)^2 + (X_L)^2}$ $X_1^2 = 5^2 - 4^2 = 9$ $X_1 = 3 \Omega$ *:*. $\omega L = 2 \pi f L = 3$ ÷ $2 \pi 50 L = 3$ $L = 3/100\pi$ Henry :. Example 14. A choke coil is needed to operate an arc lamp at 160 V (rms) and 50 Hz. The arc lamp has an effective resistance of 5 Ω when running of 10 A (rms). Calculate the inductance of the choke coil. If the same arc lamp is to be operated on 160 V (dc), what additional resistance is required? Compare the power losses in both cases. Ark lamp Solution : As for lamp $V_R = IR = 10 \times 5 = 50$ V, so when it is connected to 160 V ac source through a choke in series, $V^2 = V_R^2 + V_L^2$, L $V_1 = \sqrt{160^2 - 50^2} = 152 \text{ V}$ 00000 and as, $V_L = IX_L = I\omega L = 2\pi f L I$ 152 V, So, L = $\overline{2\pi fI} = \overline{2 \times \pi \times 50 \times 10}$ $V = V_0 \sin \omega t$ = 4.84 × 10⁻² H Ans. Now the lamp is to be operated at 160 V dc; instead of choke if additional resistance r is put in series with it, V = I(R + r), i.e., 160 = 10(5 + r) $r = 11 \Omega$ Ans. i.e., In case of ac, as choke has no resistance, power loss in the choke will be zero while the bulb will consume. $P = I^2 R = 10^2 \times 5 = 500 W$ However, in case of dc as resistance r is to be used instead of choke, the power loss in the resistance r will be. $PL = 10^2 \times 11 = 1100 W$

while the bulb will still consume 500 W, i.e., when the lamp is run on resistance r instead of choke more than double the power consumed by the lamp is wasted by the resistance r.

13. LC SERIES CIRCUIT WITH AN AC SOURCE :



IX

ίΧ_c

14. RLC SERIES CIRCUIT WITH AN AC SOURCE :





From the phasor diagram

$$V = \sqrt{(IR)^{2} + (IX_{L} - IX_{C})^{2}} = I\sqrt{(R)^{2} + (X_{L} - X_{C})^{2}} = IZ Z = \sqrt{(R)^{2} + (X_{L} - X_{C})^{2}}$$

tan $\phi = \frac{I(X_{L} - X_{C})}{IR} = \frac{(X_{L} - X_{C})}{R}$

14.1 Resonance :

Alternating Current

Amplitude of current (and therefore I_{ms} also) in an RLC series circuit is maximum for a given value of V_m and R, if the impedance of the circuit is minimum, which will be when $X_L-X_C = 0$. This condition is called **resonance**.



15. ADMITTANCE, SUSCEPTANCE AND CONDUCTANCE

• Admittance :

(a) The reciprocal of the impedance of an ac circuit is called admittance. It is represented by Y .

$$\therefore \text{ Admittance} = \frac{1}{\text{Impedance}} \quad Y = \frac{1}{Z}$$

(b) The unit of admittance is (ohm)-1 or mho.

Susceptance :

(a) The reciprocal of the reactance of an ac circuit is called susceptance. It is represented by S.

 \therefore Susceptance = Reactance or S = X

1

- (b) The unit of susceptance is $(ohm)_{-1}$ or mho.
- (c) The susceptance of a coil of inductance L is called inductive susceptance. It is equal to the reciprocal of inductive reactance.

1

(d) The susceptance of a capacitor of capacitance C is called capacitive susceptance. It is equal to the reciprocal of capacitive reactance.

... Capacitive susceptance = Capacitive reactance

$$S_{C} = \frac{1}{X_{C}} = \frac{1}{1/\omega C} = \omega C \text{ mho}$$

 \therefore Inductive susceptance =

Conductance :

(a) The reciprocal of resistance of a circuit is called conductance. It is represented by G.

$$\therefore \text{ Conductance} = \frac{1}{\text{Resistance}} \text{ or } G = \frac{1}{R}$$

(b) The unit of conductivity is also $(ohm)_{-1}$ or mho.

In the circuit in which different components are connected in parallel and same emf is applied on them its analysis in terms of admittance, susceptance and conductance becomes simpler because current in a component = voltage/(Impedance or Reactance or Resistance) = Voltage × (Admittance or Susceptance or Conductance)

16. HALF-POWER POINTS OR FREQUENCIES, BAND WIDTH & QUALITY FACTOR OF A SERIES RESONANT CIRCUIT

- (A) Half power frequencies
 - The frequencies at which the power in the circuit is half of the maximum power (the power at resonance), are called half-power frequencies. Thus at these freuencies



$$P = \frac{P_{max}}{2}$$

• The current in the circuit at half-power frequencies is $\sqrt{2}$ or 0.707 or 70.7% of the maximum current I_{max} (current at resonance).

$$I = \frac{I_{max}}{\sqrt{2}} = 0.707 I_{max}$$
 Thus

- There are two half power frequencies f1 and f2:
- (a) Lower half power frequency (f1): This half power frequency is less than the resonant frequency. At this frequency the circuit is capacitive.



(b) Upper half power frequency (f₂) : This half-power frequency is greater than the resonant frequency. At this frequency the circuit is inductive.

(B) Band width (Δf) :

- The difference of half-power frequencies f_1 and f_2 is called band-width (Δf)
- Band width $\Delta f = (f_2 f_1)$

For series resonant circuit :

$$\Delta f = \frac{1}{2\pi} \left(\frac{R}{L} \right)$$

(C) Quality factor (Q) :

•

• In an ac circuit Q is defined by the following ratio :

$$Q = 2\pi \times \frac{\text{Maximum energy stored}}{\text{Energy dissipation per cycle}} = \frac{2\pi}{T} \times \frac{\text{Maximum energy stored}}{\text{Mean power dissipated}}$$

$$\frac{\omega_r L}{R} = \frac{1}{\omega_r CR}$$

• For an L–C–R series resonant circuit : Q =

$$\frac{\omega_r}{\omega_2 - \omega_1} = \frac{2\pi f_r}{2\pi (f_2 - f_1)} \qquad \frac{f_r}{(f_2 - f_1)} = \frac{f_r}{\Delta f_1}$$

- Quality factor in terms of band-width : $Q = \frac{\omega_2 \omega_1}{2\pi(f_2 f_1)} = \frac{(f_2 f_1)}{e^{-f_1}}$ Resonant frequency Band width
- Quality factor = Band width
 Thus the ratio of the resonant frequency and the band-width is equal to the quality factor of the circuit.
- In the state of resonance the voltage across the resistor R will be equal to the applied voltage E. The magnitudes of voltage across the inductor and the capacitor will be equal and their values will be equal QE. Thus

$$\therefore \quad V_{L} = I\omega L = \frac{E}{R}\omega L = EQ \quad \text{and} \quad V_{C} = I \left(\frac{I}{\omega C}\right) = \frac{E}{\omega CR} = EQ$$

(D) Sharpness of resonance :



- For an ac circuit Q measures the sharpness of resonance.
- When Q is large, the resonance is sharp and when Q is small, the resonance is flat.
- The sharpness of resonance is inversely proportional to the band-width and the resistance R.
- For resonance to be sharp the resistance of the circuit should be small.

17. FORM FACTOR

Form factor for a sinusoidal current is defined as :

Form factor =
$$\frac{\text{rms value of ac}}{\text{Average value of positive half cycle}} = \frac{I_{\text{rms}}}{2I_0 / \pi} = \frac{I_0}{\sqrt{2}} \cdot \frac{\pi}{2I_0} = \frac{\pi}{2\sqrt{2}}$$

rms value of alternating voltage

• Similarly form factor for a sinusoidal voltage : F = Average value of positive half cycle = $2\sqrt{2}$

18. TRANSFORMER

- It is an instrument which changes the magnitude of alternating voltage or current.
- The magnitude of D.C. voltage or current cannot be changed by it.
- It works with alternating current but not with direct current.
- It converts magnetic energy into electrical energy.
- It works on the principle of electro-magnetic induction.
- It consists of two coils :
- (a) Primary coil : in which input voltage is applied.
- (b) Secondary coil : from which output voltage is obtained.



• The frequency of the output voltage produced by the transformer is same as that of input voltage, i.e., frequency remains unchanged.



- Transformer core is laminated and is made of soft iron.
- Let the number of turns in the primary coil be np and voltage applied to it be Ep and the number of

$$\frac{\mathsf{E}_{\mathsf{s}}}{\mathsf{E}_{\mathsf{p}}} = \frac{\mathsf{n}_{\mathsf{s}}}{\mathsf{n}_{\mathsf{p}}} \ _$$

turns in the secondary coil be n_s and voltage output be E_s, then $\Box_p = \Pi_p = K$

Thus the ratio of voltage obtained in the secondary coil to the voltage applied in the primary coil is equal to the ratio of number of turns of respective coils. This ratio is represented by K and it called transformer ratio.

- If $n_s > n_p$, then $E_s > E_p$ and K > 1. The transformer is called step-up transformer.
- If $n_s < n_p$, then $E_s < E_p$ and K < 1. The transformer is called step-down transformer.
- In ideal transformer

Input power = output power

 $E_pI_p = E_sI_s$

where $~~i_{\text{P}}-$ current in primary coil

l₅ – current in secondary coil L F n I E

or
$$\frac{I_p}{I_s} = \frac{L_s}{E_p} = \frac{I_s}{n_p} = K$$
 or $\frac{I_s}{I_p} = \frac{L_p}{E_s} = \frac{I_s}{K}$

Thus the ratio of currents in the secondary coil and the primary coil is inverse of the ratio of respective voltages.

- As the voltage changes by the transformer, the current changes in the same ratio but in opposite sense, i.e., the current decreases with the increase of voltage and similarly the current increases with the decrease of voltage. Due to this reason the coil in which voltage is lesser, the current will be higher and therefore this coil is thicker in comparison to the other coil so that it can bear the heat due to flow of high current.
- In step-up transformer

 $n_{\text{\tiny S}} > n_{\text{\tiny P}} \text{ , } K > 1 \quad \therefore \quad E_{\text{\tiny S}} > E_{\text{\tiny P}} \text{ and } I_{\text{\tiny S}} < I_{\text{\tiny P}}$

Alternating Current/

then

and in step down transformer

 $n_{s} < n_{p}, \, K < 1 \quad \ \ \, \dot{\cdot} \quad E_{s} < E_{p} \ and \ I_{s} > I_{p}$

• If Z_p and Z_s are impedances of primary and secondary coils respectively,

$$\frac{\mathsf{E}_{\mathsf{s}}}{\mathsf{E}_{\mathsf{p}}} = \frac{\mathsf{I}_{\mathsf{p}}}{\mathsf{I}_{\mathsf{s}}} = \frac{\mathsf{n}_{\mathsf{s}}}{\mathsf{n}_{\mathsf{p}}} = \sqrt{\frac{\mathsf{Z}_{\mathsf{s}}}{\mathsf{Z}_{\mathsf{p}}}}$$

• Law of conservation of energy is applicable in the transformer.

Power obtained from secondary coil Power applied in primary coil

• Efficiency of tranformer

Generally the efficiency of transformers is found in between 90% to 100%.

- Energy losses in transformers : Losses of energy are due to following reasons :
 - (a) Copper losses due to resistance of coils
 - (b) Eddy current losses in core.
 - (c) Hysteresis losses in core.
 - (d) Flux leakage due to poor linking of magnetic flux.

Uses of transformer :

- (a) Step down and step up transformer are used in electrical power distribution.
- (b) Audio frequency transformer are used in radiography, television, radio, telephone etc.
- (c) Ratio frequency transformer are used in radio communication.
- (d) Transformers are also used in impedance matching.

Solved Examples-

A 50 Hz a.c. current of crest value 1A flows through the primary of a transformer. If the mutual Example 16 inductance between the primary and secondary be 1.5 H, the crest voltage induced in secondary is (1) 75V (2) 150V (3) 225V (4) 300V Solution : The crest value is attained in T/4 time where T is the time period of A.C. Thus dI = 1A in dt = T/4 sec. 1 1 $T = \frac{1}{50}$ or $dt = \frac{1}{200}$ $M \frac{dI_1}{dt}$ The induced emf is $|E_2| =$ 1 $1.5 \times \frac{1}{(1/200)} = 1.5 \times 200 = 300 \text{ V}$ The correct answer is (4)