	Exercise-	-1		
		ONLY ONE OPTIC	N CORRECT TYPE	
SECT	ION (A) : AVERAGE	E, PEAK AND RMS	ALUES	
1.	If the value of potential 10	in an A.C. circuit is 10V,	, then the peak value of p	potential is - [CPMT-2003] 20
	(1) <u>√2</u>	(2) ¹⁰ √2	(3) 20√2	(4) $\overline{\sqrt{2}}$
2.	In a A.C. circuit of capa (1) Forward (3) Both are in the sam	acitance the phase of cur e phase	rrent from potential is - (2) Backward (4) None of these	[CPMT-2003]
3.	A coil of 200 Ω resistar Phase angle between (1) 30°	nce and 1.0 H inductance potential and current will (2) 90º	e is connected to an A.C be - (3) 45º	source of frequency 200/2π Hz. [MP PMT-2003] (4) 0°
4.	The hot wire ammeter (1) D.C. current	measures : (2) A.C. Current	(3) none of above	[R_PMT 2004] (4) both (1) and (2)
5.	A capacitor is a perfect (1) constant direct curr (3) direct as well as alter	t insulator for : ent ernating current	(2) alternating current (4) variable direct curre	ent
6.	A choke coil sould have (1) high inductance and (3) high inductance and	e : d high resistance d low resistance	(2) low inductance and (4) low inductance and	low resistance high resistance
7.	An AC voltage source reads rms value) and c (1) 10 mA	V = $200 \sqrt{2}$ sin 100 t is capacitor of capacity 1 μ F (2) 20 mA	connected across a circu F. The reading of ammete (3) 40 mA	uit containing an AC ammeter (it er is : (4) 80 mA
8.	Average value of A.C. (1) positive	current in a half time per (2) negative	iod may be : (3) zero	(4) All of these
9.	An alternating current i	s given by $I = I_1 \cos \omega t +$	I2 sin ω t. The rms current	is given by- [MPPMT-1994]
	(1) $\frac{1}{\sqrt{2}} (I_1 + I_2)$	(2) $\frac{1}{\sqrt{2}} (I_1 + I_2)^2$	(3) $\frac{1}{\sqrt{2}} (I_1^2 + I_2^2)^{1/2}$	(4) $\frac{1}{2}(I_1^2 + I_2^2)^{1/2}$
10.	The peak value of A.C. (1) 1	is $2\sqrt{2}$ amp., its appare (2) 2	ent value is- (in amp.) (3) 4	[RPMT-1996] (4) zero
11.	r.m.s. value of current	$i = 3 + 4 \sin (\omega t + \pi/3)$ is	:	7
	(1) 5 A	(2) √17 A	(3) $\frac{5}{\sqrt{2}}$ A	(4) $\frac{1}{\sqrt{2}}$ A
12.	The peak value of an a $t = (1/600)$ sec, the inst	lternating e.m.f E given b tantaneous value of e.m.	oy E = E₀ cos ωt is 10 volt f is :	t and frequency is 50 Hz. At time
13.	(1) 10 voltAn alternating voltage is given by :	(2) $5\sqrt{3}$ volt is given by : $e = e_1 \sin \omega t$	(3) 5 volt + e₂ cos ωt. Then the ro	(4) 1 volt ot mean square value of voltage
	(1) $\sqrt{e_1^2 + e_2^2}$	(2) $\sqrt{e_1 e_2}$	$(3) \sqrt{\frac{e_1 e_2}{2}}$	(4) $\sqrt{\frac{e_1^2 + e_2^2}{2}}$

14.	An AC voltage is given by :				
	$E = E_0 \sin \frac{2\pi t}{T}$				
	Then the mean value of	voltage calculated over	time interval of T/2 second	nds :	
	(1) is always zero	(2) is never zero	(3) is $(2e_0/\pi)$ always	(4) may be zero	
15.	The voltage of an AC so Where t is in second an	ource varies with time ac d V is in volt. Then :	cording to the equation,	V = 100 sin 100 π t cos 100 π t.	
	(1) the peak voltage of t(3) the peak voltage of t	he source is 100 volt he source is 50 volt	(2) the peak voltage of t(4) the frequency of the	the source is (100/ $\sqrt{2}$) volt source is 50 Hz	
		$\left(2\pi50t+\frac{\pi}{2}\right)$			
16.	An AC voltage of $V = 22$	$20\sqrt{2} \sin \left(\frac{2\pi 667}{2}\right)$ is	applied across a DC vol	tmeter, its reading will be:	
	(1) 220 √ ² ∨	(2) √ ² ∨	(3) 220 V	(4) zero	
17.	The r.m.s value of an A. zero to maximum value (1) 2×10^{-2} sec and 14.	C. of 50 Hz is 10 amp. T find the peak value will b 14 amp	he time taken by the alte be - (2) 1 × 10-2 sec and 7.0	rnating current in reaching from [Karnataka CET-2003] 7 amp	
	(3) 5 × 10 $_{-3}$ sec and 7.0	7 amp	(4) 5 × 10 ₋₃ sec and 14.	14 amp	
18.	If instantaneous current	is given by i = 4 cos (ω t	+ φ) amperes, then the r	r.m.s value of current is – [RPET-2000]	
	(1) 4 amperes	(2) $2\sqrt{2}$ amperes	(3) $4\sqrt{2}$ amperes	(4) zero amperes	
19.	A 40Ω electric heater is flowing in the circuir is a	connected to a 200V, 5 pproximately-	50 Hz mains supply. The	e peak value of electric current [MPPET-1992]	
	(1) 2.5 A	(2) 5.0 A	(3) 7 A	(4) 10 A	
20.	When magnet is approached then the current through	ched near a glowing bulb h the filament is-	, the vibrations are produ	iced in filament carrying current, [DRM-1993]	
	(1) D.C.(3) Mixture of A.C. and I	D.C.	(2) A.C.(4) Nothing can be said		
21.	An AC ammeter is used through the circuit, the circuit, the AC ammeter the circuit simultaneous	d to measure current in AC ammeter reads 3 an reads 4 ampere. Then ly, is :	a circuit. When a given npere. When an alternat the reading of this amm	direct constant current passes ing current passes through the eter if DC and AC flow through	
	(1) 3 A	(2) 4 A	(3) 7 A	(4) 5 A	
SECT	ION (B) : POWER CO	ONSUMED IN AN AG	C CIRCUIT		
1.	A choke coil is preferred (1) it consumes almost a (3) it increases power	to a rheostat in AC circu zero power	uit as : (2) it increases current (4) it increases voltage		
2.	Average power consumed in an A.C. series circuit is given by (symbols have their usual meaning) : $E_{max}^2 R$				
	(1) Erms Irms cosφ	(2) (Irms) ₂ R	(3) $\frac{2(z)^2}{2(z)^2}$	(4) All of these	
3.	A circuit with e.m.f. $E = 2$ will be-	200 sin ωt, contains a cap	pacitance and inductance	e, then the value of power factor [RPET-1995]	
	(1) 0	(2) 1	(3) 0.6	(4) 0.3	
4.	If a chocke coil of neglig it, then the loss of powe (1) 0	ible resistance works on r in chocke coil is- (2) 11 watt	220 volt source and 5m. (3) 44 \times 10 ³ watt	Amp. current is flowing through [RPMT-1995] (4) 1.1 watt	
	· / -	· / · · · · · · · · · · · · · · · · · ·	(-)	· / · · · · · · · · · · · · · · · · · ·	

5.	The value of current at	half power point is-		[RPET-1995]	
	I /2	$\frac{I_m}{\sqrt{2}}$		$\frac{I_m}{2}$	
	(1) $I_{m} \sqrt{2}$	(2) $\sqrt{2}$	(3) 2 Im	(4) 2	
				I = 100 sin $\left(314 + \frac{\pi}{3} \right)$	
6.	Expressions for emf an amp. The power factor	d current in an A.C. circ	uit are E = 200 sin 314 t	t volt and (RPMT-1996)	
	1	1			
	(1) 2	(2) 4	(3) 1	(4) –1	
7.	In a series LR circuit, th	e voltage drop across in	ductor is 8 volt and acros	s resistor is 6 volt. Then voltage	
	applied and power factor (1) 14 V 0.8	or of circuit respectively a	are:	(4) 14 \/ 0.6	
	(1) 14 V, 0.8	(2) 10 V, 0.8	(3) 10 V, 0.0	(4) 14 V, 0.0	
8.	In an a.c. circuit the e.m	n. f, (e) and the corrent (i) at any instant are givan	respectively by :	
	$i = l_0 \sin(\omega t - \phi)$				
	The average power in t	he circuit over one cycle	of a.c. is :	[AIPMT 2008]	
	$\frac{E_0 I_0}{2} \cos \varphi$		$\frac{E_0 I_0}{2}$	$\frac{E_0 I_0}{2} \sin \varphi$	
	(1) 2	(2) Eolo	(3) 2	(4) 2	
9.	The power factor of an angular velocity ω is –	A.C. circuit having resis	tance R and inductance	L (connected in series) and an	
	R	$R_{(-2)}$	<u>ωL</u>	$\frac{R}{(r^2 - 2r^2)^{1/2}}$	
	(1) ^{ωL}	(2) $(R^2 + \omega^2 L^2)^{n/2}$	(3) R	(4) $(R^2 - \omega^2 L^2)^{n/2}$	
10.	The average power del	ivered to a series AC cire	cuit is given by (symbols	have their usual meaning) :	
	(1) Erms Irms	(2) Erms Irms COS φ	(3) Erms Irms sin φ	(4) zero	
11.	The potential difference	e V across and the curre	ent I flowing through an	instrument in an AC circuit are	
	given by : $V = 5 \cos \omega t v c$	514			
	$V = 5 \cos \omega t V c$ $I = 2 \sin \omega t volt$				
	The power dissipated in	the instrument is :			
	(1) zero	(2) 5 watt	(3) 10 watt	(4) 2.5 watt	
12.	A direct current of 2 A an	nd an alternating current	having a maximum value	of 2 A flow through two identical	
	(1) 1 : 1	(2) 1 : 2	(3) 2 : 1	(4) 4 : 1	
13.	A sinusoidal AC curren power dissipated is :	t flows through a resisto	or of resistance R. If the	peak current is Ip, then average	
		1 ₁₂	$\frac{4}{2}$ I ² R	$\frac{1}{I^2R}$	
	(1) $I_p^2 R \cos \theta$	(2) $\overline{2}^{r_{p}}$	(3) π^{1}	(4) $\pi^{2^{-1}p^{+1}}$	
14.	What is the rms value which is thrice that proc	of an alternating current luced by a current of 2 a	t which when passed thr mpere in the same resist	ough a resistor produces heat, or in the same time interval?	
	(1) 6 ampere	(2) 2 ampere	(3) $2\sqrt{3}$ ampere	(4) 0.65 ampere	
		$(, \pi)$			
15.	If a current I given by I_{ω} wt has been applied, th	$\int_{0}^{\infty} \sin \left(\frac{\omega \tau - 2}{2} \right)$ flows in an enthe power consumption	n A.C. circuit across whic on P in the circuit will be	h an A.C. potential of E = E₀ sin - [MP PET-2001,02]	

	$P = \frac{E_0 I_0}{\sqrt{2}}$	$P = \sqrt{2}F$ I	$P = \frac{E_0I_0}{2}$	
	(1) $\sqrt{2}$	(2) $\Gamma = \sqrt{2}L_0 I_0$	(3) 2	(4) $P = 0$
16.	You have two copper c	ables of equal length for	carrying current. One o	f them has a single wire of area
	of cross-section A, the transporting AC and DC (1) Only single strand for (2) Either for DC, only r (3) Only single strand for (4) Only single strand for	e other has ten wires C- or DC and only multiple s nultiple strands for AC or AC, either for DC or DC, either for AC	of cross-section ¹⁰ e	ach. Judge their suitability for [CPMT-1994]
17.	The self inductance of a of power is 20 watt. Who of A.C. source will be-(1) 50 Hz	a choke coil is 10 mH. W en it is connected with 10 (2) 60 Hz	hen it is conected with a volt A.C. source loss of (3) 80 Hz	a 10V D.C. source, then the loss power is 10 watt. The frequency [RPMT-1995] (4) 100 Hz
18.	If the frequency of the s (1) n	source e.m.f. in an AC cir (2) 2 n	cuit is n, the power varie (3) n/2	es with a frequency : (4) zero
19.	A coil of inductive read capacitative reactance 2 of the circuit is : (1) 0.56	ctance 31Ω has a resist 25 Ω . The combination is $(2) = 0.64$	tance of 8Ω It is placed connected to an a.c. sou	d in series with a condenser of rce of 110 volt. The power factor [AIPMT 2006] (4) 0.33
~~		(2) 0.04		
20.	A circuit has a resistant : (1) 0.8	(2) 0.4	(3) 1.25	[AIEEE 2005; 4/300] (4) 0.125
21.	A coil of inductance $V = 10 \sin (100 t)$. The p (1) 2 amp	5.0 mH and negligible beak current in the circuit (2) 1 amp	e resistance is connec t will be : (3) 10 amp	cted to an alternating voltage (4) 20 amp
22.	A resistor and a capacit circuit is 2 ampere. If th	tor are connected to an A e power consumed in the	AC supply of 200 volt, 50 e circuit is 100 watt, ther) Hz in series. The current in the the resistance in the circuit is:
	(1) 100 Ω	(2) 25 Ω (3) [√] 1	$25 \times 75\Omega$ (4) 400	Ω
23.	The impedance of a se	ries circuit consists of 3	ohm resistance and 4 o	hm reactance. The power factor
	(1) 0.4	(2) 0.6	(3) 0.8	(4) 1.0
SECT 1.	ION (C) : AC SOUR A series LCR circular ir of variation of impendar	CE WITH R, L, C CO n connected to a.c. source nce 'z' of the circuit with f	NNECTED IN SERII ce of variable frequency frequency f will be	ES 'f'. The graphical represenration [RPMT-2014]
	(1) [⊂] f→		(2) f	\rightarrow

٠



11. If the readings of v_1 and v_3 are 100 volt each then reading of v_2 is :



200 V, 50 Hz

- (1) 0 volt
- (2) 100 volt
- (3) 200 volt
- (4) cannot be determined by given information.
- In an LRC series circuit at resonance current in the circuit is $10\sqrt{2}$ A. If now frequency of the source is 12. changed such that now current lags by 45° than applied voltage in the circuit. Which of the following is correct :
 - (1) Frequency must be increased and current after the change is 10 A
 - (2) Frequency must be decreased and current after the change is 10 A
 - (3) Frequency must be decreased and current is same as that of initial value
 - (4) The given information is insufficient to conclude anything [Made 2006, CSS, GRSTU]
- 13. In a pure inductive circuit or in an A.C. circuit containing inductance only, the current-

[UPCPMT-1990, MPPMT, RPMT-1993]

- (1) Leads the e.m.f. by 90°
- (2) Lags behind the e.m.f. by 90°
- (3) Sometimes leads and sometime lags behind the e.m.f.
- (4) Is in phase with the e.m.f.
- 14. A series combination of R, L, C is connected to an a.c. source. If the resistance is 30 and the reactance is 4Ω , the power factor of the circuit is-[CPMT-1994] (4) 1.0 (1) 0.4(3) 0.8 (2) 0.6
- 15. A 12Ω resistor and a 0.21 henry inductor are connected in series to an AC source operating at 20 volt, 50 Hz. The phase angle between the current and the source voltage is-[BHU-1994] (4) 90° (1) 30° (2) 40° $(3) 80^{\circ}$
- 16. When 100 V DC is applied across a solenoid, a steady current of 1 A flows in it. When 100 V AC is applied 150 √3 across the same solenoid, the current drops to 0.5 A. If the frequency of the AC source is $/\pi$ Hz, the impedance and inductance of the solenoid are : (1) 200 Ω and 1/3 H (2) 100 Ω and 1/16 H
 - (3) 200 Ω and 1.0 H (4) 1100 Ω and 3/117 H
- If in a series LCR AC circuit, the rms voltage across L, C and R are V₁, V₂ and V₃ respectively, then the 17. rms voltage of the source is always : (1) $\overline{\text{output}}$ (1) $\overline{\text{otput}}$

(1) equal to $v_1 +$	$\mathbf{v}_2 + \mathbf{v}_3$
(3) more than V ₁	$+ V_2 + V_3$

```
(2) equal to V_1 - V_2 + V_3
(4) none of these is true
```

18. In the series LCR circuit as shown in figure, the voltmeter and ammeter readings are :



19. An AC voltage source of variable angular frequency ω and fixed amplitude V connected in series with a capacitance C and an electric bulb of resistance R (inductance zero). When ω is increased :

[JEE 2010; 3/163, -1]

(1) the bulb glows dimmer

(2) the bulb glows brighter

(3) total impedence of the circuit is unchanged

(4) total impedence of the circuit increases

20. In a circuit L,C and R are connected in series with an alternating voltage source of frequency f. The current leads the voltage by 45₀ The value of C is : [AIPMT 2005]

 $\frac{1}{(1)} \frac{1}{2\pi f(2\pi fL - R)}$ (2) $\frac{1}{2\pi f(2\pi fL + R)}$ (3) $\frac{1}{\pi f(2\pi fL - R)}$ (4) $\frac{1}{\pi f(2\pi fL + R)}$

21.	In an LCR series a.c. ci across the LC combina	rcuit, the voltage across tion will be :	each of the components.	L, C and R is 50 V. The voltage [AIEEE 2004, 4/300]
	(1) 50 V	(2) ^{50√3} s	(3) 100 V	(4) 0 V (zero)
22.	The phase difference b the constituent of the ci (1) C alone	etween the alternating o rcuit? (2) R, L	current and emf is π/2. W (3) L, C	/hich of the following cannot be [AIEEE 2005; 4/300] (4) L alone
23.	An alternating voltage ammeter. The reading ((1) 10 mA	$E = 200\sqrt{2}$ sin (100 t) is of the ammeter shall be - (2) 20 mA	connected to a 1 microf (3) 40 mA	arad capacitor through an A.C. [UPSEAT-2000] (4) 80 mA
24.	A 0.21-H inductor and a in the circuit and the ph Use $\pi = 22/7$.	a 88- Ω resistor are conne ase angle between the c (2) 14.4 A tan $\sqrt{7/8}$	ected in series to a 220-V current and the source vo	(4) 3 28 A tap ± 2/11
25.	An LCR series circul angular frequency 300 behind the voltage by 6 Then the current and po (1) 1A, 200 watt.	it with 100 Ω resistant radians per second. W 50°. When only the induct ower dissipated in LCR of (2) 1A, 400 watt.	(c) 14.4 A, tan 10/7 ince is connected to an i/hen only the capacitanc ctance is removed, the co circuit are respectively (3) 2A, 200 watt.	n AC source of 200 V and e is removed, the current lags urrent leads the voltage by 60°. (4) 2A, 400 watt.
26.	A 100 volt AC source C = 5 μ F and R = 10 Ω , $\frac{100}{\Gamma}$	of angular frequency 5 all connected in series.	00 rad/s is connected to The potential difference a	a LCR circuit with L = 0.8 H, across the resistance is $\sqrt{2}$
	(1) $\sqrt{2}$ volt	(2) 100 volt	(3) 50 volt	(4) $50\sqrt{3}$
27.	A pure resistive circuit of current of 5 A which is same AC supply also of series combination of X $\frac{10}{\sqrt{2}}$ amp	element X when connect in phase with the volta- gives the same value of and Y is connected to the $\frac{5}{\sqrt{2}}$ amp	ted to an AC supply of pe ge. A second circuit eler peak current but the cu he same supply, what wil $\frac{5}{2}$ amp	eak voltage 200 V gives a peak nent Y, when connected to the rrent lags behind by 90°. If the I be the rms value of current ?
	(I) amp	(2) amp	(0) – amp	(+) 0 amp
28.	In an L-R series circ	suit (L = $\frac{113}{11}$ mH and	R = 12Ω), a variable e	emf source (V = V ₀ sin ω t) of
	$V_{rms} = 130 \sqrt{2} V$ and fre with respect to voltage	quency 50 Hz is applied. are respectively (Use π = 5	The current amplitude in = 22/7) 5	the circuit and phase of current 5
	(1) 14.14A, 30°	(2) $10\sqrt{2}$ A, tan-1 12	(3) 10 A, tan-1 12	(4) 20 A, tan-1 12
29.	In an AC circuit, a resist voltage and current be (1) R/4 (3) R	ance of R ohm is connect 45°, the value of inductiv	ted in series with an induc /e reactance will be. (2) R/2 (4) cannot be found with	tance L. If phase angle between n the given data
30.	In an AC circuit the p respectively 16 V and 2 (1) 20 V	otential differences acro 20 V. The total potential o (2) 25.6 V	bss an inductance and u difference across the circu (3) 31.9 V	resistance joined in series are uit is (4) 53.5 V
31.	An alternating current of series. The impedance	of frequency 'f' is flowing of this circuit is -	in a circuit containing a	resistance R and a choke L in [RPET-2001,03]
	(1) R + 2πfL	(2) $\sqrt{R^2 + 4\pi^2 f^2 L^2}$	(3) $\sqrt{R^2 + L^2}$	$(4) \sqrt{R^2 + 2\pi fL}$

32. An alternating current flows through a circuit consisting of inductance L and resistance R. Periodicity of the supply is 2π which of the following is true-[MPPMT-1993] (1) The limiting value of impedance is L for low frequency (2) The limiting value of impedance for high frequency is $L\omega$ (3) The limiting value of impedance for high frequency is R (4) The limiting value of impedance for low frequency is $L\omega$ 33. In following diagram voltage on L and C is-[UPPMT-1993] 000000 (2) With phase angle of 90° (1) In same phase (3) In phase angle of 180° (4) It will depends on the value of L and C 34. An LCR series circuit is connected to a source of alternating current. At resonance, the applied voltage and the current flowing through the circuit will have a phase difference of-[CPMT-1994] π π (2) 2 (3) 4 (1) π (4) 0Same current is flowing in two alternating circuits. The first circuit contains only inductance and the other 35. contains only a capacitor. If the frequency of the e.m.f. is increased, the effect on the value of the current will be-[MPPET-1993] (1) increase in first circuit and decrease in the other (2) increase in both circuits (3) decrease in both circuits (4) decrease in first circuit and increase in other 36. Energy dissipates in LCR circuit in : (3) R only (4) all of these (1) L only (2) C only 2.2 A coil has an inductance of π H and is joined in series with a resistance of 220 Ω . When an alternating 37. e.m.f. of 220 V at 50 cps is applied to it, then the wattless component of the rms current in the circuit is (1) 5 ampere (2) 0.5 ampere (3) 0.7 ampere (4) 7 ampere 38. An electric bulb and a capacitor are connected in series with an AC source. On increasing the frequency of the source, the brightness of the bulb : (1) increase (2) decreases (3) remains unchanged (4) sometimes increases and sometimes decreases 39. By what percentage the impedance in an AC series circuit should be increased so that the power factor changes from (1/2) to (1/4) (when R is constant)? (1) 200% (2) 100%(3) 50% (4) 400% SECTION (D) : RESONANCE The self inductance of the motor of an electric fan is 10 H. In order to impart maximum power at 50 Hz, it 1. [AIEEE 2005, 4/300] should be connected to a capacitance of : (4) 2µF (1) 4µF (2) 8µF (3) 1µF In an LCR circuit, capacitance is changed from C to 2C. For the resonant frequency to remain unchanged, 2. the inductance should be changed from L to : [AIEEE 2004; 4/300] (1) 4L (2) 2L (3) L/2 (4) L/4 In an oscillating LC circuit the maximum charge on the capacitor is Q. The charge on the capacitor when 3. the energy is stored equally between the electric and magnetic field is : [AIEEE 2003; 4/300] (2) Q/ $\sqrt{3}$ (3) Q/√2 (1) Q/2 (4) Q

4.	What is the value of ind C =10 μ F and ω = 1000 (1) 10 mH	uctance L for which the o) radian/s?	current is a maximum in a	a series LCR circuit with [AIPMT 2007]
	(3) 1 mH		(4) cannot be calculated	d unless R is Known
5.	A transistor – oscillator u C in series produce osc will be:	using a resonant circuit wi cillations of frequency f.	th an inductor L (of neglig If L is doubled and C is a [AIPM]	gible resistance) and a capacitor changed to 4C, then frequency [2006]
	$\frac{f}{d}$		$\frac{1}{\sqrt{2}}$	$\frac{f}{2}$
	(1) 4	(2) 8 f	(3) 2√2	(4) 2
6.	A $2\mu F$ capacitor is initia value of the current in the	Illy charged to 20 Volts ane circuit is :	and then shorted across	a 8 μ H inductor. The maximum
	(1) 10.0 A	(2) 7.5 A	(3) 12.0 A	(4) 8.2 A
7.	For an A.C. circuit at the (1) impedance = R	e condition of resonance		[RPET-1996]
	$\omega L -$	$\frac{1}{\omega C}$		
	 (2) impedance = (3) potential difference a (4) The current and emf 	across L and C in same p are having a phase diffe	bhase. erence φ.	
8.	A series A.C. circuit or respectively. 1 henry an	consist of an inductor and $25 \ \mu$ F. If the current is	and a capacitor. The ir maximum in circuit then	nductance and capacitance is angular frequency will be- [RPMT-1999]
				200
	(1) 200	(2) 100	(3) 50	(4) ^{2π}
9.	The value of power fact (1) zero	or cosφ in series LCR ciı (2) 1	cuit at resonance is : (3) 1/2	(4) 1/2 ohm
10.	A series LCR circuit $4 \times 10_3$ rad s ₋₁ . At 40 V respectively. The v	containing a resistand resonance, the voltag alues of L and C are res	ce of 120 ohm has a e across resistance a pectively :	angular resonance frequency nd inductance are 60V and
	(1) 20 mH, 25/8 μF	(2) 2mH, 1/35 μF	(3) 20 mH, 1/40 μF	(4) 2mH, 25/8 nF
11.	In an LCR circuit, the c change in inductance, s	capacitance is made one to that the circuit remains	e-fourth, when in resona	nce. Then what should be the
	(1) 4 times	(2) 1/4 times	(3) 8 times	(4) 2 times
12.	A resistor R, an inductor resonant frequency is n	r L and a capacitor C are	connected in series to an ehind voltage, when :	n oscillator of frequency n. If the
	(1) n = 0	(2) n < n _r	(3) $n = r_r$	(4) n > n _r
13.	A 10 ohm resistance 0. alternating current sour the resonance frequence	5 mH coil and 10µF cap ce is joined to this comb ;y-	acitor are joined in serie ination, the circuit resona	s when a suitable frequency of ates. If the resistance is halved [MPPET-1995]
	(1) is halved	(2) is doubled	(3) remains unchanged	(4) is quadrupled
14.	At a frequency more that	an the resonance frequer	ncy, the nature of an anti	-resonant cicuit is- [RPMT-1996]
	(1) resistive	(2) capacitive	(3) inductive	(4) all of the above
15.	If resonance frequency becomes-	is f and then the capaci	ty is increased 4 times,	then new resonance frequency [RPMT-1996]
	$\frac{1}{2}$		(2)	$(A) \frac{1}{A}$
	(1) 2	(2) 21	(3)†	(4) 4

SECT	TION (E) : TRANSFO	RMER		
1.	The core of any transfo	[AIEEE 2003, 4/300]		
	(1) reduce the energy loss due to eddy currents			
	(2) make it light weight			
	(3) make is robust and	strong		
	(4) increase the second	dary voltage		
2.	In a transformer, numb	er of turns in the primary	v are 140 and that in the	secondary are 280. If current in
	primary is 4 A, then that	at in the secondary is :(as	sume that the transform	er is ideal) [AIEEE 2002; 4/300]
	(1) 4 A	(2) 2 A	(3) 6 A	(4) 10 A
3.	A transformer is used for	or a 100 watt, 20 volt elec	ctric bulb at a place when	e the A.C. mains potential is 200
	volt and the current dra	awn is 0.6 A. The efficien	cy of the transformer is r	early
	(1) 48%	(2) 68%	(3) 30 %	(4) 83%
4.	In a step-up transforme	er the turns ratio is 10. If	the frequency of the cur	rent in the primary coil is 50 Hz
	then the frequency of the	he current in the seconda	ary coil will be	
	(1) 500 Hz	(2) 5 Hz	(3) 60 Hz	(4) 50 Hz
5.	A power (step up) trar	nsformer with an 1 : 8 tur	n ratio has 60 Hz, 120 \	across the primary; the load in
	the secondary is $10_4 \Omega$.	The current in the secor	ndary is	
	(1) 96 A	(2) 0.96 A	(3) 9.6 A	(4) 96 mA
6.	A transformer is used	to light a 140 watt, 24 v	olt lamp from 240 V AC	mains. The current in the main
	cable is 0.7 amp. The e	efficiency of the transform	ner is :	
	(1) 48%	(2) 63.8%	(3) 83.3%	(4) 90%
7.	In a step-up transforme	er the voltage in the prima	ary is 220 V and the curre	ent is 5A. The secondary voltage
	is found to be 22000 V	. The current in the seco	ndary (neglect losses) is	
	(1) 5 A	(2) 50 A	(3) 500 A	(4) 0.05 A
8.	The core of a transform	ner is laminated to reduce	e	
	(1) eddy current loss	(2) hysteresis loss	(3) copper loss	(4) magnetic loss

Paragraph for Questions 9 and 10

A thermal power plant produces electric power of 600 kW at 4000 V, which is to be transported to a place 20 km away from the power plant for consumers' usage. It can be transported either directly with a cable of large current carrying capacity or by using a combination of step-up and step-down transformers at the two ends. The drawback of the direct transmission is the large energy dissipation. In the method using transformers, the dissipation is much smaller. In this method, a step-up transformer is used at the plant side so that the current is reduced to a smaller value. At the consumers' end, a step-down transformer is used to supply power to the consumers at the specified lower voltage. It is reasonable to assume that the power cable is purely resistive and the transformers are ideal with a power factor unity. All the currents and voltages mentioned are rms values.

[JEE(Advanced)-2013; 3/60]]



- 9. If the direct transmission method with a cable of resistance 0.4 Ω km⁻¹ is used, the power dissipation (in %) during transmission is :
 (1) 20
 (2) 30
 (3) 40
 (4) 60
- 10. In the method using the transformers, assume that the ratio of the number of turns in the primary to that in the secondary in the step-up transformer is 1 : 10. If the power to the consumers has to be supplied at 200V, the ratio of the number of turns in the primary to that in the secondary in the step-down transformer is :

```
(1) 200 : 1(2) 150 : 1(3) 100 : 1(4) 50 : 1
```

Exercise-2

1. An ac voltage source V = V₀ sin ω t is connected across resistance R and capacitance C as shown in figure. It is given that R = $\frac{1}{\omega C}$. The peak current is I₀. If the angular frequency of the voltage source is changed to $\frac{\omega}{\sqrt{3}}$, keeping the voltage amplitude constant, then the new peak current in the circuit is : $V_0 \sin \omega t$ C C $V_0 \sin \omega t$ C C $V_0 \sin \omega t$ C C C $V_0 \sin \omega t$ C C C $V_0 \sin \omega t$ C C $V_0 \sin \omega t$ C C $V_0 \sin \omega t$ C $V_0 \sin \omega t$ C C $V_0 \sin \omega t$ $V_0 \sin \omega t$ C $V_0 \sin \omega t$ C $V_0 \sin \omega t$ $V_0 \sin$

2.	An AC voltage source of variable angular frequency ω and fixed amplitude V connected in series with a capacitance C and an electric bulb of resistance R (inductance zero). When ω is increased :				
	(1) the bulb glows dimm(3) total impedence of the	er ne circuit is unchanged	(2) the bulb glows bright(4) total impedence of the	ter ne circuit increases	
3.	 Alternating current cannot be measured by D.C. ammeter because : [AIEEE 2004; 4/300] (1) A.C. current pass through d.C. ammeter (2) A.C. change direction (3) average value of current for complete cycle is zero (4) D.C. ammeter will get damaged 				
4.	The overall efficiency of a transformer is 90%. The transformer is rated for an output of 9000 watt. The primary voltage is 1000 volt. The ratio of turns in the primary to the secondary coil is 5 : 1. The iron losses at full load are 700 watt. The primary coil has a resistance of 1 ohm.				
(i)	The voltage in secondar (1) 1000 volt	ry coil is : (2) 5000 volt	(3) 200 volt	(4) zero volt	
(ii)	In the above, the curren (1) 9 amp	t in the primary coil is : (2) 10 amp	(3) 1 amp	(4) 4.5 amp	
(iii)	In the above, the coppe (1) 100 watt	r loss in the primary coil (2) 700 watt	is : (3) 200 watt	(4) 1000 watt	
(iv)	In the above, the coppe (1) 100 watt	er loss in the secondary ((2) 700 watt	coil is : (3) 200 watt	(4) 1000 watt	
(v)	In the above, the curren (1) 45 amp	t in the secondary coil is (2) 46 amp	: (3) 10 amp	(4) 50 amp	
(vi)	In the above, the resistat (1) 0.01 Ω	ince of the secondary co (2) 0.1 Ω	il is approximately : (3) 0.2 Ω	(4) 0.4 Ω	

Exercise-3

PART - I : NEET / AIPMT QUESTION (PREVIOUS YEARS)

Power dissipated in an LCR series circuit connected to an a.c.source of emf is : [AIPMT 2009] $\epsilon^2 R / \sqrt{R^2 + \left(L \omega - \frac{1}{C\omega}\right)^2}$ (1) $\epsilon^2 R / \{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2\}$ (2) $\epsilon^2 \left| \mathsf{R}^2 + \left(\mathsf{L} \ \omega - \frac{1}{\mathsf{C} \omega} \right)^2 \right|$ $\epsilon^2 / \sqrt{R^2 + \left(L \omega - \frac{1}{C\omega}\right)^2} R$ R (3) (4) 2. The r.m.s. value of potential difference V shown in the figure is : [AIPMT (MAINS) 2011] ٧Ą V.

T/2 (4) V₀/ $\sqrt{3}$ (2) V₀/ $\sqrt{2}$ (3) V₀/2 (1) V₀

0

1.

- 3. A coil has resistance 30 ohm and inductive reactance 20 Ohm at 50 Hz frequency. If an ac source, of 200 volt, 100 Hz, is connected across the coil, the current in the coil will be : [AIPMT (MAINS) 2011]
- (3) $\frac{20}{\sqrt{13}}$ A (2) 8.0 A (1) 4.0 A (4) 2.0 A In an electrical circuit R,L, C and an a.c. voltage source are all connected in series. When L is removed 4. from the circuit, the phase difference between the voltage the current in the circuit is $\pi/3$. If instead, C is removed from the circuit, the phase difference is again $\pi/3$. The power factor of the circuit is : [AIPMT (Pre) 2012]

(1)
$$1/2$$
 (2) $1/\sqrt{2}$ (3) 1 (4) $\sqrt{3}/2$

5. The instantaneous values of alternating current and voltages in a circuit are given as

$$i = \frac{1}{\sqrt{2}} \sin(100 \,\pi t) \text{ amper} \qquad [AIPMT 2012 (Mains)]$$

$$e = \frac{1}{\sqrt{2}} \sin(100 \,\pi t + \pi \,/\, 3) \text{ Volt}$$
The average power in Watts consumed in the circuit is :
$$(1) \frac{1}{4} \qquad (2) \frac{\sqrt{3}}{4} \qquad (3) \frac{1}{2} \qquad (4) \frac{1}{8}$$

- 6. A coil of self-inductance L is connected in series with a bulb B and an AC source. Brightness of the bulb decreases when : [NEET-2013]
 - (1) number of turns in the coil is reduced.
 - (2) a capacitance of reactance $X_c = X_{\perp}$ is included in the same circuit
 - (3) an iron rod is inserted in the coil
 - (4) frequency of the AC source is decreased
- 7. A resistance 'R' draws power 'P' when connected to an AC source. If an inductance is now placed in series with the resistance, such that the impedance of the circuit becomes 'Z', the power drawn will be: [AIPMT-2015]

(1)
$$P\sqrt{\frac{R}{Z}}$$
 (2) $P\left(\frac{R}{Z}\right)$

An inductor 20 mH, a capacitor 50 μF and a resistor. 40Ω are connected in series across a source of emf 8. V = 10 sin 340t. The power loss in A.C. circuit is [AIPMT-2016] (1) 0.89 W (2) 0.51 W (3) 0.67W (4) 0.76W

(3) P

- 9. A small signal voltage $V(t) = V_0 \sin \omega t$ is applied across an ideal capacitor C :
 - (1) Current I(t), leads voltage V(t) by 180°
 - (2) Current I(t), lags voltage V(t) by 90°
 - (3) Over a full cycle the capacitor C does not consume any energy from the voltage source. [AIPMT-2016]
 - (4) Current I(t) is in phase with voltage V(t)
- 10. Which of the following combinations should be selected for better tuning of an L-C-R circuit used for [NEET-2016] communication?

(1) R = 25 Ω, L = 1.5 H, C = 45 μF	(2) R = 20 Ω, L = 1.5 H, C = 35 μF
(3) R = 25 Ω , L = 2.5 H, C = 45 μ F	(4) R = 15 Ω , L = 3.5 H, C = 30 μ F

- 11. The potential differences across the resistance, capacitance and inductance are 80 V, 40 V and 100 V respectively in an L-C-R circuit. The power factor of this circuit is [NEET-2016] (1) 1.0 (3) 0.5(4) 0.8 (2) 0.4
- 12. A 100 Ω resistance and a capacitor of 100 Ω reactance are connected in series across a 220 V source. When the capacitor is 50% charged, the peak value of the displacement current is [NEET-2016]

13.	(1) $11\sqrt{2}A$ A inductor 20 mH a V = 10 sin 314 t. Th (1) 0.79 W	(2) 2.2 A capacitor 100 μF and a ne power loss in the circu (2) 1.13 W	(3) 11 A resistor 50 Ω are connecte uit is : (3) 2.74 W	 (4) 4.4 A d in series across a source of emf, [NEET-2018] (4) 0.43 W
14.	A circuit when con connected to a DC (1) series LR	nected to an AC source source of 12 V, gives a o (2) series RC	e of 12 V gives a current current of 0.4 A. The circui (3) series LC	t of 0.2A. The same circuit when t is : [NEET-2019-II] (4) series LCR
	PART - II : JE	EE (MAIN) / AIEE	EPROBLEMS (PR	EVIOUS YEARS)
1.	In a series LCR circ Hz respectively. On On taking out the ir the LCR circuit is	cuit R = 200 Ω and the voltation of the capacitan nductor from the circuit the capacitation (2) 210 W	oltage and the frequency of the from the circuit the curr the current leads the voltage [AIE (2) Zoro W(of the main supply is 220 V and 50 ent lags behind the voltage by 30° . ge by 30° . The power dissipated in EE 2010; $4/144$, -1]
	(1) 305 W	(2) 210 VV	(3) Zero W	(4) 242 VV
2.	An arc lamp require AC supply, the serie (1) 0.08 H	es a direct current of 10 A es inductor needed for it (2) 0.044 H	A at 80 V to function. if it is to work is close to : [JEE (3) 0.065 H	connected to a 220 V(rms), 50 Hz E Main 2016; 4/120, -1] (4) 80 H
3.	For an RLC circuit resonance. The qua	driven with voltage of a ality factor, Q is given by <u>CR</u>	Implitude v_m and frequen : : $\underline{\omega_0 L}$	cy $\omega_0 = \frac{1}{\sqrt{LC}}$ the current exhibits [JEE-Main-2018] $\omega_0 R$
	(1) ^{(ω} ₀ C)	(2) ⁰⁰ 0	(3) R	(4) L
4.	In an a.c circuit, the e = 100 sin 30t i = 20 sin $(30t - \frac{\pi}{4})$	e instantaneous e.m.f and	d current are given by	
	In one cycle of a.c t $\frac{50}{\sqrt{2}},0$	(2) 50 0	(3) 50 10	[JEE-Main-2018] $(4) \frac{1000}{\sqrt{2}}, 10$
5.	A power transmiss windings having 40 the primary of the tr	ion line feeds input pov 00 turns. The output pov ransformer is 5A and its	ver at 2300 V to a step over is delivered at 230 V to efficiency is 90%, the outp	down transformer with its primary by the transformer. If the current in ut current would be :
	(1) 45 A	(2) 25 A	(3) 35 A	(4) 50 A
6.	A series AC circuit	containing an inductor (2 4 V	20 mH), a capacitor (120 μ	F) and a resistor (60 Ω) is driven by
	an AC source of $\frac{50}{(1)}$ (1) 3.39 × 10 ³ J	^{DHz} . The energy dissipa (2) 5.65 × 10 ² J	ated in the circuit in 60 s is (3) 5.17 × 10 ² J	: [JEE-Main-2019] (4) 2.26 × 10 ³ J

7. In the circuit shown the switch S_1 is closed at time t = 0 and the switch S_2 is kept open. At some later time (t_0) , the switch S₁ is opened and S₂ is closed. The behavior of the current I as a function of time 't' given [JEE-Main-2019] by:



In the above circuit 8.

and $R_1 = 10\Omega$. Current in L-R₁ path is I₁ and in C-R₂

 $V = 200\sqrt{2} \sin(100t)$ volts, the phase difference path it is I2. The voltage of A.C. source is given by between I₁ and I₂ is : [JEE-Main-2019]



