TOPIC : CURRENT ELECTRICITY EXERCISE # 1

SECTION (A)

- 1. The drift velocity of electrons in a conducting wire is of the order of 1mm/s. But electric field is set up in the wire very quickly, producing a current through each cross section, almost intantaneousty.
- 2. In the presence of an applied electric field (E) in a metallic conductor. The electrons also move randomly but slowly drift in a direction opposite to E.

3.
$$n = \frac{I}{e} = \frac{4.8}{1.6 \times 10^{-19}} = 3 \times 10^{19}$$

SECTION (B)

3.

- 1. Specific resistance depends only on the material of the wire.
- 2. Specific resistance depends only on the material of the wire.

$$R = \frac{\rho \ell}{A} = \frac{\rho \times 2\ell}{2A} = \frac{\rho \ell}{A}$$
 (unchanged)

4. V = IR Equation of straight line

6.
$$R = \frac{\rho \ell}{A} \Rightarrow 0.1 = \frac{3.14 \times 10^{-8} \times \ell}{\pi (1 \times 10^{-3})^2} \Rightarrow \ell = 10 \text{ m}$$

7.
$$R_1 = \frac{\rho \ell}{A}, R_2 = \frac{\rho \times 2\ell}{A/2} = 4R_1, R_2 = \frac{\rho \ell/2}{2A} = \frac{R_1}{4}$$

8.
$$\mathbf{R} = \frac{\rho \ell}{a}, \mathbf{R}' = \frac{\rho \times \ell}{4a} = \frac{\mathbf{R}}{4}$$

9. Volume will remain same so

$$V_{1} = V_{2} \implies \ell_{1} A_{1} = \ell_{2}A_{2} \implies \frac{A_{1}}{A_{2}} = \frac{\ell_{2}}{\ell_{1}}$$
$$\implies \frac{r_{1}^{2}}{r_{2}^{2}} = \frac{\ell_{2}}{\ell_{1}} \implies \frac{\ell_{2}}{\ell_{1}} = 4$$
$$\implies \ell_{2} = 4\ell_{1} \implies R = \frac{\rho\ell}{A}, R' = \frac{\rho4\ell}{A/4} = 16R$$

10. If a same wire is stretched, its length increases but cross-sectional area decreases.

$$R \propto I_2 \quad \therefore \qquad \frac{R'}{R} = \frac{\left(\frac{l'}{l}\right)^2}{= 4} \quad \Rightarrow \quad R' = 4R$$

Α

$$R_{max} = \frac{\rho a}{bc} \implies R_{min} = \frac{\rho c}{ab} \implies \frac{R_{max}}{R_{min}} = \frac{a^2}{c^2} = 4$$

12. In semiconductor resistance decrease with increase in the temperature. Therefore resistivity also decrease. In conducting solid resistance increase with increase the temperature because the rate of collisions between free electron and ions increases with increase of temperature both the statements are true.

13.
$$R = \frac{\rho \ell}{A}$$

$$R = \frac{2 \times 10^{-7} \times 1 \times 10^{-2}}{100 \times 1 \times 10^{-4}} = 2 \times 10^{-7} \Omega$$

14.
$$X = \frac{\rho \times 4a}{a \times 2a} = 2\frac{\rho}{a}$$
$$Y = \frac{\rho \times a}{4a \times 2a} = \frac{1}{8}\frac{\rho}{a}$$
$$Z = \frac{\rho \times 2a}{4a \times a} = \frac{1}{2}\frac{\rho}{a}$$
So, X > Z >

15. Wire is stretched, therefore its volume remains unchanged $A_1 I_1 = A_2 I_2$ $A_1 I = A_2 \times 3I$ $A_{2} = \frac{A_{1}}{3} \text{ Ratio of resistane } \frac{R_{1}}{R_{2}} = \frac{I_{1}}{I_{2}} \times \frac{A_{2}}{A_{1}} = \frac{I}{3I} \times \frac{1}{3} = \frac{1}{9} = \frac{20}{R_{2}} = \frac{1}{9} \Rightarrow$ $\rho_{eq} \ \frac{2\ell}{A} = \rho_1 \frac{\ell}{A} + \rho_2 \frac{\ell}{A}$

Υ

 $\rho_{eq} = 1/2 (\rho_1 + \rho_2)$

17.
$$R_{AB} = 2 + 2 + 2 = 6\Omega$$

18. In the balance condition of bridge circuit, no current will flow through 70 resistance. The bridge circuit can be shown as :

 $R_2 = 180 \Omega$

The balanced condition of bridge circuit is given by

$$\frac{\mathsf{P}}{\mathsf{Q}} = \frac{3}{4}, \frac{\mathsf{R}}{\mathsf{S}} = \frac{6}{\mathsf{R}} = \frac{3}{4} \therefore \frac{\mathsf{P}}{\mathsf{Q}} = \frac{\mathsf{R}}{\mathsf{S}}$$

Thus, it is balanced Wheatstone's bridge, so potential at F is equal to potential at H. Therefore, no current will flow through 7Ω resitance. So, circuit can be redrawn as shown above.



P and Q are in series, so their equivalent resistance = $3 + 4 = 7\Omega$ R and S are also in series, the their equivalent resistance = $6 + 8 = 14\Omega$

Now,
$$7\Omega$$
 and 14Ω resistance are in parallel, so $R_{AB} = \overline{7+14} = \overline{21} = \overline{3}^{1/2}$.
NOTE: Normally, in wheastone's bridge in middle arm galvanometer must be connected. In wheatstone's bridge, cell and galvanometer arms are interchangeable.
In both the cases, condition of balanced bridge is

7×14

7×14

14

$$\frac{P}{Q} = \frac{R}{S}$$

19. $A_1 I_1 = A_2 I_2$

A₁ × I = A₂ × 2I

$$\frac{R_1}{R_2} = \frac{I_1}{I_2} \times \frac{A_2}{A_1} = \frac{I}{2I} \times \frac{I}{2}$$

$$\frac{R_1}{R_2} = \frac{1}{4} \implies R_2 = 4R_1$$
Resistance becomes 4 times the initial resistance becomes 4 times 4 times

4 times the initial resistance.

20. Resistivity of a metal is directly proportional to temperature and resistivity of semiconductor is inversely proportional to temperature.

Resistivity of metal ∝ Temperature

1

Resistivity fo semicondutor ~ Temperature This implies that with decreases in temperature resistivity of metal decreases while that of emiconductor increases.

Here, Si is a semiconductor and Cu is a metal. So, resistivity of Si increases but that of Cu decreases.

21. Here: Thickness of first wire $r_1 = 2r$ The thickness of second wire $r_2 = r$ Using the relation for resistance of wire is,

$$R = \frac{S \times I}{A} = S \times \frac{I}{\pi r^2} \propto \frac{1}{r^2} \qquad \qquad Hence \quad \frac{R_1}{R_2} = \left(\frac{r_2}{r_1}\right)^2 = \frac{(r)^2}{(2r)^2} = \frac{1}{4}$$

22. $R_t = R_0 (1 + \alpha \Delta t)$ $5 R = R_0 (1 + \alpha \times 50)$

...(i) $6R = R_0 (1 + \alpha \times 100)$ and ...(ii) On dividing Eq. (i) by (ii) and solving it, we get

$$\alpha = \frac{1}{200} \Omega / 0^{\circ} C$$

On putting in Eq. (i), we get

5 1+ 4 $R_0 = 4RO$

23. The resistance of metallic wire at temperature t ° C is given by $R_t = R_0 (1 + \alpha t)$ Where α is coefficient of expansion.

> Hence, resistance of wire increases on increasing thetemperature. Also, from Ohm's law, ratio of equal to R ie, t = R

Hence, on increasing the temperature the ratio *i* increases.

24. Given : l' = l + 100% = 2l Initial volume = final volume

 $\pi \mathbf{r}_2 = \mathbf{p}\mathbf{r}'_2 \mathbf{I}$ ie. $\mathsf{R}' = \rho \quad \frac{\mathsf{I}}{\mathsf{A}'} = \rho \quad \frac{2\mathsf{I}}{\pi \mathsf{r}'^2} \qquad \left(\because \mathsf{R} = \frac{\rho\mathsf{I}}{\mathsf{A}} \right) = \frac{\rho\mathsf{4}\mathsf{I}}{\pi \mathsf{r}^2}$ $\Rightarrow r'_2 = \frac{r^2}{2} \therefore$ r^2 $\mathbf{r}_{2}^{\prime} = \mathbf{I}_{2} = \mathbf{r}_{2} \times \mathbf{Z}$ 3R $\% \Delta R = R \times 100\% = 300\%$ $\Delta R = R' - R = 4R - R = 3R$ *.*:. 1 Conductane = Resistance 25. Resistance (R) = $\frac{8}{9} \Omega$ Current flowing through the conductor :. :. $I = \frac{V}{R} = \frac{20 \times 8}{1} = 160 \text{ A}$ $V = \epsilon - ir$ 26. so y- intercept = $\epsilon = 1 \text{ V}$ slope = -r =_ 4 so $r = 0.25 \Omega$ $R = \rho \overline{A} = \rho \overline{V}$ $R \propto \ell_2$ as $\ell \longrightarrow 2\ell$ 27. $\Rightarrow R \longrightarrow 4R$ % change in R = 300 % Ans. ⇒ $H_2 = \frac{V^2}{R/2}t$ $\frac{1}{H_1} = 2$ R ÷ 28. $H_2 = 2H_1$ \Rightarrow Ans. 29. $\rho B = 2\rho A$ $r_B = 2r_A$ $\rho_{A} = \left(\frac{\ell_{A}}{\pi r_{A}^{2}}\right) \rho_{B} \left(\frac{\ell_{B}}{\pi r_{B}^{2}}\right) \Rightarrow \frac{\ell_{A}}{\ell_{B}} = \frac{1}{2}$ $R_A = R_B$ Ans. 30. Let $R = R_0$ at $0^{\circ}C$ $5 = R_0 (1 + \alpha \times 50)$(i) $6 = R_0 (1 + \alpha \times 100)$(ii) $R_0 = 4\Omega$ Solving (i) and (ii) \Rightarrow ρΙ R = A31. ρL R = tL = t. Independent of L. 32. The specific resistance (resistivity) of a metallic conductor nearly increases with increasing temperature as shown in figure. This is because, with the increases in temperature the ions of the conductor vibrate with greater amplitude, and the collision between electrons and ions become more frequent, over all small temperature range (up to 100°C). The resistivity of a metal can be represented approximately by the equation ρ

 $\rho_t = \rho_0 (1 + \alpha t)$. The factor α is called the temperature cofficient of resistivity.

→t

33. The electric fuse is a device which is used to limit the current in an electric circuit. Thus, the use of fuse safeguards the circuit and the applicanes connected in the circuit from being damaged. It is always connected with the live (or phase) wire. The fuse wire is a short piece of wire made of a material of high resistance and low melting point so that it may easily melt due to overheating when excessive current passes through it.

Note : A fuse wire is an alloy made of tin and lead.

34. The formula for resistance of wire is

ρl R = Awhere ρ = specific resistance of the wire l $\Rightarrow R \propto \overline{r^2}$ $(:: A = \pi r_2)$ $\therefore \frac{\mathsf{R}_1}{\mathsf{R}_2} = \frac{\ell_1}{\ell_2} \times \frac{\mathsf{r}_2^2}{\mathsf{r}_1^2}$(i) $\ell_1 = \ell, \ \ell_2 = 2\ell, \ r_1 = r, \ r_2 = 2r, \ R_1 = R$ Substituting these values in Eq. (i), we have $\frac{\mathsf{R}_1}{\mathsf{R}_2} = \frac{\ell}{2\ell} \times \frac{(2r)^2}{r^2}$ $\frac{\mathsf{R}_1}{\mathsf{R}_2} = \frac{\ell}{2\ell} \times \frac{(2r)^2}{r^2}$ R_1 $\overline{R}_2 = 2$ R $R_2 = 2$

Therefore, resistance will be halved. Now the specific resistance of the wire does not depend on the geometry of the wire hence, it remains unchanged.

35. Total current drawn from the battery

$$\frac{E}{I = R + r} = \frac{6}{100 + 0} = 0.06A$$
Resistance of 50 cm wire is
$$R' = \frac{\rho \ell'}{A} = \left(\frac{\rho}{A}\right)_{\ell'} \qquad \left(\because R = \frac{\rho \ell}{A}\right) = \frac{100}{300} \times 50$$

$$R' = \frac{50}{3}$$

so, R' = $\frac{3}{\Omega}$

Hence, the potential difference between two points on the wire separated by a distance ℓ' is

$$V = iR' = 0.06 \times \frac{50}{3} = 1V$$

36. When wire is bent to form a complete circle then

2πr = R

 $\Rightarrow r = \frac{R}{2\pi}$ Resistance of each semicirle $\pi R = R$

$$= \pi r = \frac{\frac{\pi R}{2\pi}}{A} = \frac{\frac{R}{2}}{B}$$

Thus, net resistance in parallel combination of two semicircular resistances

$$R' = \frac{\frac{R}{2} \times \frac{R}{2}}{\frac{R}{2} + \frac{R}{2}} = \frac{\frac{R^2}{4}}{R} = \frac{R}{4}$$

37. In stretching, specific resistance remains unchanged. After stretching, specific resistance (ρ) will remain same. Original resistance of the wire,

0	r
o	L

or
or
or
or
or
or
or
or
or

$$R = \frac{\rho I}{A}$$
or

$$R \approx \frac{1}{A}$$
or

$$R \approx \frac{\rho I}{A}$$
or

$$R \approx \frac{\rho I}{V}$$
(as

$$R \approx \frac{(I+10\% I)^{2}}{V}$$
(as

$$\frac{R'}{R} = \frac{\left(I+\frac{10}{100}I\right)^{2}}{I^{2}}$$

$$\frac{R'}{R} = \frac{\left(\frac{1}{10}I\right)^{2}}{I^{2}} = \frac{121}{100}$$
or
or
or
or

$$R' = 1.21 R$$

38. Heat evolved due to joule's effect is used up in boiling water. As per key idea

> ms∆T VI VIt = ms∆T or t = Putting under given values I = 4 Å, V = 220 volt, m = 1 kg, $\Delta T = (100 - 20)^{\circ} C$, s = 4200 J/kg°C $1 \times 4200 \times 80$ 220×4 :. t = = 6.3 min

SECTION (C)

In an electric circuit containing a battery, the positive charge inside the battery may go from the positive 1. terminal to the negative terminal

V = AI)

2. (a)
$$V = E - ir$$
, $V < E$ (b) $V = E + ir$, $V > E$ (c) $V = E$ (d) $V = E$
3. $\eta = \frac{E - Ir}{E} - \frac{r}{r + R} = \frac{R}{r + R} = 0.6 \Rightarrow R = 0.6 r + 0.6 R$
 $r = \frac{4}{6} R = \frac{2R}{3}$
 $\frac{6R}{r + 6R} = \frac{6R}{\frac{2R}{3} + 6R} = \frac{18R}{2R + 18R}$
 $\eta = 0.9 = 90\%$
4. Power of electric bulb
 $V^2 P = \frac{V^2}{R}$
So, resistance of electric bulb
 $\frac{V^2}{R} = \frac{V^2}{P}$
Given, P1 = 25W P2 = 100W, V1 = V2 = 200V
Therefore, for same potential difference V,
 $R \propto \frac{1}{P}$

Thus, we observe that for minimum power, resistance will be maximum and vice-versa. Hence, resistance of 25W bulb is maximum and 100W bulb is minimum.

5. Power p =
$$\frac{\sqrt{2}}{R}$$

 $\therefore p \propto \frac{1}{R}$
 $\therefore p \propto \frac{1}{R}$
 $\therefore \frac{p_1}{p_2} = \frac{R_2}{R_1} = \frac{2}{1} \implies p_1 : p_2 = 2 : 1$
 $R_1 = 10\Omega$
 $10V \longrightarrow R_2 = 20\Omega$
 $10V \longrightarrow R_3 = 30\Omega$
7. $\frac{V-10}{10} + \frac{V-6}{20} + \frac{V-5}{30} = 0$
 $6V - 60 + 3V - 18 + 2V - 10 = 0 \implies 11V = 88 \implies V = 8V$
current in resistance R1 is = $\frac{10-8}{10} = 0.2$ amp
 $\frac{20V}{A} \longrightarrow \frac{\epsilon}{2} = \frac{20+\epsilon}{C} \longrightarrow \frac{r}{B}$

Potential at C point is greater than potential at point B. Therefore current flow in resistance from B to A.

10. Internal resistance of the cell is given by

$$r = \begin{pmatrix} E - V \\ V \end{pmatrix} R$$

Given, E = 1.5V, V = 1.0V, R = 2Ω
$$\therefore r = \begin{pmatrix} 1.5 - 1.0 \\ 1.0 \end{pmatrix} \times 2 = \frac{0.5}{1.0} \times 1.0\Omega$$

11. Power p = $\frac{V^2}{R}$ ∴ p ∝ $\frac{1}{R}$

$$\therefore \qquad \frac{p_1}{p_2} = \frac{R_2}{R_1} = \frac{2}{1}$$
$$p_1 : p_2 = 2 : 1$$

13. Power p =
$$\frac{V^2}{R}$$

 $\therefore \quad p \propto \frac{1}{R}$
 $\therefore \quad \frac{p_1}{p_2} = \frac{R_2}{R_1} = p_1 : p_2 = 1 : 2$

14. Here : Resistance $R = 80\Omega$

 $\frac{1}{2}$

V = 200 VVoltage Time t - 2 hr The relation of power is given by = power x time $= 500 \times 2 = 1000$ Wh 15. From Joule's law, $H = i_2 Rt$ H = 80 J, i = 2A, t = 10s 80 $R = \overline{4 \times 10} = 20$ $80 = (2)_2 \times R \times 10$ ⇒ :. 16. Given, $R = 6 \Omega$, t = 10 min = 600 sv = 120 volt $\sqrt{2}$ Energy liberated = \overline{R} .t $120 \times 120 \times 600$ 6 = $= 144 \times 10_4 J$ = 14.4 × 10₅ J Using the formula P = R17. ...(i) Where R is resistance of wire, V is voltage across wire and P is power dissipation in wire and ρl R = A...(ii) From Eqs. (i) and (ii) V^2 V^2 $P_1 = \overline{\rho \ell / A} = \overline{\rho \ell}$. A V^2 $P_1 = \overline{\rho \ell}$. A ...(iii) In 2nd case Let R₂ is net resistance. $R \times R$ R $R_2 = \overline{R + R} = \overline{2}$ Where, R is the resistance of half wire. l 2 ρl = 4A R₂ = A.2 ... V^2 $P_2 = \rho \ell \cdot 4A$:. ... (iv) Hence, from Eqs. (iii) and (iv) $\frac{\frac{P_2}{P_1}}{\frac{P_1}{P_1}} = \frac{4}{1}$ P_1 1 $\overline{P_2} = \overline{4}$ Ans. $=\frac{(220)^2}{1000}$ V^2 R = P 1000 18. Where, V and P are denoting rated voltage and power respectively.

:.
$$P_{consumed} = \frac{V^2}{R} = \frac{110 \times 110}{220 \times 220} \times 1000 = 250 \text{ watt Ans}$$

19. Let time taken in boiling the water by the heater is t sec. Then

Pt 836 4.2 t = 1 × 1000 (40° – 10°) J Q = ms∆T = ms∆T ⇒ \rightarrow $1000 \times 30 \times 4.2$ 836 836 $4.2 t = 1000 \times 30$ = 150 second Ans. \rightarrow t = V^2 V^2 200×200 100 P = RР 20. $R_{hot} =$ = 400 Ω ÷ 400 $R_{cold} = 10 = 40 \Omega$ Ans. 21. $P = V_2/R$, putting values we get $R = (22)_2$ ohm

- When operated at 110 V, $P' = (110)_2/R = 25$ watt
- 22. KCL is based on conservation of charge and KVL is based on conservation of energy
- 23. Let R₁ and R₂ be the resistances of the coils, V the supply voltage, H the heat required to boil the water. $V^2 t_1$
 - R_1 For first coil, H =(i) $V^2 t_2$ For second coil, $H = R_2$(ii) Equating Eqs. (i) and (ii), we get $t_1 t_2$ R_2 40 $R_1 = R_2$ $R_1 = t_1 = 10$ = 4 i.e.. $R_2 = 4R_1$ (iii) when the two heating coils are in parallel, R_1R_2 $R_1 \times 4R_1$ 4R₁ $R = R_1 + R_2 = R_1 + 4R_1 = 5$ V_t^2 and H = R.....(iv) Comparing Eqs. (i) and (iv) we get V²t₁ V^2 t $R_1 = R$ R 4 \Rightarrow t = $\overline{R_1}$ xt₁ = $\overline{5}$ x10 = 8 min. Let, P1 = 100W, P2 = 100W, V = 220 volt V^2 V^2 $P_1 = \overline{R_1}$ and $P_2 = \overline{R_2}$ V^2 $220 \times 220 \Omega$ $(220)^2$ $(220)^2$ 220×220 100 _ P_1 100 100 100 ∴ R1 = Ω = and $R_2 =$ Case I : When two bulbs are connected in series.



25. Watt-hour efficiency of a battery is the ratio of output energy to the input energy. Input energy when the battery is charged

= Vit = 15 x 10 x 8 = 1200 W-h Energy released when the battery is discharged = 14 x 5 x 15 = 1050 W-h Hence, W-h efficiency of battery is given by $\frac{\text{energy output}}{\text{energy input}} = \frac{1050}{1200} = 0.875 = 87.5\%$

Since, power rating of bulb in both the countries India and USA should be same, so

$$\frac{V_1^2}{R_1} = \frac{V_2^2}{R_2} \qquad \Rightarrow \qquad \frac{220 \times 220}{R_1} = \frac{110 \times 110}{R_2}$$

$$\Rightarrow \qquad \frac{R_2}{R_1} = \frac{110 \times 110}{220 \times 220} \qquad \Rightarrow \qquad R_2 = \frac{R}{4} (\because R_1 = R)$$

27. Power $P = i_2 R$

$$\Rightarrow R = \frac{F}{i^2}$$
Given, P = 1 W, i = 5A

$$\frac{1}{(5)^2} = 0.040$$

- 28. Kirchhoff' first law is junction rule, according to which the algebraic sum of the currents into any junction is zero. The junction rule is based on conservation of electric charge. No charge can accumulate at a junction, so the total charge entering the junction per unit time must equal to charge leaving per unit time. Kirchhoff's second law is loop rule according to which the algebraic sum of the potential difference in any loop including those associated emf's and those of resistive elements, must equal to zero. This law is basically the law of conservation of energy.
- 29. In series order, the resistance of three bulbs must be added to give resultant resistance of the circuit. Let R1, R2 and R3 are the resistances of three bulbs respectively. In series order

 $\alpha = \frac{54}{900 \times 30}$

= 500 degree-1

$$R = R_1 + R_2 + R_3$$
$$V^2$$

but R = P and supply voltage in series order is the same as the rated voltage.

$$\therefore \frac{V^2}{P} = \frac{V^2}{P_1} + \frac{V^2}{P_2} + \frac{V^2}{P_3}$$

or $\frac{1}{P} = \frac{1}{60} + \frac{1}{60} + \frac{1}{60}$ or $P = \frac{60}{3} = 20 \text{ W}$

SECTION (D)

1. (1) $\begin{aligned} R_1 &= R_{01} \, (1 + \alpha_1 \, \Delta \theta) = 600 \, (1 + 0.001 \times 30) = 618 \, \Omega \\ R_2 &= R_{02} \, (1 + \alpha_2 \, \Delta \theta) = 300 \, (1 + 0.004 \times 30) = 336 \, \Omega \\ R_{eq} &= R_1 + R_2 = 618 + 336 = 954 \, \Omega \end{aligned}$

(b) $R_{eq} = R_{0eq} (1 + \alpha_{eq} \Delta \theta)$ 954 = 900 (1 + α 30)





113 | Page



21. The given circuit (between A and B) is a balanced Wheatstone's bridge.Therefore, resistance between C and D is ineffective.

The resistances 2R and 2R are in parallel, so, effective resistance



22. The figure can be shown as equivalent resistance of R_1 , R_2 and R_3

23.

Resistance
$$R = P$$

1

 V^2

R∝ P

So, the resistance of 40 watt is maximum, heat produced $H \propto R$

 \therefore heat produced in 40 watt bulb will be maximum, so it will gllow more.

<u>P R</u>

24. In a Wheatstone's bridge, if $\overline{Q} = \overline{S}$, then resistance of galvanometer will be inaffective. The given circuit can be shown as,

Therefore, the galvanometer will be ineffective.

The above wheatstone's bridge can be redrawn as.

$$\begin{bmatrix} 10\Omega & 10\Omega \\ P & Q \\ R & S \\ 10\Omega & 10\Omega \end{bmatrix}$$
Resistances P and Q are in series, so
$$R' = 10 + 10 = 20 \Omega$$
Resistances R and S are in series, to
$$R'' = 10 + 10 = 20\Omega$$
Now, R' and R'' are in parallel hence, net resistance of the circuit
$$\frac{R' \times R''}{R' + R''} = \frac{20 \times 20}{20 + 20} = 10\Omega$$

25. As there is no change in the reading of galvanometer with switch S open or closed. It implies that bridge is balanced. Current through S is zero and I_R , = I_G , $I_P = I_Q$.

Current Electricity

26. The given circuit can be shown in the following way. No current will be flown in the middle resistance. Equivalent resistance of R and R' = 2R

= 1.6 amp







 $R_{AB} = \frac{8 \times 8}{8 + 8} = 4\Omega$ From equipotential point



Y

$$R_{eq.} = 3$$

Х R 32. rR R = 2r + r + R $R_2 - 2rR - 2r_2 = 0$ ⇒ $R = (1 + \sqrt{3})R$ ⇒ 33. Due to equi potentional points R = R + R = 2R 34. $P = i_2 R$ current is same, so $P \propto R$ 2 In the first case it is 3r, in second case it is $\overline{3}$ r, in third case it is $\overline{3}$ and in fourth case the net resistance Зr $\frac{1}{2}$ $P_3 < P_2 < P_4 < P_1$ $R_3 < R_2 < R_4 < R_1$:. V^2 V^2 R 35. P so R = V² $R_1 = 100$ $R_2 = R_3 = 60$ ÷ and (250)² $W_1 = (R_1 + R_2)^2 \cdot R_1$ Now $(250)^2$ $W_2 = \overline{(R_1 + R_2)^2} \cdot R_2$ $(250)^2$ $W_3 = R_3$ and $W_1 : W_2 : W_3 = 15 : 25 : 64$ $W_1 < W_2 < W_3$ or $\frac{V_1}{V_2} = \frac{R_1}{R_2} = \frac{4}{1}$ $4\pi r^2$ R₁ Δ $V_{BC} = 4V_{AB}$ A₁ πr^2 = 1 36. ... 37. Here: Resistance of arm PQ (R_1) = 100 Ω Resistance of arm QR (R_2) = 100 Ω Resistance of arm RS (R_3) = 100 Ω Resistance of arm SP (R_4) = 100 Ω Resistance of upper arm R1 and R2 are connected in series. Hence, their resultant resistance $R_{U} = R_{1} + R_{2} = 100 + 100 = 200 \ \Omega$ Similarly the resistance of lower half R3 and R4 are also connected in series Hence, their resultant resistance is $R_L = R_3 + R_4 = 100 + 100 = 200 \Omega$ So, equivalent resistance $=\frac{1}{R_{\rm U}}+\frac{1}{R_{\rm L}}=\frac{1}{200}+\frac{1}{200}=\frac{2}{200}=\frac{1}{100}$ R_{PR} So, $R_{PR} = 100 \Omega$

38. The equivalent resistance of the circuit

39.

40.

 $\left(\frac{4\times 2}{4+2}\right)_{+2=}$ $\frac{8}{6}_{+2=}$ $\frac{20}{6}_{+2=}$ R = 10 3_Ω = Current through the circuit ÷ 2 6 3 V $i = \frac{1}{R} = \frac{1}{10/3} = \frac{1}{10} = \frac{1}{5}$ A Therefore, potential difference across BC 3 (<u>4</u>×2) $V = \frac{1}{5} \left(\frac{1}{4+2} \right)$ = 0.8 volt Let R1 and R2 be the resistances of two wires . In parallel combination, R_1R_2 6 $\overline{R_1 + R_2} = \overline{5}$... (i) If one of the wires breaks, then effective resistance becomes 2Ω , that is , $R_1 = 2\Omega$ Substituting in Eq. (i), we have $2R_2$ 6 $2 + R_2 - \overline{5}$ $10R_2 = 12 + 6R_2$ $4R_2 = 12$ ⇒ 12 $R_2 = 4 = 3 \Omega$:. In the given circuit, the ratio of resistances in the opposite arms is same Ρ 10 1 $\overline{Q} = \frac{11}{10} = \frac{1}{1}$ R 10 1 $\overline{S} = \overline{10} = \overline{1}$ Hence bridge is balanced. The given circuit now reduces to 10Ω 10Ω -• B 10Ω 10Ω Here, 10Ω and 10Ω resistors are in series in both arms, therefore, reduced circuit is shown 20Ω • B ~~~~ 20Ω Now, the two 20 Ω resistors are connected in parallel, hence equivalent resistance is $\frac{1}{R} = \frac{1}{20} + \frac{1}{20} = \frac{4}{20 \times 20} = \frac{1}{10}$ R = 10 Ω

41. The bridge formed with given resistances is a balanced Wheatstone's bridge. The situation can be depicted as shown in figure. As resistances S and 6 Ω are in parallel their effective resistance is



42. In the given circuit,

$$\frac{\mathsf{R}}{\mathsf{R}} = \frac{\mathsf{R}}{\mathsf{R}} \qquad \qquad \left(\frac{\mathsf{P}}{\mathsf{Q}} = \frac{\mathsf{R}}{\mathsf{S}}\right)$$

Therefore, it is a balanced Wheatstone bridge, and no current will flow through resistance between B and D.

Resistance of arm ADC R' = R + R = 2RResistance of arm ADC.

$$R^{"} = R + R = 2R$$

: Now, resistance R' and R" are in parallel.

Therefore, their resultant resistance

$$\frac{\frac{1}{R_{eq}}}{\frac{1}{2R}} = \frac{1}{2R} + \frac{1}{2R} = \frac{1}{R} \therefore R_{eq} = R$$

- **43.** In series $R = R_1 + R_2$
- $\Rightarrow \frac{2\ell}{\sigma A} = \frac{\ell}{\sigma_1 A} + \frac{\ell}{\sigma_2 A}$ $\frac{2}{\sigma} = \frac{1}{\sigma_1} + \frac{1}{\sigma_2}$ $2\sigma_1 \sigma_2$ $\sigma_1 + \sigma_2$ 2 so. $\overline{\sigma} = \sigma_1 \sigma_2$ $\sigma = \sigma_1 + \sigma_2$ so 15² R_{eq} = 150(i) 44. 2R $R_{eq} = 2 + R$(ii) Solving (i) and (ii), $R = 6 \Omega$ Ans. 3 3 - = 2 6×3 6+3 45. i = = 1.5 A 46. ∴ 2Ω and 6Ω are in parallel $\Rightarrow \mathsf{Req} = \frac{3 \times (1.5 + 1.5)}{3 + (1.5 + 1.5)} = \frac{3}{2}\Omega$ $i = \overline{R_{eq}} = 4A$ ⇒ Ans. $R_1 + R_2 = S$ $\frac{R_1 R_2}{R_1 + R_2} = P$ 47. $s = np \Rightarrow (R_1 + R_2)_2 = n R_1R_2$ $\left(\frac{R_1}{R_2} + \frac{R_2}{R_1} + 2\right)$ Nmin = 2 + 2 = 4 **Ans.** ⇒ ⇒



52. The balanced condition of wheat-stone's bridge is

R_{AB} R_{AD}

 $R_{BC} = R_{DC}$

As bridge is in balanced condition, no current will flow through BD.

 $R_{1} = R_{AB} + R_{BC}$ = R + R = 2R R₂ = RAD + RCD = R + R = 2R R₁ and R₂ are in parallel combination. Hence, equivalent resistance between A and C will be.

$$\therefore R_{eq} = \frac{R_1 R_2}{R_1 + R_2} = \frac{4R^2}{4R} = R$$

53. Equivalent resistance of n resistances each of r ohm in parallel is given by

 $\begin{array}{ccc} \frac{1}{R} & \frac{1}{r} & \frac{1}{r} & \frac{1}{r} & \frac{n}{r} \\ \text{so, } r = nR \\ \text{When these resistances are connected in series, effective resistance is} \\ R' = r + r & + \dots + n \text{ times } = nr \\ R' = n (nR) = n_2R \end{array}$

54. The given circuit can be redrawn as shown. From circuit,



$$\frac{FC}{CE} = \frac{FD}{DE} = 1$$

 ΓC

Thus, it is balanced Wheastone's bridge, so resistance in arm CD is ineffective and so, current do not flows in this arm.

Net resistance of the circuit is

$$\frac{1}{R'} = \frac{1}{(R+R)} + \frac{1}{(R+R)} = \frac{1}{2R} + \frac{1}{2R} = \frac{2}{2R} = \frac{1}{R}$$

$$\therefore R' = R$$

So, net current drawn from the battery

$$\frac{V}{R'} = \frac{V}{R}$$

As from symmetry, upper circuit AFCEB is half of the whole circuit and is equal to AFDEB. So, in both the halves half of the total current will flow.

Hence, in AFCEB, the current flowing is

$$i = \frac{i'}{2} = \frac{V}{2R}.$$

 $\frac{4}{2}$ $\frac{2}{2}$

55. The circuit given resembles the balanced Wheatstone Bridge as $\overline{6} = \overline{3}$. Thus, middle arm containing 4Ω resistance will be ineffective and no current flows through it. 56.

The equivalent circuit is shown as below : Net resistance of AB and BC $R' = 4 + 2 = 6\Omega$ Net resistance of AD and DC $R'' = 6 + 3 = 9\Omega$ Thus, parallel combination of R' and R" gives $R' \times R''$ $R = \overline{R' + R''}$ 6×9 54 18 $=\overline{6+9} = \overline{15} = \overline{5}$ Hence, current i = $\frac{V}{R} = \frac{V}{18/5} = \frac{5V}{18}$ Current will flow from higher to lower potential. Resistance 4Ω and 4Ω are connected in series, so their effective resistance is $R' = 4 + 4 = 8\Omega$ Similarly, 1Ω and 3Ω are in series So, $R'' = 1 + 3 = 4\Omega$ Now R' and R" will be in parallel, hence effective resistance 8×4 32 $R' \times R''$ 8 $\mathsf{R} = \overline{\mathsf{R}' + \mathsf{R}''} = \overline{\mathsf{8} + \mathsf{4}} = \overline{\mathsf{12}} = \overline{\mathsf{3}}_{\mathsf{0}}$ Current through the circuit, from Ohm's law 3V V $i = \overline{R} = {}^8 A$ Let currents i1 and i2 flow in the branches as shown. $8i_1 = 4i_2$. $i_2 = 2i_1$ \rightarrow 3V . В д 8 $= i_1 + 2i_1$ Also $i = i_1 + i_2$ 4 Δ and 8 _ Potential drop at A. $V_A = 4 \times i_1 =$ Potential drop at B, $V_B = 1 \times i_2 = 1 \times \overline{4} = \overline{4}$ Since, drop of potential is greater in 40 resistance so. It will be at lower potential than B, hence on connecting wire between points A and B, the current will flow from B to A.

57. Resistances 1Ω and 3Ω are connected in series, so effective resistance

 $R' = 1 + 3 = 4\Omega$

Now, R' and 8Ω are in parallel. We known that potential difference across resistances in parallel order is same

my 4Ω

30

R

ЧЬ

40



or
$$i_1 = \frac{8}{4}$$
 $i_2 = 2i_2$ (i)
Power dissipated across 8Ω resistance is
 i_{22} (8) $t = 2W$
or $i_{22}t = \frac{8}{8} = 0.25 W$ (ii)
Power dissipated across 3Ω resistance is
 $H = i_{12}$ (3) t
 $= (2i_2)_2$ (3) t
 $= 12i_{22} t$
but $i_{22}t = 0.25 W$
 \therefore $H = 12 \times 0.25 = 3W$

58. The resistances of 6Ω and 3Ω are in parallel in the given circuit, their equivalent resistance is

 $\frac{1}{R_1} = \frac{1}{6} + \frac{1}{3} = \frac{1+2}{6} = \frac{1}{2}$ or $R_1 = 2\Omega$ Again, R_1 is in series with 4Ω resistance, hence $R = R_1 + 4 = 2 + 4 = 6 \Omega$ Thus, the total power dissipated in the circuit $\frac{V^2}{P} = \frac{R}{R}$ Here, $V = 18 \text{ V}, R = 6 \Omega$ Thus, $p = \frac{(18)^2}{6} = 54 \text{ W}$

59. The bridge formed with given resistances is a balanced Wheatstone's bridge. The situation can be depicted as shown in figure.

As resistance S and 6 Ω are in parallel their effective resistance is

$$\frac{6S}{6+5}_{\Omega}$$

Hence it is balanced, hence, it is balanced Wheatstone's bridge. balancing condition,

or

$$\frac{P}{Q} = \frac{R}{\left(\frac{6S}{6+5}\right)}$$

$$\frac{2}{2} = \frac{2(6+5)}{6S}$$
or

$$3S = 6+5$$
or

$$S = 3 \Omega$$

For

60. Voltage across 2Ω is same as voltage across arm containing 1Ω and 5Ω resistances. Voltage across 2Ω resistance,

 $V = 2 \times 3 \ 6 \ V$ So, voltage across lowest arm, $V_1 = 6V$ Current across 5 Ω , I = $I = \frac{6}{1+5} = 1A$ Thus, power across 5 Ω , P = I₂R = (1)₂ × 5 = 5W

61. In parallel resistances potential difference across them is same.



SECTION (E)

1.
$$E_{eq} = \frac{\frac{E_1}{r_1} + \frac{E_2}{r_2}}{\frac{1}{r_1} + \frac{1}{r_2}} = \frac{E_1 r_2 + E_2 r_1}{r_1 + r_2}$$
 $r_{eq} = \frac{r_1 r_2}{r_1 + r_2}$

Therefore statement II is correct bul I is wrong.

2. Assume M cells are connected correct and N cells connected wrong. M + N = 12.....(1) ~

(M + 2) E – NE = 3R	⇒	$M - N + 2 = \frac{\frac{3R}{E}}{2R}$	(2)
ME - (N + 2)E = 2R	\Rightarrow	M - N - 2 = E	(3)
-M + N + 10 = 0 from eq. (1) and (4)	⇒	M – N = 10	(4)
M = 11, N = 1			

3. It is clear that the two cells oppose each other hence, the effective emf in closed circuit is 18 - 12 = 6Vand net resistance is $1 + 2 = 3\Omega$ (because in the closed circuit the internal resistances of two cells are in series).

The current in circuit will be in direction of arrow shown in figure.



effective emf

I = total resistance 3 = 2A

The potential difference across V will be same as the terminal voltage of either cell. Since, current is drawn from the cell of 18 volt, hence,

 $V_1 = E_1 - ir_1$ $= 18 - (2 \times 2) = 18 - 4 = 14 \text{ V}$ Similarly, current enters in the cell of 12V hence $V_2 = E_2 + ir_2$ $= 12 + 2 \times 1$ = 12 + 2 = 14 V Hence, V = 14V



7. Let emf of both cells are E_1 and E_2 and internal resistances are r_1 and r_2 . In parallel order, we have $E = E_1 = E_2$

Effective internal resistance of both cells

 $\frac{1}{R} = \frac{1}{r} + \frac{1}{r}$ $R = \frac{r}{2}$

So, emf is equal to the emf of any of the cell and internal resistance is less than the resistance of any of cell.

Hence, (ii) is right and (i) is wrong.

 $R_{eq} = R_1 + R_1 + R$ $\frac{2E}{R_1 + R_2 + R}$ $\therefore I = \frac{R_1 + R_2 + R}{R_1 + R_2 + R}$ According to the questions, $V_A - V_B = E - IR_2$ $0 = E - IR_2$ $E = IR_2$

 \Rightarrow



$$E = \frac{2E}{R_1 + R_2 + R} R_2$$

$$R_1 + R_2 + R = 2R_2$$

$$R = R_2 - R_1 \quad Ans.$$
9.
$$V_R = 2V = \frac{\left(\frac{R}{500 + R}\right) \times 12}{R = 100 \Omega}$$
10.
$$E_{eq} = \frac{\left(\frac{5}{2} - \frac{2}{1}\right)}{\left(\frac{1}{2} + 1\right)} V \qquad r_{eq} = \frac{2 \times 1}{2 + 1} = \frac{2}{3} \Omega$$

$$i = \frac{E_{eq}}{10 + r_{eq}} = 0.03 \text{ A} \quad \text{from P2 to P1}$$



11. Current in the circuit is given by Ohm's law. Net resistance of the circuit = $r_1 + r_2 + R$ Net emf in series = E + E = 2E

> Therefore, from Ohm's law, current in the circuit $i = \frac{\frac{\text{Net emf}}{\text{Net resistance}}}{\frac{2E}{r_1 + r_2 + R}} \Rightarrow 2r_1 = r_1 + r_2 + R$

 \therefore R = external resistance = r₁ - r₂

Note: The question is wrong as the statement is when the circuit is closed, the potential difference across the first cell is zero which implies that in a series circuit, one part cannot conduct current which is wrong, Kirchhoff's law is violated. The equation must have been modified.

SECTION (F)

1.
$$R_{eq} = 200 + \frac{300 \times 600}{300 + 600} + 100 = 500 \Omega$$
$$I = \frac{100}{500} = \frac{1}{5} \text{ amp}$$
$$\frac{\frac{1}{600}}{\frac{1}{300} + \frac{1}{600}} \times \frac{1}{5} = \frac{1}{15} \text{ amp}$$
Reading of volt meter = I R₆₀₀ = $\frac{1}{15} \times 600 = 40 \text{ V}$
2.
$$R_{eq} = 2 + \frac{4}{2} + \frac{15}{3} + R_A = 9 + R_A$$
$$\frac{\frac{V}{I} = \frac{V}{R_{eq}}}{R_{eq}} \Rightarrow 1 = \frac{10}{9 + R_A} \Rightarrow R_A = 1\Omega$$
if 4Ω replace by 2Ω resistance then
$$R_{eq} = 2 + \frac{2}{2} + \frac{15}{3} + 1 = 9\Omega$$



Potential gradient = $\frac{V}{\ell} = \frac{IR}{\ell} = \frac{2 \times 0.5}{1} = 1$ 13. 3 $r_{eq} = 10 + 20 = 30$, $I = \frac{3}{30} = \frac{1}{10}$, $V = \varepsilon - IR = 3 - \frac{1}{10} \times 10 = 2$ 14. Potential gradient = $\overline{\ell} = \overline{10} = 0.2$ 15. $V = 2 \times 0.1 = 0.2 V$ $\frac{V}{1} = 0.2$ $I = \frac{V}{0.2} = \ell$ = 1 m Potential gradient = $V = 2 \times 0.1 = 0.2 V$ 1.5 5 Potential gradient = ℓ = 7.5 16. Voltage across resistor = $IR = 3.5 \times 0.2 V$ $\frac{1}{5} = 0.2 \times$ 3.5 ℓ = 3.5 m 17. $V \propto \ell$ $\ell \propto R$ $\frac{\ell_1}{\ell_2} = \frac{\mathsf{R}_1}{\mathsf{R}_2}$ $\frac{50}{\ell} = \frac{4+4}{4}$

- **18.** Potentiometer is used to measure the exact potential difference between two points of an electric circuit or to measure the emf of a cell.
- **19.** The voltmeter in an electric circuit is always connected in parallel. Therefore, for resistance of circuit to be minimum, the resistance of voltmeter should be high. The resistance of ideal voltmeter is infinite.
- **20.** Ammeter has low resistance and voltmeter has very high resistance. So, ammeter can be converted into series.
- 21. According to formula of potentiometer

$$\frac{I_1 - I_2}{I_1 - I_2}$$
 125 - 100

$$r = I_2 \times R = 100 \times 2 = 0.5 \Omega$$

- 22. When we measure the emf of a cell by the potentiometer then no current draws in the circuit in zero-deflection condition i.e., cell is in open circuit. Thus, in this condition the actual value of a cell is found. In this way potentiometer is equivalent to an ideal voltmeter of infinite resitance. NOTE : The emf by the potentiometer is measured from null method in which zero deflection position is found on the wire.
- **23.** To increase the range of voltmeter, resistance will have to increase.
- **24.** Potential gradient of a wire equal to potential fall per unit length.

Potential gradient = Potential fall per unit length = Current × Resistance per unit length = i × ℓ but $R = \frac{\rho \ell}{A} \implies \frac{R}{\ell} = \frac{\rho}{A}$ \therefore Potential gradient = i × $\frac{\rho}{A}$ Here, $\rho = 10-7 \ \Omega-m$, i = 0.1 A × A = 10-6 m₂ Hence, potential gradient = 0.1 x $\frac{10^{-7}}{10^{-6}} = \frac{0.1}{10} = 0.01 = 10_{-2}$ V/m

25. In electrolysis, according to first law of Faraday, the mass of a substance deposited at an electrode is directly proportional to the charge passed through the electrolyte i.e., $m \propto a$

If a current i passes for a time t, then as we know,

∝i

Hence,
$$\dot{m} \propto it$$
 or m

Thus, mass deposited at an electrode is directly proportional to current.



27.

Equaivalent resistance decrease so current will increases.

$$V_A + V_V = V$$

Due to change, $V_{\mbox{\tiny A}}$ increases so voltmeter reading will decrease.

AC

- 28. The ratio ^{CB} will remain unchanged.
- **29.** When we have to convert galvanometer into an ammeter, we connect a small resistance in parallel with the coil of galvanometer, whose value depends upon the range of the ammeter.
- 30. Sensitivity of potentiometer

$$\frac{1}{\infty}$$
 potential gradient

But potential gradient = L

Where, v is the emf of the cell and L is the length of the wire.

: Sensitivity of a potentiometer $\propto L$ Sensitivity of a potentiometer can be increased by increasing the length of the potentiometer wire.

- **31.** The wire of potentiometer is of manganin because its resistivity is very high and temperature coefficient of resistivity is low.
- 32. Voltmeter has high resistance. So, option is (3) 9A S 10A 1A 0.81Ω $0.8 \times 1 = 9$ S \Rightarrow S = 0.09 Ω

34. Potential gradient =
$$\frac{E}{100}$$
 V/cm \Rightarrow e.m.f. of battery = 30 x $\frac{E}{100}$
 $\frac{x}{20} = \frac{y}{20}$

35. $20 \quad 80 \qquad \Rightarrow \qquad 4x = y \Rightarrow \qquad$ New position of null point will be at the mid point.



$$r = \left(\frac{\ell_1 - \ell_2}{\ell_2}\right)_{R \Rightarrow} = \frac{240 - 120}{120} \times 2 = 2\Omega \quad \text{Ans.}$$

37. $I_a = 15 \text{ mA}$ Vg = 75 mV Vg Galvanometer resistance, $G = I_g = 5\Omega$ Required. full scale deflection voltage = 150 V -^////____ -G) ١, R -150V- $150 = I_q (R + G)$ R = 9995 Ω Ans. ⇒ 55 R

38. $\overline{20} = \overline{80} \Rightarrow R = 220 \Omega$

39. A galvanometer has its own resistance low but a voltmeter must have high resistance. A voltmeter indeed is a modified from of a pivoted coil galvanometer. Since the resistance of coil of galvanometer of its own is low, its resistance is to be increased as is a necessary condition for a voltmeter. For this an appropriate high resistance should be connected in series with the galvanometer as shown.



Note : The resistance of an ideal voltmeter should be infinite.

40. To convert a galvanometer into voltmeter, high resitance should be connected in series with it. Let R is the resistance connected in series with the galvanometer.

$$\frac{V}{i_{g}} = \frac{V}{G+R} \text{ or } R = \frac{V}{i_{g}} - G$$

Given, G = 50Ω,
 $i_{g} = 25 \times 4 \times 10^{-4} = 10^{-2} \text{ A}, V = 25V$
 $\therefore R = \frac{25}{10^{-2}} - 50 = 2500 - 50 = 2450\Omega$

- **41.** To work as voltmeter, the resistance of galvanometer should be high.
 - A voltmeter indeed is a modified form of a pivoted coil galvanometer. Since, the resitance of coil of galvanometer of its own is low, hence to convert a galvanometer into a volmeter, its resitance is to be increased. For this an appropriate high resistance is joined in series with the galvanometer as shown in figure.



The value of this resistance to be connected depends on the range of the voltmeter. **Note:** A voltmeter is always connceted in parallel in an electric circuit.

42. The potential difference across ammeter and shunt is same. Let i_{α} is the current flowing through ammeter and i is the total current. So, a current i – i_a will flow through shunt resistance.

Potential difference across ammeter and shunt resistance is same.



43. 3



Current for 30 divisions = 10_{-3} A

 $30 \times 20 = 3 \times 10^{-3} \text{ A}$ Current for 20 divisions = For the same deflection to obtain for 20 division, let resistance added be R

2

$$\frac{2}{3} \times 10^{-3} = \frac{3}{(50 + 1R)}$$
 ⇒ R = 4450 Ω

44. This problem is based on the application of potentiometer in which we find the internal resistance of a cell.

In potentiometer experiment in which we find internal resistance of a cell, let E be the emf of the cell and V the terminal potential difference, then where I1 and I2 are lengths of potentiometer wire with and without short circuited through a resistance.

$$\frac{E}{V} = \frac{I_1}{I_2} \sum_{\text{Since, }} \frac{E}{V} = \frac{R+r}{R} [:: E = I (R+r) \text{ and } V = IR] :: \frac{R+r}{R} = \frac{I_1}{I_2}$$
or
$$1 + \frac{r}{R} = \frac{110}{100} \text{ or } \frac{r}{R} = \frac{10}{100} \text{ or } r = \frac{1}{10} \times 10 = 1\Omega$$

$$EXERCISE \# 2$$

$$X = \frac{\varepsilon_0 L \frac{\Delta v}{\Delta t}}{I_1}$$

$$[X] = \frac{[\varepsilon_0][L] \left[\frac{\Delta v}{\Delta t}\right]}{[X] = [Electric field] [Length] = \frac{[Force]}{[charge]} [Length] = \frac{MLT^{-2}L}{Q} = MQ_{-1}L_2T_{-2}$$

 $[\varepsilon_0] = M_{-L_{-3}T_{412}}$ (as in question no. 6) = $M_{-1}L_{-3}Q_2T_2$





8. ° 2R ⊷ ₩₩

9.

12. 14. Current flow in 2R resistance is from right to left.

$$R = \frac{R/2 \times 2R}{R/2 + 2R} = \frac{2R}{5}$$

3

10. Current I can be independent of R₆ only when R₁, R₂, R₃, R₄ and R₆ form a balanced wheatstone bridge. $\frac{R_1}{R_1} = \frac{R_3}{R_1}$

Therefore $\overline{R_2}^{-} \overline{R_4}$ or $R_1 R_4 = R_2 R_3$

11. Condition for maximum power is

$$r = R$$

$$4 = \frac{\frac{6R \times 3R}{9R}}{9R} \Rightarrow R = 2$$

$$R_{AB} = \frac{9 \times 12}{9 + 12} + 7 = \frac{85}{7}$$

$$L \alpha \ell$$

 $L \rightarrow \text{total length}$ $\ell \rightarrow \text{balanced length}$ $\frac{L_1}{L_2} = \frac{\ell_1}{\ell_2} = \frac{400}{500} = \frac{100}{\ell_2} \implies \ell_2 = 125 \text{ cm}$

16. 60 Ω resistance and resistance of voltmeter 40 Ω are in parallel. \therefore Their effective resistance 60×40

 $\begin{array}{l} \mathsf{R}_1 = \overline{60 + 40} = 24 \ \Omega & \therefore \\ \mathsf{R}_t = 24 + 40 = \Omega \\ \mathsf{i} = \overline{\mathsf{R}_t} = \overline{64} = \overline{32} \\ \mathsf{i} = \overline{\mathsf{R}_t} = \overline{64} = 2.25 \ \mathsf{volt} \end{array}$ Total resistance of circuit Current in main circuit potential difference across 60 \Omega read by voltmeter, $\begin{array}{l} \mathsf{v} = \mathsf{i} \mathsf{R}_1 = \overline{32} \\ \mathsf{v} = \mathsf{i} \mathsf{R}_1 = \overline{32} \\ \mathsf{v} = \mathsf{i} \mathsf{R}_1 = 1 \end{array}$

$$H = \frac{V^2}{R_1} t_1 \Rightarrow \qquad R_1 = \frac{V^2}{H} t_1 \qquad ...(i)$$
For second filament

$$H = \frac{\sqrt{R_2}}{R_2} t_2 \implies R_2 = \frac{\sqrt{2}}{H} t_2 \qquad \dots (ii)$$
When placed in parallel
$$H = \frac{\sqrt{2}}{R_p} t_2 \implies R_p = \frac{\sqrt{2}}{H} t_p \qquad \dots (iii)$$
From Eqs. (i),(ii), (iii) we get
$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\Rightarrow \frac{H}{\sqrt{2}t_p} = \frac{H}{\sqrt{2}t_1} + \frac{H}{\sqrt{2}t_2} \implies \frac{1}{t_p} = \frac{1}{10} + \frac{1}{15} \implies t_p = 6 \text{ min.}$$

$$\frac{1}{R_p} = \frac{1}{R} + \frac{1}{R} + \frac{1}{R} = \frac{3}{R} \implies R_p = \frac{R}{3}\Omega$$

$$R_s = R + R = 2R\Omega$$

$$R_{ret} = R_P + R_s = 2R + \frac{R}{3} = \frac{7R}{3}\Omega$$

19. From the given figure, current through lower branch of resistance which are joined in series is $\frac{10}{10} = \frac{10}{10}$

$$i_1 = \frac{4+3}{7} A$$

Again current through upper branch of resistance which are also connected in series, si

$$=\frac{10}{8+6}=\frac{10}{14}$$
 A

Now, according to the Kirchhoff's voltage law

$$V_B - V_A = 8 \times i_2 - 4 \times i_1 = 8 \times \frac{10}{14} - 4 \times \frac{10}{7} = 0$$

20. The given circuit is redrawn as shown in the fig.

İ2



It is balanced Wheatstone bridge, therefore 10Ω resistance is ineffective. In the upper arm 4Ω and 8Ω are in series, their effective resistance is

similarly, in the lower arm resistances 2 Ω and 4 Ω are also in series their effective resistance is $R_L=2+4=6~\Omega$

Now, resistances R_U and R_L are in parallel. So, resultant resistant between points A and B is

$$R_{AB} = \frac{R_{U}R_{L}}{R_{U} + R_{L}} = \frac{12 \times 6}{12 + 6} = 4 \Omega$$

21. After adjoining two conductors, the circuit will acquire the form shown in the following figure. From symmetry considerations, we conclude that the central conductor will not be effective in electric charge

transfer. Therefore, if the initial resistane R_1 of circuit was 5 Ω , where resistance of each conductor is 1 Ω , the new resistance of the circuit will become



- **22.** The conduction electrons while moving towards the positive end of the conductor (responsible for the current in conductor) with the atoms/ions of the condcutor, which is produced as heat.
- **23.** The resistance of a wire of length ℓ and area of cross-section A is given by

$$R = \rho \overline{A}$$

Where ρ is specific resistane.

Also, $A = \pi r_2$, being radius of wire.

$$\frac{\overline{R_2}}{R_2} = \frac{\overline{r_1^2}}{r_1^2}$$
$$\frac{5}{R_2} = \frac{3^2}{9^2}$$

R₁

Given, $r_1 = 9 \text{ mm}$, $R_1 = 5 \Omega$, $r_2 = 3 \text{ mm}$ \therefore

Equivalent resistance of 6 wires each of resistance R₂ connected in parallel is

..

$$R' = \frac{R_2}{6} = \frac{45}{6} = 7.5 \,\Omega$$

24. As shown if i is the maximum current, then a part i_g should pass through G and rest $i - i_g$ through S. Potential across G and S is same, therefore

$$i_{g} \times G = (i - i_{g}) \times S \implies S = \frac{i_{g}G}{i - i_{g}}$$
Given, G = 400 Ω , i_{g} = 0.21 mA = 0.2 × 10-3 A,
 $i = 3A$

$$\therefore S = \frac{0.0002 \times 400}{3 - 0.0002} = 0.027 \Omega$$

25. The potential difference across ammeter and shunt is same. Let i₁ is the current flowing through ammeter and i si the total current. So, a current i – i₂ will flow through shunt resistane.



Potential difference across ammeter and shunt resistance is same.

ie,
$$i_a \times R = (i - i_a) \times S$$

or $S = \frac{\frac{i_a R}{i - i_a}}{100 \times 13}$... (i)
Given, $S = \frac{750 - 100}{100} = 2 \Omega$

- 26. $V \propto I \implies \frac{V}{E} = \frac{I}{L}$ Where, I = balance point ℓ = lenght of potentiometer wire $V = \frac{I}{L} = 0$ or $V = \frac{30 \times E}{100} = \frac{30}{100} = 1$
- 27. To increase the range of ammeter we have to connect a small resistane in parallel (shunt), let its value be R.

Apply KCL at junction to divide the current. Voltage across R = Voltage across ammeter



28. Accordintg to Kirchhoff's junction rule,



Sum of incoming currents

= Sum of out going currents 2 + 2 = 1 + 1.3 + I \therefore I = 1.7 A

29. If R is the resistance of the voltmeter and I current is flowing through it, then

V = IR or R =If now resistance connected in series is R', then

$$R + R' = \frac{3V}{1}$$

$$R + R' = 3R \quad \therefore \qquad R' = 2R$$

30. Resistances R, R and $\frac{R}{2}$ are in series, their resultant resistance, R' = R + R + $\frac{R}{2} = \frac{5R}{2}$ Resistances R' and $\frac{R}{2}$ are in parallel. Their resultant resistance $\frac{1}{R} = \frac{2}{5R} + \frac{2}{R} = \frac{2+10}{5R} = \frac{5R}{12}$

31. $R_4 = 40 \Omega$, in balanced condition

so. $R_{1} R'_{4} = R_{2} R_{3} \text{ so } R_{4}' = \frac{16 \times 24}{48} = 8 \Omega$ $\frac{40R}{40+R} \Rightarrow 8 R + 320 = 40 R$ so. $R = 10 \Omega = \text{Black, brown, brown in parallel with } R_{4}$

EXERCISE #3

PART-I

1. To convert a galvanometer to ammeter a small resistance is connected in parallel to the coil of the galvanometer.

Here, $G_1 = 60 \Omega$, $I_g = 1.0 A$, I = 5A $I_gG_1 = (I - I_g)S$ I_gG_1 1 $I - I_g = \overline{5 - 1} \times 60 = 15 \Omega$

S = Putting 15 Ω resistance in parallel.

2.

3. According to ohm's law

$$\frac{dV}{dI} = -r$$

and V = ϵ if I = 0 [As V + Ir = ϵ]
 \therefore Slope of the graph = -r and intercept = ϵ

- Apply Kirchhoff's second law also called loop rule. 4. The algebraic sum of the changes in potential in complete transversal of a mesh (closed loop) is zero i.e, $\Sigma V = 0$ Here $\epsilon_1 - (i_1 + i_2)R - i_1r_1 = 0$ If there are n meshes in a circuit, the number of independent equation in accordance with loop law will be (n-1).
- 5. 1 division $\equiv 1\mu A$

Current for
$$1^{\circ}C = \frac{40\mu\nu}{10} = 4\muA$$

 $1\mu A \equiv {}^{\circ}C = \frac{1}{4} = 0.25^{\circ}C.$

Since deflection in galvanometer is zero so current will flow as shown in the above diagram.

9.

10.

current
$$I = \frac{V_A}{R_1 + R} = \frac{12}{500 + 100} = \frac{12}{600} \Rightarrow$$
 So, $V_B = IR = \frac{12}{600} \times 100 = 2 V$
Resistance of bulb is constant
 $P = \frac{v^2}{R} \Rightarrow \frac{\Delta p}{p} = \frac{2\Delta v}{v} + \frac{\Delta R}{R} \Rightarrow \frac{\Delta p}{p} = 2 \times 2.5 + 0 = 5\%$
Let x is the resistance per unit legth then equivalent resistance
 $R_i = x \ell_i$

В $R_2 = x \ell_2$ $x\frac{\ell_1}{\frac{\ell_1}{\ell_2}+1}$ $\frac{(\mathbf{x}_1 \ell_1)(\mathbf{x}_2 \ell_2)}{\mathbf{x} \ell_1 + \mathbf{x} \ell_2} \quad \Rightarrow \quad \frac{8}{3} = \mathbf{x} \frac{\ell_1 \ell_2}{\ell_1 + \ell_2} \Rightarrow$ R_1R_2 R =(i) $R_1 + R_2$ ⇒ R₀ $= \mathbf{X}\ell_1 + \mathbf{X}\ell_2$ also $\left(\frac{\ell_1}{\ell_2} + 1\right)$ $= \mathbf{x} \left(\ell_1 + \ell_2 \right) = \mathbf{x} \ell_2$ 12 xl₁ $\frac{\frac{1}{\left(\frac{l_1}{l_2}+1\right)}}{Xl_2\left(\frac{l_1}{l_2}+1\right)}$ $\frac{\frac{8}{3}}{\frac{12}{1}}$ $\frac{\ell_1}{\ell_2 \left(\frac{\ell_1}{\ell_2} + 1\right)^2}$ $\Rightarrow \qquad \left(\frac{\ell_1}{\ell_2} + 1\right)^2 \times \frac{8}{36} = \frac{\ell_1}{\ell_2}$ (i) (ii) ⇒ $\frac{\ell_1}{\ell_2}$) 8 $(y_2 + 1+2y) \times \frac{36}{36} = y$ (where $y = 8y_2 + 8 + 16y = 36 y$ $8y_2 - 20y + 8 = 0$ $2y_2 - 5y + 2 = 0$ \Rightarrow \Rightarrow $2y_2 - 4y - y + 2 = 0$ ⇒ 2y[y-2] - 1(y-2) = 0⇒ $y = \frac{\ell_1}{\ell_2} = \frac{1}{2} \text{ or } 2$ ⇒ (2y - 1)(y - 2) = 0⇒ v² R_{eq} P = v = 10volt $\left(\frac{5R}{5+R}\right)$ R_{eq} = P = 30W(10)² $\overline{(5R)}$

$$30 = \begin{pmatrix} 5R \\ 5+R \end{pmatrix}$$

$$\Rightarrow \frac{15R}{5+R} = 10$$

$$15R = 50 + 10R$$

$$\Rightarrow 5R = 50$$

 \Rightarrow R = 10 Ω



18. Internal resistance of the unknown cell is

$$r = \left(\frac{\ell_1}{\ell_2} - 1\right)_{R} = \left(\frac{3}{2.85} - 1\right)_{(9.5\Omega)} = 0.5\Omega$$



19.

20.

nbination $i_g R_g = i_s R_s \Rightarrow \left(\frac{i}{500}\right)(G) = \left(\frac{499}{500}i\right)(S)$

⇒

Equivalent resitance of the ammeter

$$\frac{1}{R_{eq}} = \frac{1}{G} + \frac{1}{\frac{G}{499}} \implies \qquad R_{eq} = \frac{G}{500}$$



Current remainssame

21. Total potential difference across potentio meter wier = $10_{-3} \times 400$ volt = 0.4 volt 12\





<u>500</u> = 5A $i = \frac{100}{100}$ 130 = 5Rso R = 26 Ω 1 __time On stretching length will be n times. Area of cross section will be n 29. So, resistance will become n²R. 30. Potentiometer is more accure because it doesn't draw any current at the balance point $\frac{\theta}{\theta} = \frac{5 \, \text{div}}{1000}$ $\frac{\theta}{\Delta V} = 20 \frac{\text{div}}{\text{volt}}$ $\frac{\sigma}{i_{g}} = \frac{1}{10^{-3} \text{ A}} = 5000 \text{ div}$ 31. (5000 div / A) × $\frac{1}{R_g} = 20 \left(\frac{\text{div}}{\text{volt}}\right)$ 5000 $R_g = \frac{3000}{20} = 250 \Omega$ ⇒ $\dot{R} = 47 \times 10^3 \pm 10\%$ 32. B B R O Y Great Britain Very good wife 0 1 2 3 4 6 7 5 8 9 yellow violet orange ± silver $\frac{1}{n} + 1 = \frac{n+1}{10} \Rightarrow \frac{n+1}{n} = \frac{n+1}{10} \Rightarrow n = 10$ Е Е $i' = \overline{R + R/n} = 10i$ i = R + nRSO, 33. $\frac{n\epsilon}{nr} = \frac{\epsilon}{r}$ 34. So i = constant 35. Resistance for ideal voltmeter = ∞ Resistance for ideal ammeter = 0For Ist circuit $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$ $\frac{1}{R_{eq}} = \frac{1}{10} + \frac{1}{\infty}$ $\frac{1}{R_{eq}} = \frac{1}{10} + 0$ $R_{eq} = 10 \Omega$ $i_i = \frac{V}{R} = \frac{10}{10} = 1A$ $V_1 = 10 V$ In IInd circuit $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$ $\frac{1}{R_{eq}} = \frac{1}{10} + \frac{1}{10 + \infty}$ $\frac{1}{R_{eq}} = \frac{1}{10} + 0$

 $R_{eq} = 10 \Omega$

$$i_2 = \frac{10}{10} = 1A$$

V₂ = 10 V

36. Fuse is used as a circuit protector



38. For ideal voltmeter $R_v = \infty$ 20 4

so
$$V_{20 \Omega} = \frac{1}{20 + 30} \times 2 = \frac{1}{5}$$
 volt
 $V_{30 \Omega} = \frac{30}{20 + 30} \times 2 = \frac{6}{5}$ volt
 $V = V_{30} - V_{20} = \frac{6}{5} - \frac{4}{5} = \frac{2}{5} = 0.4$ volt

39. In bridge network, No effect will occur if galvanometer and cell are inter changed so

PART - II

1. Let R be their individual resistance at 0° C. Their resistance at any other temperature t is $R_1 = R (1 + \alpha_1 t)$ and $R_2 = R (1 + \alpha_2 t)$. In series

Rseries = R1 + R2 = R [2 + (
$$\alpha$$
1 + α 2) .t] = 2R $\left[1 + \frac{\alpha_1 + \alpha_2}{2}t\right]$

 $\alpha_1 + \alpha_2$ 2 α Series = In Parallel $R_{\text{Parallel}} = \frac{\frac{R_1 + R_2}{R_1 + R_2}}{R_1 + R_2} = \frac{\frac{R(1 + \alpha_1 t)R(1 + \alpha_2 t)}{R(2 + \alpha_1 + \alpha_2)t)}}{R(2 + \alpha_1 + \alpha_2)t)} \approx \frac{\frac{R^2(1 + \alpha_1 + \alpha_2)t}{2}}{2R(1 + \frac{\alpha_1 + \alpha_2}{2}t)} \approx \frac{R}{2} \left(1 + \frac{\alpha_1 + \alpha_2}{2}t\right)$ $\alpha_1 + \alpha_2$ 2 α Parallel = ρl R = A (:: $V = A\ell$ const.) 2. $V = A\ell$ By differentiation $0 = \ell dA + Ad\ell$(1) $\rho(\mathsf{Ad}\ell - \ell \mathsf{d}\mathsf{A})$ A² By differentiation dR =....(2) 2Adℓ $dR = \rho A^2$ $dR = \frac{2\rho d\ell}{A} \text{ or } \frac{dR}{R} = 2.\frac{d\ell}{\ell}$ So, $\frac{dR}{R}\% = 2.\frac{d\ell}{\ell}\% = 2 \times 0.1\%$ $\frac{dR}{R}\% = 0.2\%$ Ans. $\mathbf{x} = \frac{\mathbf{V}}{\boldsymbol{\ell}} = \frac{\mathbf{IR}}{\boldsymbol{\ell}} = \frac{\mathbf{IR}}{\boldsymbol{\ell}} \left(\frac{\boldsymbol{\rho}\boldsymbol{\ell}}{\boldsymbol{A}}\right) = \frac{\mathbf{I}\boldsymbol{\rho}}{\boldsymbol{A}}$ 3. $\frac{0.2 \times 4 \times 10^{-7}}{8 \times 10^{-7}} = \frac{0.8}{8} = 0.1 \text{ V/m}.$ x = 25W-220V 100W-220V R, R 4. 440V and $R_2 = \frac{220}{100} \times 220$ 220 ×220 25 As $R_1 =$ $R = R_1 + R_2 = 220 \times 220 \left(\frac{1}{25} + \frac{1}{100}\right)$ $= 220 \times 220 \frac{1}{20}$ $\frac{440}{220 \times 220} = \frac{40}{220} A$ 440 20 \therefore live = ∴ 1st bulb (25 W) will fuse only $\pm \frac{\Delta R}{R} = \pm \frac{\Delta V}{V} \pm \frac{\Delta I}{I} = 3 + 3 = 6\%$ V Ι 5. R =

6. Statements I is false and Statement II is true



8. Total power (P) = $(15 \times 40) + (5 \times 100) + (5 \times 80) + (1 \times 1000) = 2500W$ P = VI

 $\Rightarrow I = \frac{2500}{220} A = \frac{125}{11} = 11.3 A$ Minimum capacity should be 12 A

9.
$$\begin{array}{c} \overleftarrow{\qquad} = 0.1 \text{ m} \longrightarrow \\ \hline \\ & \swarrow \\ v_{d} = 2.5 \times 10_{-4} \text{ m/s} \\ n = 8 \times 10_{28}/m_{3} \\ I = ne \text{ A } v_{d} \\ \hline \\ \frac{VA}{\rho \ell} = ne \text{ A } v_{d} \\ \hline \\ \rho = \frac{V}{nev_{d}\ell} = \frac{5}{8 \times 10^{28} \times 1.6 \times 10^{-19} \times 2.5 \times 10^{-4} \times 0.1} = 1.6 \times 10_{-5} \Omega \text{ m} \end{array}$$

145 | Page



- 11. $S = \frac{g}{1 i_g}$ here $i_g = 10^{-3} A$ $G = 10^2 \Omega$, I = 10A $S \approx 10^{-2} \Omega$
- **12.** For conductor (Cu) resistance increases linearly and for semiconductor resistance decreases Exponentially in given temperature range.



13.

p.d. across each resistance is zero so current is also zero.

- **14.** In a balanced Wheatstone bridge if the position of cell and galvanometer is exchanged the null point remains same.
- **15.** Full deflection current, $I_g = 5mA$ Resistance of galvanometer, $G = 15\Omega$.

$$R = \frac{V}{I_g} - G$$

= $\frac{10}{5 \times 10^{-3}} - 15$
= 2000 - 15
= 1985 \Omega
= 1.985 \times 10^3 \Omega



Color Codes	Values	Multiplier	Tolerance (%)
Black	0	1	

Current Electricity

Brown	1	10	
Red	2	100	
Orange	3	1K	
Yellow	4	10K	
Green	5	100K	
Blue	6	1M	
Violet	7	10M	
Grey	8	100M	
White	9	1G	
Gold			5
Silver			10

19. $i = neAv_d$

 $\frac{1.5}{1.6 \times 10^{-19} \times 5 \times 10^{-6} \times 9 \times 10^{28}} = v_d$ 1.5 ⇒



$$\frac{100}{64} \times 10^{-3} = V_d \Rightarrow V_d = 0.02 \text{ mm/s}$$

$$\frac{\Delta R}{R} = 0.5\% + 0.5\% = 1\%$$

22. $V_{500} = 5V = I_1 R_4$

10 $\Rightarrow i = \frac{12}{2} = 5$ Amp.



- $\Rightarrow \qquad V_{400} = 18 6 = 12V \\ I = \frac{12}{400} = \frac{3}{100} \Rightarrow \qquad I_2 = \frac{3}{100} \frac{1}{100} = \frac{2}{100} \\ V_{R_2} = 6V = I_2R_2 \Rightarrow \qquad R_2 = \frac{6 \times 100}{2} = 300\Omega$
- 23. 1st digit corresponding to green will be 5 2nd digit corresponding to orange will be 3 3rd digit corresponding to yellow will be 4 Tolerance corresponding to gold will be ±5% ∴ Resistance is 53 × 10⁴ ± 5%
- 24. Green \rightarrow 5, Black \rightarrow 0 Red \rightarrow 10² Brown \rightarrow 1% tolerance I²R = P 2

$$I^{2} = \frac{50 \times 10^{2}}{50 \times 10^{2}} = 4 \times 10^{-4} \text{A}$$

I = 2 × 10⁻² A = 20 mA

25.
$$x = \frac{\varepsilon}{13r} \times \frac{12r}{\Box} = \frac{12\varepsilon}{13\Box}$$
$$\frac{\varepsilon}{2} = x\Box$$
$$\frac{\varepsilon}{2} = \frac{12\varepsilon}{13\Box}$$
$$\Box = \frac{13\Box}{24}$$



$$\mathsf{P} = \frac{\mathsf{V}^2}{\mathsf{R}} = \frac{(11)^2}{1.1 \times 10^6} = 11 \times 10^{-5} \, \mathrm{W}$$

29. Orange Red Brown 10¹ 3 2 = 320 $\frac{320}{R_3} = \frac{80}{40}$ R₃ = 160 Brown Blue Brown 1 6 10¹

30. Let the measured voltage be V_m and Let the measured current be i_m and Let the ammeter be ideal, thus

31. Initially

$$\frac{P}{Q} = \frac{R_1}{X} \qquad \dots(i)$$
After interchanging P and Q
$$\frac{Q}{P} = \frac{R_2}{X} \qquad \dots(ii)$$
From (i) and (ii)
$$1 = \frac{R_1 R_2}{X^2}$$

$$X = \sqrt{R_1 R_2}$$

$$= \sqrt{400 \times 405}$$

$$= 402.5 \Omega$$

32. In circuit, when $R_h = 2\Omega$

$$i_{1} = \frac{6}{4+2} = 1A, \quad \epsilon = \frac{1 \times 4}{AB} \times AJ$$

$$AJ = \frac{AB}{4} \times \epsilon$$
when $R_{h} = 6\Omega$

$$i_{2} = \frac{6}{4+6} = 0.6A$$

$$\epsilon_{2} = \frac{0.6 \times 4}{AB} \times AJ$$

150 | Page



$$\frac{\frac{1}{1} + \frac{2}{1} + \frac{3}{1}}{\frac{1}{1} + \frac{1}{1} + \frac{1}{1}} = \frac{1+2+3}{3} = \frac{6}{3}$$
35. $V_{AB} = \frac{1}{1} + \frac{1}{1} + \frac{1}{1}} = \frac{1+2+3}{3} = \frac{6}{3}$
36. Full deflection current lg = nk = 30 × 0.005 × R
R = 80 Ω
37. $R_1 = \frac{\sqrt{2}}{P} = \frac{220 \times 220}{25} = 1936\Omega$
 $R_2 = \frac{220 \times 220}{100} = 484\Omega$
 $i = \frac{220}{1936 + 484} = \frac{220}{2420} = \frac{11}{121} = \frac{1}{11} \text{ Amp}$
 $P_1 = i^2R = \frac{1}{121} \times 1936 = 16 \text{ W}$
 $P_2 = \frac{1}{121} \times 484 = 4W$
38. $dR = \frac{\sqrt{2}}{\sqrt{2}}$
 $Acording to Question$
 $\int_{0}^{1} c \frac{d\Pi}{\sqrt{2}} = \int_{0}^{1} c \frac{d\Pi}{\sqrt{2}} \Rightarrow (2\sqrt{1})_{0}^{1} = (2\sqrt{1})_{0}^{1}$
 $2\sqrt{1} = 2 - 2\sqrt{1}$
 $4\sqrt{1} = 2$
 $\Pi = \frac{1}{4} = 0.25 \text{ m.}$
39. Potential gradient = $x = \frac{5 \times 10^{-3}}{10 \times 10^{-2}} = (\frac{4}{R+5} \times 5) \times \frac{1}{1}$
 $\Rightarrow \frac{1}{20} = \frac{20}{R+5}$
 $\Rightarrow 400 = R + 5$
 $R = 395\Omega$.
40. $Q_0 \propto i_G \Rightarrow Q_0C = i_G$
 $I_{-case} CQ_0 = \frac{V}{220 + R} \qquad(1)$
 $C \frac{\theta_0}{5} = \frac{V}{(220 + \frac{5R}{5+R})} \times \frac{5}{5+R}$
 $I_{-case} CQ_0 = \frac{V}{220}$



$$\Rightarrow I_2 = I_3 + I_6 - I_7 = 0.4 + 0.4 - (-0.3) = 1.1 \text{ A} \qquad ...(3)$$