Capacitance /

Exercise-1

Marked Questions can be used as Revision Questions.

E

OBJECTIVE QUESTIONS

Section (A) : Definition of Capacitance

A-1.	The radii of two metallic spheres are 5 cm and 10 cm and both carry equal charge of 75μ C. If th spheres are shorted then charge will be transferred– (1) 25 μ C from smaller to bigger (2) 25 μ C from bigger to smaller				
	(3) 50 μ C from smaller to bigger		(4) 50 μ C from bigger to smaller		
A-2.	 A parallel plate capacito Charge (1) remains consta (2) remains consta (3) remains consta (4) increases 	or is charged and then is Potential ant remains consta ant increases ant decreases increases	olated. On increas Capacita ant decrease decrease increase decrease	ing the plate separation– nce es es s s	
A-3.	The capacitance of a sp (1) C \propto R ²	oherical conductor is pro (2) $C \propto R^{-2}$	portional to (3) C ∝ R	(4) C ∝ R ⁻¹	
A-4.	Stored energy in a char	ged conductor is			
	$\frac{1}{(1)^2}$ CV ²	(2) $\frac{1}{2}Q^2V^2$	$\frac{1}{2}\frac{Q^2}{C^2}$	(4) $\frac{1}{2} \frac{Q}{C^2}$	
A-5.	Unit of capacitance is (1) coulomb	(2) volt	(3) henry	(4) farad	
A-6.	The capacitance of a capacitor is (1) directly proportional to the dielectric constant of the medium between the plates (2) inversely proportional to the dielectric constant of the medium between the plates (3) proportional to the square of the dielectric constant of the medium between the plates (4) independent of the dielectric constant of the medium between the plates				
A-7.	If the energy of a capac (1) 800 V	itor of capacitance 2μF i (2) 400 V	is 0.16 joule, then i (3) 16 × 10 ⁴ V	ts potential difference will be (4) 16 × 10 ⁻⁴ V	
A-8.⊵	A capacitor of 6μ F is charged to such an extent that the potential difference between the plates become 50 V. The work done in this process will be				
	(1) 7.5 × 10 ⁻² J	(2) 7.5 × 10⁻³ J	(3) 3 × 10⁻⁰ J	(4) 3 × 10 ^{−3} J	
A-9.	 The potential of earth is zero because it is (1) uncharged (2) an object of zero capacitance (3) net charge is very small but radius is very large (4) having infinite charge 				
Section	on (B) : Circuits wit	h capacitor and us	e of KCI and K	VL	
B-1.	The work done against electric forces in increasing the potential difference of a condenser from 20V to 40V is W. The work done in increasing its potential difference from 40V to 50V will be				

(1) 4W	(2) 4	(3) 2W	(4) 2

B-2. The plate separation in a parallel plate condenser is d and plate area is A. If it is charged to V volt & battery is disconnected then the work done in increasing the plate separation to 2d will be–

Capacitance /					
	$3 \frac{\varepsilon_0 AV^2}{V}$	$\epsilon_0 AV^2$	$2\varepsilon_0 AV^2$	$\frac{\varepsilon_0 AV}{2}$	2
	(1) 2 d	(2) ^d	(3) ^d	(4) 2 c	
В-3.	A capacitor of capacita uncharged capacitor, th is	nce $10\mu F$ is charged ne resultant potential c	to a potential of 100 V. N lifference becomes 40 vc	Now connectin It. The capacit	g it in parallel with an ance of this capacitor
	(1) 2.5μF	(2) 5µF	(3) 10μF	(4) 15μF	
B-4.	The capacitance of a p and the area of plates (1) $24\mu F$	arallel plate capacitor is doubled, then the ca (2) 12µF	is 12μF. If the distance b apacitance of the capaci (3) 16μF	between its pla tor will becom (4) 48μF	ates is reduced to half e
B-5.ൔ	Two conducting sphere are connected togethe (1) 400 V	es of capacitances 3μ r. The common poten (2) 425 V	F and 5μF are charged to tial in steady state will be (3) 350 V	o 300 V and 5 • (4) 375 V	00 V respectively and
Section	on (C) : Combinatio	on of capacitors			
C-1.ൔ	In the adjoining circuit,	the capacity between	the points A and B will b	e 🦳	
	- (1) C (2) 2C (3) 3C (4) 4C			A•	
C-2.	The resultant capacity be - (1) C (2) 2C (3) 3C (4) 4C	between the points A	and B in the adjoining	circuit will	C C C C C C C C C C C C C C C C C C C
C-3.ൔ	The equivalent capacit figure, will be (1) 1.5μF	ance between A and I	B of the combination, sho) 3.0μF	own in the	
	(3) $\frac{6}{11} \mu F$	(4)) 6µF		
C-4.	The effective capacitar (1) 1μF	nce between A and B	is		\wedge

- (1) 1μF (2) 2μF (3) 1.5μF (4) 2.5μF

^{2μ}F 2μF --||--1μF В

Ă

Capacitance

C-5. In the figure given, the effective capacitance between A and B will be (1) C (2) C/2 (3) 2C Ā (4) 3C

Section (D) : Equation of charging and discharging

- D-1.🖎 The plates of a capacitor of capacitance 10 μ F, charged to 60 μ C, are joined together by a wire of resistance 10 Ω at t = 0, then
- (i) the charge on the capacitor in the circuit at t = 0 is : (2) 60 μC (4) 44 μC (1) 120 μC (3) 30 µC (ii) the charge on the capacitor in the circuit at $t = 100 \ \mu s$ is : (1) 120 μC (2) 60 µC (3) 22 μC (4) 18 μC (iii) the charge on the capacitor in the circuit at t = 1.0 ms is : (1) 0.003 μC (2) 60 µC (3) 44 µC (4) 18 μC 25 Ω The charge on each of the capacitors 0.20 ms after the switch S D-2.🖎 is closed in figure is : (1) 24 µC 井2.0μF 2.0µF (2) 16.8 µC (3) 10.37 µC (4) 4.5 μC

D-3. If the two plates of the charged capacitor are connected by a wire, then

- (1) potential will become infinite
- (2) charge will become infinite (4) charge will become double that of earlier one

6.0 V

(3) capacitor will get discharged

The instantaneous charge on capacitor in two discharging RC circuits is D-4.ເ⊳̀ plotted with respect to time in figure. Choose the correct statement(s) (where E1 and E2 are emfs of two DC sources in two different charging circuits and capacitor are fully charged).

(1) $R_1C_1 < R_2C_2$ (3) $R_1 > R_2$ if $E_1 = E_2$

 $\frac{\mathsf{R}_1}{\mathsf{R}_2} < \frac{\mathsf{C}_2}{\mathsf{C}_1}$ (2) (4) $C_2 > C_1$ if $E_1 = E_2$



R

D-5. An uncharged capacitor of capacitance 4μ F, a battery of emf 12 volt and a resistor of 2.5 M Ω are connected in series. The time after which $V_{C} = 3V_{R}$ is (take ln2 = 0.693)

(1) 6.93 seconds	(2) 13.86 seconds
(3) 7 seconds	(4) 14 seconds

Section (E) : Capacitor with dielectric

E-1. The distance between the plates of a parallel plate condenser is d. If a copper plate of same area but d

thickness	2	is placed between the	plates then the new capacitanc	e will become-
(1) half		(2) double	(3) one fourth	(4) unchanged

E-2. A parallel plate condenser is connected to a battery of e.m.f. 4 volt. If a plate of dielectric constant 8 is inserted into it, then the potential difference on the condenser will be-(1) 1/2 V (3) 4V (4) 32V (2) 2V

- **E-3.** In the above problem if the battery is disconnected before inserting the dielectric, then potential difference will be-
 - (1) 1/2 V (2) 2V (3) 4V (4) 32V
- E-4. A parallel plate condenser with plate separation d is charged with the help of a battery so that U₀ energy is stored in the system. A plate of dielectric constant K and thickness d is placed between the plates of condenser while battery remains connected. The new energy of the system will be-

(1)
$$KU_0$$
 (2) K_2U_0 (3) $\frac{U_0}{K}$ (4) $\frac{U_0}{K^2}$

E-5. In the above problem if the battery is disconnected before placing the plate, then new energy will be-

(1)
$$K_2 U_0$$
 (2) $\frac{U_0}{K^2}$ (3) $\frac{U_0}{K}$ (4) $K U_0$

- E-6. If a thin metal foil of same area is placed between the two plates of a parallel plate capacitor of capacitance C, then new capacitance will be
 (1) C
 (2) 2C
 (3) 3C
 (4) 4C
- **E-7.** To reduce the capacitance of a parallel plate capacitor, the space between the plates is (1) filled with dielectric material
 - (2) reduced and area of the plates is increased
 - (3) increased and area of the plates is decreased
 - (4) increased and area is increased relatively
- **E-8.** After charging a capacitor the battery is removed. Now by placing a dielectric slab between the plates (1) the potential difference between the plates and the energy stored will decrease but the charge on plates will remain same

(2) the charge on the plates will decrease and the potential difference between the plates will increase(3) the potential difference between the plates will increase and energy stored will decrease but the charge on the plates will remain same

(4) the potential difference, energy stored and the charge will remain unchanged