# TOPIC : CAPACITANCE EXERCISE # 1

#### **SECTION (A)**

1.  $Q_t = Q_1 + Q_2 = 150 \mu C$ 

$$\frac{\mathbf{Q}'_1}{\mathbf{Q}'_2} = \frac{\mathbf{C}_1}{\mathbf{C}_2} = \frac{1}{2} \qquad \Rightarrow \qquad \mathbf{Q}_1' = 50\mu\mathbf{C}$$

 $Q_{2^{\prime}}=100\mu C \label{eq:Q2}$  25  $\mu C$  charge will flow from smaller to bigger sphere .

2. Charge is flow untill potential are equal and in charge flow energy is decrease

$$\frac{\mathbf{Q}_1}{\mathbf{C}_1} = \frac{\mathbf{Q}_2}{\mathbf{C}_2} \qquad \Rightarrow \qquad \mathbf{Q}_1 \mathbf{R}_2 = \mathbf{Q}_2 \mathbf{R}_1.$$

3. The charge on the capacitot remains constants

Capacitance 
$$C = \frac{\varepsilon_0 A}{d}$$
  
Energy  $U = \frac{1}{2} \frac{Q^2}{C}$   
Potential  $V = \frac{Q}{C}$   
Isolated capacitor  $\Rightarrow$   $Q = constant$   
sepration d increase  $\Rightarrow$   $C = decrease$   
 $Q = CV$   $\Rightarrow$   $V = increase$ 

**14.** Capacitance of spherical conductor=  $4\pi \in a$  where a is radius of conductor

Therefore 
$$C = \frac{1}{9 \times 10^9} = \frac{1}{9} \times 10^{-9} = 0.11 \times 10^{-9} F = 1.1 \times 10^{-10} F$$
 Ans.  
15.  $C = 12 \,\mu F$   
 $d' = \frac{d}{2}$   
 $A' = 2A$   
 $\frac{C'}{C} = \frac{A'}{A} \frac{d}{d'} = 2 \times 2 = 4 \implies C' = 4C = 4 \times 1C = 48 \,\mu F$ 

 $16. \qquad C = \frac{\varepsilon_0(\pi K^-)}{x} = 4\pi \varepsilon_0 R$ 

#### **SECTION (B)**

4.

1. 
$$W = V_{f} - V_{i} = \frac{1}{2}CV_{f}^{2} - \frac{1}{2}CV_{1}^{2} = \frac{1}{2}C(40_{2} - 20_{2}) W = 600 C$$
$$\frac{1}{2}C(50_{2} - 40_{2}) = \frac{900}{2}C \qquad W_{1} = \frac{900}{2} \cdot \frac{W}{600} = \frac{3}{4}W \text{ Ans}$$
2. Charge on capacitor = CV = capacitance × (voltage across it) In steady state, there will be no current through capacitor.

 $\Rightarrow$  x = R/4



Where,  $Q = CV = \frac{A\varepsilon_{o}V}{d}$   $C = \frac{A\varepsilon_{o}}{d}$   $C' = \frac{A\varepsilon_{o}}{2d}$ Now, work done  $= \frac{\frac{\omega_{o}AV^{2}}{2d}}{2d}$  Ans. is (4)

- 14. If S<sub>1</sub> is closed and S<sub>2</sub> is open then, condenser C is fully charged at potential V.
- 18. Charge on each capacitor will be same. In steady state current through capacitor will be zero



current in steady state = i = 5 = 2 amp potential across AB = iR = 2 × 4 = 8 V. Potential across each capacitor = 4 V on each plate Q = C V = 3 × 4 = 12 µC



19.

Common potential V =  $\frac{C_1V_1 + C_2V_2}{C_1 + C_2} = \frac{600 + 600}{20 + 30} = 24 \text{ V}$ 

20. 
$$W = \frac{1}{2} \frac{1}{CV_2} = \frac{1}{2} \frac{q^2}{C}$$
$$= \frac{1}{2} \times \frac{(8 \times 10^{-18})^2}{100 \times 10^{-6}} = \frac{1}{2} \times \frac{64 \times 10^{-36}}{100 \times 10^{-6}} = 32 \times 10^{-32} J$$

**21. Key Idea :** On removing the battery after charging, the charge stored in the capacitor remains constant. When a capacitor is charged by connecting a battery across its plates, the initial energy stored,

$$U = \frac{q^2}{2C}$$

When the battery is disconnected, then the charge remains constant i.e., q = constant. Now another identical capacitor is connected across it i.e., the capacitors are connected in parallel, so the equivalent capacitance

 $C_{eq} = C_1 + C_2 = C + C = 2C$ 

Thus, final energy stored by the system of capacitors,

$$U' = \frac{q^2}{2C_{eq}} = \frac{q^2}{2(2C)} = \frac{1}{2} \qquad \qquad U' = \frac{U}{2}$$

 $1 Q^2$ 

**Key Idea :** Energy stored between the plates of a capacitor is equal to  $\frac{1}{2}C$ 22.

Energy stored, 
$$U = \frac{1}{2} \frac{Q^2}{C}$$
 but  $\sigma = \frac{Q}{A}$  and  $C = \frac{\varepsilon_0 A}{d}$   
 $\therefore \quad U = \frac{\frac{1}{2} \frac{(\sigma A)^2}{(\varepsilon_0 A / d)}}{\sigma}$  or  $U = \frac{\frac{A \sigma^2 d}{2\varepsilon_0}}{U}$   
or  $U = \frac{\frac{1}{2} \left(\frac{\sigma}{\varepsilon_0}\right)^2 \times \varepsilon_0 A d}{\sigma}$  or  $U = \frac{1}{2} E^2 \varepsilon_0 A d$   
Energy stored per unit volume i.e., energy density is thus a

stored per unit volume i.e., energy density is thus given by

$$u = \frac{U}{V} = \frac{U}{Ad} = \frac{1}{2}\varepsilon_0 E^2 = \frac{1}{2}\varepsilon_0 \left(\frac{V}{d}\right)^2 = \frac{1}{2}\frac{\varepsilon_0 V^2}{d^2}$$

Note : 2  $\epsilon_0 E_2$  is also a force on a conductor per unit area which is every where along the outward drawn normal to the surface.

23. The common potential difference across two capacitors connected in parallel

$$V' = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2}$$
 Here,  $V_1 = V$ ,  $V_2 = 0$   $\therefore$   $V' = \frac{C_1 V}{C_1 + C_2}$ 

25. The two condensers in the circuit are in parallel order, hence

$$C' = C + \frac{C}{2} = \frac{3C}{2}$$

the work done in charging the equivalent capacitor is stored in the form of potential energy.

Hence, W = U =  $\frac{1}{2} C' V_2 \frac{1}{2} \left(\frac{3C}{2}\right)$  $= V_2 = \frac{3}{4} CV_2$ 

Energy stored by any system of capacitors is =  $\frac{1}{2}$  C<sub>net</sub> V<sub>2</sub> where V is source voltage 28. Thus, n capacitors are connected in parallel,

 $E_{net} = \frac{1}{2} nCV_2$ Therefore  $C_{net} = nC$ •

Work done by battery = (CV)  $V = CV_2$ 29. Energy stored in capacitor =  $CV_2$ 

 $\frac{\frac{1}{2}CV^2}{CV^2} = \frac{1}{2}$ Energy stored in capacitor Work done by battery Correct choice is (4)  $C' = \frac{\frac{A \in_{0}}{d_{1}}}{3 + \frac{d_{2}}{6}} = \frac{\frac{A \in_{0}}{d}}{9 + \frac{2d}{18}} = \frac{18A \in_{0}}{4d}$ 30. C = 9 PF3 6 C' = 40.5 PF Correct choice is (3).  $U = \frac{1}{2}CV^2$ 31.  $V = \sqrt{\frac{2V}{C}} = \sqrt{\frac{2 \times 0.16}{2 \times 10^{-6}}} = \sqrt{\frac{16}{10^{-4}}} = 400 \text{ V}$  $W = \frac{1}{2} \quad CV_2 = \frac{1}{2} \times 6 \times 10^{-6} \times (50)_2$ 32.  $= 3 \times 10_{-4} \times 25$ = 75 × 10<sub>-4</sub> J = 7.5 × 10<sub>−3</sub> J 33. ΔU = decrease in potential energy  $= U_i - U_f$  $= \frac{1}{2} \frac{1}{C(V_{12} + V_{22})} - \frac{1}{2} \frac{1}{(2C)} \left( \frac{V_1 + V_2}{2} \right)^2 = \frac{1}{4} \frac{1}{C(V_1 - V_2)_2}$ 

- **34.** When capacitor is fully charged, it draws no current. When no current in the circuit, potential difference across the cell = emf of the cell = potential difference across the capacitor.
- **37.** In steady state condition, no current will flow through the capacitor C. Current in the outer circuit, 2V V = V

$$i = \overline{2R + R} = \overline{3R}$$

potential difference between A and B -

$$V = V + V + iR = V_B$$

$$\therefore V_{B} - V_{A} = iR = \left(\frac{V}{3R}\right)_{R} = \frac{V}{3}$$

In this problem charge stored in the capacitor can also be asked which is equal to  $q = C^{\frac{1}{3}}$  with positive charge on B side and negative on A side because  $V_B > V_A$ .

Ans.

٧

### **SECTION (C)**







1.

$$C_{eq} = C + \frac{2}{2} + C = 3C.$$

3. 
$$\frac{\frac{1}{C_1} = \frac{1}{3} + \frac{1}{3} + \frac{1}{3}}{C_{eq}} = 1 \mu F.$$
  $\Rightarrow$   $C_1 = 1 \mu F, C_2 = 2 + 1 = 3 \mu F$ 





 $\frac{1}{C_{eq}} = \frac{17}{12} \Rightarrow C_{eq.} = \frac{12}{17}$ 

$$\frac{1}{C_{eq}} = \frac{1}{6} + \frac{1}{2} \times 4$$

$$\frac{1}{C_{eq}} = \frac{13}{6} \Rightarrow C_{eq} = \frac{13}{13} \mu F$$

$$\frac{1}{C_{eq}} = \frac{1}{10} + \frac{1}{2} + \frac{1}{2}$$

$$\frac{1}{C_{eq}} = \frac{1}{10} + \frac{1}{2} + \frac{1}{2}$$

$$\frac{1}{C_{eq}} = \frac{10}{11} \mu F$$

**37.** Key Idea : Charge on a capacitor is the product of capacitance and potential difference across it. The charge flowing through C<sub>4</sub> is  $q_4 = C_4 \times V = 4 \text{ CV}$ 

The series combination of  $C_1$ ,  $C_2$  and  $C_3$  gives

$$\frac{1}{C'} = \frac{1}{C} + \frac{1}{2C} + \frac{1}{3C}$$

$$= \frac{6+3+2}{6C} = \frac{11}{6C}$$

$$\Rightarrow C' = \frac{6C}{11}$$
Now, C' and C<sub>4</sub> form parallel combination giving
$$C'' = C' + C_4$$

$$= \frac{6C}{11} + 4C = \frac{50C}{11}$$
Net charge q = C'' V
$$= \frac{50}{11} CV$$
Total charge flowing through C<sub>1</sub>, C<sub>2</sub>, C<sub>3</sub> will be
$$q' = q - q_4$$

$$= \frac{50}{11} CV - 4CV = \frac{6CV}{11}$$
Since, C<sub>1</sub>, C<sub>2</sub> and C<sub>3</sub> are in series combination hence, charge flowing through these will be same.

$$q_{2} = q_{1} = q_{3} = q' = \frac{6CV}{11}$$
$$\frac{q_{2}}{q_{4}} = \frac{6CV/11}{4CV} = \frac{3}{22}$$

Thus,

#### 38. Capacitance between any two adjacent plates is 'C'



Capacitor consists of n plates, then there are (n -1) combinations joined in parallel.  $C_{AB} = (n-1)C$ *:*..

39.

 $C_1 = 3\mu F$ 

$$C_{2} = 5\mu F \qquad V_{2} = 500V$$

$$V_{C} = \frac{C_{1}V_{1} + C_{2}V_{2}}{C_{1} + C_{2}} = \frac{3 \times 300 + 5 \times 500}{3 + 5} = \frac{900 + 2500}{8}$$

$$\frac{3400}{8} = 425 V$$

 $V_1 = 300v$ 

40. 
$$\frac{1}{2} = \left(\frac{1/C_2}{1/C_2 + 1/C_2 + 1/C_3}\right)^{V_0} = \left(\frac{1/3}{1/2 + 1/3 + 1/6}\right)^6 = \frac{(1/3)}{\left(\frac{3+2+1}{6}\right)}^{.6} = 2V_0$$

41. Seeing in the given circuit C1 and C2 are connected in parallel. Hence, their equivaleInt capacitance  $C_{eq} = C_1 + C_2 = 5 + 10$ 

As Ceq and C3 are connected in series, Hence, resultant capacitance between P and Q is given by 19 1 1 1 1 1

$$\frac{1}{C_{PQ}} = \frac{1}{C_{eq}} + \frac{1}{C_3} = \frac{1}{15} + \frac{1}{4} = \frac{19}{60}$$
$$C_{PQ} = \frac{\frac{60}{19}}{\frac{19}{19}} = 3.2 \,\mu\text{F}$$

42. Capacitors C<sub>3</sub> and C<sub>4</sub> are in parallel, therefore their resultanct capacitance,

$$A \leftarrow C_{1} \rightarrow C_{2} \mu F$$

$$A \leftarrow C_{1} \rightarrow C_{2} \mu F \rightarrow C_{2} \mu F \rightarrow C_{2} \mu F \rightarrow C_{3} \mu F$$

$$2 \mu F \rightarrow C_{2} \mu F \rightarrow C_{4} \mu F$$

$$1 \mu F \rightarrow C_{3} \rightarrow C_{4}$$

→Β Now, capacitors C<sub>2</sub> and C' are in series, therefore their resultant capacitance,

$$\frac{1}{C''} = \frac{1}{2} + \frac{1}{2} = \frac{2}{2}$$

C" = 1 μF

Capacitors C<sub>6</sub> and C<sub>7</sub> are in series, therefore their resultanct capacitance,

$$\frac{1}{C'''} = \frac{1}{2} + \frac{1}{2} = \frac{2}{2} = 1$$

C''' = 1 μF. Now, C''' and C $_{8}$  are in parallel, therefore their resultant capacitance,  $C'''' = 1 + 1 = 2 \mu F.$ 

Now, C"" and C5 are in series. Therefore, their resultant capacitance,



47.  $C_{AB} = (C/2) ||C_{Bridge}|| (C/2) = 2C$ SECTION (D) 1. (i) **(2)** at to;  $q = q_0 = 60 \ \mu C$ (ii) (3)  $q = q_0 e_{-\nu RC} = 60 \times 10^{-6} e^{-100 \times 10^{-6} \times 10^{-6} \times 10} = \frac{60}{e} \mu C = 22 \mu C.$ 60 (iii) (1)  $q = q_0 e_{-t/RC} = 60 \times 10^{-6} e^{-1 \times 10^{-3} / 10 \times 10^{-6} \times 10} = \frac{e^{10}}{e^{10}}$  $\mu C = 0.003 \ \mu C.$ 6  $i_0 = \overline{R} = \overline{24} = 0.25 \text{ A}$ (i) **(1)** 2. 0.25 (ii) (2)  $i = i_0 e_{-t/RC} = 0.25 e_{-1} = e = 0.09 A.$  $e^{-12 \times 10^{-6}/12 \times 10^{-6} \times 1}$ 1 (i) **(3)** 3. amp = E = 2.21 amp. (ii) (2)  $P = V.i = 6 \times 2.21 = 13.2 W$ dH  $dt = i_2 R$ (iii) **(4)** = (2.21)2 × 1 = 4.88 W (iv) (4)  $P_{\text{battery}} = P_{\text{Heat}} + P_{\text{C}}$  $P_{C} = P_{\text{battery}} - P_{\text{Heat}}$ = 13.2 - 4.87 = 8.37 W.  $1 - e^{\frac{0.2 \times 10^{-3}}{4 \times 10^{-6} \times 25}}$  $4 \times 10^{-6} \times 6$  $q_1$ q = 2 =4. (3)  $q = 12(1 - e_{-2})\mu C$  $(e^2 - 1)$ e<sup>2</sup> 12 μC = 10.37 µC =

7. If  $S_1$  is closed and  $S_2$  is open then, condenser C is fully charged at potential V.

8. Charge on each capacitor will be same. In steady state current through capacitor will be zero current in steady state = i =  $\frac{10}{5}$  = 2 amp potential across AB = iR = 2 × 4 = 8 V.

Potential across each capacitor = 4 V on each plate  $Q = C V = 3 \times 4 = 12 \mu C$ 

## Capacitance

9. (i) **(B)** at  $t_0$ ;  $q = q_0 = 60 \ \mu C$ (ii) (C)  $q = q_0 e_{-t/RC} = 60 \times 10_{-6} e^{-100 \times 10^{-6}/10 \times 10^{-6} \times 10} = \frac{60}{e} \mu C = 22 \mu C.$ (iii) (A)  $q = q_0 e_{-t/RC} = 60 \times 10^{-6} e^{-1 \times 10^{-3} / 10 \times 10^{-6} \times 10} = e^{10} \mu C = 0.003 \mu C.$  $\mathsf{logi} = \frac{-\mathsf{t}}{\mathsf{RC}} + \mathsf{log} \begin{pmatrix} \frac{\mathsf{E}}{\mathsf{R}} \end{pmatrix}; \mathsf{Compare with} \quad \mathsf{y} = \mathsf{mx} + \mathsf{c}$ 10. Е  $|m| = \overline{RC}$ ;  $c = \log \left( \frac{\overline{R}}{R} \right)$  as R increases, |m| and C both decreases so (B) is the correct option. F F Е C KR ξR С С ₹R E 0  $\cap$ 11.  $Q_{first} = Q_{lost} = CE$ Q<sub>first</sub> Ratio =  $Q_{lost} = 1$ . **SECTION (E)**  $C' = \frac{\frac{\epsilon_0}{d}A}{d/2} = \frac{2\epsilon_0}{d} = 2C.$ 1. 2. (3) Q = constant New capacitance = KC (increases)  $V' = \overline{K}$  (decreases)  $Q^2$  $U' = \overline{2CK}$  (decreases) Q  $E = A \in O$  $\Rightarrow$  E' =  $\overline{KA} \in_0$  (decreases) C

3.

4V

Here, Potential difference on the capacitor will depend on emf of battery i.e., 4V

Charge or battery = Q = CV = 4 C
 Now charge remains same, as battery is disconnected new capacitance = C´ = KC = 8C

$$C'V' = Q \qquad V' = \frac{Q}{C} = \frac{4C}{8C} = \frac{1}{2} V \qquad (1)$$

$$U_0 = \frac{1}{2}CV^2 \text{ (given)} \qquad \text{Now energy} = U' = \frac{1}{2}C'V^2$$

$$C' = CK$$

$$U' = \frac{1}{2}CV^{2}K = U_{0}K$$
 Ans. is (1)

- 6. Now, charge remains same on the plates.  $U_{0} = \frac{\frac{Q^{2}}{2C}}{(given)}$ Now energy = U' =  $\frac{\frac{Q^{2}}{2C'}}{\frac{Q^{2}}{2CK}} = \frac{\frac{U_{o}}{K}}{(3)}$
- **33.** No change in the energy of the system. Hence, not net work done by the system is zero. Correct choice is (4)
- 34. Conceptual

:.

**35.** In the arrangement shown two capacitors each of area A and separation d/2 are in series.

$$\therefore \qquad C_1 = \frac{\frac{K_2 \varepsilon_0 A}{d/2}}{\frac{K_2 \varepsilon_0 A}{d}} = \frac{\frac{2K_1 \varepsilon_0 A}{d}}{d}$$
$$C_2 = \frac{\frac{K_2 \varepsilon_0 A}{d/2}}{\frac{d}{2}} = \frac{\frac{2K_2 \varepsilon_0 A}{d}}{d}$$

: Effective capacitance C is given by

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{d}{2K_1\epsilon_0 A} + \frac{d}{2K_2\epsilon_0 A} = \frac{d}{2\epsilon_0 A} \left(\frac{1}{K_1} + \frac{1}{K_2}\right)$$
$$C = \frac{\frac{2\epsilon_0 A}{d} \left(\frac{K_1 + K_2}{K_1 + K_2}\right)}{C = \frac{2\epsilon_0 A}{d} \left(\frac{K_1 + K_2}{K_1 + K_2}\right)}$$

- **36.** As insulator plate is passed between the plates of the capacitor, its capacity increases first and then decreases as the plate slips out. As a result, positive charge on plate A increases first and then decreases, hence current in outer circuit flows from B to A and then from A to B.
- **37.** Aluminium is a metal, so when we insert an aluminium foil, equal and opposite charges appear on its two surfaces. Since it is of negligible thickness, it will not affect the capacitance. Alternative : From the formula,



Here,  $K = \infty$  and  $t \rightarrow 0$ ⇒  $\frac{\varepsilon_0 A}{\varepsilon_0 A} = \frac{\varepsilon_0 A}{\varepsilon_0 A}$  $C = \frac{d}{d+0} = \frac{d}{d} = C_0$ so,  $\mathsf{V}_{\mathsf{C}_2} = \mathsf{V}_{\mathsf{C}_2} = \mathsf{V}$ 38.  $C_1 = C$  $C_2 = KC$  $q_1 = {}^{C_1V_{C_1}} = CV$  $q_2 = C_2 V_{C_2} = KCV$  $q_1 < q_2$ . σ  $E = {}^{\epsilon_0} = 2.1 \times 10_{-5}$ 39.  $\frac{\mathsf{E}}{\mathsf{E}'} = \frac{\sigma}{\epsilon_0} \times \frac{\epsilon_0 \mathsf{K}}{\sigma} = \frac{2.1 \times 10^{-5}}{1 \times 10^{-5}}$ σ  $E' = {\epsilon_0}^K = 1 \times 10^{-5}$ :. K = 2.1 ≈ 2 or ∈<sub>0</sub> A  $\begin{array}{c} C = & d \\ d' = 2d, \end{array}$ 40. K = 3  $C' = \frac{3}{2}C.$ 

# EXERCISE # 2

1. 
$$V_2 = \frac{(1/C_2)}{1/C_1 + 1/C_2} V_0 = \left(\frac{1/6}{1/6 + 1/2}\right) 100 = 25 V$$

**2.** 
$$V_1 = V_0 - V_2 = 100 - 25 = 75 V$$



5.



Due to symetric charge distribution for loop ACDB

$$V_{A} - \frac{q}{3C} - \frac{q}{6C} - \frac{q}{3C} = V_{B} \qquad \Rightarrow V_{A} - V_{B} = \frac{5q}{6C} \qquad V_{A} - V_{B} = \frac{q}{C_{eq}} \Rightarrow \qquad C_{eq} = \frac{6C}{5} \text{ Ans}$$

$$\frac{dq}{dt} = C \frac{dV}{dt}$$

$$\frac{dV}{dt} = 0.2 \text{ V/s}$$

$$V = \begin{pmatrix} \frac{dV}{dt} \\ 123456 \\ \Delta t = 100 \text{ s} \end{pmatrix}$$

6. Immediately after the key is closed, capacitor be have like a conductory wire, therefore.



After a long time interval, capacitor be have like a open circuit. Therefore.

Е

7. 
$$q_3 = \frac{\frac{C_3}{C_2 + C_3}}{\frac{3}{3 + 2} \times 80} = \frac{3}{5} \times 80 = 48 \,\mu\text{C}$$

### EXERCISE # 3 PART - I

1. In series arrangement charge on each plate of each capacitor has same magnitude. The potential difference is distributed inversely in the ratio of capacitors ie.

$$\frac{1}{C_{s}} = \frac{1}{C_{1}} + \frac{1}{C_{2}} + \frac{1}{C_{3}} + \dots$$

$$C_{s} = \frac{C}{3}$$

2. A series combination of n1 capacitors each of capacitance C1 are connected to 4V source as shown in the figure.



Total capacitance of the series combination of the capacitors is

$$\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_1} + \frac{1}{C_1} + \frac{1}{C_1} + \dots \text{ upto } n_1 \text{ terms} = \frac{n_1}{C_1} \text{ or } C_s = \frac{C_1}{n_1}$$

Total energy stored in a series combination of the capacitors is

$$u_{s} = \frac{1}{2}C_{s}(4V)^{2} = \frac{1}{2}\left(\frac{C_{1}}{n_{1}}\right)(4V)^{2}$$

A parallel combination of  $n_2$  capacitors each of capacitance  $C_2$  are connected to V source as shown in the figure.



Total capacitance of the parallel combination of capacitors is  $C_p = C_2 + C_2 + .... + upto n_2 terms = n_2C_2$  $C_{p} = n_{2}C_{2}$ or ...(iii) Total energy stored in a parallel combination of capacitors is  $u_p = \frac{1}{2}C_pV^2$  $=\frac{1}{2}(n_2C_2)(V)^2$ (Using (iii))....(iv) According to the given problem,  $U_{\text{s}} = U_{\text{p}}$ Substituting the values of us and up from equations (ii) and (iv), we get  $\frac{C_{1}16}{n_{1}} = n_{2}C_{2}$ 16C<sub>1</sub>  $\frac{1}{2}\frac{C_1}{n_1}(4V)^2 = \frac{1}{2}(n_2C_2)(V)^2$ or  $C_2 = n_1 n_2$ or  $U = \overline{2} cv_2$  $U = \frac{1}{2} \left( \frac{A \in_0}{d} \right) (Ed)^2 = \frac{1}{2} A \in_0 E_2 d$ 

.

3.



Energy less = 
$${2(C_1 + C_2)}$$
 (V1 - V2)2 =  ${2(2\mu + 8\mu)}$  (V - 0)2  
Eloss =  ${5 \over 4}$  V2 J  $\Rightarrow$  % loss =  ${5/4 V^2 \over V^2}$  × 100 = 80%





3. Time constant for parallel combination = 2RC Time constant for series combination =  $\frac{RC}{2}$ In first case :  $V = V_0 e^{-\frac{t_1}{2RC}} = \frac{V_0}{2}$  .....(i) In second case  $V = V_0 e^{-\frac{t_2}{(RC/2)}} = \frac{V_0}{2}$  .....(ii)

From (i) & (ii),

5.

$$\begin{array}{l} \displaystyle \frac{t_1}{2RC} = \frac{t_2}{(RC/2)} & \Rightarrow & t_2 = \frac{t_1}{4} = \frac{10}{4} = 2.5 \ \text{sec.} \end{array}$$

$$\begin{array}{l} Q = c_{\epsilon_0} e_{\text{-t/cR}} \\ 4\epsilon = 4\epsilon_0 \epsilon_{\text{-t/t}} \\ \epsilon = \epsilon_0 \epsilon_{\text{-t/t}} \end{array}$$

$$\begin{array}{l} When \ t = 0 \Rightarrow \epsilon_0 = 25 \\ \epsilon = \epsilon_0 = 25 \end{array}$$

$$\begin{array}{l} \text{when } t = 200 \Rightarrow \epsilon = 5 \\ \hline 5 = 25 \ e^{-\frac{200}{\tau}} \\ 1n \ 5 = \frac{\frac{200}{\tau}}{\tau} \\ r = \frac{200}{\tau n 5} = \frac{200}{\tau n 10 - \ell n 2} = \frac{200}{\ell n 10 - 0.693} \end{array}$$

$$\begin{array}{l} \text{Alternative :} \\ \text{Time constant is the time in which 63\% discharging is completed.} \\ \text{So remaining charge } = 0.37 \times 25 = 9.25 \ V \end{array}$$

For potential to be made zero, after connection  $120C_1 = 200 C_2$   $\Rightarrow 3C_1 = 5C_2$ Ans. (2)

6. Electric field inside dielectric 
$$\frac{\sigma}{K\epsilon_0} = 3 \times 10_4$$
  
 $\Rightarrow \sigma = 2.2 \times 8.85 \times 10_{-12} \times 3 \times 10_4$   
 $= 6 \times 10_{-7} \text{ C/m}_2$ 

7.  $Q_{2} = \frac{2}{2+1} Q_{2} = \frac{2Q}{3}$   $Q_{2} = E = \frac{2Q}{3}$ 





10.



98 | Page

current in the circuit Е  $I = r + r_2$ potential difference across AB = Ir<sub>2</sub>  $Er_2$  $= r + r_2$ charge on capacitor =  $Q = C(\Delta V)_{AB}$  $CEr_2$  $Q = r + r_2$  $Q_{cap} = KC_0 V$ 11.  $\left|\mathbf{Q}_{\text{polarised}}\right| = \left|\mathbf{Q}_{\text{cap}}\left(1 - \frac{1}{k}\right)\right| = (90 \times 10^{-12}) (20) \left(\frac{5}{3}\right) \left(1 - \frac{3}{5}\right) \text{Coulomb}$ = 1200 × 10<sup>-12</sup> Coulomb = 1.2 nc C<sub>3.L/2</sub> ↔ d/2 12.  $\frac{K_1}{2}\frac{r}{2}\varepsilon_0}{=} = \frac{K_1A\varepsilon_0}{1}$ d 2  $C_1 =$  $K_2A\epsilon_0$ d C<sub>2</sub> =  $K_3A\epsilon_0$ d C3 =  $K_4 A \epsilon_0$ d C4 =  $C_{eq} = \frac{\frac{C_1 C_3}{C_1 + C_3} + \frac{C_2 C_4}{C_2 + C_4}}{C_2 + C_4}$  $C_{eq} = \frac{K_{eq} \frac{A\varepsilon_0}{d}}{\Gamma_{eq}} = \left[\frac{K_1 K_3}{K_1 + K_3} + \frac{K_2 K_4}{K_2 + K_4}\right] \frac{A\varepsilon_0}{d}$  $K_{eq} = \left[\frac{K_1 K_3}{K_1 + K_3} + \frac{K_2 K_4}{K_2 + K_4}\right]$ According to this all options are incorrect E<sub>0</sub>A d 13.

$$C_{1} = \frac{K_{1}E_{0}A}{3d} = \frac{K_{1}C}{3} \qquad \Rightarrow \qquad C_{2} = \frac{K_{2}C}{3} \qquad \Rightarrow \qquad C_{3} = \frac{K_{3}C}{3}$$
$$C_{eq} = K_{eq} = \frac{C}{3}(K_{1} + K_{2} + K_{3}) \qquad \Rightarrow \qquad K_{eq} = \frac{K_{1} + K_{2} + K_{3}}{3} = \frac{36}{3} = 12$$

99 | Page

14. 
$$W = -(U_{f} - U_{i}) = -\left(\frac{(\varepsilon C)^{2}}{2KC} - \frac{(\varepsilon C)^{2}}{2C}\right) = \frac{\varepsilon^{2}C}{2}\left(\frac{K-1}{K}\right) = \frac{10^{2} \times 12 \times 10^{-12}}{2}\left(\frac{5.5}{6.5}\right) = 508 \text{pJ}$$
14. 
$$W = -(U_{f} - U_{i}) = \frac{1}{2} + \frac{1}{2} +$$

# Capacitance

**16.** Applying the concept of charge conservation on isolated plates of  $10\mu$ F,  $6\mu$ F &  $4\mu$ F and distribuiting the charge we get



17.  $E = \frac{\sigma}{\varepsilon_0} = \frac{Q}{A\varepsilon_0} = 100 \text{ V/m}$  $Q = 100 \times A \varepsilon_0$ 

- $\Rightarrow \qquad Q = 100 \times 1 \times 8.85 \times 10^{-12} \text{ C} = 8.85 \times 10^{-10} \text{ C}$
- **18.** Energy dissipated when switch is thrown from 1 to 2.

