

TOPIC : ALTERNATING CURRENT EXERCISE # 1

SECTION (A)

1. $I_0 = \sqrt{2} I_{rms}$
 $I_0 = 10\sqrt{2}$

2. In a capacitance circuit the current leads voltage by phase angle $\pi/2$.

3. $\tan\phi = \frac{\omega L}{R}$ $\tan\phi = 1$

4. Hot wire ammeter is used to measure A.C. current.

7. $I = \frac{200\sqrt{2}}{(X_C) \times \sqrt{2}} = 200 \times \omega C = 20 \text{ mA.}$

9. $I = I_1 \cos\omega t + I_2 \sin\omega t$
 $I = \sqrt{I_1^2 + I_2^2} \cdot \sin(\omega t + \alpha)$
 $I_{rms} = \frac{I_0}{\sqrt{2}} = \sqrt{\frac{I_1^2 + I_2^2}{2}}$


10. $I_0 = 2\sqrt{2}$
 $I_{rms} = \frac{I_0}{\sqrt{2}} = 2A$

11. $I_{rms} = \left[\frac{\int_0^T i^2 dt}{T} \right]^{\frac{1}{2}}$

12. $E = 10 \cos \left(2\pi \times 50 \times \frac{1}{600} \right) = 5\sqrt{3}$

13. $V_{rms2} = \sqrt{\frac{\int_0^T (e_1 \sin\omega t + e_2 \cos\omega t)^2 dt}{T}} = \sqrt{\frac{e_1^2 + e_2^2}{2}}$ where $\omega = \frac{2\pi}{T}$.

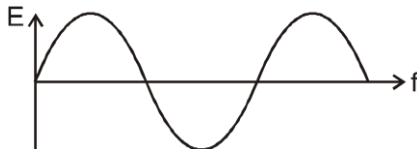14. If net area of $E - t$ curve is zero for given interval then average value will be zero.



15. $V = 100 \sin 100\pi t \cos 100\pi t$
 $V = 50 \sin 200\pi t$
 here $V_0 = 50$ & $\omega = 200\pi$ $f = 100 \text{ Hz}$

16. D.C. Voltmeter measures Average value only

17. $\frac{T}{4} = \frac{1/f}{4} = 5 \times 10^{-3} \text{ s}$

18. $i = 4 \cos(\omega t + \phi)$

Alternating Current

$$i_{rms} = \frac{4}{\sqrt{2}} \text{ A} = 2\sqrt{2} \text{ A}$$

$$19. \quad i_{rms} = \frac{200}{40} = 5 \text{ A}$$

$$i_0 = \sqrt{2} \cdot i_{rms} = 5\sqrt{2} \text{ A}$$

SECTION (B)

2. In second mode of transmission since $I = \frac{P}{V}$ the current is less hence during transmission I^2R losses are least.

3. $E = 200 \sin \omega t$
It contains capacitor or inductor, so power factor $= \cos 90^\circ = 0$

4. $V = 220 \text{ V}$, $i = 5 \text{ mA}$
Loss of power $= 0$
because power factor $= 0$
 $R = 0$

5. $P = V_{rms} \cdot I_{rms} \cdot \cos \phi$
at maximum power $\cos \phi = 1$

$$\text{but at half power } \cos \phi = \frac{1}{2}$$

$$V_{rms} \times I_{rms} \times \frac{1}{2} = P$$

$$V_{rms} \times I_{rms} \times \frac{1}{2} = \frac{V_{rms}}{\sqrt{2}} \times I$$

$$I = \frac{I_{rms}}{\sqrt{2}}$$

$$I = \frac{I_{rms}}{\sqrt{2}}$$

6. $E = 200 \sin 314 t$,
 $I = 100 \sin \left(314 t + \frac{\pi}{3} \right)$ power factor $= \cos \phi = \cos \frac{\pi}{3} = \frac{1}{2}$

7. $V_L = 8 \text{ V}$, $V_R = 6 \text{ V}$, $V = \sqrt{V_L^2 + V_R^2} = 10 \text{ V}$ power factor $= \cos \phi = \frac{V_R}{V} = \frac{6}{10} = 0.6$

9. From the relation, $\tan \phi = \frac{\omega L}{R}$

$$\text{Power factor } \cos \phi = \frac{1}{\sqrt{1 + \tan^2 \phi}} = \frac{1}{\sqrt{1 + \left(\frac{\omega L}{R} \right)^2}} = \frac{R}{\sqrt{R^2 + \omega^2 L^2}}$$

11. $P_{av} = V_{rms} I_{rms} \cos \phi$
Here $\phi = 90^\circ$ so $P_{av} = 0$

Alter. $v = 5 \cos(\omega t)$

$$i = 2 \sin \omega t$$

$$P = V_{rms} \cdot I_{rms} \cdot \cos \phi \quad \therefore \phi = 90^\circ \quad \Rightarrow P = 0$$

Alternating Current

$$12. \frac{H_{D.C.}}{H_{A.C.}} = \frac{I^2 R}{I_{rms}^2 R} = 2$$

$$13. <P> = I_{rms} R = \left(\frac{I_p}{\sqrt{2}} \right)^2 R = \frac{I_p^2 R}{2}$$

$$14. (2)^2 R = P_2 \quad \dots (i)$$

$$I_{rms}^2 \times R = 3P_2 \quad \dots (ii)$$

$$15. P = I_{rms} V_{rms} \cos \frac{\pi}{2} = 0$$

$$17. P = \frac{V^2}{R}$$

$$R = \frac{10 \times 10}{20} = 5 \Omega$$

for AC source
P = 10 watt

$$\therefore P = V_{rms} \cdot \frac{V_{rms}}{Z} \times \frac{R}{Z}$$

$$10 = 10 \times \frac{10 \cdot R}{Z^2}$$

$$Z^2 = 10R$$

$$R_2 + X_{L2} = 10 \times R$$


$$25 + X_{L2} = 10 \times 5$$

$$X_{L2} = 25$$

$$X_L = \sqrt{25} = 5$$

$$\omega \times L = 5$$
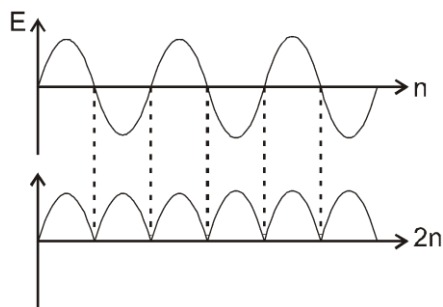
$$f = \frac{5 \times 10^2}{2\pi} = \frac{250}{3.14} \approx 80 \text{ Hz}$$



$$18.$$

$$20. \text{Power factor} = \cos \phi = \frac{R}{Z} = \frac{12}{15} = \frac{4}{5} = 0.8$$

$$21. I_0 = \frac{V_0}{\omega L} = \frac{10}{100 \times 5 \times 10^{-3}}$$

$$22. I_2 R = 100$$

$$R = \frac{100}{I^2} = \frac{100}{(2)^2} = 25.$$

$$23. \tan \phi = \frac{X}{R} = \frac{4}{3}$$

Alternating Current

$$\cos \phi = \frac{3}{5} = 0.6$$

SECTION (C)

1. $Z = \sqrt{R^2 + (X_L - X_C)^2}$ as $f \uparrow X_L \uparrow X_C \downarrow$ so. ans (a)

5. $E = 4 \cos 1000t$,
 $L = 3\text{mH}$, $R = 4\Omega$
 $X_L = 1000 \times 3 \times 10^{-3} = 3$
 $Z = 5$

$$\frac{E_0}{2} = \frac{4}{5} = 0.8\text{A}$$

6. $Z = 100 \Omega$ at $f = 50\text{Hz}$

$$2\pi f \times L = X_L$$

$$f_1 = X_{L_1}$$

$$f_2 = X_{L_2}$$

$$\frac{150}{50} = \frac{100}{X_{L_2}}$$

$$X_{L_2} = 300\Omega$$

7. $\tan \phi = \frac{X_C}{R} = \frac{1/\omega C}{R} \Rightarrow \phi = \tan^{-1} \frac{1}{\omega CR}$

8. $\tan \phi = \frac{\omega L}{R} = \frac{10 \times 0.1}{1} = 1$
 $\phi = 45^\circ = \pi/4$

9. Power factor = $\frac{R}{Z} = \frac{30}{50} = \frac{3}{5}$

$$\text{here } Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(30)^2 + (60 - 20)^2}$$

$$Z = 50$$

$$I = \frac{V}{Z} = \frac{100}{50} = 2 \text{ Amp.}$$

10. The current lags the EMF by $\pi/2$, so the circuit should contain only an inductor.

11. Resultant voltage = 200 volt

Since V_1 and V_3 are 180° out of phase, the resultant voltage is equal to V_2

$$\therefore V_2 = 200 \text{ volt}$$

12. Initially at resonance: $X_L = X_C \Rightarrow Z = R$.

$$\therefore i_0 = \frac{\varepsilon_0}{R} = 10\sqrt{2} = A$$

After increasing frequency : $X_L > X_C$

$$\omega L > 1/\omega C$$

$$\omega > \frac{1}{\sqrt{LC}} \Rightarrow \omega > \omega_0 \quad i' = \frac{\varepsilon_0}{\sqrt{R^2 + X^2}} = \frac{\varepsilon_0}{\sqrt{2}R} = i_0 / \sqrt{2} = 10 \text{ amp.}$$

14. $R = 3\Omega$, $X = 4\Omega$

$$\text{Power factor} = \frac{R}{Z} = \frac{3}{5} = 0.6$$

15. $R = 12\Omega$, $H = 0.21$

Alternating Current

$$16. \quad R = \frac{100}{1} = 100 \, \Omega \quad x = \sqrt{Z^2 - R^2}$$

$$Z = \frac{100}{0.5} = 200 \, \Omega \quad L = \frac{x}{\omega} = \frac{1}{3} \, \text{H.}$$

$$17. \quad \text{Voltage of source is always less than } (V_1 + V_2 + V_3), \quad V_{\text{net}} = \sqrt{V_1^2 + V_2^2 + V_3^2}$$

$$18. \quad \text{At resonance } (V_C = V_L)$$

$$V = I_{\text{rms}} \times R$$


$$= \frac{V_{\text{rms}}}{Z} \times R \quad (\text{here } z = R)$$

$$V = V_{\text{rms}} = 100 \, \text{volt} \quad \& \quad I_{\text{rms}} = \frac{100}{50} = 2 \, \text{Amp.}$$

$$19. \quad i_{\text{rms}} = \frac{V_{\text{rms}}}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}}$$

when ω increases, i_{rms} increases so the bulb glows brighter

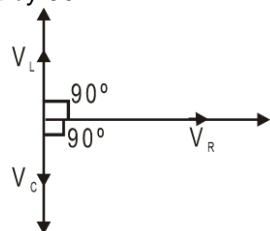21. In an LCR series a.c. circuit, the voltage across inductor L leads the current by 90° and the voltage across capacitor C lags behind the current by 90°



Hence, the voltage across LC combination will be zero.

$$22. \quad \tan \phi = \frac{X}{R} = \frac{\infty}{0} \Rightarrow R = 0$$

$$23. \quad I_{\text{rms}} = \frac{V_{\text{rms}}}{Z} = \frac{200}{(1/\omega C)} = 20 \times 10^{-3} \, \text{A}$$

$$24. \quad I_{\text{rms}} = \frac{V_{\text{rms}}}{Z} = \frac{V_{\text{rms}}}{\sqrt{R^2 + (\omega L)^2}}$$

$$\tan \phi = \frac{\omega L}{R}$$

25. When all (L,C,R) are connected then net phase difference = $60 - 60 = 0$. So, there will be resonance.

$$I = \frac{V}{R} = 2 \, \text{A}$$

$$\& \quad P = I^2 R = 400 \, \text{watt.}$$

$$26. \quad I_{\text{rms}} = \frac{V_{\text{rms}}}{Z} = \frac{100}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

P.d. across resistance = $R I_{\text{rms}}$.

$$27. \quad R = \frac{V_{\text{rms}}}{I_{\text{rms}}} = \frac{200}{5/\sqrt{2}} = 40\sqrt{2} \, \Omega \quad (\text{For ckt x})$$

Alternating Current

$$X_L = \frac{V}{I_{rms}} = \sqrt{2} \times 40 \, \Omega \quad (\text{For ckt y})$$

If x & y are in series

$$I = \frac{200}{40 \times 2} = \frac{5}{2} \text{ Amp.}$$

$$28. \quad I_0 = \sqrt{2} \quad I_{rms} = \frac{\sqrt{2} V_{rms}}{Z}$$

$$I_0 = \frac{\sqrt{2} \times 130 \sqrt{2}}{\sqrt{R^2 + (\omega L)^2}}$$

$$\tan \phi = \frac{\omega L}{R}$$

$$\phi = \tan^{-1} \left(\frac{\omega L}{R} \right)$$

$$29. \quad \tan \phi = \tan 45^\circ = \frac{\omega L}{R}$$

$$X_L = \omega L = R.$$

$$30. \quad V_{net} = \sqrt{V_R^2 + V_L^2} = \sqrt{(20)^2 + (16)^2} = 25.6.$$

$$37. \quad \text{Wattless current} = I_{rms} \sin \phi$$

$$\text{Where } \tan \phi = \frac{\omega L}{R} = \frac{2\pi f L}{R} \quad \text{and } I_{rms} = \frac{V_{rms}}{Z} = \frac{V_{rms}}{\sqrt{R^2 + (\omega L)^2}}$$

$$38. \quad X_C = \frac{1}{\omega C} \text{ will decrease if we increase frequency then } z \text{ will decrease so current will increase \& intensity will increase.}$$

$$39. \quad \cos \phi = \frac{Z_1}{Z_2} \propto \frac{Z_2}{Z_1}$$

$$\% \text{ change in impedance} = 100\%$$

SECTION (D)

$$1. \quad \text{Given : } L = 10 \text{ H, } f = 50 \text{ Hz.}$$

For maximum power

$$X_C = X_L$$

$$\frac{1}{\omega C} = \frac{1}{\omega L}$$

$$C = \frac{1}{\omega^2 L}$$

$$C = \frac{1}{4\pi^2 \times 50 \times 50 \times 10} \therefore C = 0.1 \times 10^{-5} \text{ F} = 1 \, \mu\text{F}$$

$$2. \quad \text{In the condition of resonance}$$

$$X_L = X_C$$

$$\text{or } \omega L = \frac{1}{\omega C} \quad \dots\dots\dots(i)$$

Since, resonant frequency remains unchanged,

$$\text{so, } \sqrt{LC} = \text{constant} \quad \text{or } LC = \text{constant} \therefore L_1 C_1 = L_2 C_2$$

Alternating Current

$$\Rightarrow L \times C = L_2 \times 2C \quad \Rightarrow \quad L_2 = \frac{L}{2}$$

$$3. \quad \frac{q^2}{2C} + \frac{1}{2}LI^2 = \frac{Q^2}{2C} \quad \text{but} \quad \frac{1}{2}LI^2 = \frac{q^2}{2C} \quad \text{So,} \quad 2\left(\frac{q^2}{2C}\right) = \frac{Q^2}{2C} \quad \Rightarrow \quad q = \frac{Q}{\sqrt{2}}$$

$$6. \quad I_m = \omega Q_0 = \frac{CV_0}{\sqrt{LC}} = \frac{2\mu F \cdot 20V}{\sqrt{(8\mu H)(2\mu F)}} = 10.0 \text{ A.}$$

$$10. \quad I_{rms} = \frac{60}{120} = \frac{1}{2} \text{ Amp.}$$

$$V_L = I_{rms} \times (\omega L)$$

$$40 = \frac{1}{2} \times (40 \times 10^3) \times L$$

$$L = 20 \text{ mH}$$

$$\text{At resonance} \quad V_C = I_{rms} \left(\frac{1}{\omega C} \right) = V_L$$

$$C = \frac{1}{2} \times \frac{1}{4 \times 10^3} \times \frac{1}{40} \quad \Rightarrow \quad C = \frac{25}{8} \mu F.$$

$$11. \quad \text{At resonance} \quad \omega L = \frac{1}{\omega C}$$

$$L \propto \frac{1}{C}.$$

$$12. \quad \text{If } n > n_r \quad \omega L > \frac{1}{\omega C} \quad X_L > X_C$$

So, current lags behind voltage.

SECTION (E)

1. The core of transformer is laminated to reduce energy loss due to eddy currents.

2. Given: $i_p = 4 \text{ A}$, $N_p = 140$,
 $N_s = 280$
 From the formula

$$\frac{i_p}{i_s} = \frac{N_s}{N_p} \quad \text{or} \quad \frac{4}{i_s} = \frac{280}{140}$$

So, $i_s = 2 \text{ A}$

3. $P_{out} = 100 \text{ watt}$
 $p_{in} = 200 \times 0.6 \text{ watt.}$
 $= 120 \text{ watt}$
 so $\eta = \frac{100}{120} \times 100\% = \frac{5}{6} \times 100\% = \frac{500}{6}\% = 83.33\%$

4. Frequency of the current remains same, only magnitudes of current changes in a transformer.

5. $\frac{V_2}{V_1} = \frac{N_2}{N_1} = \frac{8}{1}$
 $V_2 = 8 \times 120 = 960 \text{ volt}$
 $I = \frac{960}{10^4} = 96 \text{ mA.}$

6. $\eta\% = \frac{E_2 I_2}{E_1 I_1} \times 100$
7. $I_1 E_1 = I_2 E_2$
 $I_2 = \frac{I_1 E_1}{E_2} = \frac{5 \times 220}{22000} = .05 \text{ A}$
9. $P = 600 \times 1000 = 4000 \times I \Rightarrow I = 150 \text{ A}$
 Power loss = $I^2 r = (150)^2 \times 0.4 \times 20 \times 2 = 360 \text{ kW}$
 Power loss percentage = $\frac{\text{Power loss}}{\text{Power input}} \times 100 = \frac{360}{600} \times 100$
 $\Rightarrow 60 \%$
10. $\frac{N_p}{N_s} = \frac{40,000}{200} = \frac{200}{1}$

EXERCISE # 2

1. The peak value of the current is
 $I_0 = \frac{V_0}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}} = \frac{V_0}{\sqrt{2} R}$ when the angular frequency is changed to $\frac{\omega}{\sqrt{3}}$
 The new peak value is
 $I_0' = \frac{V_0}{\sqrt{R^2 + \frac{3}{\omega^2 C^2}}} = \frac{V_0}{\sqrt{4R^2}} = \frac{V_0}{2R} \therefore I_0' = \frac{I_0}{\sqrt{2}}$
2. $i_{\text{rms}} = \frac{V_{\text{rms}}}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}}$ when ω increases, i_{rms} increases so the bulb glows brighter
3. The full cycle of alternating current consists of two half cycles. For one half, current is positive and for second half, current is negative. Therefore, for an a.c. cycle, the net value of current average out to zero. While for the half cycle, the value of current is different at different points. Hence, the alternating current cannot be measured by D.C. ammeter
4. (i) $\frac{E_2}{E_1} = \frac{N_2}{N_1} = \frac{1}{5} \Rightarrow E_2 = \frac{1000}{5} = 200 \text{ volt.}$
 (ii) $E_2 I_2 = E_1 I_1 \times \eta\%$
 $9000 = 1000 \times I_1 \times \frac{90}{100}$
 $I_1 = 10 \text{ amp.}$
 (iii) The copper loss in the primary coil is = $I_1^2 R_1 = (10)^2 \times 1 = 100$.
 (iv) Total loss = $E_1 I_1 - E_2 I_2 = 1000 \text{ W}$
 Loss in secondary = $1000 - 700 - 100 = 200 \text{ W}$

EXERCISE # 3

PART - I


2. $V_{\text{rms}} = \sqrt{\frac{(T/2)V_0^2 + 0}{T}} = \frac{V_0}{\sqrt{2}}$

Alternating Current

3. If $\omega = 50 \times 2\pi$ then $\omega L = 20\Omega$
 If $\omega' = 100 \times 2\pi$ then $\omega' L = 40\Omega$
- $$I = \frac{200}{Z} \frac{200}{\sqrt{R^2 + (\omega' L)^2}} = \frac{200}{\sqrt{30^2 + (40)^2}}$$
- $I = 4 \text{ A.}$


4. 

$$\frac{X_C}{R} = \tan \frac{\pi}{3}$$

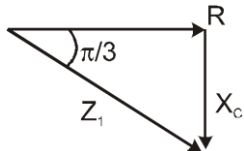

$$X_C = R \tan \frac{\pi}{3} \quad \dots\dots\dots(1)$$

$$\frac{X_L}{R} = \tan \frac{\pi}{3}$$

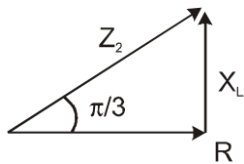

$$X_C = R \tan \frac{\pi}{3} \quad \dots\dots\dots(3)$$

$$\text{net impedance } Z = \sqrt{R^2 + (X_L - X_C)^2} = R$$

$$\text{power factor } \cos \phi = \frac{R}{Z} = 1$$

Ans. (3)

5. $\langle P \rangle = V_{\text{Rms}} \cdot I_{\text{Rms}} \cos \phi$



$$V_{\text{Rms}} = \frac{1}{\frac{\sqrt{2}}{2}} = \frac{1}{2} \text{ volt}$$

$$\Rightarrow I_{\text{Rms}} = \frac{1}{\frac{\sqrt{2}}{2}} = \left(\frac{1}{2}\right) \text{ A}$$

$$\cos \phi = \cos \frac{\pi}{3} = \frac{1}{2}$$

$$\Rightarrow \langle P \rangle = \frac{1}{2} \times \frac{1}{2} \times \frac{1}{2} = \frac{1}{8} \text{ W}$$

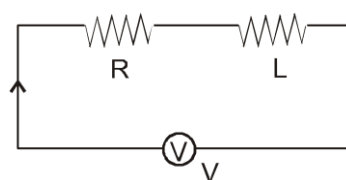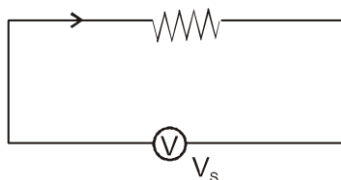6. $L \uparrow \Rightarrow Z \uparrow \Rightarrow I \downarrow$ so brightness \downarrow




- 7.

$$P = i_{\text{rms}}^2 R = \left(\frac{V_s}{R}\right)^2 \cdot R = \frac{V_s^2}{R}$$

$$\Rightarrow P' = i_{\text{rms}}^2 R = \left(\frac{V_s}{Z}\right)^2 \cdot R$$

Alternating Current

$$L\omega = 6.8\Omega$$

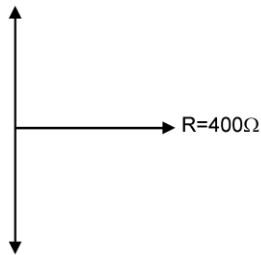

8. $1/C\omega = 58.8$

$$\text{So } |z| = \sqrt{(40)^2 + (58.8 - 6.8)^2} = 65$$

$$i_0 = \frac{v_0}{|z|} = \frac{10}{65} \text{ A} \Rightarrow i_{\text{rms}} = \frac{i_0}{\sqrt{2}} = \frac{10}{65\sqrt{2}}$$

$$P_{\text{loss}} = i_{\text{rms}}^2 R = \left(\frac{10}{65\sqrt{2}} \right)^2 \times 40 = 0.46 \text{ watt}$$

So the nearest answer will be (2)


9. Capacitor does not consume energy effectively over full cycles

10. Option with highest quality factor could be chosen as most appropriate answer.


$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

11. Power factor = $\frac{R}{z} = \frac{iR}{iz} = \frac{80}{\sqrt{(80)^2 + (60)^2}} = \frac{80}{100} = 0.8$

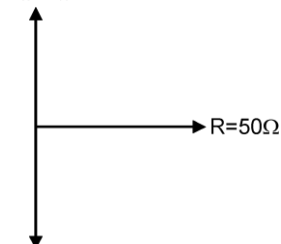12. $z = \sqrt{R^2 + X_c^2} = \sqrt{(100)^2 + (100)^2} = 100\sqrt{2} \Rightarrow i_{\text{max}} = \frac{v_{\text{max}}}{z} = \frac{220\sqrt{2}}{100\sqrt{2}} = 2.2$
 $L\omega = 2\pi$



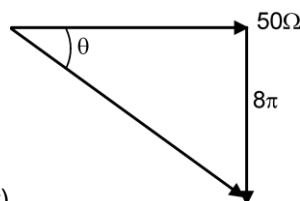13. $V = 10 \sin(100\pi t)$
 $\omega = 100\pi$



$$x_L = L\omega = (20 \times 10^{-3}) 100\pi = 2\pi \Rightarrow c = \frac{1}{L\omega} = \frac{1}{(100 \times 10^{-6}) \times 100\pi} = 10\pi$$

$$|z| = \sqrt{(x_L - x_C)^2 + R^2} \Rightarrow |z| = \sqrt{(8\pi)^2 + (50)^2}$$

$$|z| = \sqrt{3140} \approx 56\Omega \Rightarrow i_0 = \frac{V_0}{|z|} = \frac{10}{56} = 0.18 \text{ A}$$


$$P = i_{\text{rms}}^2 R = \frac{i_0^2 R}{2} = \frac{(0.18)^2 \times 50}{2} = 0.81 \text{ watt}$$

14. If we connect a D.C. source, the steady state current is not blocked ($i_{\text{ss}} = 0.4\text{A}$), so the circuit should not contain capacitor. The circuit should be either only R or LR. Since current in AC circuit and D.C. circuit is different, so the circuit shouldn't be only R so it should be an L-R circuit.


PART - II

$$\begin{aligned}
 1. \quad \tan 30^\circ &= \frac{X_L}{R} \Rightarrow X_L = \frac{R}{\sqrt{3}} = \frac{200}{\sqrt{3}} \\
 \tan 30^\circ &= \frac{X_C}{R} \Rightarrow X_C = \frac{200}{\sqrt{3}} \\
 Z &= \sqrt{R + (X_L - X_C)^2} = 200 \, \Omega \\
 i_{rms} &= \frac{220}{200} = 1.1 \\
 P &= (i_{rms})^2 \times R = (1.1)^2 \times 200 \\
 P &= 242 \, \text{W}
 \end{aligned}$$

$$2. \quad R = 80/10 = 8 \, \Omega$$

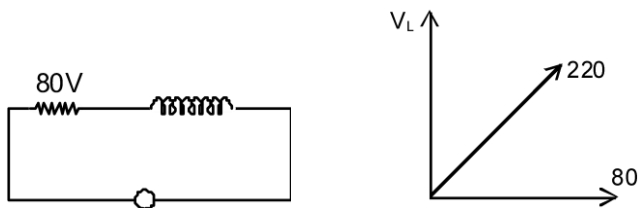
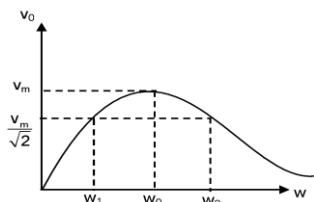
$$\begin{aligned}
 V_L^2 + 80^2 &= 220^2 \Rightarrow V_L^2 = (220 + 80)(220 - 80) = 300 \times 140 \Rightarrow V_L = 204.9 \\
 I_{rms} X_L &= 204.9 \\
 X_L &= 2.5
 \end{aligned}$$



$$\begin{aligned}
 3. \quad \text{Band width} \quad \omega_2 - \omega_1 &= \frac{R}{L} \Rightarrow \text{Quality factor} \quad Q = \frac{\omega_0}{\omega_2 - \omega_1} = \frac{\omega_0 L}{R}
 \end{aligned}$$

$$4. \quad e = 100 \sin 30t$$

$$i = 20 \sin \left(30t - \frac{\pi}{4} \right)$$

$$P_{av} = e_{rms} i_{rms} \cos \phi = \frac{100}{\sqrt{2}} \cdot \frac{20}{\sqrt{2}} \cdot \frac{1}{\sqrt{2}} = \frac{1000}{\sqrt{2}} \, \text{W} \Rightarrow \text{wattless current} = \frac{I_0 \sin \phi}{\sqrt{2}} = \frac{20}{\sqrt{2}} \cdot \frac{1}{\sqrt{2}} = 10 \, \text{A}$$


$$\begin{aligned}
 5. \quad \eta &= \frac{e_s i_s}{e_p i_p} \times 100 \Rightarrow 90 = \frac{230 \times i_s}{2300 \times 5} \times 100 \\
 i_s &= 45 \, \text{A}
 \end{aligned}$$

$$\begin{aligned}
 6. \quad \omega &= 2\pi f = 100\pi \\
 X_L &= \omega L = 6.28 \, \Omega \\
 X_C &= \frac{1}{\omega C} = \frac{250}{3\pi} \\
 X &= X_C - X_L = 20.25 \\
 Z &= \sqrt{R^2 + X^2}
 \end{aligned}$$


Alternating Current

$$I_{\text{rms}} = V_{\text{rms}} / Z$$
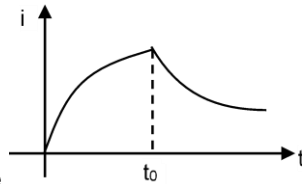
$$\text{Energy dissipated} = i_{\text{rms}}^2 \times R \times t, \quad t = 60 \text{ sec} = 3000T \quad \left(T = \frac{1}{f} = 0.02\text{s} \right) = 5.17 \times 10^2 \text{ J}$$



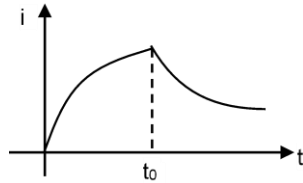7. The correct graph will be
Growth and decay of current is of exponential nature
 $i = i_0(1 - e^{-t/\tau}) \rightarrow$ during growth
 $i = i_{\text{max}} e^{-t/\tau} \rightarrow$ during decay



8. $X_L = \omega L$
 $= 100 \times \frac{\sqrt{3}}{10} = 10\sqrt{3} \Omega$
 $\tan \phi_1 = \frac{10\sqrt{3}}{10} = \sqrt{3}, \phi_1 = 60^\circ$ (Current is lagging)
 $\tan \phi_2 = \frac{1}{\omega CR} = \frac{1}{\sqrt{3}}, \phi_2 = 30^\circ$ (Current is leading)
Total phase difference = 90°