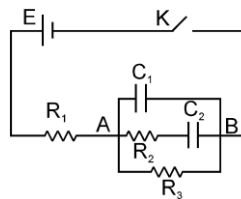


## Exercise-2

▶ Marked Questions can be used as Revision Questions.


### PART - I : OBJECTIVE QUESTIONS

- 1.▶ A network of uncharged capacitors and resistances is shown  
Current through the battery immediately after key K is closed and after a long time interval is :




- (1)  $\frac{E}{R_1}, \frac{E}{R_1 + R_3}$       (2)  $\frac{E}{R_1 + R_3}, \frac{E}{R_1 + \frac{R_2 R_3}{R_2 + R_3}}$   
(3) Zero,  $\frac{E}{R_1}$       (4)  $\frac{E}{R_1 + \frac{R_2 R_3}{R_2 + R_3}}, \frac{E}{R_1}$

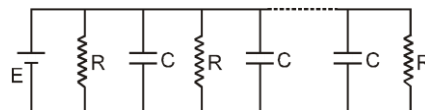2. n resistances each of resistance R are joined with capacitors of capacity C (each) and a battery of emf E as shown in the figure. In steady state condition ratio of charge stored in the first and last capacitor is




- (1)  $n : 1$       (2)  $(n - 1) : (n + 1)$   
(3)  $(n^2 + 1) : (n^2 - 1)$       (4)  $1 : 1$
3. Eight drops of mercury of same radius and having same charge coalesce to form a big drop. Capacitance of big drop relative to that of small drop will be  
(1) 16 times      (2) 8 times      (3) 4 times      (4) 2 times

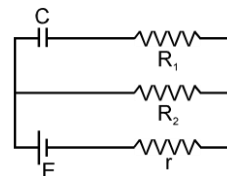- 4.▶ The magnitude of charge in steady state on either of the plates of condenser C in the adjoining circuit is-



- (1) CE      (2)  $\frac{CER_2}{(R_1 + r)}$   
(3)  $\frac{CER_2}{(R_2 + r)}$       (4)  $\frac{CER_1}{(R_2 + r)}$

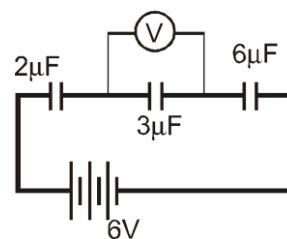- 5.▶ In the combination shown in the figure, the ideal voltmeter reading will be







- (1) 4.5 V  
(2)  $\left(\frac{18}{11}\right)V$   
(3) 3 V  
(4) 2 V

- 6.▶ Three capacitors of same capacitance are connected in parallel. When they are connected to a cell of 2 volt, total charge of  $1.8\mu C$  is accumulated on them. Now after discharging they are connected in series and then charged by the same cell. The total charge stored in them will be  
(1)  $1.8\mu C$       (2)  $0.9\mu C$       (3)  $0.6\mu C$       (4)  $0.2\mu C$




## Capacitance

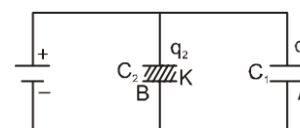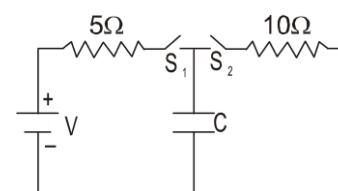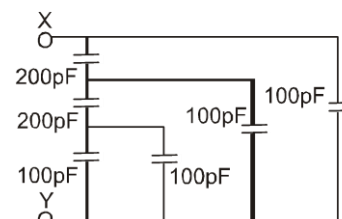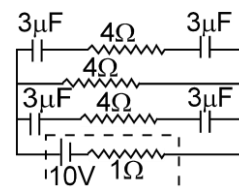7. An uncharged capacitor of capacitance  $8.0 \mu\text{F}$  is connected to a battery of emf  $6.0 \text{ V}$  through a resistance of  $24 \Omega$ , then  
 (i) the current in the circuit just after the connections are made is :  
 (1)  $0.25 \text{ A}$  (2)  $0.5 \text{ A}$  (3)  $0.4 \text{ A}$  (4)  $0 \text{ A}$   
 (ii) the current in the circuit at one time constant after the connections are made is :  
 (1)  $0.25 \text{ A}$  (2)  $0.09 \text{ A}$  (3)  $0.4 \text{ A}$  (4)  $0 \text{ A}$
8. A capacitor of capacitance  $500 \mu\text{F}$  is charged at the rate of  $100 \mu\text{C/s}$ . The time in which the potential difference will become  $20 \text{ V}$ , is  
 (1)  $100 \text{ s}$  (2)  $50 \text{ s}$  (3)  $20 \text{ s}$  (4)  $10 \text{ s}$
9. The radius of the circular plates of a parallel plate capacitor is  $R$ . Air is dielectric medium between the plates. If the capacitance of the capacitor is equal to the capacitance of a sphere of radius  $R$ , then the distance between the plates is  
 (1)  $R/4$  (2)  $R/2$  (3)  $R$  (4)  $2R$
10. A parallel plate condenser of capacity  $C$  is connected to a battery and is charged to potential  $V$ . Another condenser of capacity  $2C$  is connected to another battery and is charged to potential  $2V$ . The charging batteries are removed and now the condensers are connected in such a way that the positive plate of one is connected to negative plate of another. The final energy of this system is—  
 (1) zero (2)  $\frac{25CV^2}{6}$  (3)  $\frac{3CV^2}{2}$  (4)  $\frac{9CV^2}{2}$
11. In the following figure, the charge on each condenser in the steady state will be—  
 (1)  $3 \mu\text{C}$  (2)  $6 \mu\text{C}$   
 (3)  $9 \mu\text{C}$  (4)  $12 \mu\text{C}$
12. The equivalent capacitance between the terminals X and Y in the figure shown will be—  
 (1)  $100 \text{ pF}$   
 (2)  $200 \text{ pF}$   
 (3)  $300 \text{ pF}$   
 (4)  $400 \text{ pF}$
13. In the adjoining diagram, (assuming the battery to be ideal) the condenser C will be fully charged to potential  $V$  if  
 (1)  $S_1$  and  $S_2$  both are open  
 (2)  $S_1$  and  $S_2$  both are closed  
 (3)  $S_1$  is closed and  $S_2$  is open  
 (4)  $S_1$  is open and  $S_2$  is closed.
14. In the adjoining diagram two geometrically identical capacitors A and B are connected to a battery. Air is filled between the plates of  $C_1$  and a dielectric is filled between the plates of  $C_2$ , then -  
 (1)  $q^1 < q^2$  (2)  $q^1 > q^2$   
 (3)  $q^1 = q^2$  (4) None of these



## Capacitance

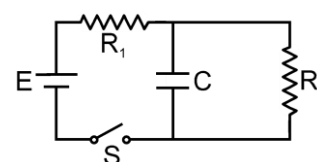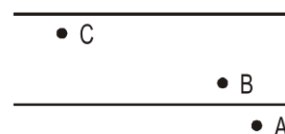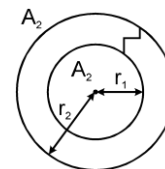15. An uncharged capacitor of capacitance  $C$  is connected to a battery of emf  $\varepsilon$  at  $t = 0$  through a resistance  $R$ , then  
 (i) the maximum rate at which energy is stored in the capacitor is :  
 (1)  $\frac{\varepsilon^2}{4R}$  (2)  $\frac{\varepsilon^2}{2R}$  (3)  $\frac{\varepsilon^2}{R}$  (4)  $\frac{2\varepsilon^2}{R}$   
 (ii) time at which the rate has this maximum value is  
 (1)  $2CR \ln 2$  (2)  $\frac{1}{2} CR \ln 2$  (3)  $CR \ln 2$  (4)  $3CR \ln 2$
16. Two spherical conductors  $A_1$  and  $A_2$  of radii  $r_1$  and  $r_2$  are placed concentrically in air. The two are connected by a copper wire as shown in figure. Then the equivalent capacitance of the system is  
 (1)  $\frac{4\pi\varepsilon_0 kr_1 r_2}{r_2 - r_1}$  (2)  $4\pi\varepsilon_0 (r_1 + r_2)$   
 (3)  $4\pi\varepsilon_0 r_2$  (4)  $4\pi\varepsilon_0 r_1$
17. The plates of a parallel plate condenser are being moved away with a constant speed  $v$ . If the plate separation at any instant of time is  $d$  then the rate of change of capacitance with time is proportional to—  
 (1)  $\frac{1}{d}$  (2)  $\frac{1}{d^2}$  (3)  $d^2$  (4)  $d$
18. For a charged parallel plate capacitor shown in the figure, the force experienced by an alpha particle will be :  
 (1) maximum at C (2) zero at A  
 (3) same at A and C (4) zero at C
19. In the circuit shown in figure the switch is closed at  $t = 0$ . A long time after closing the switch  
 (1) voltage drop across the capacitor is  $E$   
 (2) current through the battery is  $\frac{E}{R_1 + R_2}$   
 (3) energy stored in the capacitor is  $C \left( \frac{R_2 E}{R_1 + R_2} \right)^2$   
 (4) current through the capacitor becomes none zero



## PART - II : MISCELLANEOUS QUESTIONS


### Section (A) : Assertion/Reasoning

- A-1. **STATEMENT-1** : If the potential difference across a plane parallel plate capacitor is doubled then the potential energy of the capacitor becomes four times under all conditions.


**STATEMENT-2** : The potential energy  $U$  stored in the capacitor is  $U = \frac{1}{2} CV^2$ , where  $C$  and  $V$  have usual meaning.

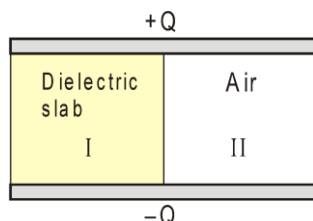- (1) Statement-1 is True, Statement-2 is True; Statement-2 is a correct explanation for Statement-1.  
 (2) Statement-1 is True, Statement-2 is True; Statement-2 is NOT a correct explanation for Statement-1  
 (3) Statement-1 is True, Statement-2 is False  
 (4) Statement-1 is False, Statement-2 is True

- A-2. STATEMENT-1 :** A charged plane parallel plate capacitor has half interplanar region (I) filled with dielectric slab. The other half region II has air. Then the magnitude of net electric field in region I is less than that in region II.



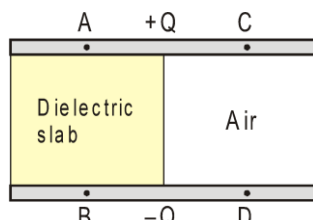**STATEMENT-2 :** In a dielectric medium induced (or polarised) charges tend to reduce the electric field inside the dielectric.



- (1) Statement-1 is True, Statement-2 is True; Statement-2 is a correct explanation for Statement-1
- (2) Statement-1 is True, Statement-2 is True; Statement-2 is NOT a correct explanation for Statement-1
- (3) Statement-1 is True, Statement-2 is False
- (4) Statement-1 is False, Statement-2 is True.


- A-3. Statement-1 :** The circuits containing capacitor be handled cautiously even when there is no current.

**Statement-2 :** A charged capacitor, can discharge through our body and harm us.

- (1) Statement-1 is True, Statement-2 is True; Statement-2 is a correct explanation for Statement-1
- (2) Statement-1 is True, Statement-2 is True; Statement-2 is NOT a correct explanation for Statement-1
- (3) Statement-1 is True, Statement-2 is False
- (4) Statement-1 is False, Statement-2 is True.
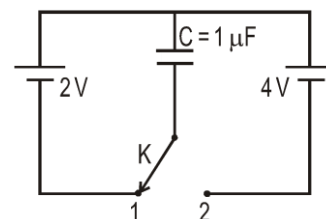
### Section (B) : Match the column

- B-1.** The circuit involves two ideal cells connected to a  $1\ \mu\text{F}$  capacitor via a key K. Initially the key K is in position 1 and the capacitor is charged fully by 2V cell. The key is then pushed to position 2. Column I gives physical quantities involving the circuit after the key is pushed from position 1. Column II gives corresponding results. Match the statements in Column I with the corresponding values in Column II.



#### Column I

- (1) The net charge crossing the 4 volt cell in  $\mu\text{C}$  is
- (2) The magnitude of work done by 4 Volt cell in  $\mu\text{J}$  is
- (3) The gain in potential energy of capacitor in  $\mu\text{J}$  is
- (4) The net heat produced in circuit in  $\mu\text{J}$  is

#### Column II

- (p) 2
- (q) 6
- (r) 8
- (s) 16


### Section (C) : One or More Than One Options Correct

- C-1.** In the circuit shown in figure the switch S is closed at  $t = 0$ . A long time after closing the switch

- (1) voltage drop across the capacitor is  $E$

- (2) current through the battery is  $\frac{E}{R_1 + R_2 + R_3}$

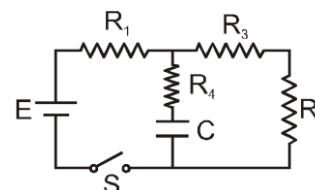- (3) energy stored in the capacitor is  $\frac{1}{2} C \left( \frac{(R_2 + R_3)E}{R_1 + R_2 + R_3} \right)^2$
- (4) current through the resistance  $R_4$  becomes zero



- C-2.** When a charged capacitor is connected with an uncharged capacitor, then which of the following is/are correct option/options.

- (1) the magnitude of charge on the charged capacitor decreases.


## Capacitance

- (2) a steady state is obtained after which no further flow of charge occurs.
- (3) the total potential energy stored in the capacitors remains conserved.
- (4) the charge conservation is always true.

**C-3.** The charge on capacitor in two different RC circuits 1 and 2 are plotted as shown in figure.

Choose the correct statement(s) related to the two circuits.

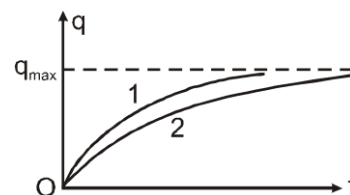- (1) Both the capacitors are charged to the same magnitude of charge
- (2) The emf's of cells in both the circuits are equal.
- (3) The emf's of the cells may be different
- (4) The emf  $E_1$  is more than  $E_2$



**C-4.** Capacitor  $C_1$  of the capacitance 1 microfarad and capacitor  $C_2$  of capacitance 2 microfarad are separately charged fully by a common battery. The two capacitors are then separately allowed to discharge through equal resistors at time  $t = 0$ .

- (1) the current in each of the two discharging circuits is zero at  $t = 0$ .
- (2) the current in the two discharging circuits at  $t = 0$  are equal but non zero.
- (3) the current in the two discharging circuits at  $t = 0$  are unequal
- (4) capacitor  $C_1$  loses 50% of its initial charge sooner than  $C_2$  loses 50% of its initial charge

**C-5.** The terminals of a battery of emf  $V$  are connected to the two plates of a parallel plate capacitor. If the space between the plates of the capacitor is filled with an insulator of dielectric constant  $K$ , then :

- (1) the electric field in the space between the plates does not change
- (2) the capacitance of the capacitor increases
- (3) the charge stored in the capacitor increases
- (4) the electrostatic energy stored in the capacitor decreases

**C-6.** The plates of a parallel plate capacitor with no dielectric are connected to a voltage source. Now a dielectric of dielectric constant  $K$  is inserted to fill the whole space between the plates with voltage source remaining connected to the capacitor.

- (1) the energy stored in the capacitor will become  $K$ -times
- (2) the electric field inside the capacitor will decrease to  $K$ -times
- (3) the force of attraction between the plates will increase to  $K^2$  – times
- (4) the charge on the capacitor will increase to  $K$ -times