• C	urrent Electricity			
	Exercise	-1		
	C		ON CORRECT T	YPE
SEC	TION (A) : DEFINITIO	ON OF CURRENT, (CURRENT DENSITI	ES, DRIFT
1.	The drift velocity of elec after the switch is put of (1) The random speed (2) The electrons trans (3) Electric field is set of intantaneously (4) All of above	ctrons in a conducting w on because of electrons is very hig fer their energy very qu up in the wire very quic	wire is of the order of 1m gh, of the order of 10₅ m/ uickly through collisions kly, producing a current t	m/s, yet the bulb glows very quickly s through each cross section, almost
2.	In the presence of an a (1) The electrons move (2) The electrons move (3) The electrons may (4) The electrons move	applied electric field (E e in the direction of E e in a direction opposite move in any direction r e randomly but slowly o) in a metallic conductor e to E randomly, but slowly drift drift in a direction opposit	t in the direction of \vec{E} .
3.	A current of 4.8 A is flo per second is (1) 3 × 1019	owing in a conductor. T (2) 76.8 × 10 ₂₀	The number of electrons (3) 7.68 × 10 ₁₂	passing through any cross-section (4) 3 × 10 ₁₀
SEC	TION (B): RESISTAN	ICE		
1.	Specific resistance of a (1) mass	a wire depends on its (2) length	(3) area of cross-se	ction(4) None of the above
2.	There are two wires of specific resistance is (1) 1 : 2	f the same length and (2) 1 : 1	of the same material an (3) 1 : 4	nd radii r and 2r. The ratio of their (4) 4 : 1
3.	If the length and cross (1) become half	-section of a wire is do (2) increase two time	ubled, then the resistanc s (3) remain unchange	e will ed (4) increase four times
4.	V-i graph for an ohmic (1) straight line	resistance is (2) hyperbola	(3) parabola	(4) circle
5.	When a resistance wire resistance of the wire i (1) 1% decrease	e is passed through a c s (2) 1% increase	die the cross–section are (3) 2% decrease	ea decreases by 1%, the change in (4) 2% increase
6.	When the resistance of resistance of copper is (1) 10 cm	f copper wire is 0.1 Ω ar 3.14 × 10-₀ ohm x m) (2) 10 m	nd the radius is 1 mm, the (3) 100 m	en the length of the wire is (specific (4) 100 cm
7.	Three copper wires of minimum in (1) wire of cross–sectio (3) wire of cross–sectio	f length and cross–seo onal area A onal area 2A	ctional area (L, A), (2L, (2) wire of area A/2 (4) same in all three	A/2) and (L/2, 2A). Resistance is cases
8.	The resistance of a wi	re of cross-section 'a' a	and length ' / ' is R ohm	The resistance of another wire of

8. The resistance of a wire of cross-section 'a' and length 'ℓ' is R ohm. The resistance of another wire of the same material and of the same length but cross-section '4a' will be



If a wire of resistance R is stretched to double of its length, then the new resistance will be 10. [R-PMT 2003]

(1)
$$\frac{R}{2}$$
 (2) 2R (3) 4R (4) 16R

11. All the edges of a block in cuboidal shape with parallel faces are unequal. Its longest edge is twice its shortest edge. The ratio of the maximum to minimum resistance between parallel faces is: (a > b > c)



Read the following statements carefully :

Y: The resistivity of semiconductor decreases with increase of temperature.

Z: In a conducting solid, the rate of collisions between free electrons and ions increases with increase of temperature. Select the correct statement (s) from the following :

- (1) Y is true but Z is false
- (3) Both Y and Z are true

(1) 2

12.

- (2) Y is false but Z is true

- (4) Y is true and Z is the correct reason for Y
- The dimensions of a block are 1 cm x 1 cm x 100 cm. If the specific resistance of its material is 13. $2 \times 10^{-7} \text{ ohm} \times \text{metre}$, then the resistance between the opposite rectangular faces is

(3) 2×10⁻⁵Ω (2) $2 \times 10^{-7} \Omega$ (1) $2 \times 10^{-9} \Omega$ (4) $2 \times 10^{-3} \Omega$

14. A conductor with rectangular cross section has dimension (a x 2a x 4a) as shown in fig. Resistance across AB is x, across CD is y and across EF is z. Then



(1) x = y = z

be

(1) ρ₁

Resistance of a wire is 20 ohm, it is stretched upto, three times of its length, then its new resistance will

(4) 180 Ω

and B is

[RPMT 2001]

(4) x > z > y

(2) 60 Ω 6.67 Ω (3) 120 Ω

 $\left(\rho_1 + \rho_2\right)$

Two wires of same dimension but resistivities p1 and p2 are connected in series. The equivalent resistivity 16. of the combination is

(1)
$$\rho_1 + \rho_2$$
 (2) (3) $\sqrt{\rho_1 \rho_2}$
In the given figure, the equivalent resistance between the points A

(4) $2(\rho_1 + \rho_2)$ [AIIMS 1999]

15.

17.





35.	hiform thickness and resistance ated by a distance of 50 cm will 2004]			
	(1) 2V	(2) 3V	(3) 1V	(4) 1.5 V
36.	When a wire of uniform of between two of diametrics	cross-section a, length ℓ a cally opposite points will R	and resistance R is bent in be :	nto a complete circle, resistance [AIPMT 2005] R
	(1) $\frac{1}{4}$	(2) 8	(3) 4R	(4) $\frac{1}{2}$
37.	A wire of a certain mate become respectively. (1) 1.2 times, 1.1 times	rial is stretched slowly be	e ten per cent. Its new res (2) 1.21 times, same	sistance and specific resistance [AIPMT 2008]
	(3) both remain the sam	ie	(4) 1.1 times, 1.1 times	
38.	An electric kettle takes temperature 20°C? The	4 A current at 220 V. temperature of boiling w	How much time will it ta ater is 100°C	ake to boil 1 kg of water from [AIPMT 2008]

SECTION (C): POWER, ENERGY, BATTERY, EMF, TERMINAL VOLTAGE, KCL & KVL

(3) 12.6 min

(4) 4.2 min

[RPMT 2000]

- 1. In an electric circuit containing a battery, the positive charge inside the battery
 - (1) always goes from the positive terminal to the negative terminal
 - (2) may go from the positive terminal to the negative terminal

(2) 8.4 min

- (3) always goes from the negative terminal to the positive terminal
- (4) does not move.

(1) 6.3 min

2. In which of the above cells, the potential difference between the terminals of a cell exceeds its emf.



Q.3 for the following circuits, the potential difference between X and Y in volt is

- The efficiency of a cell when connected to a resistance R is 60%. What will be its efficiency if the external resistance is increased to six times.
 (1) 80 % (2) 90% (3) 55% (4) 95%
- Two bulbs 25W, 220V and 100W, 220V are given. Which has higher resistance ? [AIPMT 2000]
 (1) 25W bulb
 (2) 100 W bulb
 (3) Both bulbs will have equal resistance
 (4) Resistance of bulbs cannot be compared
- 5. The resistors whose ratio is 1 : 2, are connected in parallel, the ratio of power dissipated is :

(1) 1 : 2 (2) 1 : 4 (3) 4 : 1 (4) 2 : 1

6. Find the current flowing through the resistance R_1 of the circuit shown in figure if the resistances are equal to $R_1 = 10 \Omega$, $R_2 = 20 \Omega$, and $R_3 = 30 \Omega$, and the potentials of points 1, 2 and 3 are equal to $\phi_1 = 10 V$, $\phi_2 = 6 V$, and $\phi_3 = 5 V$.



18.	A 220 volt, 1000	watt bulb is connecte	d across a 110 volt mains sup	ply. The power consumed will be-
	(1) 750 watt	(2) 500 watt	(3) 250 watt	(4) 1000 watt
19.	Time taken by a (1) 50 s	836 W heater to heat (2) 100 s	one litre of water from 10°C to (3) 150 s	40°C is : [AIEEE 2004, 4/300] (4) 200 s
20.	The resistance of 100 W and 20 (1) 40 Ω	of hot tungsten filamen 00 V lamp when not in (2) 20 Ω	t is about 10 times the cold res use : (3) 400 Ω	sistance. What will be the resistance [AIEEE 2005, 4/300] (4) 200 Ω
21.	An electric bulb	is rated 220 volt - 100	watt. The power consumed by	it when operated on 110 volt will be
	(1) 25 watt	(2) 50 watt	(3) 75 watt	(4) 40 watt
22.	The Kirchhoff's f meanings, are re (1) conservation (2) conservation (3) conservation (4) conservation	$\left(\sum_{i=0}^{i=0}\right)$ and spectively based on of charge, conservation of charge, conservation of energy, conservation of momentum, conserv	second law $\left(\sum iR = 0 = \sum E\right)$ of energy of momentum of charge ation of charge	, where the symbols have their usual [AIEEE 2006, 1½/180]
23.	An electric kettle the kettle boils connected in pa (1) 25 min	e has two heating coils in 10 min. When the rallel, the time taken b (2) 15 min	. When one of the coils is conr other coil is used the water b y the same quantity of water to (3) 8 min	nected to an AC source, the water in oils in 40 min. If both the coils are boil will be : [AIPMT 2003] (4) 4 min
24.	Two 220V, 100V connected to a 2 be : (1) 200W, 150W	W bulbs are connected 220V AC supply line. T (2) 50W, 200V	d first in series and then in pa he power drawn by the combi N (3) 50W, 100W	rallel. Each time the combination is nation in each case respectively will [AIPMT 2003] (4) 100W, 50W
25.	A battery is char supplies a curre efficiency of the (1) 82.5 %	ged at a potential of 15 ent of 5A for 15H. The battery is : (2) 80%	V for 8H when the current flow mean terminal voltage during (3) 90%	ing is 10A. The battery on discharge discharge is 14V. The "watt-hour" [AIPMT 2004] (4) 87.5 %
26.	In India electrici 60W bulb for us	ty is supplied for dome e in India. is R, the res	estic use at 220V. It is supplie istance of a 60W bulb for use R	d at 110V in USA. If resistance of a in USA will be : [AIPMT 2004] R
	(1) R	(2) 2R	(3) 4	(4) 2
27.	A 5-A fuse wire	can withstand a maxin	num power of 1W in circuit. Th	e resistance of the fuse wire is : [AIPMT 2005]
	(1) 0.2Ω	(2) 5Ω	(3) 0.4Ω (4) 0.04Ω	
28.	Kirchhoff's first a (1) Conservation (3) Conservation	and second laws for el n of energy n of electric charge	ectrical circuits are consequer (2) Conservation of electric (4) Conservation of energy	cs of :- [AIPMT 2006] charge and energy respectively and elecric charge respectivelay
29.	When three iden drawn by them v (1) 60 W	ntical bulbs of 60W, 2 will be : (2) 180 W	00 V rating are connected in (3) 10 W	series to a 200V supply, the power [AIPMT 2004] (4) 20 W

SECTION (D): COMBINATION OF RESISTANCE

1.	Two coils connected in series have resistances 600 Ω and 300 Ω at 20°C and temperature coefficient resistivity 0.001 k ₋₁ and 0.004 k ₋₁ respectively. (a) The resistance of the combination at temperature 50°C is (1) 426 Ω (2) 954 Ω (3) 1806 Ω (4) 214 Ω								ent of				
	(b)	The effective te	emperatu	re coeffic	cient of	the com	ibinati	on is		(.	,		
		$\frac{1}{1000}$	-	$\frac{1}{250}$			(a) -	1		<i>.</i> .	3	<u> </u>	
2	Δ wire I	(1) toot degree (1)	ee₋₁ • of 12 oh	(2) 250 ms If it	degre is bent	e_1 in the fo	(3) (3) arm of	a circle	gree₋₁ > The e	(4 ffective		degree	e-1
2.	the two (1) 6 Ω	points on any d	liameter is (2) 3 Ω	s equal t	0	(3) 9 Ω			(4)	12 Ω	100101		ween
3.	A wire I	nas a resistance	12 ohms	. if it is b	ent in tl	he form o	of a eo	quilater	al triangl	e. The	e resist	tance bet	ween
	(1) 8/3	terminais is	(2) 3/4			(3) 4			(4)	3			
4.	There a are join	are five resistand ed in series, the	ces of 1 o en the fina	hm each al resista	i. If the nce is	initial th	iree re	esistanc	e are joi	ned in	paralle	el and res	st two
	(1) 3 oh	nm	(2) 8 oh	m		(3) 7/3	ohm		(4)	5 ohm			
	Que-5-	11 For the follo	wing cire	cuits, th	e equi	valent re	esista	ince be	tween >	(and Y	í in vo	olt is	
5.	(Take F	R = 3 Ω)											
	R Z ZF	R 2R 2R 2R 2R 2R 2R 2R 2R 2R 2R 2R 2R 2R) R										
	(1) R	Δ	(2) 2R			(3) 3R			(4)	R/2			
6	R, FR, K	ZZR ZR RZ RZ yb											
0.	(1) 4 R	'	(2) 8 R/	3		(3) R			(4)	3 R			
7.	X	ZR YR YR YR											
	(1) R		(2) 4 R			(3) 5 R			(4)	6 R			
8.	10Ω+4 	οχ οχ ογ γ γ γ γ 10Ω											



11. For the network of resistance shown in the figure the equivalent resistance of the network between the points A and B is 18 ohm. The value of unknown resistance R is:- [RPET-97]



- 12.If 2 bulbs rated 2.5 W 110 V and 100 W 110 V are connected in series to a 220 V supply then
(1) 2.5 W bulb will fuse
(3) both will fuse(2) 100 W bulb will fuse
(4) both will not fuse
- **13.**A 50 W bulb is in series with a room heater and the combination is connected across the mains. To get
max. heater output, the 50 W bulb should be replaced by
(1) 25 W(2) 10 W(3) 100 W(4) 200 W

In the following Questions (14 to 19), find the potential difference between points X and Y.







21. The equivalent resistance between A and B in the given circuit will be [RPMT 2003]



27. If the reading of ammeter A₁ in figure is 2.4 A. Neglecting the resistances of the ammeters, the reading of ammeter A₂ will be :



33. Y R. R. R. R.

- (1) R (2) 2R (3) R/2 (4) 4 R
- **34.** Arrange the order of power dissipated in the given circuits, if the same current is passing through the system. The resistance of each resistor is 'r'. [JEE(Scr.) 2003, 3/84]



35. A 100 W bulb B₁ and two 60 W bulbs B₂ and B₃ are connected to a 250 V source as shown in the figure. Now W₁, W₂ and W₃ are the output powers of the bulbs B₁, B₂ and B₃ respectively. Then:

[JEE(Scr.) - 2002, 3/105]



(1) $W_1 > W_2 = W_3$ (2) $W_1 > W_2 > W_3$ (3) $W_1 < W_2 = W_3$ (4) $W_1 < W_2 < W_3$ **36.** Two bars of equal resistivity ρ and radii 'r' and '2r' are kept in contact as shown. An electric current I is passed through the bars. Which one of the following is correct?[JEE' 2006 ; 3/184]



- (1) Heat produced in bar (1) is 2 times the heat produced in bar (2)
- (2) Electric field in both halves is equal
- (3) Current density across AB is double that of across BC.
- (4) Potential difference across BC is 4 times that of across AB.
- **37.** From resistances of 100 ohm each are connected in the form of a square. The effective resistance along the diagonal points P R is : [RPMT 2005]



38. The potential difference across BC in the following figure will be :

[RPMT 2004]



(1) 1/3 A

(1) 1 A

- (1) 2Ω (2) 6Ω (3) 5Ω (4) 4Ω
- 45. A 3 volt battery with negligible internal resistance is connected in a circuit as shown in the figure. Current i will be : [AIEEE 2003, 4/300]



[AIEEE 2004, 4/300]

46. The total current supplied to the circuit by the battery is :

(2) 2 A



(4) 6 A

(4) 2 A

- 47.The resistance of the series combination of two resistances is S. When they are joined in parallel, the
total resistance is P. If S = nP, then the minimum possible value of n is :
(1) 4[AIEEE 2004, 4/300]
(4) 1
- An electric current is passed through a circuit containing two wires of the same material, connected in parallel. If the lengths and radii of the wires are in the ratio of 4/3 and 2/3, then the ratio of the currents passing through the wire will be : [AIEEE 2004, 4/300]
 (1) 3 (2) 1/3 (3) 8/9 (4) 2
- **49.** The current I drawn from the 5 volt source will be

[AIEEE 2006, 3/180]



50. In a Wheat stone's bridge, three resistances P, Q and R are connected in the three arms and the fourth arm is formed by two resistances S₁ and S₂ connected in parallel. The condition for the bridge to be balanced will be [AIEEE 2006, 3/180]

$$\frac{P}{Q} = \frac{R(S_1 + S_2)}{2S_1S_2} \qquad \frac{P}{Q} = \frac{R}{S_1 + S_2} \qquad (3) \frac{P}{Q} = \frac{2R}{S_1 + S_2} \qquad (4) \frac{P}{Q} = \frac{R(S_1 + S_2)}{S_1S_2}$$

51. For a cell the terminal potential difference is 2.2V when circuit is open and reduces to 1.8V when cell is connected to a resistance $R = 5\Omega$, the internal resistance (r) of cell is : [AIPMT 2002]

$$(1) \frac{10}{9}_{\Omega} \qquad (2) \frac{9}{10}^{\Omega} \qquad (3) \frac{11}{9}^{\Omega} \qquad (4) \frac{5}{9}^{\Omega}$$

3V

R

(1)

52. In a Wheatstone's bridge all the four arms have equal resistance R. If the resistance of the galvanometer arm is also R, the equivalent resistance of the combination as seen by the battery is : [AIPMT 2003]

		R	R
		(0) 1	(n) $\overline{2}$
(1) R	(2) 2R	(3) 4	(4) 2

53. Resistances n, each of r ohm, when connected in parallel given an equivalent resistance of R ohm. If these resistances were connected in series, the combination would have a resistance in ohms, equal to: [AIPMT 2004]

54. Five equal resistances each of resistance R are connected as shown in the figure. A battery of V volts is connected between A and B. The current flowing in AFCEB will be : [AIPMT 2004]



55. For the network shown in the figure, the value of the current i is :



56. In the circuit shown, if a conducting wire is connected between points A and B, the current in this wire will :-[AIPMT 2006]



[AIPMT 2005]

(1) Flow from A to B (3) Be zero

(2) Flow in the direction which will be decided by the value of V (4) Flow from B to A

2V

57. Power dissipated across the 80 resistor in the circuit shown here is 2 watt. The power dissipated in watt units across the 30 resistor is :-[AIPMT 2006]





61. In the circuit shown, the current through the 4Ω resistor is 1 A when the points P and M are connected to a DC voltage source. The potential difference between the points M and N is [AIPMT 2008]



SECTION (E): COMBINATION OF CELLS

- 1. Two nonideal batteries are connected in parallel. Consider the following statements
 - (I) The equivalent emf is smaller than either of the two emfs.
 - (II) The equivalent internal resistance is smaller than either of the two internal resistance.

2.

- (1) Both I and II are correct (2) I is
- (3) II is correct but I is wrong

- (2) I is correct but II is wrong (4) Each of I and II is wrong.
- 12 cells each having the same emf are connected in series and are kept in a closed box. Some of the cells are wrongly connected. This battery is connected in series with an ammeter and two cells identical with each other and also identical with the previous cells. The current is 3 A when the external cells aid this battery and is 2 A when the cells oppose the battery. How many cells in the battery are wrongly connected? (1) one (2) two (3) three (4) none
- **3.** Two batteries, one of emf 18V and internal resistance 2Ω and the other of emf 12 V and internal resistance 1Ω , are connected as shown. The voltmeter V will record a reading of :**[AIPMT 2005]**



4. n equal cell having e.m.f. E and internal resistance r, are connected in circuit of a resistance R. Same current flows in circuit either they connected in series or parallel, if : [R_PMT 2002]

(1)
$$R = nr$$
 (2) $R = n$ (3) $R = n_2 r$ (4) $R = 1$

r

5. Two cells of e.m.f. 10 V & 15 V are connected in parallel to each other between points A & B. The cell of e.m.f. 10 V is ideal but the cell of e.m.f. 15 V has internal resistance 1 Ω. The equivalent e.m.f. between A and B is:



6. Two ideal batteries of emf V₁ and V₂ and three resistances R₁, R₂ and R₃ are connected as shown in the figure. The current in resistance R₂ would be non-zero, if **[JEE (Advanced)-2014,P-1, 3/60]**



- 7. Two non-ideal batteries are connected in parallel. Consider the following statements. **[R_PMT 2008]** (i) The equivalent emf is smaller than either of the two emfs.
 - (ii) The equivalent internal resistance is smaller than either of the two internal resistances.
 - (1) Both (i) and (ii) are correct
 - (3) (ii) is correct but (i) is wrong
- (2) (i) correct but (ii) is wrong(4) Both (i) and (ii) are wrong

8. Two sources of equal emf are connected to an external resistance R. The internal resistances of the two sources are R₁ and R₂ (R₂ > R₁). If the potential difference across internal resistance R₂, is zero, then: **[AIEEE 2005, 4/300]**

(1)
$$R = \frac{R_2 \times (R_1 + R_2)}{(R_2 - R_1)}$$
 (2) $R = R_2 - R_1$ (3) $R = \frac{R_1 R_2}{(R_2 + R_1)}$ (4) $R = \frac{R_1 R_2}{(R_2 - R_1)}$

9. In the circuit, the galvanometer G shows zero deflection. If the batteries A and B have negligible internal resistance, the value of the resistor R will be : [AIEEE 2005, 4/300]



10. A 5 V battery with internal resistance 2 Ω and a 2V battery with internal resistance 1 Ω are connected to a 10 Ω resistor as shown in the figure. [AIEEE 2008, 3/105]



The current in the 10 Ω resistor is -(1) 0.03 A P₁ to P₂ (2) 0.03 A P₂ to P₁ (3) 0.27 A P₁ to P₂ (4) 0.27 A P₂ to P₁

11. Two cells, having the same e.m. f., are connected in series through an external resistance R. Cells have internal resistances r_1 and r_2 ($r_1 > r_2$) respectively. When the circuit is closed, the potential difference across the first cell is zero. The value of R is :- [AIPMT 2006]

(1)
$$r_1 - r_2$$
 (2) $\frac{r_1 + r_2}{2}$ (3) $\frac{r_1 - r_2}{2}$ (4) $r_1 + r_2$

SECTION (F): INSTRUMENT

1. The reading of voltmeter is



2. The current through the ammeter shown in figure is 1 A. If each of the 4Ω resistor is replaced by 2Ω resistor, the current in circuit will become nearly :



(1)
$$\frac{10}{9}_{A}$$
 (2) $\frac{5}{4}$ (3) $\frac{9}{8}_{A}$ (4) $\frac{9}{8}_{A}$

3. The meter-bridge wire AB shown in figure is 50 cm long. When AD = 30 cm, no deflection occurs in the galvanometer. Find R.



Reading of ammeter in ampere for the following circuit is (Q. 4 to 6)





	(3) Voltmeter of range 1	.0 V	(4) ammeter of range 1	0 A	•
24.	Resistivity of potentioner i = 0.1A flows through the (1) 10-2 V/m	eter wire is 10-7 ohm-met ne wire, its potential grac (2) 10-4 V/m	re and its area of cross-se dient is : (3) 0.1 V/m	ection is 10 [AIPMT 2 (4) 10V/r	0–6m2. When a current 2001] n
25.	In electrolysis the mass (1) Current (3) Concentration of sol	deposited on an electro ution	de is directly proportiona (2) Square of current (4) Inverse of current	l to :	[AIPMT 2000]
26.	The material of wire of p (1) Copper	ootentiometer is (2) Steel	(3) Manganin] (4) Alum	MP PMT 2002] inium
27.	An ammeter and a volter resistance is now joined (1) both A and V will inc (3) A will decrease, V w	meter are joined in serie d in parallel with the voltr crease vill increase	s to a cell. Their reading neter, (2) both A and V will de (4) A will increase, V wi	s are A a crease Il decreas	nd V respectively. If a e
28.	In the given circuit, no c wire AB is doubled, the	urrent is passing through n for null point of galvand	n the galvanometer. If the pometer, the value of AC v	cross-see would be: [JEE(Sc	ctional diameter of the r.) - 2003, 3/84]
	(1) 2 X	(2) X	$(3)\frac{2}{2}$	(4) None	
29.	A galvanometer can be (1) high resistance in pa (3) low resistance in pa	changed into ammeter b arallel rallel	by connecting : (3) high resistance in se (4) low resistance in se	eries. ries	R_PMT 2005]
30.	Sensitivity of potention (1) increasing the emf of (2) increasing the length (3) decreasing the length (4) None of the above	eter can be increased by If the cell In of the potentiometer wi th of the potentiometer w	re vire	I	R_PMT 2009]
31.	The material of wire of p (1) copper	ootentiometer is (2) steel	(3) manganin	[(4) alumi	R_PMT 2009] nium
32.	If an ammeter is to be u	ised in place of a voltme	ter then we must connec	t with the	ammeter a
	(1) Low resistance in pa(3) High resistance in se	arallel eries	(2) High resistance in p (4) Low resistance in se	arallel eries	AIEEE 2002, 4/300]
33.	An ammeter reads upto value of the required sh $(1) 0.09 \Omega$	1 ampere. Its internal re unt is (2) 0.03 Ω	esistance is 0.81 ohm. Τα (3) 0.3 Ω	o increase [AIEEE 2 (4)0.9 Ω	the range to 10 A the 2003, 4/300]
34.	The length of a wire of a to measure the emf of a 30 cm from the positive $\begin{pmatrix} 30E\\100\\ \hline 100\\ \hline (4) & \hline 100\\ \hline 100\\ \hline 100\\ \hline 100\\ \hline 100\\ \hline 100 & \hline 100 \end{pmatrix}$	a potentiometer is 100 cm a battery whose internal i end, the emf of the batter 30E (2) 100.5 0.5i) , where i is the curr	n, and the emf of its stand resistance is 0.5 ohm. If ery is $\frac{30E}{(100-0.5)}$ rent in the potentiometer	lard cell is the baland [AIEEE 2	E volt. It is employed ce point is obtained at 2003, 4/300]

- 35. In a metre bridge experiment, null point is obtained at 20 cm from one end of the wire when resistance X is balanced against another resistance Y. If X < Y, then where will be the new position of the null point from the same end, if one decides to balance a resistance of 4X against Y? [AIEEE 2004, 4/300] (1) 50 cm (2) 80 cm (3) 40 cm (4) 70 cm
- 36. In a potentiometer experiment the balancing with a cell is at length 240 cm. On shunting the cell with a resistance of 20, the balancing length becomes 120 cm. The internal resistance of the cell is : [AIEEE 2005, 4/300]

- 37. A moving coil galvanometer has 150 equal divisions. Its current sensitivity is 10 divisions per milli ampere and voltage sensitivity is 2 divisions per millivolt. In order that each division reads 1 volt, the resistance in ohms needed to be connected in series with the coil will be : [AIEEE 2005, 4/300] $(1) 10_3$ $(2) 10_5$ (3) 99995(4) 9995
- 38. Shown in the figure below is a meter-bridge set up with null deflection in the galvanometer.

[AIEEE 2008, 3/105]

[AIPMT 2004]



(4) 13.75 Ω

The value of the unknown resistor R is (1) 220 Ω (2) 110 Ω (3) 55 Ω

- To convert a galvanometer into a voltmeter, one should connect a : 39. [AIPMT 2002] (1) High resistance in series with galvanometer (2) Low resistance in series with galvanometer (3) High resistance in parallel with galvanometer (4) Low resistance in parallel with galvanometer
- 40. A galvanometer of 50 Ω resistance has 25 divisions. A current of 4 x 10-4 A gives a deflection of one division. To convert this galvanometer into a voltmeter having a range of 25V, it should be connected [AIPMT 2004] with a resistance of : (1) 2500Ω as a shunt (2) 245Ω as a shunt (3) 2550Ω in series (4) 2450Ω in series
- A galvanometer acting as a voltmeter will have : 41. (1) A high resistance in parallel with its coil (2) A high resistance in series with its coil (3) A low resistance in parallel with its coil (4) A low resistance in series with its coil
- 42. The resistance of an ammeter is 13Ω and its scale is graduated for a current upto 100 amps. After an additional shunt has been connected to this ammeter it becomes possible to measure currents upto 750 amperes by this meter. The value of shunt-resistance is :-**[AIPMT 2007]** (1) 20Ω (2) 2Ω (3) 0.2 Ω (4) 2kΩ
- A galvanometer of resistance 50 Ω is connected to a battery of 3 V along with a resistance of 2950 Ω in 43. series. A full scale deflection of 30 divisions is obtained in the galvanometer. In order to reduce this deflection to 20 divisions, the resistance in series should be [AIPMT 2008] (1) 5050 Ω (2) 5550 Ω (3) 6050 Ω (4) 4450 Ω
- A cell can be balanced against 110 cm and 100 cm of potentiometer wire, respectively with and without 44. being short circuited through a resistance of 10 Ω . Its internal resistance is [AIPMT 2008] (1) 1.0 Ω (2) 0.5 Ω (3) 2.0 Ω (4) zero

Exercise-2

ΔV

- A quantity X is given by $\varepsilon_0 L^{\Delta t}$ where ε_0 is the permittivity of free space, L is a length, ΔV is a potential 1. difference and Δt is a time interval. The dimensional formula for X is the same as that of : [JEE (Scr.) 2001, 3/105] (1) Resistance (2) Charge (3) Voltage (4) Current 2. When a current flows through a conductor its temperature [MHCET 2002] (1) May increase or decrease (2) Remains same (3) Decreases (4) Increases 3. Find the current through the 10 Ω resistor shown in figure 10Ω <u>1'3</u>/ 3Ω 6Ω 4 5\ (1) zero (2) 1 A (3) 2A (4) 5 A 4. Two batteries of e.m.f. 4 V and 8 V with internal resistances 1 Ω and 2 Ω are connected in a circuit with a resistance of 9 Ω as shown in figure. The current and potential difference between the points P and Q are [AFMC 1999] 9Ω (1) 1/3 A 3 V (2) 1/6 A 4 V (3) 1/9 A 9 V (4) 1/2 A 12 V 5. For driving a current of 2 A for 6 minutes in a circuit, 1000 J of work is to be done. The e.m.f. of the source in the circuit is [CPMT 1999] (3) 2.04 V (1) 1.38 V (2) 1.68 V (4) 3.10 V [BHU 2003] 6. The potential difference between point A and B is 6Ω 8Ω В 10 V ¹⁰_V 20 7 (1) (3)
- 7. A wire is in the form of a tetrahedron. The resistance of each edge is r. The equivalent resistances between corners 1-2 and 1-3 are respectively

(4) 0



(2)

(1)
$$\frac{r}{2}, \frac{r}{2}$$
 (2) r, r (3) $\frac{r}{2}, r$ (4) r, $\frac{r}{2}$

8. In the figure shown the current flowing through 2 R is :



(1) from left to right

(3) no current

(4) None of these

[AFMC 2001]

9. The net resistance between points P and Q in the circuit shown in fig. is



- 10.In the given circuit, it is observed that the current I is independent of the value of the resistance R6. Then
the resistance values must satisfy:[JEE(Scr.) 2001,3/105]
 - $(1) R_{1} R_{2} R_{5} = R_{3} R_{4} R_{6}$ $(3) R_{1} R_{4} = R_{2} R_{3}$ $(1) R_{1} R_{2} R_{5} = R_{3} R_{4} R_{6}$ $(2) R_{1} R_{4} = R_{2} R_{3}$ $(2) R_{1} R_{4} = R_{2} R_{3}$ $(3) R_{1} R_{4} = R_{2} R_{3}$ $(4) R_{1} R_{3} = R_{2} R_{4} = R_{5} R_{6}$
- 11. A battery of internal resistance 4 ohm is connected to the network of resistance as shown. In the order that the maximum power can be delivered to the network, the value of R in ohm should be:[JEE 1995]



- **13.** The measurement (approx) of ideal voltmeter in the following circuit is





20. Find the equivalent resistance between the points A and B :

[RPMT 2006]



21. A circuit consists of five identical conductors as shown in figure. The two similar conductors are added as indicated by dotted lines. The ratio of resistances before and after addition will be [R-PMT 2007]



- 22. The electric current passes through a metallic wire produces heat because of [R_PMT 2007] (1) collisions of conduction electrons with each other
 (2) collisions of the atoms of the metal with each other
 - (3) the energy released in the ionization of the atoms of the metal
 - (4) collisions of the conduction electrons with the atoms of the metallic wire
- **23.** An electrical cable of copper has just one wire of radius 9 mm. Its resistance is 5 Ω . The single wire of the cable is replaced by 6 different well insulated copper wires each of radius 3 mm. The total resistance of the cable will now be equal to
 (1) 270 Ω (2) 90 Ω (3) 45 Ω (4) 7.5 Ω
- **24.** A galvanometer has resistance of 400 Ω and deflects full scale for current of 0.2 mA through it. The shunt resistance required to convert it into 3 A ammeter is [RPMT 2007] (1) 0.027 Ω (2) 0.054 Ω (3) 0.0135 Ω (4) none of these
- **25.** The resistance of an ammeter is 13 Ω and its scale is graduated for a current upto 100 A. After an additional shunt has been connected to this ammeter it becomes possible to measure currents upto 750 A by this meter. The value of shunt resistance is [RPMT 2008] (1) 20 Ω (2) 2 Ω (3) 0.2 Ω (4) 2k Ω
- **26.** The length of a wire in a potentiometer is 100 cm, and the emf of its standard cell is E volt. It is employed to measure the emf of a battery whose internal resistance is 0.5Ω . If the balance point is obtained at $\ell = 30$ cm from the positive end, the emf of the battery is **[RPMT 2008]**
 - (1) 30E 100.5 30E
 - (2) 100 0.530(E - 0.5i)
 - (3) $100 \\ 30E$, where i is the current in the potentiometer wire
 - (4) 100
- 27. An ammeter reads upto 1A. Its internal resistance is 0.81 Ω . To increase the range to 10 A the value of the required shunt is [RPMT 2008] (1) 0.03 Ω (2) 0.3 Ω (3) 0.9 Ω (4) 0.09 Ω

28. The value of current *I* in the circuit will be

[RPMT 2009]



29. There is a voltameter in a circuit. In order to triple its range, the resistance of how much value should be used?
(1) 2R (2) R/2 (3) 3R (4) 4R

30. A wire is bent in the form of a triangle now the equivalent resistance R between its one end and the mid point of the side is [RPMT 2009]



31. A 'Wheatstone Bridge' circuit has been set up as shown. The resistor R₄ is an ideal carbon. The resistor R₄ is an ideal carbon resistance (tolerance = 0%) having bands of colours black, yellow and brown marked on it. The galvanometer, in this circuit, would show a 'null point' when another ideal carbon resistance X is connected across R₄, having bands of colours [RPMT-2014]



- (1) black, brown, black, is put in parallel with R4
- (2) black, brown, brown, is put in parallel with R4
- (3) brown, black, brown, is put in parallel with R4
- (4) black, brown, black, is put in parallel with R₄

Exercise-3

PART - I : NEET / AIPMT QUESTION (PREVIOUS YEARS)

- 1. A galvanometer having a coil resistance of 60 Ω shows full scale deflection when a current of 1.0 A passes through it. It can be converted into an ammeter to read currents up to 5.0 A by[AIPMT 2009] (1) putting in parallel a resistance of 240 Ω (2) putting in series a resistance of 15 Ω (3) putting in series a resistance of 240 Ω (4) putting in parallel a resistance of 15 Ω
- 2. A wire of resistance $12\Omega m_{-1}$ is bent to form a complete circle of radius 10 cm. The resistance between its two diametrically opposite points. A and B as shown in the figure, is **[AIPMT 2009]**

(3) 6π Ω

(1) 0.6π Ω (2) 3 Ω

3. A student measures the termainal potential difference (V) of a cell (of emf ε and internal resistance r) as a function of the current (I) flowing through it. The slope and intercept of the graph between V and I, then respectively equal [AIPMT 2009] (3) r and $-\epsilon$ (2) -r and ϵ (4) –ε and r

λR

(4) 6Ω

(1) ε and-r

4.

See the electrical circuit shown in this figure. Which of the following equations is a correct equation for it? [AIPMT 2009]



5. A thermocouple of negligible resistance produces an e.m.f. of 40 μ V/°C in the linear range of temperature. A galvanometer of resistance 10 ohm whose sensitivity is 1μ A/div, is employed with the termocouple. The smallest value of temperature difference that can be detected by the system will be :

			[AIPMT (MAINS) 2011]
(1) 0.5°C	(2) 1°C	(3) 0.1°C	(4) 0.25°C

In the circuit shown in the figure, if potential at point A is taken to be zero the potential at point B is : 6. [AIPMT (MAINS) 2011]



- 7. A milli voltmeter of 25 milli volt range is to be converted into an ammeter of 25 ampere range. The value (in ohm) of necessary shunt will be : [AIPMT_Pre_2012] (1) 0.001(2) 0.01(3)1(4) 0.05
- 8. In the circuit shown the cells A and B have negligible resistances. For $V_A = 12V$, $R_1 = 500\Omega$ and $R = 100\Omega$ the galvanometer (G) shows no deflection. The value of V_B is : [AIPMT_Pre_2012]



- 9.If voltage across a bulb rated 220 Volt 100 Watt drops by 2.5 % of its rated value, the percentage of the rated value by which the power would decrease is :[AIPMT_Pre_2012](1) 20 %(2) 2.5 %(3) 5 %(4) 10 %
- **10.** A ring is made of a wire having a resistance $R_0 = 12 \Omega$. Find the points A and B as shown in the figure, at which a current carrying conductor should be connected so that the resistance R of the sub circuit



11. The power dissipated in the circuit shown in the figure is 30 Watts. The value of R is : [AIPMT 2012 (Mains)]



12. Cell having an emf ε and internal resistance r is connected across a variable external resistance R .As the resistance R is increased, the plot of potential difference V across R is given by :



- **13.** A wire of resistance 4 Ω is stretched to twice its original length. The resistance of stretched wire would be: (1) 4 Ω (2) 8 Ω (3) 16 Ω (4) .2 Ω
- **14.** The internal resistance of a 2.1 V cell which gives a current of 0.2 A through a resistance of 10Ω is :: [NEET-2013]

(1) 0.5 Ω	(2) 0.8 Ω	(3) 1.0 Ω	(4) 0.2 Ω
(1) 0.0 32	(2) 0.0 32	(0) 1.0 32	(1) 0.2 32

15. The resistances of the four arms P, Q, R and S in a Wheatstone's bridge are 10 ohm, 30 ohm, 30 ohm and 90 ohm, respectively. The e.m.f. and internal resistance of the cell are 7 Volt and 5 ohm respectively. If the galvanometer resistance is 50 ohm, the current drawn from the cell will be :

(1) 0.2 A (2) 0.1 A (3) 2.0 A

17. The resistance in the two arms of the meter bridge are 5Ω and R Ω , respectively. When the resistance R is shunted with an equal resistance, the new balance point is at $1.6\ell_1$. The resistance 'R' is :

[AIPMT-2014]

[NEET 2013]

(4) 1.0 A





20.Across a metallic conductor of non-uniform cross section a constant potensial difference is applied. The
quantity which remains constant along the conductor is[AIPMT-2015](1) current(2) drift velocity(3) electric field(4) current density

A potentiometer wire has length 4m and resistance 8Ω. The resistance that must be connected in series with the wire and an accumulator of e.m.f 2V, so as to get a potential gradient 1mV per cm on the wire is :
 [AIPMT-2015]

(1) 40Ω (2) 44Ω (3) 48Ω (4) 32Ω

22. A, B and C are voltmeters of resistance R, 1.5R and 3R respectively as shown in the figure. When some potential difference is applied between X and Y, the voltmeter readings are V_A, V_B and V_C respectively. Then : [AIPMT-2015]

(1) $V_A \neq V_B = V_C$



23. A circuit contains an ammeter, a batter of 30 V and a resistance 40.8 ohm all connected in series. If the ammeter has a coil of resistance 480 ohm and a shunt of 20 ohm, the reading in the ammeter will be:

[AIPMT-2015] (1) 0.25 A (3) 1 A (4) 0.5 A (2) 2A

24. Two metal wires of identical dimension are connected in series. If σ_1 and σ_2 are the conductivities of the metal wires respectively, the effective conductivity of the combination is :[AIPMT-2015]

(1)
$$\frac{\sigma_1 + \sigma_2}{2\sigma_1 \sigma_2}$$
 (2) $\frac{\sigma_1 + \sigma_2}{\sigma_1 \sigma_2}$ (3) $\frac{\sigma_1 \sigma_2}{\sigma_1 + \sigma_2}$ (4) $\frac{2\sigma_1 \sigma_2}{\sigma_1 + \sigma_2}$

25. A potentiometer wire of length L and a resistance r are connected in series with a battery of e.m.f. E. and a resistance r1. An unknown e.m.f. E is balanced at a length I of the potentiometer wire. The e.m.f. E will be given by : [AIPMT-2015]

(1)
$$\frac{E_0 r}{(r+r_1)} \cdot \frac{L}{L}$$
 (2) $\frac{E_0 l}{L}$ (3) $\frac{LE_0 r}{(r+r_1) l}$ (4) $\frac{LE_0 r}{lr_1}$

26. The charge flowing through a resistance R varies with time t as $Q = at - bt^2$, where a and b are positive constants. The total heat produced in R is : [AIPMT-2016]

$$(1) \frac{a^{3}R}{b} \qquad (2) \frac{a^{3}R}{6b} \qquad (3) \frac{a^{3}R}{3b} \qquad (4) \frac{a^{3}R}{2b}$$

The potential difference $(V_A - V_B)$ between the points A and B in the given figure is **[NEET 2016]** 27.

- 28. A filament bulb (500 W, 100 V) is to be used in a 230 V main suply. When a resistance R is connected in series, it works perfectly and the bulb consumes 500 W. The value of R is : [NEET 2016] (1) 13 Ω (2) 230 Ω (3) 46 Ω (4) 26 Ω
- 29. The resistance of a wire is 'R' ohm. If it is melted and stretched to 'n' times its original length, its new resistance will be [NEET-2017] R

(4) n^{2}

(1) nR (2)
$$\frac{12}{n}$$
 (3) n^2 R

- 30. A potentiometer is an accurate and versatile device to meke electrical measurements of E.M.F. because the method involves : [NEET 2017]
 - (1) cells
 - (2) potential gradients (3) a condition of no current flow through the galvanometer
 - (4) a combination of cells, galvanometer and resistance
- 31. Current sensitivity of a moving coil galvanometer is 5 div/mA and its voltage sensitivity (angular deflection per unit voltage applied) is 20 div/V. The resistance of the galvanometer is :[NEET 2018]

(1) 10 0	(2) EOO O	(2) 250 0	
$(1) 40 \Omega$	$(Z) = 0 \cup \Omega$	(3) ZOU (2	(4) 20 (2
(. /	(=) 000 ==	(0) = 0 0 ==	(. / = = =

- **32.** A carbon resistor of (47 ± 4.7) k Ω is to be marked with rings of different colours for its identification. The colour code sequence will be **[NEET 2018]**
 - (1) Violet Yellow Orange Silver
 (2) Green Orange Violet Gold
 (3) Yellow Green Violet Gold
 (4) Yellow Violet Orange Silver
- 33. A set of 'n' equal resistors, of value 'R' each, are connected in series to a battery of emf 'E' and internal resistance 'R'. The current drawn is I. Now, the 'n' resistors are connected in parallel to the same battery. Then the current drawn from battery becomes 10 I. The value of 'n' is :- [NEET 2018]

 (1) 10
 (2) 9
 (3) 20
 (4) 11
- A battery consists of a variable number 'n' of identical cells (having internal resistance 'r' each) which are connected in series. The terminals of the battery are short-circuited and the current I is measured. Which of the graphs shows the correct relationship between I and n? [NEET 2018]



35. In the circuits shown below, the readings of the voltmeters and the ammeters will be: [NEET_ 2019-I]



- 36.
 Which of the following acts as a circuit protection device?
 [NEET_ 2019-I]

 (1) fuse
 (2) conductor
 (3) inductor
 (4) switch
- **37.** Six similar bulbs are connected as shown in the figure with a DC source of emf E, and zero internal resistance.

The ratio of power consumption by the bulbs when (i) all are glowing and (ii) in the situation when two from section A and one from section B are glowing, will be: **[NEET_2019-I]**





PART - II : JEE (MAIN) / AIEEE PROBLEMS (PREVIOUS YEARS)

Two conductors have the same resistance at 0°C but their temperature coefficients of resistance are a1 1. and α_2 . The respective temperature coefficients of their series and parallel combinations are nearly [AIEEE 2010, 8/144]

	$\frac{\alpha_1 + \alpha_2}{2}$	$\frac{\alpha_1 + \alpha_2}{2}$	$\frac{\alpha_1 \alpha_2}{\alpha_1 + \alpha_2}$	$\frac{\alpha_1 + \alpha_2}{\alpha_1 + \alpha_2} = \frac{\alpha_1 + \alpha_2}{\alpha_1 + \alpha_2}$
	(1) ² , α1 + α2	(2) $\alpha_1 + \alpha_2$, 2	(3) $\alpha_1 + \alpha_2$, $\alpha_1 + \alpha_2$	(4) 2 , 2
2.	If a wire is stretched to	make it 0.1% longer, its	resistance will :	[AIEEE - 2011, 4/120, –1]
	(1) increase by 0.05%	(2) increase by 0.2%	(3) decrease by 0.2%	(4) decrease by 0.05%
3.	The current in the prim the potentiometer wire equal to :	ary circuit of a potentiom are 4 × 10-7 ohm metre a	eter is 0.2 A. The specific and 8 × 10 ₋₇ m ₂ respective [AIEEI	c resistance and cross-section of ely. The potential gradient will be E 2011, 11 May; 4/120, –1]
	(1) 1 V/ m	(2) 0.5 V/m	(3) 0.1 V/m	(4) 0.2 V/m
4.	Two electric bulbs mar Which of the bulbs will	ked 25W – 220V and 10 fuse ?	00W – 220 V are connec	ted in series to a 440 V supply. [AIEEE 2012; 4/120, -1]
		(2) 10000	(3) 2377	(4) heimei
5.	Resistance of a given applied across it. If the are 3% each, then erro (1) 6%	wire is obtained by mea e percentage errors in the or in the value of resistan (2) zero	suring the current flowing e measurement of the cu ce of the wire is : (3) 1%	g in it and the voltage difference irrent and the voltage difference [AIEEE 2012; 4/120, -1] (4) 3%
6.	This questions has Sta	tement I and Statement	II. Of the four choices giv	en after the Statements, choose
	the one that best desci	ribes the two Statements	. [JEE-M	Main 2013; 4/120, –1]
	Statement - I : For high	her range, the resistance	e of ammeter (R _A ≈ shunt	resistance) should be more.
	Statement - II : To incr	ease the range of amme	eter, additional shunt need	ds to be used across it.
	(1) Statement -I is true	e, Statment -II is true, Sta	tement -II is the correct e	explanation of Statement -I.
	(2) Statement -I is true	, Statment- II is true, Sta	tement - II is not the corre	ect explanation of Statement- I.
	(3) Statement -I is true	, Statment - II is false.		
	(4) Statement -I is false	e, Statment - II is true.		
7.	The supply voltage to switched on. What is t parallel to the bulb ?	room is 120 V. The resinned the decrease of voltage a	istance of the lead wires across the bulb, when a	is 6 Ω. A 60 W bulb is already 240 W heater is switched on in [JEE-Main 2013; 4/120, –1]
	(1) zero Volt	(2) 2.9 Volt	(3) 13.3 Volt	(4) 10.04 Volt
8.	In a large building, the	re are 15 bulbs of 40W.	5 bulbs of 100 W, 5 fans	s of 80 W and 1 heater of 1 kW.
	The voltage of the elec	tric mains is 220 V. The	minimum capacity of the	main fuse of the building will be:
				[JEE- Main - 2014]
	(1) 8 A	(2) 10 A	(3) 12 A	(4) 14 A

٠

9. When 5V potential difference is applied across a wire of length 0.1 m, the drift speed of electrons is $2.5 \times 10_{-4}$ ms₋₁. If the electron density in the wire is $8 \times 10_{28}$ m₋₃, the resistivity of the material is close to:

(1) $1.6 \times 10_{-8} \Omega m$ (2) $1.6 \times 10_{-7} \Omega m$ (3) $1.6 \times 10_{-6} \Omega m$

[JEE(Main)-2015; 4/120, -1]

(4) 1.6 × 10₋₅ Ωm

(3) 0.13 A, from Q to P (4) 0.13 A, from P to Q

10. In the circuit shown, the current in the 1 Ω resistor is : [JEE(Main)-2015; 4/120, -1]

(1) 1.3 A, from P to Q (2) 0 A

11. A galvanometer having a coil resistance of 100 Ω gives a full scale deflection, when a current of 1 mA is
passed through it. The value of the resistance, which can convert this galvanometer into ammeter giving
a full scale deflection for a current of 10 A, is :[JEE(Main)-2016](1) 2 Ω (2) 0.1 Ω (3) 3 Ω (4) 0.01 Ω

- 12.
 The temperature dependence of resistances of Cu and undoped Si in the temperature range 300 400

 K, is best described by :
 [JEE(Main)-2016]
 - (1) Linear increase for Cu, exponential increase for Si
 - (2) Linear increase for Cu, exponential decrease for Si
 - (3) Linear decrease for Cu, linear decrease for Si
 - (4) Linear increase for Cu, linear increase for Si



- 14. Which of the following statements is false ?
 - (1) Krichhoff's second law represents energy conservation.
 - (2) Wheatstone bridge is the most sensitive when all the four resistance are of the same order of magnitude
 - (3) In a balanced wheatstone bridge if the cell and the galvanometer are exchanged, the null point is disturbed

[JEE Main 2017]

- (4) A rheostat can be used as a potential divider.
- 15. When a current of 5mA is passed through a galvanometer having a coil of resistance 15Ω, it shows full scale defection. The value of the resistance to be put in series with the galvanometer to convert it into a voltmeter of range 0 10 V is : [JEE Main 2017]
 (1) 4 005 = 403 0 = (0) 4 005 = 403 0 = (0) 0.045 = 403 0 = (1) 0.555 = 403 0

(1) $4.005 \times 10^{3} \Omega$ (2) $1.985 \times 10^{3} \Omega$ (3) $2.045 \times 10^{3} \Omega$ (4) $2.535 \times 10^{3} \Omega$

- 16. On interchanging the resistances, the balance point of a meter bridge shifts to the left by 10 cm. The resistance of their series combination is 1KΩ. How much was the resistance on the left slot before interchanging the resistances? [JEE-Main-2018]
 (1) 550 Ω
 (2) 910 Ω
 (3) 990 Ω
 (4) 505Ω
- **17.** Two batteries with e.m.f 12V and 13V are connected in parallel across a load resistor of 10Ω . The internal resistance of the two batteries are 1Ω and 2Ω respectively. The voltage across the load lies between :

[JEE-Main-2018]

- (1) 11.4V and 11.5 V (2) 11.7V and 11.8V (3) 11.6V and 11.7V (4) 11.5V and 11.6V
- 18. A resistance is shown in the figure. Its value and tolerance are given respectively by :[JEE Main 2019]



- **19.** Drift speed of electrons, when 1.5A of current flows in a copper wire of cross section 5 mm², is v. If the electron density in copper is 9×10^{28} /m³ the value of v in mm/s is close to (Take charge of electron to be = 1.6×10^{-19} C)[JEE Main 2019](1) 0.2(2) 3(3) 2(4) 0.02
- A copper wire is stretched to make it 0.5% longer. The percentage change in its electrical resistance if its volume remains unchanged is : [JEE Main 2019]
 (1) 2.5%
 (2) 0.5%
 (3) 2.0%
 (4) 1.0%
- 21. When the switch S, in the circuit shown, is closed, then the value of current i will be :[JEE Main 2019]

(1) 3A



22. In the given circuit the internal resistance of the 18v cell is negligible. If $R_1 = 400\Omega$, $R_3 = 100 \Omega$ and $R_4 = 500 \Omega$ and the reading of an ideal voltmeter across R_4 is 5V, then the value of R_2 will be :

[JEE Main 2019]



-									
	which can be passed th	nrough this resistor is :		[JEE Main 2019]					
	(1) 20mA	(2) 63 mA	(3) 0.4 mA	(4) 100 mA					

25. A potentiometer wire AB having length L and resistance 12 r is joined to a cell D of emf ε and internal resistance r. A cell C having emf $\varepsilon/2$ and internal resistance 3r is connected. The length AJ at which the galvanometer as shown in figure. shows no deflection is : **[JEE Main 2019]**



In the given circuit the cells have zero internal resistance. The currents (in Amperes) passing through resistance R1 and R2 respectively are : [JEE Main 2019]



- 27.A uniform metallic wire has a resistance of 18 Ω and is bent into an equilateral triangle. Then, the resistance between any two vertices of the triangle is :[JEE Main 2019](1) 4 Ω (2) 12 Ω (3) 2 Ω (4) 8 Ω
- A current of 2 mA was passed through an unknown resistor which dissipated a power of 4.4 W. Dissipated power when an ideal power supply of 11V is connected across it is : [JEE Main 2019] (1) 11 × 10⁻⁴ W (2) 11 × 10⁵ W (3) 11 × 10⁻³ W (4) 11 × 10⁻⁵ W
- 29. The Wheatstone bridge shown in figure here, gets balanced when the carbon resistor used as R₁ has the colour code (Orange, Red, Brown). The resistors R₂ and R₄ are 80Ω and 40Ω, respectively. Assuming that the colour code for the carbon resistors gives their accurate values, the colour code for the carbon resistor, used as R₃, would be : [JEE Main 2019]



(1) Red, Green, Brown (2) Grey, Black, Brown (3) Brown, Blue, Brown (4) Brown, Blue, Black

30. The actual value of resitance R, shown in the figure is 30Ω . This is measured in an experiment as shown V

using the standard formula R = I, where V and I are the readings of the voltmeter and ammeter, respectively. If the measured value of R is 5% less, then the internal resistance of the voltmeter is :



31. In a wheatstone bridge (see fig.), Resistances P and Q are approximately equal. When R = 400 Ω, the bridge is balanced. On interchanging P and Q, the value of R, for balance, is 405 Ω. The value of X is close to :
[JEE Main 2019]



32. The resistance of the meter bridge AB in given figure is 4Ω . With a cell of emf $\varepsilon = 0.5$ V and rheostat resistance $R_h = 2\Omega$ the null point is obtained at some point J. When the cell is replaced by another one of emf $\varepsilon = \varepsilon_2$ the same null point J is found for $R_h = 6 \Omega$. The emf ε_2 is, : [JEE Main 2019]



34. In the experimental set up of meter bridge shown in the figure, the null point is obtained at a distance of 40 cm from A. If a 10 Ω resistor is connected in series with R₁, the null point shifts by 10 cm. The resistance that should be connected in parallel with (R₁ + 10) Ω such that the null point shifts back to its initial position is : **[JEE Main 2019]**







- 41.A galvanometer, whose resistance is 50 ohm, has 25 divisions in it. When a current of 4 × 10⁻⁴ A passes
through it, its needle (pointer) deflects by one division. To use this galvanometer as a voltmeter of range
2.5 V, It should be connected to a resistance of :[JEE Main 2019](1) 250 ohm(2) 200 ohm(3) 6200 ohm(4) 6250 ohm
- 42. In the given circuit diagram, the currents, $I_1 = -0.3A$, $I_4 = 0.8 A$ and $I_5 = 0.4 A$, are flowing as shown. The currents I_2 , I_3 and I_6 respectively, are : [JEE Main 2019]



(1) 1.1 A, 0.4 A, 0.4 A (2) –0.4 A, 0.4 A, 1.1 A (3) 0.4 A, 1.1 A, 0.4 A (4) 1.1 A, -0.4 A, 0.4 A

Answers

F

	EXERCISE - 1												
SECT	SECTION (A) :												
1.	(3)	2.	(4)	3.	(1)								
SECT	ON (B)	:											
1.	(4)	2.	(2)	3.	(3)	4.	(1)	5.	(4)	6.	(2)	7.	(3)
8.	(2)	9.	(4)	10.	(3)	11.	(2)	12.	(3)	13.	(2)	14.	(4)
15.	(4)	16.	(2)	17.	(2)	18.	(4)	19.	(1)	20.	(1)	21.	(3)
22.	(4)	23.	(2)	24.	(4)	25.	(2)	26.	(1)	27.	(1)	28.	(1)
29.	(3)	30.	(3)	31.	(3)	32.	(1)	33.	(4)	34.	(2)	35.	(3)
36.	(1)	37.	(2)	38.	(1)								
SECTI	ON (C)	:											
1.	(2)	2.	(2)	3.	(2)	4.	(1)	5.	(4)	6.	(2)	7.	(4)
8.	(2)	9.	(4)	10.	(3)	11.	(1)	12.	(2)	13.	(3)	14.	(3)
15.	(2)	16.	(2)	17.	(2)	18.	(3)	19.	(3)	20.	(1)	21.	(1)
22.	(1)	23.	(3)	24.	(2)	25.	(4)	26.	(3)	27.	(4)	28.	(2)
29.	(4)												
SECT	ON (D)	:											
1.	(a)	(2)	(b)	(3)	2.	(2)	3.	(1)	4.	(3)	5.	(1)	
6.	(2)	7.	(1)	8.	(1)	9.	(1)	10.	(3)	11.	(3)	12.	(1)
13.	(4)	14.	(1)	15.	(1)	16.	(2)	17.	(2)	18.	(4)	19.	(1)
20.	(2)	21.	(1)	22.	(4)	23.	(3)	24.	(1)	25.	(1)	26.	(1)
27.	(1)	28.	(3)	29.	(3)	30.	(3)	31.	(1)	32.	(1)	33.	(2)
34.	(1)	35.	(4)	36.	(4)	37.	(1)	38.	(3)	39.	(4)	40.	(1)
41.	(2)	42.	(1)	43.	(4)	44.	(2)	45.	(3)	46.	(3)	47.	(1)
48.	(2)	49.	(4)	50.	(4)	51.	(1)	52.	(1)	53.	(1)	54.	(3)
55.	(2)	56.	(4)	57.	(4)	58.	(4)	59.	(3)	60.	(4)	61.	(4)
SECT	ON (E)	:											
1.	(3)	2.	(1)	3.	(3)	4.	(4)	5.	(4)	6.	(3)	7.	(3)
8.	(2)	9.	(2)	10.	(2)	11.	(1)						
SECT	ON (F)	:											
1.	(3)	2.	(1)	3.	(4)	4.	(3)	5.	(2)	6.	(2)	7.	(1)
8.	(3)	9.	(2)	10.	(2)	11.	(3)	12.	(2)	13.	(3)	14.	(2)
15.	(2)	16.	(1)	17.	(2)	18.	(1)	19.	(2)	20.	(3)	21.	(1)
22.	(3)	23.	(3)	24.	(1)	25.	(1)	26.	(3)	27.	(4)	28.	(2)
29.	(3)	30.	(2)	31.	(3)	32.	(3)	33.	(1)	34.	(1)	35.	(1)
36.	(4)	37.	(4)	38.	(1)	39.	(1)	40.	(4)	41.	(2)	42.	(2)
43.	(4)	44.	(1)										

•														
						EXER	CISE	- 2						
	PART – I													
1.	(4)	2.	(4)	3.	(1)	4.	(1)	5.	(1)	6.	(4)	7.	(1)	
8.	(2)	9.	(2)	10.	(3)	11.	(2)	12.	(3)	13.	(4)	14.	(2)	
15.	(3)	16.	(1)	17.	(1)	18.	(2)	19.	(4)	20.	(2)	21.	(3)	
22.	(4)	23.	(4)	24.	(1)	25.	(2)	26.	(4)	27.	(4)	28.	(1)	
29.	(1)	30.	(1)	31.	(2)									
						EXER	CISE	- 3						
						PA	RT – I							
1.	(4)	2.	(1)	3.	(2)	4.	(1)	5.	(4)	6.	(4)	7.	(1)	
8.	(2)	9.	(3)	10.	(4)	11.	(3)	12.	(3)	13.	(3)	14.	(1)	
15.	(1)	16.	(2)	17.	(2)	18.	(3)	19.	(3)	20.	(1)	21.	(4)	
22.	(4)	23.	(4)	24.	(4)	25.	(1)	26.	(2)	27.	(1)	28.	(4)	
29.	(3)	30.	(3)	31.	(3)	32.	(4)	33.	(1)	34.	(1)	35.	(4)	
36.	(1)	37.	(3)	38.	(4)	39.	(4)							
						PA	RT – II							
1.	(4)	2.	(2)	3.	(3)	4.	(3)	5.	(1)	6.	(4)	7.	(4)	
8.	(3)	9.	(4)	10.	(3)	11.	(4)	12.	(2)	13.	(1)	14.	(3)	
15.	(2)	16.	(1)	17.	(4)	18.	(4)	19.	(4)	20.	(4)	21.	(2)	
22.	(4)	23.	(2)	24.	(1)	25.	(4)	26.	(4)	27.	(1)	28.	(4)	
29.	(3)	30.	(3)	31.	(2)	32.	(2)	33.	(4)	34.	(1)	35.	(4)	
36.	(1)	37.	(3)	38.	(3)	39.	(4)	40.	(4)	41.	(2)	42.	(1)	