

# CAPACITANCE

## 1. INTRODUCTION

A capacitor can store energy in the form of potential energy in an electric field. In this chapter we will discuss the capacity of conductors to hold charge and energy.

## 2. CAPACITANCE OF AN ISOLATED CONDUCTOR

When a conductor is charged its potential increases. It is found that for an isolated conductor (conductor should be of finite dimension, so that potential of infinity can be assumed to be zero) potential of the conductor is proportional to charge given to it.

$q$  = charge on conductor

$V$  = potential of conductor

$q$



Isolated conductor

$q \propto V$

$\Rightarrow q = CV$

Where  $C$  is proportionality constant called capacitance of the conductor.

### 2.1 Definition of capacitance :

Capacitance of conductor is defined as charge required to increase the potential of conductor by one unit.

### 2.2 Important points about the capacitance of an isolated conductor :

(i) It is a scalar quantity.

(ii) Unit of capacitance is farad in SI units and its dimensional formula is  $M^{-1} L^{-2} I^2 T^4$

(iii) **1 Farad** : 1 Farad is the capacitance of a conductor for which 1 coulomb charge increases potential by 1 volt.

$$1 \text{ Farad} = \frac{1 \text{ Coulomb}}{1 \text{ Volt}}$$

$1 \mu\text{F} = 10^{-6} \text{ F}$ ,  $1 \text{ nF} = 10^{-9} \text{ F}$  or  $1 \text{ pF} = 10^{-12} \text{ F}$

### (iv) Capacitance of an isolated conductor depends on following factors :

(1) **Shape and size of the conductor :**

On increasing the size, capacitance increases.

(2) **On surrounding medium :**

With increase in dielectric constant  $K$ , capacitance increases.

(3) **Presence of other conductors :**

When a neutral conductor is placed near a charged conductor capacitance of conductors increases.

### (v) Capacitance of a conductor do not depend on

(1) Charge on the conductor

(2) Potential of the conductor

(3) Potential energy of the conductor.

## 3. POTENTIAL ENERGY OR SELF ENERGY OF AN ISOLATED CONDUCTOR

Work done in charging the conductor to the charge on it against its own electric field or total energy stored in electric field of conductor is called self energy or self potential energy of conductor.

### 3.1 Electric potential energy (Self Energy) :

Work done in charging the conductor

$$W = \int_0^q \frac{q}{C} dq = \frac{q^2}{2C}$$

$$W = U = \frac{q^2}{2C} = \frac{1}{2} CV^2 = \frac{qV}{2}$$

$q$  = Charge on the conductor  
 $V$  = Potential of the conductor  
 $C$  = Capacitance of the conductor.

- 3.2** Self energy is stored in the electric field of the conductor with energy density (Energy per unit volume)

$$\frac{dU}{dV} = \frac{1}{2} \epsilon_0 E^2 \quad \left[ \text{The energy density in a medium is } \frac{1}{2} \epsilon_0 \epsilon_r E^2 \right]$$

where  $E$  is the electric field at that point.

- 3.3** In case of charged conductor energy stored is only outside the conductor but in case of charged insulating material it is outside as well as inside the insulator.

## 4. CAPACITANCE OF AN ISOLATED SPHERICAL CONDUCTOR

### *Solved Example*

**Example 1.** Find out the capacitance of an isolated spherical conductor of radius  $R$ .

**Solution :** Let there is charge  $Q$  on sphere.

$$\therefore \text{Potential } V = \frac{KQ}{R}$$

Hence by formula :  $Q = CV$

$$Q = \frac{CKQ}{R}$$

$$C = 4\pi\epsilon_0 R \quad (\because C_{\text{Earth}} = 711 \mu\text{F})$$

Capacitance of an isolated spherical conductor

$$C = 4\pi\epsilon_0 R$$

- (i) If the medium around the conductor is vacuum or air.

$$C_{\text{vacuum}} = 4\pi\epsilon_0 R$$

$R$  = Radius of spherical conductor. (may be solid or hollow.)


- (ii) If the medium around the conductor is a dielectric of constant  $K$  from surface of sphere to infinity.

$$C_{\text{medium}} = 4\pi\epsilon_0 KR$$

- (iii)  $\frac{C_{\text{medium}}}{C_{\text{air/vacuum}}} = K = \text{dielectric constant.}$


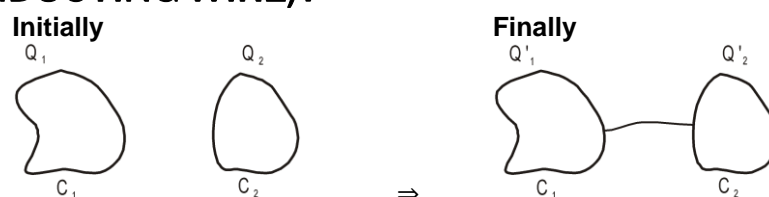
## 5. SHARING OF CHARGES ON JOINING TWO CONDUCTORS (BY A CONDUCTING WIRE):



- (i) Whenever there is potential difference, there will be movement of charge.
- (ii) If released, charge always have tendency to move from **high potential energy** to **low potential energy**.
- (iii) If released, positive charge moves from **high potential** to **low potential** [if only electric force act on charge].

## Capacitance

- (iv) If released, negative charge moves from **low potential** to **high potential** [if only electric force act on charge].
- (v) The movement of charge will continue till there is potential difference between the conductors (finally potential difference = 0).
- (vi) Formulae related with redistribution of charges :

Before connecting the conductors		
Parameter	I <sup>st</sup> Conductor	II <sup>nd</sup> Conductor
Capacitance	$C_1$	$C_2$
Charge	$Q_1$	$Q_2$
Potential	$V_1$	$V_2$

After connecting the conductors		
Parameter	I <sup>st</sup> Conductor	II <sup>nd</sup> Conductor
Capacitance	$C_1$	$C_2$
Charge	$Q_1'$	$Q_2'$
Potential	$V$	$V$

$$\begin{aligned}
 V &= \frac{Q_1'}{C_1} = \frac{Q_2'}{C_2} \Rightarrow \frac{Q_1'}{Q_2'} = \frac{C_1}{C_2} \quad \text{But, } Q_1' + Q_2' = Q_1 + Q_2 \\
 \therefore V &= \frac{Q_1 + Q_2}{C_1 + C_2} = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2} \quad \therefore Q_1' = \frac{C_1}{C_1 + C_2} (Q_1 + Q_2) \\
 \& \quad Q_2' &= \frac{C_2}{C_1 + C_2} (Q_1 + Q_2)
 \end{aligned}$$


$$\text{Heat loss during redistribution : } \Delta H = \frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} (V_1 - V_2)^2$$

The loss of energy is in the form of Joule heating in the wire.

**Note :** Always put  $Q_1$ ,  $Q_2$ ,  $V_1$  and  $V_2$  with sign.

### Solved Example

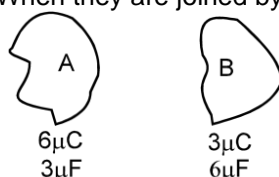**Example 2.** A and B are two isolated conductors (that means they are placed at a large distance from each other). When they are joined by a conducting wire:



- (i) Find out final charges on A and B ?
- (ii) Find out heat produced during the process of flow of charges.
- (iii) Find out common potential after joining the conductors by conducting wires?

**Solution :**

$$(i) \quad Q_A' = \frac{3}{3+6} (6+3) = 3\mu C, \quad Q_B' = \frac{6}{3+6} (6+3) = 6\mu C$$

$$(ii) \quad \Delta H = \frac{1}{2} \cdot \frac{3\mu F \cdot 6\mu F}{(3\mu F + 6\mu F)} \cdot \left(2 - \frac{1}{2}\right)^2 = \frac{1}{2} \cdot (2\mu F) \cdot \left(\frac{3}{2}\right)^2 = \frac{9}{4} \mu J$$

$$(iii) \quad V_C = \frac{3\mu C + 6\mu C}{3\mu F + 6\mu F} = 1 \text{ volt.}$$

**Example 3.** When  $30\mu C$  charge is given to an isolated conductor of capacitance  $5\mu F$ . Find out the following

- Potential of the conductor
- Energy stored in the electric field of conductor
- If this conductor is now connected to another isolated conductor by a conducting wire (at very large distance) of total charge  $50\mu C$  and capacity  $10\mu F$  then
  - find out the common potential of both the conductors.
  - Find out the heat dissipated during the process of charge distribution.
  - Find out the ratio of final charges on conductors.
  - Find out the final charges on each conductor.

**Solution**

$$Q_1 = 30\mu C, \quad C_1 = 5\mu F$$

$$(i) \quad V_1 = \frac{Q_1}{C_1} = \frac{30}{5} = 6V \quad \text{Ans.}$$

$$(ii) \quad U = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} \frac{(30 \times 10^{-6})^2}{(5 \times 10^{-6})} = 90 \mu J \quad \text{Ans.}$$

$$(iii) \quad Q_2 = 50\mu C, \quad C_2 = 10\mu F, \quad V_2 = \frac{Q_2}{C_2} = \frac{50}{10} = 5V.$$

$$(1) \quad \text{Common potential } V = \frac{Q_1 + Q_2}{C_1 + C_2} = \frac{30 + 50}{5 + 10} = \frac{16}{3} V \quad \text{Ans.}$$

$$(2) \quad \Delta H = \frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} (V_1 - V_2)^2 = \frac{1}{2} \frac{5 \times 10}{5 + 10} (6 - 5)^2 = \frac{5}{3} \text{ mJ} \quad \text{Ans.}$$

$$(3) \quad \frac{Q_1'}{Q_2'} = \frac{C_1}{C_2} = \frac{5}{10} = \frac{1}{2} \quad \text{Ans.}$$

$$(4) \quad Q_{11} = C_1 V = 5 \times \frac{16}{3} = \frac{80}{3} \text{ mC}$$

$$Q_{22} = C_2 V = 10 \times \frac{16}{3} = \frac{160}{3} \mu C.$$



## 6. CAPACITOR:

A capacitor or condenser consists of two conductors separated by an insulator or dielectric.

(i) When uncharged conductor is brought near to a charged conductor, the charge on conductors remains same but its potential decreases resulting in the increase of capacitance.


(ii) In capacitor two conductors have equal but opposite charges.

(iii) The conductors are called the plates of the capacitor. The name of the capacitor depends on the shape of the capacitor.

(iv) Formulae related with capacitors

$$(1) \quad Q = CV \Rightarrow C = \frac{Q}{V} = \frac{Q_A}{V_A - V_B} = \frac{Q_B}{V_B - V_A}$$

## Capacitance

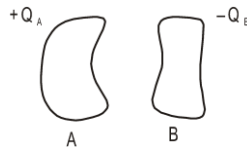

$Q$  = Charge of positive plate of capacitor.

$V$  = Potential difference between positive and negative plates of capacitor


$C$  = Capacitance of capacitor.

- (2) Energy stored in the capacitor




Initially charge = 0

Intermediate

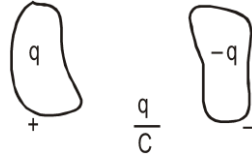

Finally,

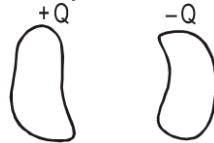


$$W = \int dW = \int_0^Q \frac{q}{C} dq = \frac{Q^2}{C}$$

$$\therefore \text{Energy stored in the capacitor} = U = \frac{Q^2}{2C} = \frac{1}{2} CV^2 = \frac{1}{2} QV.$$

This energy is stored inside the capacitor in its electric field with energy density

$$\frac{dU}{dV} = \epsilon E^2 \frac{1}{2} \text{ or } \frac{1}{2} \epsilon_0 \epsilon_r E^2.$$

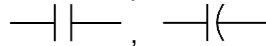- (v) The capacitor is represented as following:



- (vi) Based on shape and arrangement of capacitor plates there are various types of capacitors.

- (1) Parallel plate capacitor.
- (2) Spherical capacitor.
- (3) Cylindrical capacitor.

- (vii) Capacitance of a capacitor depends on

- (1) Area of plates.
- (2) Distance between the plates.
- (3) Dielectric medium between the plates.


### Solved Example

**Example 4.** Find out the capacitance of parallel plate capacitor of plate area  $A$  and plate separation  $d$ .

**Solution :**  $E = \frac{Q}{A\epsilon_0}$

$$V_A - V_B = E \cdot d = \frac{Qd}{A\epsilon_0} = \frac{Q}{C}$$

## Capacitance

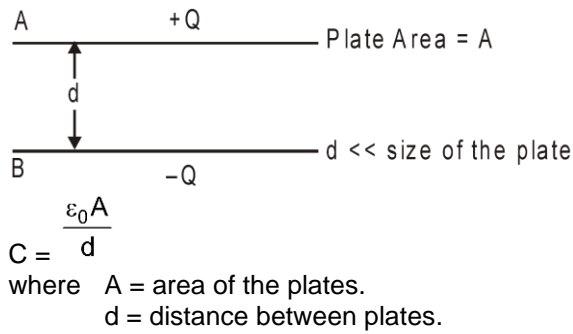

- (viii) Electric field intensity between the plates of capacitors (air filled )



$$E = \sigma/\epsilon_0 = V/d$$

- (ix) Force experienced by any plate of capacitor



$$F = \frac{q^2}{2A\epsilon_0}$$
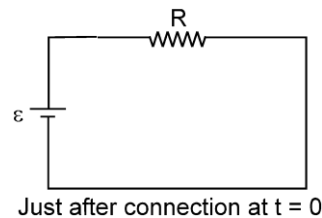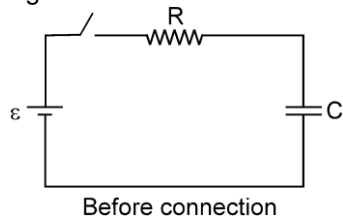
## 7. CIRCUIT SOLUTION FOR R-C CIRCUIT AT $t = 0$ (INITIAL STATE) AND AT $t = \infty$ (FINAL STATE)

- Note :** (i) Charge on the capacitor does not change instantaneously or suddenly if there is a resistance in the path (series) of the capacitor.  
 (ii) When an uncharged capacitor is connected with battery then its charge is zero initially hence potential difference across it is zero initially. At this time the capacitor can be treated as a conducting wire



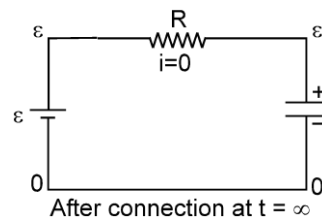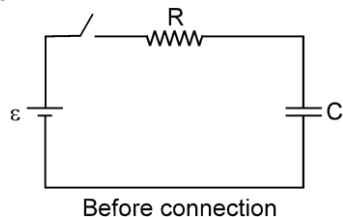
- (iii) The current will become zero finally (that means in steady state) in the branch which contains capacitor.



## Solved Examples


**Example 5.** Find out current in the circuit and charge on capacitor which is initially uncharged in the following situations.

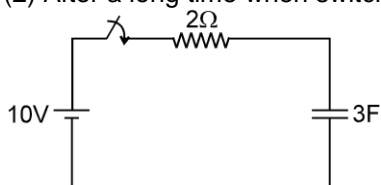- (1) Just after the switch is closed.  
 (2) After a long time when switch was closed.




**Solution :** (1) For just after closing the switch: potential difference across capacitor = 0

## Capacitance

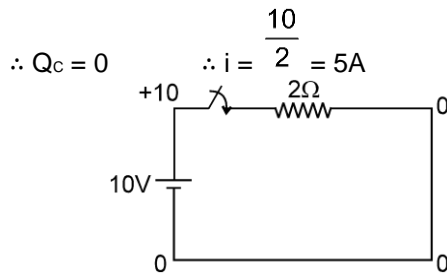

**(2) After a long time**

at steady state current  $i = 0$

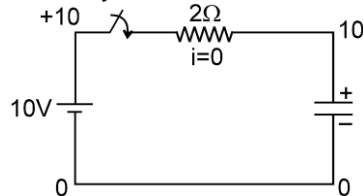

and potential difference across capacitor = 10 V


$$\therefore Q_C = 3 \times 10 = 30 \text{ C}$$

### Example 6.

Find out current  $I_1$ ,  $I_2$ ,  $I_3$ , charge on capacitor and  $\frac{dQ}{dt}$  of capacitor in the circuit which is initially uncharged in the following situations.


(1) Just after the switch is closed

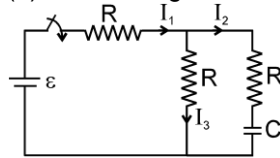(2) After a long time when switch is closed.



### Solution :

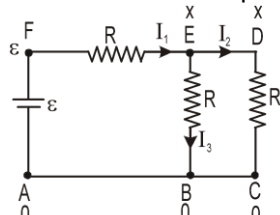**(1)** Initially the capacitor is uncharged so its behaviour is like a conductor. Let potential at A is zero so at B and C also zero and at F it is  $\epsilon$ . Let potential at E is  $x$  so at D also  $x$ . Apply Kirchhoff's 1st law at point E :



$$\frac{x - \epsilon}{R} + \frac{x - 0}{R} + \frac{x - 0}{R} = 0 \quad \Rightarrow \quad \frac{3x}{R} = \frac{\epsilon}{R}$$

$$x = \frac{\epsilon}{3} \quad Q_C = 0$$

$$\therefore I_1 = \frac{-\epsilon/3 + \epsilon}{R} = \frac{2\epsilon}{3R} \quad \Rightarrow \quad I_2 = \frac{dQ}{dt} = \frac{\epsilon}{3R} \quad \Rightarrow \quad I_3 = \frac{\epsilon}{3R}$$


**Alternatively**

$$i_1 = \frac{\epsilon}{R_{eq}} = \frac{\epsilon}{R + \frac{R}{2}} = \frac{2\epsilon}{3R} \quad \Rightarrow \quad i_2 = i_3 = \frac{i_1}{2} = \frac{\epsilon}{3R}$$

**(2) at  $t = \infty$  (finally)**

capacitor completely charged so there will be no current through it.

## Capacitance

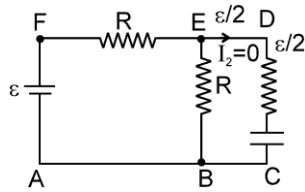

$$I_2 = 0, \quad I_1 = I_3 = \frac{\varepsilon}{2R}$$


$$V_E - V_B = V_D - V_C = (\varepsilon/2R)R = \varepsilon/2$$

$$\Rightarrow Q_C = \frac{\varepsilon C}{2}, \quad \frac{dQ}{dt} = I_2 = 0$$

Time	$I_1$	$I_2$	$I_3$	$Q$	$dQ/dt$
$t = 0$	$\frac{2\varepsilon}{3R}$	$\frac{\varepsilon}{3R}$	$\frac{\varepsilon}{3R}$	0	$\frac{\varepsilon}{3R}$
Finally $t = \infty$	$\frac{\varepsilon}{2R}$	0	$\frac{\varepsilon}{2R}$	$\frac{\varepsilon C}{2}$	0

**Example 7.** A capacitor of capacitance  $C$  which is initially uncharged is connected with a battery. Find out heat dissipated in the circuit during the process of charging.

**Solution :**

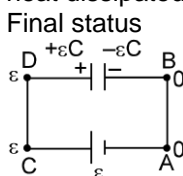

Let potential at point A is 0, so at B also 0 and at C and D it is  $\varepsilon$ .  
finally, charge on the capacitor

$$Q_C = \varepsilon C, \quad U_i = 0, \quad U_f = \frac{1}{2} C V^2 = \frac{1}{2} C \varepsilon^2$$


$$\text{work done by battery} = \int P dt = \int \varepsilon i dt = \varepsilon \int i dt = \varepsilon \cdot Q = \varepsilon \cdot \varepsilon C = \varepsilon^2 C$$

(Now onwards remember that w.d. by battery =  $\varepsilon Q$  if  $Q$  has flown out of the cell from high potential and w.d. on battery is  $\varepsilon Q$  if  $Q$  has flown into the cell through high potential)

$$\text{Heat produced} = W = (U_f - U_i) = \varepsilon^2 C - \frac{1}{2} \varepsilon^2 C = \frac{1}{2} \varepsilon^2 C$$

**Example 8.** A capacitor of capacitance  $C$  which is initially charged upto a potential difference  $\varepsilon$  is connected with a battery of emf  $\varepsilon$  such that the positive terminal of battery is connected with positive plate of capacitor. Find out heat loss in the circuit during the process of charging.

**Solution :**

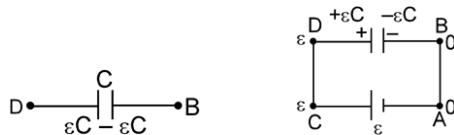

Since the initial and final charge on the capacitor is same before and after connection.  
Here no charge will flow in the circuit so heat loss = 0


**Example 9.** A capacitor of capacitance  $C$  which is initially charged upto a potential difference  $\varepsilon$  is connected with a battery of emf  $\varepsilon/2$  such that the positive terminal of battery is connected with positive plate of capacitor. After a long time

- Find out total charge flow through the battery
- Find out total work done by battery
- Find out heat dissipated in the circuit during the process of charging.



**Solution :**

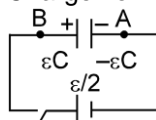
- (i) Let potential of A is 0 so at B it is  $\frac{\epsilon}{2}$ . So final charge on capacitor =  $C\epsilon/2$   
 Charge flow through the capacitor =  $(C\epsilon/2 - C\epsilon) = -C\epsilon/2$



So charge is entering into battery.

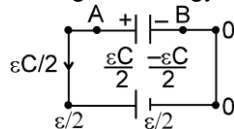- (ii) finally,

Change in energy of capacitor =  $U_{\text{final}} - U_{\text{initial}}$



$$= \frac{1}{2} C \left( \frac{\epsilon}{2} \right)^2 - \frac{\epsilon^2 C}{2} = \frac{1}{8} \epsilon^2 C - \frac{1}{2} \epsilon^2 C = -\frac{3\epsilon^2 C}{8}$$


$$\text{Work done by battery} = \frac{\epsilon}{2} \times \left( -\frac{\epsilon C}{2} \right) = -\frac{\epsilon^2 C}{4}$$

- (iii) Work done by battery = Change in energy of capacitor + Heat produced

$$\text{Heat produced} = \frac{3\epsilon^2 C}{8} - \frac{\epsilon^2 C}{4} = \frac{\epsilon^2 C}{8}$$

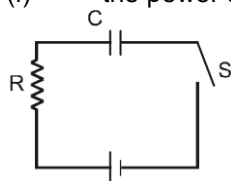**Example 10.** A capacitor of capacitance  $C$ , a resistor of resistance  $R$  and a battery of emf  $\epsilon$  are connected in series at  $t = 0$ . What is the maximum value of

- the potential difference across the resistor,
- the current in the circuit,
- the potential difference across the capacitor,
- the energy stored in the capacitors.
- the power delivered by the battery and
- the power converted into heat.



**Solution**


at  $t = 0$   $C$  is replace by wire.

- |                                                                                            |                                       |
|--------------------------------------------------------------------------------------------|---------------------------------------|
| (1) $V_{\text{max}} = \epsilon$                                                            | (2) $i = \frac{\epsilon}{R}$          |
| (3) $V_C = \epsilon$                                                                       | (4) $U_C = \frac{1}{2} C \epsilon^2$  |
| (4) $P_{\text{battery}} = i.v. = \frac{\epsilon}{R} \cdot \epsilon = \frac{\epsilon^2}{R}$ | (5) $\Delta H = \frac{\epsilon^2}{R}$ |


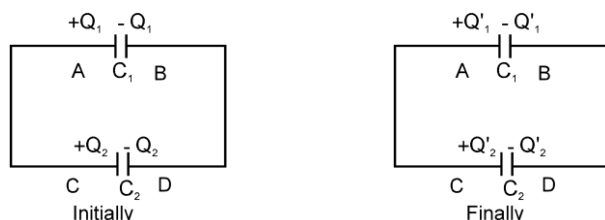
## 8. DISTRIBUTION OF CHARGES ON CONNECTING TWO CHARGED CAPACITORS:

When two capacitors are  $C_1$  and  $C_2$  are connected as shown in figure



Before connecting the capacitors		
Parameter	I <sup>st</sup> Capacitor	II <sup>nd</sup> Capacitor
Capacitance	$C_1$	$C_2$
Charge	$Q_1$	$Q_2$
Potential	$V_1$	$V_2$

After connecting the capacitors		
Parameter	I <sup>st</sup> Capacitor	II <sup>nd</sup> Capacitor
Capacitance	$C_1$	$C_2$
Charge	$Q'_1$	$Q'_2$
Potential	$V$	$V$

- (1) Common potential :  
By charge conservation of plates A and C before and after connection.

$$Q_1 + Q_2 = C_1 V + C_2 V$$

$$\Rightarrow V = \frac{Q_1 + Q_2}{C_1 + C_2} = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2} = \frac{\text{Total charge}}{\text{Total capacitance}}$$

$$(2) \quad Q'_1 = C_1 V = \frac{C_1}{C_1 + C_2} (Q_1 + Q_2)$$

$$Q'_2 = C_2 V = \frac{C_2}{C_1 + C_2} (Q_1 + Q_2)$$

- (3) Heat loss during redistribution :

$$\Delta H = U_i - U_f = \frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} (V_1 - V_2)^2$$




The loss of energy is in the form of Joule heating in the wire.

- Note :** (i) When plates of similar charges are connected with each other (+ with + and – with –) then put all values ( $Q_1$ ,  $Q_2$ ,  $V_1$ ,  $V_2$ ) with positive sign.  
(ii) When plates of opposite polarity are connected with each other (+ with –) then take charge and potential of one of the plate to be negative.



**Derivation of above formulae :**

## Capacitance

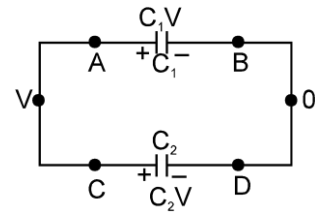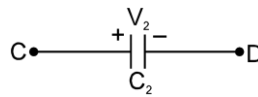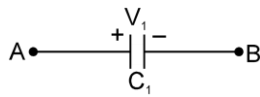

Let potential of B and D is zero and common potential on capacitors is  $V$ , then at A and C it will be  $V$

$$C_1 V + C_2 V = C_1 V_1 + C_2 V_2$$

$$V = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2} \Rightarrow H = \frac{1}{2} C_1 V_1^2 + \frac{1}{2} C_2 V_2^2 - \frac{1}{2} (C_1 + C_2) V^2$$


$$= \frac{1}{2} C_1 V_1^2 + \frac{1}{2} C_2 V_2^2 - \frac{1}{2} \frac{(C_1 V_1 + C_2 V_2)^2}{(C_1 + C_2)}$$

$$= \frac{1}{2} \left[ \frac{C_1^2 V_1^2 + C_1 C_2 V_1^2 + C_2 C_1 V_2^2 + C_2^2 V_2^2 - C_1^2 V_1^2 - C_2^2 V_2^2 - 2 C_1 C_2 V_1 V_2}{C_1 + C_2} \right]$$

$$= \frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} (V_1 - V_2)^2$$

$$H = \frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} (V_1 - V_2)^2$$

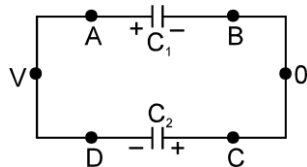when oppositely charge terminals are connected then





$$\therefore C_1 V + C_2 V = C_1 V_1 - C_2 V_2$$

$$V = \frac{C_1 V_1 - C_2 V_2}{C_1 + C_2} ; H = \frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} (V_1 + V_2)^2$$


## Solved Examples

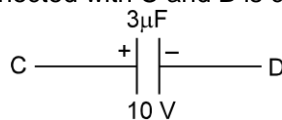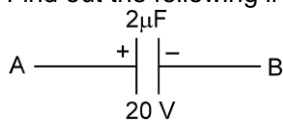**Example 11** Find out the following if A is connected with C and B is connected with D.



- How much charge flows in the circuit.
- How much heat is produced in the circuit.

**Solution :** (i)

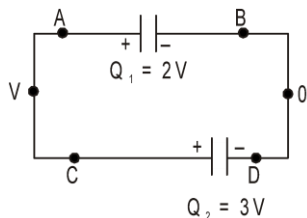

Let potential of B and D is zero and common potential on capacitors is  $V$ , then at A and C it will be  $V$ .

By charge conservation,

$$3V + 2V = 40 + 30$$

$$5V = 70$$

$$V = 14 \text{ volt}$$


## Capacitance

Charge flow

$$= 40 - 28$$

$$= 12 \mu\text{C}$$

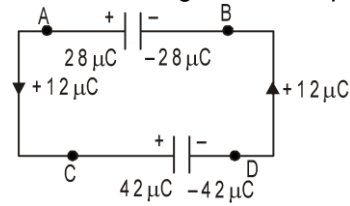
Now final charges on each plate is shown in the figure



$$\begin{aligned} \text{(ii) Heat produced} &= \frac{1}{2} \times 2 \times (20)^2 + \frac{1}{2} \times 3 \times (10)^2 - \frac{1}{2} \times 5 \times (14)^2 \\ &= 400 + 150 - 490 \\ &= 550 - 490 = 60 \mu\text{J} \end{aligned}$$

- Note :** (i) When capacitor plates are joined then the charge remains conserved.  
(ii) We can also use direct formula of redistribution as given above.

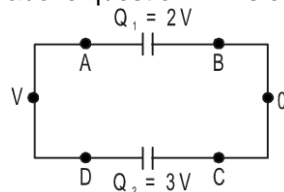**Example 12.** Repeat above question if A is connected with D and B is connected with C.




**Solution :** Let potential of B and C is zero and common potential on capacitors is V, then at A and D it will be V

$$2V + 3V = 10$$

$$\Rightarrow V = 2 \text{ volt}$$

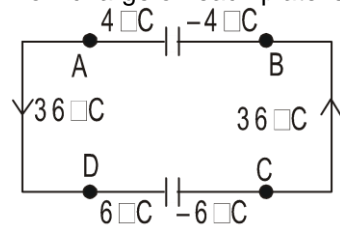
Now charge on each plate is shown in the figure



$$\begin{aligned} \text{Heat produced} &= 400 + 150 - \frac{1}{2} \times 5 \times 4 \\ &= 550 - 10 \\ &= 540 \mu\text{J} \end{aligned}$$

**Note :** Here heat produced is more. Think why?

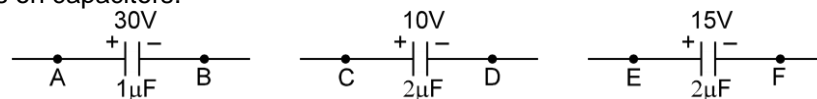**Example 13.** Three capacitors as shown of capacitance  $1 \mu\text{F}$ ,  $2 \mu\text{F}$  and  $2 \mu\text{F}$  are charged upto potential difference 30 V, 10 V and 15 V respectively. If terminal A is connected with D, C is connected with E and F is connected with B. Then find out charge flow in the circuit and find the final charges on capacitors.




**Solution :** Let charge flow is q.  
Now applying kirchhoff's voltage law

$$-\frac{(q-20)}{2} - \frac{(30+q)}{2} + \frac{30-q}{1} = 0$$

$$-2q = -25$$

$$q = 12.5 \mu\text{C}$$


Final charges on plates

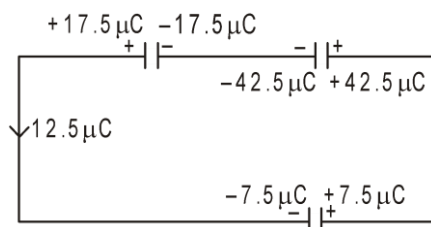

## 9. COMBINATION OF CAPACITORS:

### 9.1 Series Combination :

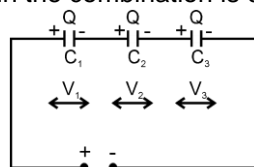- (i) When initially uncharged capacitors are connected as shown in the combination is called series combination.



- (ii) All capacitors will have same charge but different potential difference across them.  
 (iii) We can say that

$$V_1 = \frac{Q}{C_1}$$

$V_1$  = potential across  $C_1$   
 $Q$  = charge on positive plate of  $C_1$   
 $C_1$  = capacitance of capacitor similarly

$$V_2 = \frac{Q}{C_2}, V_3 = \frac{Q}{C_3} \dots\dots$$

(iv)  $V_1 : V_2 : V_3 = \frac{1}{C_1} : \frac{1}{C_2} : \frac{1}{C_3}$

We can say that potential difference across capacitor is inversely proportional to its capacitance in series combination.

$$V \propto \frac{1}{C}$$

**Note :** In series combination the smallest capacitor gets maximum potential.

## Capacitance

$$(v) \quad V_1 = \frac{\frac{1}{C_1}}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots} V \quad V_2 = \frac{\frac{1}{C_2}}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots} V$$

$$V_3 = \frac{\frac{1}{C_3}}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots} V$$

(vi) Where  $V = V_1 + V_2 + V_3$   
 Equivalent Capacitance :  
 Equivalent capacitance of any combination is that capacitance which when connected in place of the combination stores same charge and energy that of the combination.

In series :

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$$

**Note :** In series combination equivalent is always less the smallest capacitor of combination.

(vii) Energy stored in the combination

$$U_{\text{combination}} = \frac{Q^2}{2C_1} + \frac{Q^2}{2C_2} + \frac{Q^2}{2C_3} \Rightarrow U_{\text{combination}} = \frac{Q^2}{2C_{eq}}$$


Energy supplied by the battery in charging the combination


$$U_{\text{battery}} = Q \times V = Q \cdot \frac{Q}{C_{eq}} = \frac{Q^2}{C_{eq}} \Rightarrow \frac{U_{\text{combination}}}{U_{\text{battery}}} = \frac{1}{2}$$

**Note :** Half of the energy supplied by the battery is stored in form of electrostatic energy and half of the energy is converted into heat through resistance.




### Derivation of Formulae :

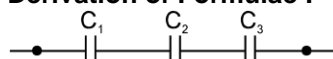  
 meaning of equivalent capacitor

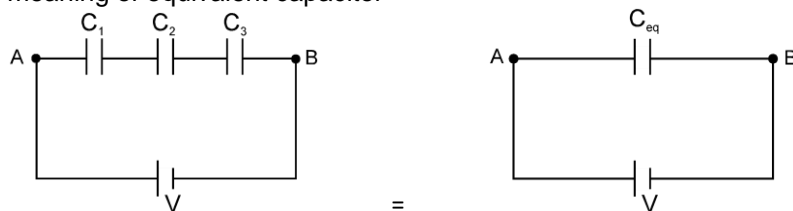

$$C_{eq} = \frac{Q}{V}$$

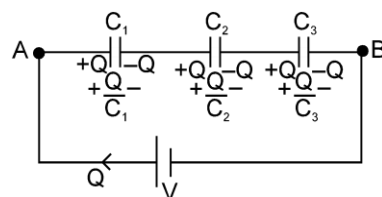


Now,  
 Initially, the capacitor has no charge.  
 Applying kirchhoff's voltage law

$$\frac{-Q}{C_1} + \frac{-Q}{C_2} + \frac{-Q}{C_3} + V = 0. \Rightarrow V = Q \left[ \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right]$$

$$\frac{V}{Q} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \Rightarrow \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \text{ in general } \frac{1}{C_{eq}} = \sum_{n=1}^n \frac{1}{C_n}$$

## Solved Examples

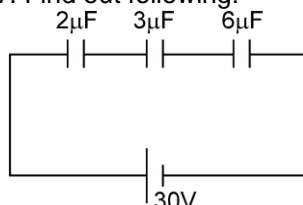**Example 14.** Three initially uncharged capacitors are connected in series as shown in circuit with a battery of emf 30V. Find out following:-



- (i) charge flow through the battery,
- (ii) potential energy in 3 μF capacitor.
- (iii)  $U_{total}$  in capacitors
- (iv) heat produced in the circuit

**Solution :**  $\frac{1}{C_{eq}} = \frac{1}{2} + \frac{1}{3} + \frac{1}{6} = \frac{3+2+1}{6} = 1$

$C_{eq} = 1\mu F.$

(i)  $Q = C_{eq} V = 30\mu C.$

(ii) charge on 3μF capacitor = 30μC  $\Rightarrow$  energy =  $\frac{Q^2}{2C} = \frac{30 \times 30}{2 \times 3} = 150\mu J$


(iii)  $U_{total} = \frac{2}{30 \times 30} \mu J = 450 \mu J$

(iv) Heat produced = (30 μC) (30) – 450 μJ = 450 μJ.

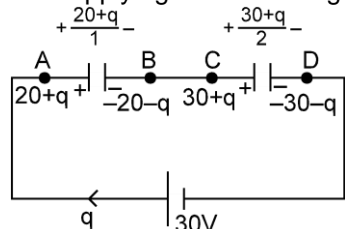**Example 15.** Two capacitors of capacitance 1 μF and 2μF are charged to potential difference 20V and 15V as shown in figure. If now terminal B and C are connected together terminal A with positive of battery and D with negative terminal of battery of emf 30 V. then find out final charges on both the capacitor



**Solution :** Now applying kirchoff voltage law



$$\frac{-(20+q)}{1} - \frac{30+q}{2} + 30 = 0$$

$$-40 - 2q - 30 - q = -60$$

$$3q = -10$$

$$\text{Charge flow} = -10/3 \mu C.$$


$$\text{Charge on capacitor of capacitance } 1\mu F = 20 + q = \frac{50}{3}$$

$$\text{Charge on capacitor of capacitance } 2\mu\text{F} = 30 + q = \frac{80}{3}$$



### 9.2 Parallel Combination :

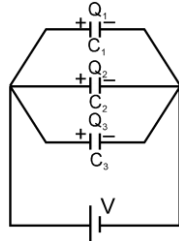- (i) When one plate of each capacitors (more than one) is connected together and the other plate of each capacitor is connected together, such combination is called parallel combination.



- (ii) All capacitors have same potential difference but different charges.

- (iii) We can say that :

$$Q_1 = C_1 V$$

$Q_1$  = Charge on capacitor  $C_1$

$C_1$  = Capacitance of capacitor  $C_1$

$V$  = Potential across capacitor  $C_1$

- (iv)  $Q_1 : Q_2 : Q_3 = C_1 : C_2 : C_3$

The charge on the capacitor is proportional to its capacitance

$$Q \propto C$$

- (v)  $Q_1 = \frac{C_1}{C_1 + C_2 + C_3} Q$      $Q_2 = \frac{C_2}{C_1 + C_2 + C_3} Q$      $Q_3 = \frac{C_3}{C_1 + C_2 + C_3} Q$   
Where  $Q = Q_1 + Q_2 + Q_3 \dots\dots$

**Note :** Maximum charge will flow through the capacitor of largest value.

- (vi) Equivalent capacitance of parallel combination  
 $C_{eq} = C_1 + C_2 + C_3$

**Note :** Equivalent capacitance is always greater than the largest capacitor of combination.

- (vii) Energy stored in the combination :

$$\begin{aligned} V_{\text{combination}} &= \frac{1}{2} C_1 V_2 + \frac{1}{2} C_2 V_2 + \dots = \frac{1}{2} (C_1 + C_2 + C_3 \dots\dots) V_2 \\ &= \frac{1}{2} C_{eq} V_2 \\ U_{\text{battery}} &= QV = CV_2 \\ \frac{U_{\text{combination}}}{U_{\text{battery}}} &= \frac{1}{2} \end{aligned}$$


**Note :** Half of the energy supplied by the battery is stored in form of electrostatic energy and half of the energy is converted into heat through resistance.

### Formulae Derivation for parallel combination :

$$\begin{aligned} Q &= Q_1 + Q_2 + Q_3 \\ &= C_1 V + C_2 V + C_3 V \\ &= V(C_1 + C_2 + C_3) \end{aligned}$$



## Capacitance

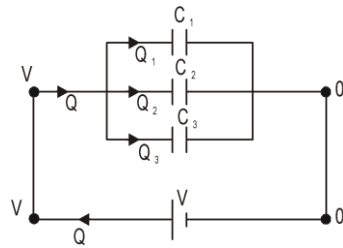

$$\frac{Q}{V} = C_1 + C_2 + C_3$$


$$C_{eq} = C_1 + C_2 + C_3$$

In general

$$C_{eq} = \sum_{n=1}^n C_n$$

### Solved Example

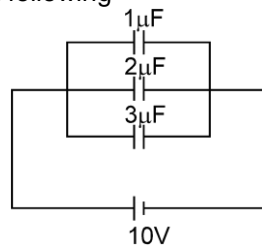**Example 16.** Three initially uncharged capacitors are connected to a battery of 10 V in parallel combination. Find out the following:



- charge flow from the battery
- total energy stored in the capacitors
- heat produced in the circuit
- potential energy in the 3 μF capacitor.

**Solution :**

- $Q = (30 + 20 + 10) \mu C = 60 \mu C$
- $U_{total} = \frac{1}{2} \times 6 \times 10 \times 10 = 300 \mu J$
- heat produced =  $60 \times 10 - 300 = 300 \mu J$
- $U_{3\mu F} = \frac{1}{2} \times 3 \times 10 \times 10 = 150 \mu J$



### 9.3 Mixed Combination :


The combination which contains mixing of series parallel combinations or other complex combinations fall in mixed category.

There are two types of mixed combinations

- Simple
- Complex.


### Solved Example

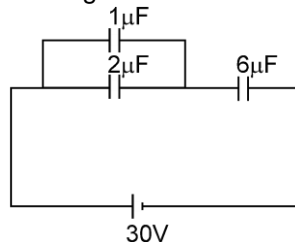**Example 17.** In the given circuit find out charge on 6 μF and 1 μF capacitor.



**Solution :** It can be simplified as

## Capacitance

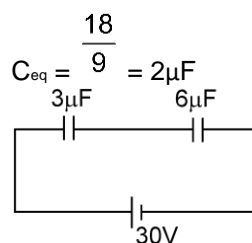

charge flow through the cell =  $30 \times 2 \mu C$

$Q = 60 \mu C$


Now charge on  $3\mu F$  = Charge on  $6\mu F$  =  $60 \mu C$

Potential difference across  $3\mu F$  =  $60 / 3 = 20 V$

$\therefore$  Charge on  $1\mu F$  =  $20 \mu C$ .
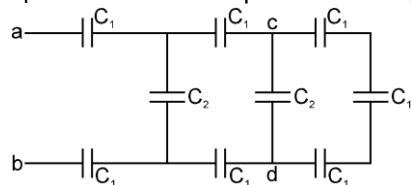
### Example 18. Comprehension :

In the arrangement of the capacitors shown in the figure, each  $C_1$  capacitor has capacitance of  $3\mu F$  and each  $C_2$  capacitor has capacitance of  $2\mu F$  then,



1. Equivalent capacitance of the network between the points a and b is :

(1\*)  $1\mu F$  (2)  $2\mu F$  (3)  $4\mu C$  (4)  $\frac{3}{2}\mu F$

2. If  $V_{ab} = 900 V$ , the charge on each capacitor nearest to the points 'a' and 'b' is :

(1)  $300 \mu C$  (2)  $600 \mu C$  (3)  $450 \mu C$  (4\*)  $900 \mu C$

3. If  $V_{ab} = 900 V$ , then potential difference across points c and d is :


(1)  $60 V$  (2\*)  $100 V$  (3)  $120 V$  (4)  $200 V$

**Solution :**

$$(i) \quad \frac{1}{C_1^1} = \frac{1}{C_1} + \frac{1}{C_2} \Rightarrow C_{11} = 1\mu F$$

$$C_{21} = C_2 + C_{11} = 3\mu F \quad C_{eq} = 1\mu F$$

**Ans.**

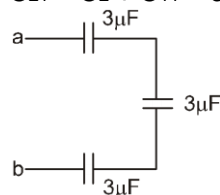


(ii)

$$C_{eq} = 1\mu F \quad Q = C_{eq} V = 900\mu F$$

charge on nearest capacitor =  $900\mu F$

**Ans**

(iii)


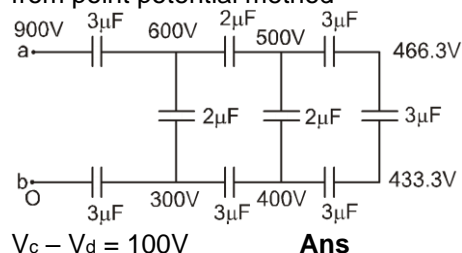


**Ans**

### Example 19. Comprehension :
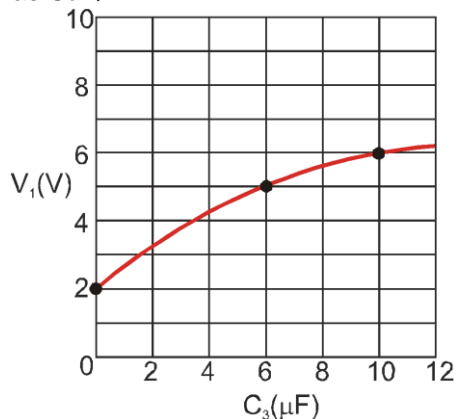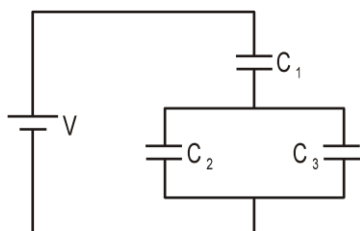
## Capacitance


Capacitor  $C_3$  in the circuit is a variable capacitor (its capacitance can be varied). Graph is plotted between potential difference  $V_1$  (across capacitor  $C_1$ ) versus  $C_3$ . Electric potential  $V_1$  approaches on asymptote of 10 V as  $C_3 \rightarrow \infty$ .



- EMF of the battery is equal to :  
 (1\*) 10 V                      (2) 12 V                      (3) 16 V                      (4) 20 V
- The capacitance of the capacitor  $C_1$  has value :  
 (1) 2  $\mu F$                       (2) 6  $\mu F$                       (3\*) 8  $\mu F$                       (4) 12  $\mu F$
- The capacitance of  $C_2$  is equal to :  
 (1\*) 2  $\mu F$                       (2) 6  $\mu F$                       (3) 8  $\mu F$                       (4) 12  $\mu F$

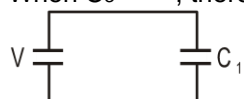**Solution**

When  $C_3 = \infty$ , there will be no charge on  $C_2$



As  $V_1 = 10 V$  therefore  $V = 10 V$


From graph when  $C_3 = 10 \mu F$ ,  $V_1 = 6 V$

Charge on  $C_1$  = Charge on  $C_2$  + Charge on  $C_3$

$$6C_1 = 4C_2 + 40 \mu C \quad \dots (1)$$

Also when  $C_3 = 6 \mu F$ ,  $V_1 = 5 V$

Again using charge equation

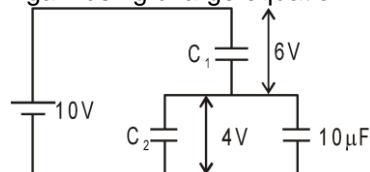


$$5C_1 = 5C_2 + 30 \mu C \quad \dots (2)$$

Solving (1) and (2)

$$C_1 = 8 \mu F$$

$$C_2 = 2 \mu F.$$

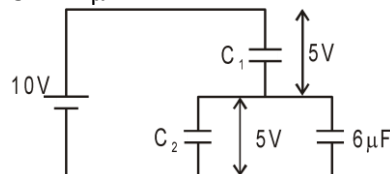


## 10. CHARGING AND DISCHARGING OF A CAPACITOR

### 10.1 Charging of a condenser :

## Capacitance

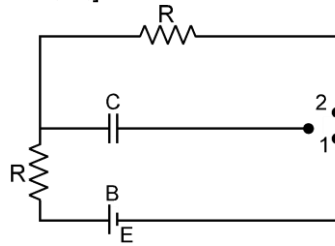
(i) In the following circuit. If key 1 is closed then the condenser gets charged. Finite time is taken in the charging process. The quantity of charge at any instant of time  $t$  is given by  $q = q_0[1 - e^{-(t/RC)}]$



Where  $q_0$  = maximum final value of charge at  $t = \infty$ .

According to this equations the quantity of charge on the condenser increases exponentially with increase of time.

(ii) If  $t = RC = \tau$  then

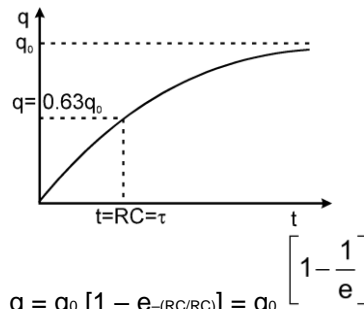

or  $q = q_0 (1 - 0.37) = 0.63 q_0$   
= 63% of  $q_0$

(iii) Time  $t = RC$  is known as time constant.

i.e. the time constant is that time during which the charge rises on the condenser plates to 63% of its maximum value.

(iv) The potential difference across the condenser plates at any instant of time is given by

$$V = V_0[1 - e^{-(t/RC)}] \text{ volt}$$

(v) The potential curve is also similar to that of charge. During charging process an electric current flows in the circuit for a small interval of time which is known as the transient current.

The value of this current at any instant of time is given by


$$I = I_0[e^{-(t/RC)}] \text{ ampere}$$

According to this equation the current falls in the circuit exponentially (Fig.).

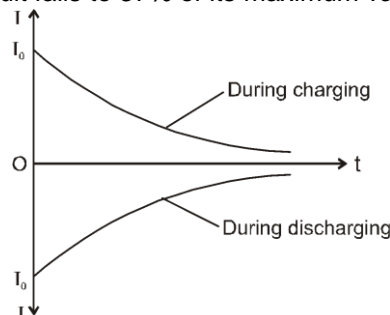
(vi) If  $t = RC = \tau$  = Time constant

$$I = I_0 e^{-(RC/RC)} = \frac{I_0}{e} = 0.37 I_0 = 37\% \text{ of } I_0$$

i.e. time constant is that time during which current in the circuit falls to 37% of its maximum value.




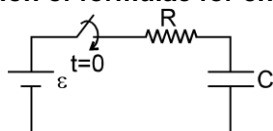**Derivation of formulae for charging of capacitor**


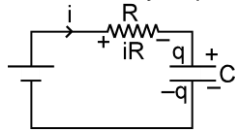
## Capacitance

it is given that initially capacitor is uncharged.



let at any time

Applying kirchoff voltage law


$$\varepsilon - iR - \frac{q}{C} = 0 \Rightarrow iR = \frac{\varepsilon C - q}{C} \Rightarrow i = \frac{\varepsilon C - q}{CR} \Rightarrow \frac{dq}{dt} = \frac{\varepsilon C - q}{CR}$$

$$\frac{dq}{dt} = \frac{\varepsilon C - q}{CR} \Rightarrow \frac{CR}{\varepsilon C - q} \cdot dq = dt \Rightarrow \int_0^q \frac{dq}{\varepsilon C - q} = \int_0^t \frac{dt}{RC}$$

$$\Rightarrow -\ln(\varepsilon C - q) + \ln \varepsilon C = \frac{t}{RC}$$

$$\ln \frac{\varepsilon C}{\varepsilon C - q} = \frac{t}{RC}$$
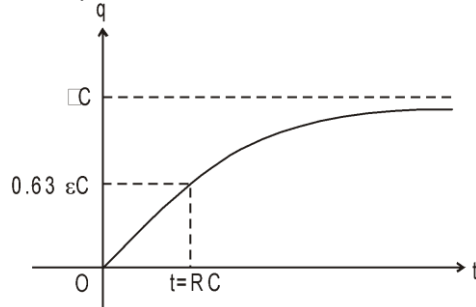
$$\varepsilon C - q = \varepsilon C \cdot e^{-t/RC}$$



$$q = \varepsilon C (1 - e^{-t/RC})$$


RC = time constant of the RC series circuit.

**After one time constant**

$$q = \varepsilon C \left(1 - \frac{1}{e}\right) = \varepsilon C (1 - 0.37) = 0.63 \varepsilon C.$$

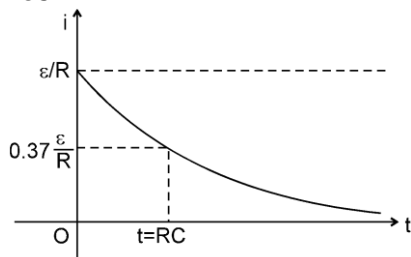**Current at any time t**


$$i = \frac{dq}{dt} = \varepsilon C \left( -e^{-t/RC} \left( -\frac{1}{RC} \right) \right) = \frac{\varepsilon}{R} e^{-t/RC}$$



**Voltage across capacitor after one time constant  $V = 0.63 \varepsilon$**

$$Q = CV, V_C = \varepsilon (1 - e^{-t/RC})$$

## Capacitance

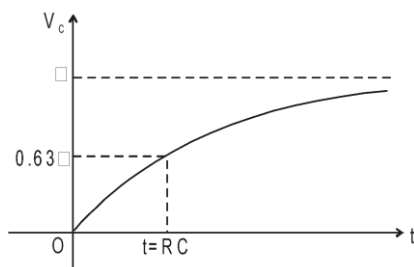


### Voltage across the resistor

$$V_R = iR = \varepsilon e^{-t/RC}$$

By energy conservation,

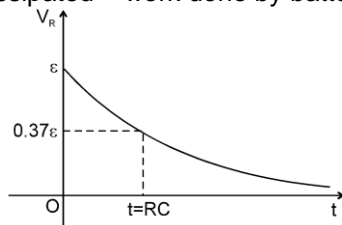
Heat dissipated = work done by battery – ΔU capacitor



$$= C\varepsilon(\varepsilon) - \left( \frac{1}{2} C\varepsilon^2 - 0 \right) = \frac{1}{2} C\varepsilon^2$$

Alternatively :
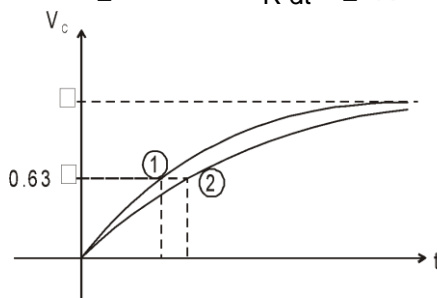
$$\text{Heat} = H = \int_0^{\infty} i^2 R dt = \int_0^{\infty} \frac{\varepsilon^2}{R^2} e^{-\frac{2t}{RC}} R dt = \frac{\varepsilon^2}{R} \int_0^{\infty} e^{-2t/RC} dt = \frac{\varepsilon^2}{R} \left[ \frac{e^{-\frac{2t}{RC}}}{-2/RC} \right]_0^{\infty}$$



In the figure time constant of (2) is more than (1)

$$= - \frac{\varepsilon^2 RC}{2R} \left[ e^{-\frac{2t}{RC}} \right]_0^{\infty} = \frac{\varepsilon^2 C}{2}$$

## Solved Examples

**Example 20 :** A capacitor is connected to a 12 V battery through a resistance of 10Ω. It is found that the potential difference across the capacitor rises to 4.0 V in 1μs. Find the capacitance of the capacitor.

**Solution :** The charge on the capacitor during charging is given by  $Q = Q_0(1 - e^{-t/RC})$ .  
Hence, the potential difference across the capacitor is  $V = Q/C = Q_0/C (1 - e^{-t/RC})$ .  
Here, at  $t = 1 \mu s$ , the potential difference is 4V whereas the steady potential difference is

$$Q_0/C = 12V. \text{ So, } \Rightarrow 4V = 12V(1 - e^{-t/RC})$$

$$\text{or } 1 - e^{-t/RC} = \frac{1}{3} \text{ or } e^{-t/RC} = \frac{2}{3} \text{ or } \frac{t}{RC} = \ln\left(\frac{3}{2}\right) = 0.405$$

$$\text{or } RC = \frac{t}{0.405} = \frac{1 \mu s}{0.405} = 2.469 \mu s \text{ or } C = \frac{2.469 \mu s}{10 \Omega} = 0.25 \mu F.$$



## Method for objective :

In any circuit when there is only one capacitor then


$$q = Q_{st} (1 - e^{-t/\tau}); \quad Q_{st} = \text{steady state charge on capacitor (has been found in article 6 in this sheet)}$$

$$\tau = R_{eff.} C$$


$R_{effective}$  is the resistance between the capacitor when battery is replaced by its internal resistance.

## 10.2 Discharging of a condenser :

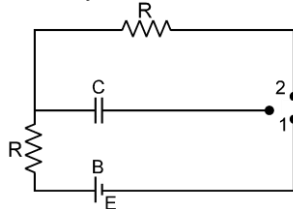- (i) In the above circuit (in article 8.1) if key 1 is opened and key 2 is closed then the condenser gets discharged.



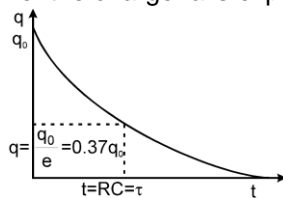- (ii) The quantity of charge on the condenser at any instant of time  $t$  is given by  $q = q_0 e^{-(t/RC)}$   
i.e. the charge falls exponentially.



- (iii) If  $t = RC = \tau = \text{time constant}$ , then



$$\frac{q_0}{e}$$

$$q = \frac{q_0}{e} = 0.37q_0 = 37\% \text{ of } q_0$$

i.e. the time constant is that time during which the charge on condenser plates discharge process falls to 37%


- (iv) The dimensions of  $RC$  are those of time i.e.  $M^0L^0T^1$  and the dimensions of  $\frac{1}{RC}$  are those of frequency i.e.  $M_0L_0T^{-1}$ .
- (v) The potential difference across the condenser plates at any instant of time  $t$  is given by  $V = V_0 e^{-(t/RC)}$  Volt.
- (vi) The transient current at any instant of time is given by  $I = -I_0 e^{-(t/RC)}$  ampere.  
i.e. the current in the circuit decreases exponentially but its direction is opposite to that of charging current.
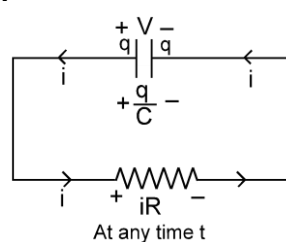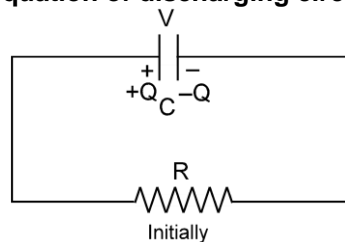
## Derivation of equation of discharging circuit :




Applying K.V.L.
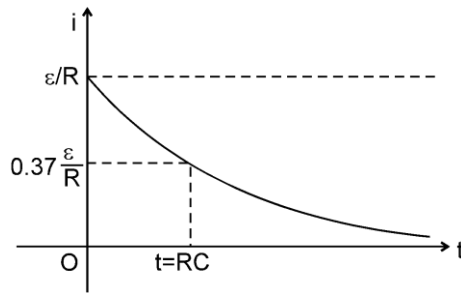
$$+\frac{q}{C} - iR = 0, \quad i = \frac{q}{CR}$$



$$\int_Q^q \frac{-dq}{q} = \int_0^t \frac{dt}{CR} \quad -\ln \frac{q}{Q} = + \frac{t}{RC}$$
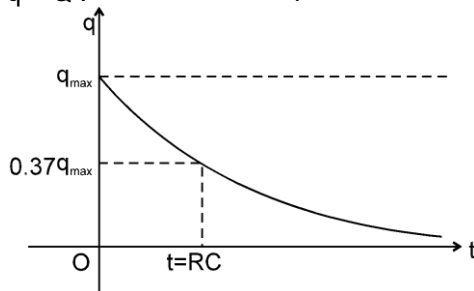
$$q = Q \cdot e^{-t/RC} \Rightarrow i = -\frac{dq}{dt} = \frac{Q}{RC} e^{-t/RC}$$




## Solved Example

**Example 21.** Two parallel conducting plates of a capacitor of capacitance  $C$  containing charges  $Q$  and  $-2Q$  at a distance  $d$  apart. Find out potential difference between the plates of capacitors.

**Solution :** Capacitance =  $C$


$$\text{Electric field} = \frac{3Q}{2A\varepsilon_0}$$
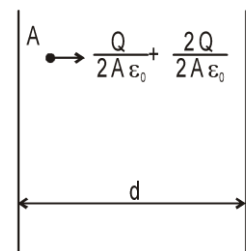
$$V = \frac{3Qd}{2A\varepsilon_0} \Rightarrow V = \frac{3Q}{2C}$$



## 11. CAPACITORS WITH DIELECTRIC


(i) In absence of dielectric

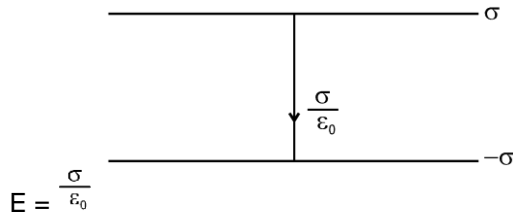



## Capacitance

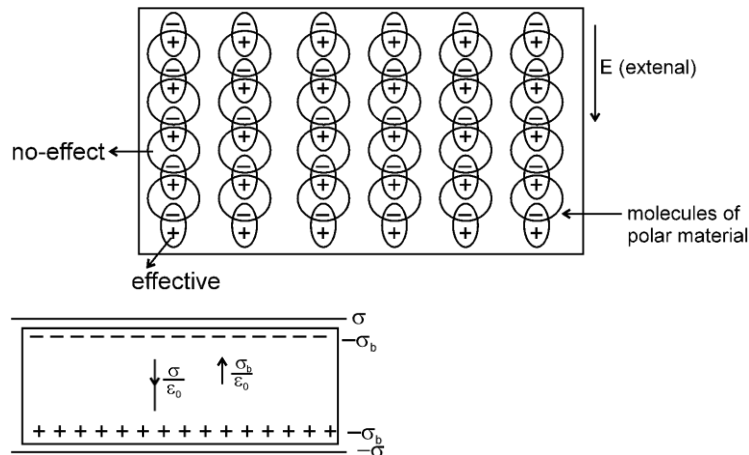- (ii) When a dielectric fills the space between the plates then molecules having dipole moment align themselves in the direction of electric field.




$\sigma_b$  = induced charge density (called bound charge because it is not due to free electrons).

\* For polar molecules dipole moment  $\neq 0$

\* For non-polar molecules dipole moment = 0

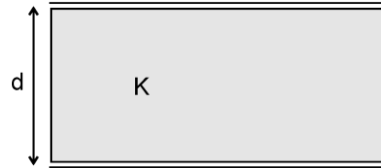- (iii) Capacitance in the presence of dielectric




$$C = \frac{\sigma A}{V} = \frac{\sigma A}{K\epsilon_0 \cdot d} = \frac{AK\epsilon_0}{d} = \frac{AK\epsilon_0}{d}$$

Here capacitance is increased by a factor K.

$$C = \frac{AK\epsilon_0}{d}$$

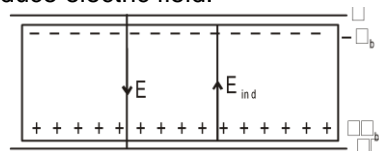- (iv) Polarisation of material :

When nonpolar substance is placed in electric field then dipole moment is induced in the molecule. This induction of dipole moment is called polarisation of material. The induced charge also produce electric field.



$\sigma_b$  = induced (bound) charge density.

$$E_{in} = E - E_{ind} = \frac{\sigma}{\epsilon_0} - \frac{\sigma_b}{\epsilon_0}$$


It is seen the ratio of electric field between the plates in absence of dielectric and in presence of dielectric is constant for a material of dielectric. This ratio is called 'Dielectric constant' of that material. It is represented by  $\epsilon_r$  or k.

$$E_{in} = \frac{\sigma}{K\epsilon_0} \Rightarrow \sigma_b = \sigma \left(1 - \frac{1}{K}\right)$$

- (v) If the medium does not filled between the plates completely then electric field will be as shown in figure


**Case : (1)**

## Capacitance

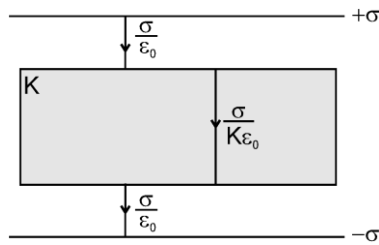


The total electric field produced by bound induced charge on the dielectric outside the slab is zero because they cancel each other.

**Case : (2)**

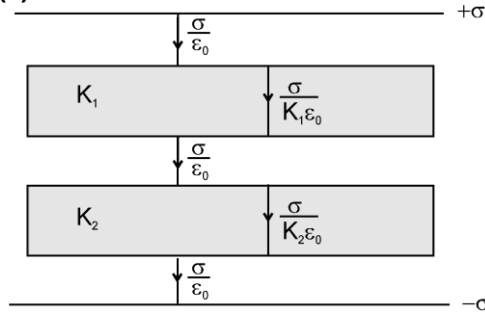

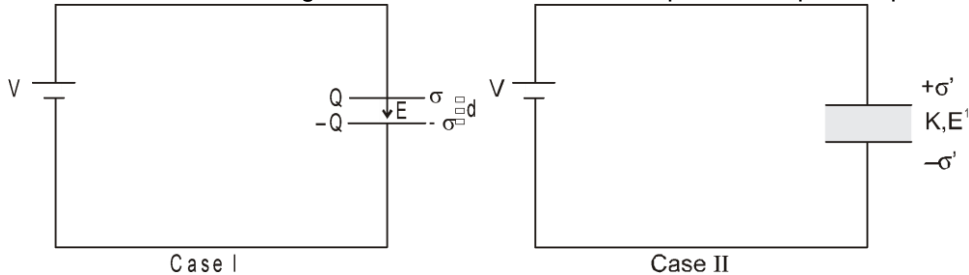(vi) Comparison of  $E$  (electric field),  $\sigma$  (surface charges density),  $Q$  (charge),  $C$  (capacitance) and before and after inserting a dielectric slab between the plates of a parallel plate capacitor.



$$C = \frac{\epsilon_0 A}{d}$$

$$Q = CV$$

$$E = \frac{\sigma}{\epsilon_0} = \frac{CV}{A\epsilon_0}$$

$$= \frac{V}{d}$$

Here potential difference between the plates,

$$Ed = V$$

$$E = \frac{V}{d}$$

$$\frac{V}{d} = \frac{\sigma}{\epsilon_0}$$

$$C' = \frac{A\epsilon_0 K}{d}$$

$$Q' = C'V$$

$$E' = \frac{\sigma'}{K\epsilon_0} = \frac{CV}{A\epsilon_0}$$

$$= \frac{V}{d} \text{ also}$$

Here potential difference between the plates

$$E'd = V$$

$$E' = \frac{V}{d}$$

$$\frac{V}{d} = \frac{\sigma'}{K\epsilon_0}$$

Equating both

$$\frac{\sigma}{\epsilon_0} = \frac{\sigma'}{K\epsilon_0}$$

$$\sigma' = K\sigma$$


In the presence of dielectric, i.e. in case II capacitance of capacitor is more.

(vii) Energy density in a dielectric =  $\frac{1}{2} \epsilon_0 \epsilon_r E^2$

## Solved Examples

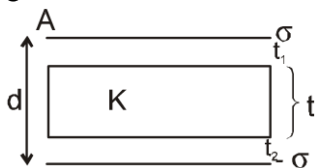**Example 22.** If a dielectric slab of thickness  $t$  and area  $A$  is inserted in between the plates of a parallel plate capacitor of plate area  $A$  and distance between the plates  $d$  ( $d > t$ ) then find out capacitance of system. What do you predict about the dependence of capacitance on location of slab?

**Solution :**  $C = \frac{Q}{V} = \frac{\sigma A}{V}$



$$\Rightarrow V = \frac{\sigma t_1}{\epsilon_0} + \frac{\sigma t}{K\epsilon_0} + \frac{\sigma t_2}{\epsilon_0} \quad (\because t_1 + t_2 = d - t) = \frac{\sigma}{\epsilon_0} \left[ t_1 + t_2 + \frac{t}{K} \right]$$


$$V = \frac{\sigma}{\epsilon_0} \left[ d - t + \frac{t}{K} \right] = \frac{Q}{C} = \frac{\sigma A}{C} \quad \Rightarrow C = \frac{\epsilon_0 A}{d - t + t/K}$$

**Note** (i) Capacitance does not depend upon the position of dielectric (it can be shifted up or down still capacitance does not change).

(ii) If the slab is of metal then :  $C = \frac{A\epsilon_0}{d - t}$

## Solved Examples

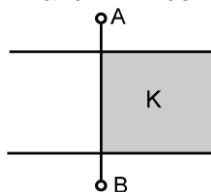**Example 23.** A dielectric of constant  $K$  is slipped between the plates of parallel plate condenser in half of the space as shown in the figure. If the capacity of air condenser is  $C$ , then new capacitance between A and B will be-



- (1)  $\frac{C}{2}$       (2)  $\frac{C}{2K}$       (3)  $\frac{C}{2} [1 + K]$       (4)  $\frac{2[1+K]}{C}$

**Solution :** This system is equivalent to two capacitors in parallel with area of each plate  $\frac{A}{2}$ .

$$C' = C_1 + C_2 = \frac{\epsilon_0 A}{2d} + \frac{\epsilon_0 AK}{2d} = \frac{\epsilon_0 A}{2d} [1 + K] = \frac{C}{2} [1 + K]$$

Hence the correct answer will be (3).

**Example 24.** The parallel plates of a capacitor have an area  $0.2 \text{ m}^2$  and are  $10^{-2} \text{ m}$  apart. The original potential difference between them is  $3000 \text{ V}$ , and it decreases to  $1000 \text{ V}$  when a sheet of dielectric is inserted between the plates filling the full space. Compute: ( $\epsilon_0 = 9 \times 10^{-12} \text{ S. I. units}$ )

- Original capacitance  $C_0$ .
- The charge  $Q$  on each plate.
- Capacitance  $C$  after insertion of the dielectric.
- Dielectric constant  $K$ .
- Permittivity  $\epsilon$  of the dielectric.
- The original field  $E_0$  between the plates.
- The electric field  $E$  after insertion of the dielectric.

**Solution**


$$\begin{aligned} \text{(i)} \quad C_0 &= \frac{\epsilon_0 A}{d} = \frac{0.2 \epsilon_0}{10^{-2}} = 20 \epsilon_0 = 20 \times 9 \times 10^{-12} = 180 \text{ pF} \\ \text{(ii)} \quad Q &= C_0 V = 180 \times 10^{-12} \times 3000 = 5.4 \times 10^{-7} \text{ C} \\ \text{(iii)} \quad C_1 &= \frac{Q}{V_1} = \frac{5.4 \times 10^{-7}}{1000} = 540 \text{ pF} \\ \text{(iv)} \quad K &= \frac{C_1}{C_0} = \frac{540}{180} = 3 \\ \text{(v)} \quad \epsilon &= \epsilon_r \epsilon_0 = K \epsilon_0 \\ \text{(vi)} \quad E_0 &= \frac{V}{d} = \frac{3000}{10^{-2}} = 3 \times 10^5 \text{ V/m} \\ \text{(vii)} \quad E &= \frac{V_1}{d} = \frac{1000}{10^{-2}} = 1 \times 10^5 \text{ V/m.} \end{aligned}$$




## 12. COMBINATION OF PARALLEL PLATES

### Solved Examples

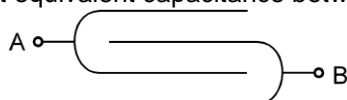**Example 25.** Find out equivalent capacitance between A and B.



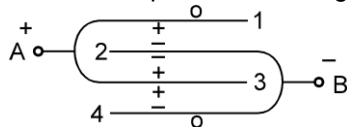**Solution :** Put numbers on the plates. The charges will be as shown in the figure.




$$V_{12} = V_{32} = V_{34}$$


so all the capacitors are in parallel combination.

$$C_{eq} = C_1 + C_2 + C_3$$

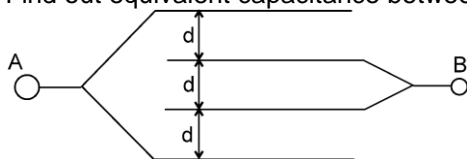**Example 26.** Find out equivalent capacitance between A and B.



**Solution :**

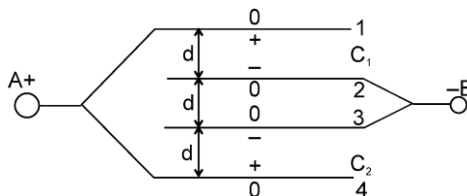


These are only two capacitors.  $C_{eq} = C_1 + C_2$



## 13. OTHER TYPES OF CAPACITORS

**Spherical capacitor :**


## Capacitance

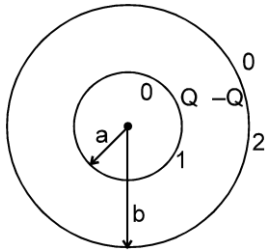

This arrangement is known as spherical capacitor.

$$V_1 - V_2 = \left[ \frac{KQ}{a} - \frac{KQ}{b} \right] - \left[ \frac{KQ}{b} - \frac{KQ}{b} \right] = \frac{KQ}{a} - \frac{KQ}{b}$$
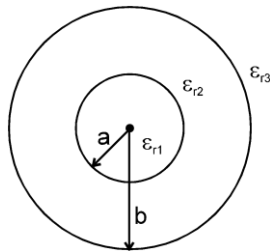
$$C = \frac{Q}{V_1 - V_2} = \frac{Q}{\frac{KQ}{a} - \frac{KQ}{b}} = \frac{ac}{K(b-a)} = \frac{4\pi\epsilon_0 ab}{b-a}$$



$$\frac{4\pi\epsilon_0 ab}{b-a}$$

$$C = \frac{4\pi\epsilon_0 ab}{b-a}$$


If  $b \gg a$

$$C = 4\pi\epsilon_0 a$$

$$\frac{4\pi\epsilon_0 \epsilon_{r2} ab}{b-a}$$

$$C = \frac{4\pi\epsilon_0 \epsilon_{r2} ab}{b-a}$$

**Cylindrical capacitor**

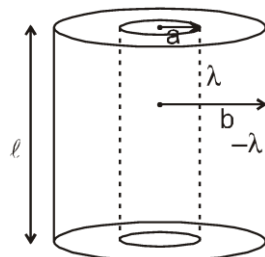

There are two co-axial conducting cylindrical surfaces where  $l \gg a$  and  $l \gg b$

where  $a$  and  $b$  is radius of cylinders.

Capacitance per unit length

$$C = \frac{\lambda}{V} = \frac{\lambda}{\frac{2K\lambda \ln \frac{b}{a}}{l}} = \frac{4\pi\epsilon_0}{2\ln \frac{b}{a}} = \frac{2\pi\epsilon_0}{\ln \frac{b}{a}}$$

$$\text{Capacitance per unit length} = \frac{2\pi\epsilon_0}{\ln \frac{b}{a}} \text{ F/m}$$


## Miscellaneous Solved Example

**Problem 1.** Find out the capacitance of the earth ? (Radius of the earth = 6400 km)

## Capacitance

**Solution :**  $C = 4\pi\epsilon_0 R = \frac{6400 \times 10^3}{9 \times 10^9} = 711 \mu\text{F}$

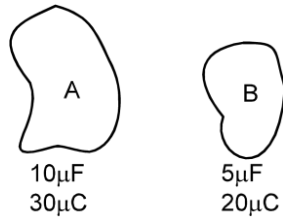**Problem 2.** When two isolated conductors A and B are connected by a conducting wire positive charge will flow from.




**Solution :** (1) A to B (2) B to A (3) will not flow (4) can not say.  
Charge always flows from higher potential body to lower potential body

Hence,  $V_A = \frac{30}{10} = 3\text{V} \Rightarrow V_B = \frac{20}{5} = 4\text{V}$ . As  $V_B > V_A \therefore$  (2) is correct Answer.

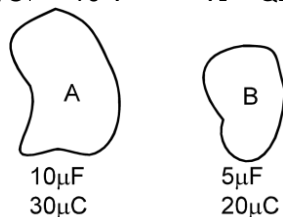**Problem 3.** A conductor of capacitance  $10\mu\text{F}$  connected to other conductor of capacitance  $40\mu\text{F}$  having equal charges  $100\mu\text{C}$  initially. Find out final voltage and heat loss during the process?

**Answer :** (i)  $V = 4\text{V}$  (ii)  $H = 225\mu\text{J}$ .

**Solution :**  $C_1 = 10\mu\text{F}$   $C_2 = 40\mu\text{F}$   
 $Q_1 = 100\mu\text{C}$   $Q_2 = 100\mu\text{C}$   
 $V_1 = Q_1/C_1 = 10\text{V}$   $V_2 = Q_2/C_2 = 2.5\text{V}$




Final voltage (V) =  $\frac{C_1 V_1 + C_2 V_2}{C_1 + C_2} = \frac{Q_1 + Q_2}{C_1 + C_2} = \frac{200\mu}{50\mu} = 4\text{V}$

Heat loss during the process =  $\frac{1}{2} [C_1 V_1^2 + C_2 V_2^2] - \frac{1}{2} V^2 (C_1 + C_2)$

=  $\frac{1}{2} [Q_1 V_1 + Q_2 V_2] - \frac{1}{2} V^2 (C_1 + C_2)$

=  $\frac{1}{2} \times 100\mu [12.5] - \frac{1}{2} \times 16 (50) \mu = 225\mu\text{J}$

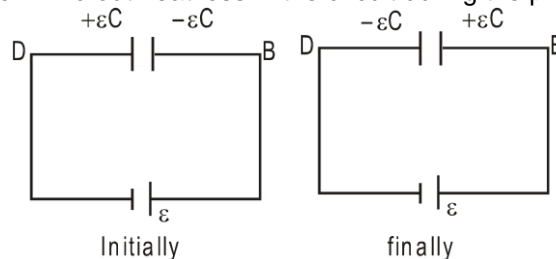**Problem 4.** In the above question, if the positive terminal of the battery is connected with negative plate of capacitor. Find out heat loss in the circuit during the process of charging.




Net charge flow through battery =  $2\epsilon C$   
Work done by battery =  $\epsilon \times 2\epsilon C = 2\epsilon^2 C$   
Heat produced =  $2\epsilon^2 C$ . **Ans.**

**Solution :** From figure  
Net charge flow through battery =  $Q_{\text{final}} - Q_{\text{initial}} = \epsilon C - (-\epsilon C) = 2\epsilon C$


## Capacitance

$\therefore$  work done by battery ( $W$ ) =  $Q \times V = 2\epsilon C \times \epsilon = 2\epsilon_2 C$   
or Heat produced =  $2\epsilon_2 C$

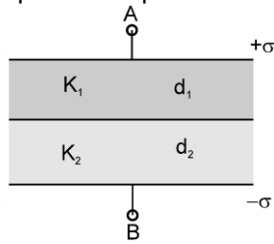**Problem 5.** Find out capacitance between A and B if two dielectric slabs of dielectric constant  $K_1$  and  $K_2$  of thickness  $d_1$  and  $d_2$  and each of area  $A$  are inserted between the plates of parallel plate capacitor of plate area  $A$  as shown in figure.




**Solution :**  $C = \frac{\sigma A}{V}$  ;  $V = E_1 d_1 + E_2 d_2 = \frac{\sigma d_1}{K_1 \epsilon_0} + \frac{\sigma d_2}{K_2 \epsilon_0} = \frac{\sigma}{\epsilon_0} \left( \frac{d_1}{K_1} + \frac{d_2}{K_2} \right)$   
 $\therefore C = \frac{\frac{\sigma A}{\frac{d_1}{K_1} + \frac{d_2}{K_2}}}{\frac{\sigma}{\epsilon_0} \left( \frac{d_1}{K_1} + \frac{d_2}{K_2} \right)} \Rightarrow \frac{1}{C} = \frac{d_1}{AK_1 \epsilon_0} + \frac{d_2}{AK_2 \epsilon_0}$

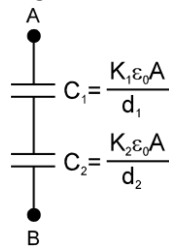


This formula suggests that the system between A and B can be considered as series combination of two capacitors.

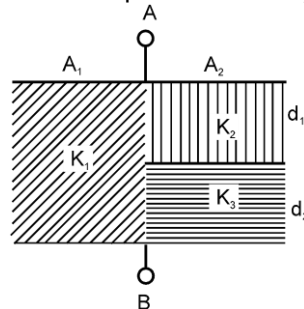**Problem 6.** Find out capacitance between A and B if three dielectric slabs of dielectric constant  $K_1$  of area  $A_1$  and thickness  $d$ ,  $K_2$  of area  $A_2$  and thickness  $d_1$  and  $K_3$  of area  $A_2$  and thickness  $d_2$  are inserted between the plates of parallel plate capacitor of plate area  $A$  as shown in figure. (Given distance between the two plates  $d = d_1 + d_2$ )



**Solution :** It is equivalent to

$$C = C_1 + \frac{C_2 C_3}{C_2 + C_3}$$

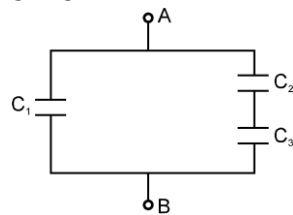


## Capacitance

$$C = \frac{A_1 K_1 \epsilon_0}{d_1 + d_2} + \frac{\frac{A_2 K_2 \epsilon_0}{d_1} \cdot \frac{A_2 K_3 \epsilon_0}{d_2}}{\frac{A_2 K_2 \epsilon_0}{d_1} + \frac{A_2 K_3 \epsilon_0}{d_2}}$$

$$= \frac{A_1 K_1 \epsilon_0}{d_1 + d_2} + \frac{A_2^2 K_2 K_3 \epsilon_0^2}{A_2 K_2 \epsilon_0 d_2 + A_2 K_3 \epsilon_0 d_1} = \frac{A_1 K_1 \epsilon_0}{d_1 + d_2} + \frac{A_2 K_2 K_3 \epsilon_0}{K_2 d_2 + K_3 d_1}$$

**Problem 7.** Find out capacitance between A and B if two dielectric slabs of dielectric constant  $K_1$  and  $K_2$  of area  $A_1$  and  $A_2$  and each of thickness  $d$  are inserted between the plates of parallel plate capacitor of plate area  $A$  as shown in figure.

**Solution :**

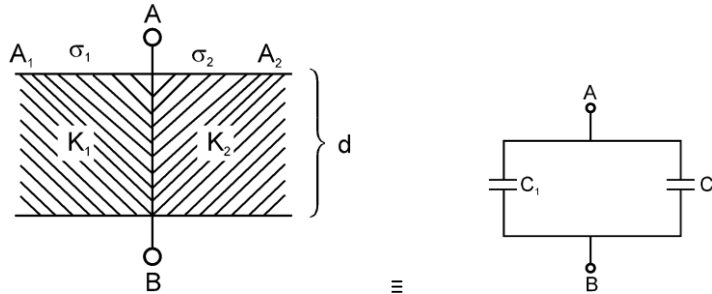


$$C_1 = \frac{A_1 K_1 \epsilon_0}{d}, C_2 = \frac{A_2 K_2 \epsilon_0}{d}$$

$$E_1 = \frac{V}{d} = \frac{\sigma_1}{K_1 \epsilon_0}, E_2 = \frac{V}{d} = \frac{\sigma_2}{K_2 \epsilon_0}$$


$$\sigma_1 = \frac{K_1 \epsilon_0 V}{d}, \sigma_2 = \frac{K_2 \epsilon_0 V}{d}$$
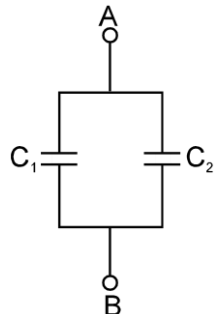
$$C = \frac{Q_1 + Q_2}{V} = \frac{\sigma_1 A_1 + \sigma_2 A_2}{V} = \frac{K_1 \epsilon_0 A_1}{d} + \frac{K_2 \epsilon_0 A_2}{d}$$



The combination is equivalent to :  
 $\therefore C = C_1 + C_2$

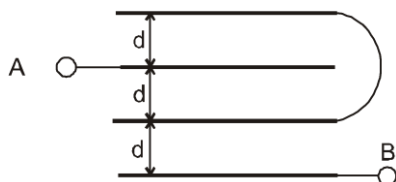
**Problem 8.** Find out equivalent capacitance between A and B.






## Capacitance

**Solution :**

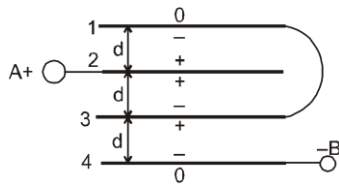


The modified circuit is

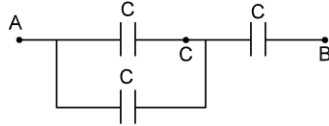

$$C_{eq} = \frac{2C}{3}$$

**Other method :**

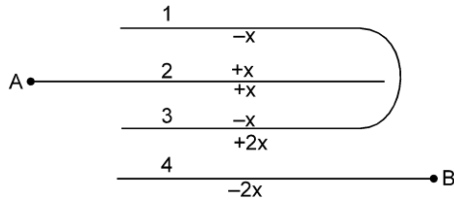

$$C_{eq} = \frac{Q}{V} = \frac{2xA}{V}$$

$$V = V_2 - V_4 = (V_2 - V_3) + (V_3 - V_4)$$



$$= \frac{xd}{\epsilon_0} + \frac{2xd}{\epsilon_0} = \frac{3xd}{\epsilon_0}$$

$$\therefore C_{eq} = \frac{2Ax\epsilon_0}{3xd} = \frac{2A\epsilon_0}{3d} = \frac{2C}{3}$$

**Problem 9.** Find out equivalent capacitance between A and B.

$$C = \frac{A\epsilon_0}{d}$$

**Solution :**

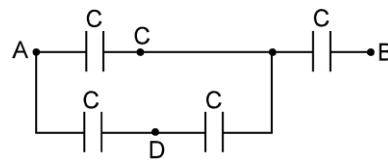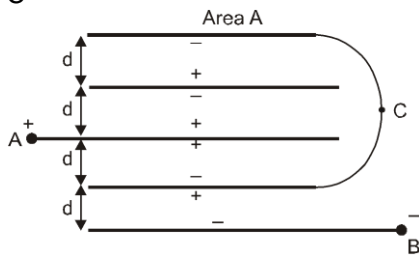


$$\frac{1}{C_{eq}} = \frac{1}{C} + \frac{2}{3C} = \frac{5}{3C}$$

$$C_{eq} = \frac{3C}{5} = \frac{3A\epsilon_0}{5d}$$

**Alternative Method :**

## Capacitance

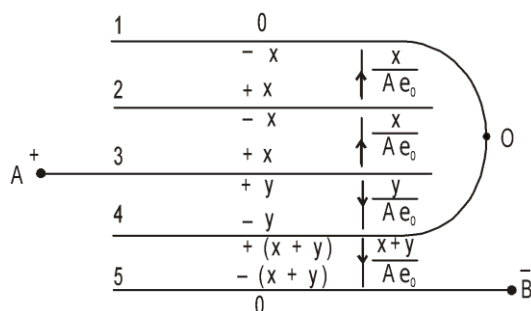

$$C = \frac{Q}{V} = \frac{x+y}{V_{AB}}$$

$$C = \frac{Q}{V} = \frac{x+y}{V_{AB}}$$

Potential of 1 and 4 is same


$$\frac{y}{A\epsilon_0} = \frac{2x}{A\epsilon_0}$$

$$y = 2x$$

$$V = \left( \frac{2y+x}{A\epsilon_0} \right) d$$

$$C = \frac{(x+2x)A\epsilon_0}{(5x)d} = \frac{3A\epsilon_0}{5d}$$

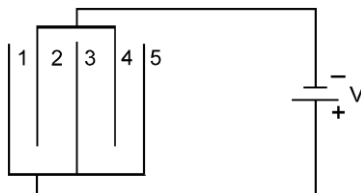**Problem 10.** Five similar condenser plates, each of area  $A$ , are placed at equal distance  $d$  apart and are connected to a source of e.m.f.  $E$  as shown in the following diagram. The charge on the plates 1 and 4 will be-



$$(1) \frac{\epsilon_0 A}{d}, \frac{-2\epsilon_0 A}{d}$$

$$(2) \frac{\epsilon_0 AV}{d}, \frac{-2\epsilon_0 AV}{d}$$


$$(3) \frac{-\epsilon_0 AV}{d}, \frac{-3\epsilon_0 AV}{d}$$

$$(4) \frac{\epsilon_0 AV}{d}, \frac{-4\epsilon_0 AV}{d}$$

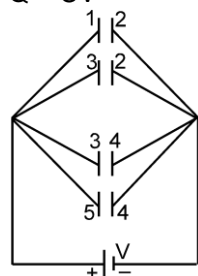**Solution :**

Equivalent circuit diagram Charge on first plate

$$Q = CV \Rightarrow Q = \frac{\epsilon_0 AV}{d}$$



Charge on fourth plate

$$Q' = C(-V) \quad Q' = \frac{-\epsilon_0 AV}{d}$$


As plate 4 is repeated twice, hence charge on 4 will be  $Q'' = 2Q'$

$$Q'' = -\frac{2\epsilon_0 AV}{d}$$

Hence the correct answer will be (2).

## KEY CONCEPT

## Capacitance

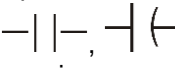- (i)  $q \propto V \Rightarrow q = CV$   
 $q$  : Charge on positive plate of the capacitor  
 $C$  : Capacitance of capacitor.  
 $V$  : Potential difference between positive and negative plates.
- (ii) Representation of capacitor : 
- (iii) It is a scalar quantity having dimensions  
 $[C] = [M^{-1} L^{-2} T^4 A^2]$
- (iv) S.I. Unit is Farad. (F).
- (v) Energy stored in the capacitor :  $U = \frac{1}{2} CV^2 = \frac{Q^2}{2C} = \frac{QV}{2}$
- (vi) Energy density =  $\frac{1}{2} \epsilon_0 \epsilon_r E^2 = \frac{1}{2} \epsilon_0 K E^2$   
 $K = \epsilon_r$  = Relative permittivity of the medium (Dielectric Constant)
- For vacuum, energy density =  $\frac{1}{2} \epsilon_0 E^2$
- (vii) Types of Capacitors :

**(a) Parallel plate capacitor**

$$C = \frac{\epsilon_0 \epsilon_r A}{d} = K \frac{\epsilon_0 A}{d}$$

$A$  : Area of plates  
 $d$  : distance between the plates (  $\ll$  size of plate )

**(b) Spherical Capacitor :**


- Capacitance of an isolated spherical Conductor (hollow or solid )

$$C = 4\pi \epsilon_0 \epsilon_r R$$


$R$  = Radius of the spherical conductor

- Capacitance of spherical capacitor


$$C = 4\pi \epsilon_0 \frac{ab}{(b-a)}$$

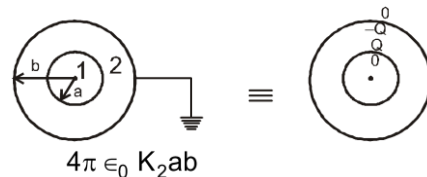
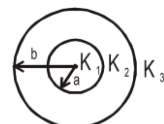
$$C = \frac{4\pi \epsilon_0 K_2 ab}{(b-a)}$$



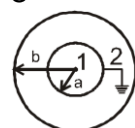
$$C = \frac{4\pi \epsilon_0 b^2}{(b-a)}$$



**(c) Cylindrical Capacitor :  $\ell \gg \{a, b\}$**

$$\text{Capacitance per unit length} = \frac{2\pi \epsilon_0}{\ln(b/a)} \text{ F/m}$$

## Capacitance

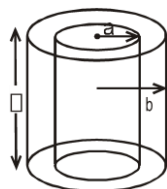

- (viii) Capacitance of capacitor depends on
- Area of plates
  - Distance between the plates
  - Dielectric medium between the plates.


- (ix) Electric field intensity between the plates of capacitor  $E = \frac{\sigma}{\epsilon_0} = \frac{V}{d}$   
 $\sigma$  : Surface charge density

- (x) Force experienced by any plate of capacitor :  $F = \frac{q^2}{2A \epsilon_0}$


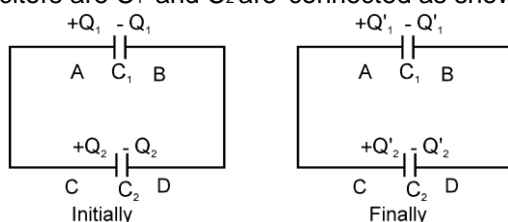
### Distribution of Charges on Connecting two Charged Capacitors:

When two capacitors are  $C_1$  and  $C_2$  are connected as shown in figure



- (a) Common potential :  $V = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2} = \frac{\text{Total charge}}{\text{Total capacitance}}$
- (b)  $Q_1' = C_1 V = \frac{C_1}{C_1 + C_2} (Q_1 + Q_2) \Rightarrow Q_2' = C_2 V = \frac{C_2}{C_1 + C_2} (Q_1 + Q_2)$
- (c) Heat loss during redistribution :

$$\Delta H = U_i - U_f = \frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} (V_1 - V_2)^2$$

The loss of energy is in the form of Joule heating in the wire.


- Note :**
- When plates of similar charges are connected with each other (+ with + and – with –) then put all values ( $Q_1$ ,  $Q_2$ ,  $V_1$ ,  $V_2$ ) with positive sign.
  - When plates of opposite polarity are connected with each other (+ with –) then take charge and potential of one of the plate to be negative.



### Combination of capacitor :

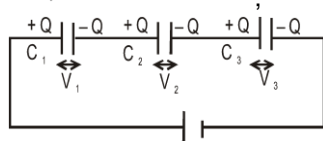
- (i) Series Combination

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}, \quad V_1 : V_2 : V_3 = \frac{1}{C_1} : \frac{1}{C_2} : \frac{1}{C_3}$$



- (ii) Parallel Combination :

## Capacitance

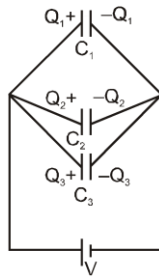


$$C_{eq} = C_1 + C_2 + C_3 + \dots$$

$$Q_1 : Q_2 : Q_3 = C_1 : C_2 : C_3$$

### Charging and Discharging of a capacitor :

(i) Charging of Capacitor ( Capacitor initially uncharged ):

$$q = q_0 ( 1 - e^{-t/\tau} )$$

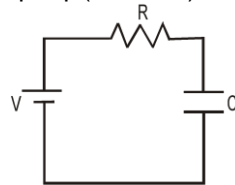


$q_0$  = Charge on the capacitor at steady

State  $\Rightarrow q_0 = CV$

$\tau$  : Time constant =  $CR_{eq}$ .
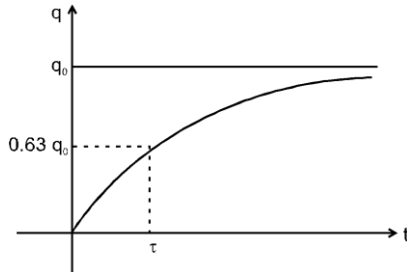
$$i = \frac{q_0}{\tau} e^{-t/\tau} = \frac{V}{R} e^{-t/\tau}$$





□ 63% of maximum charge is deposited in one time constant.

(ii) Discharging of Capacitor :

$$q = q_0 e^{-t/\tau}$$

$q_0$  = Initial charge on the capacitor

$$i = \frac{q_0}{\tau} e^{-t/\tau}$$

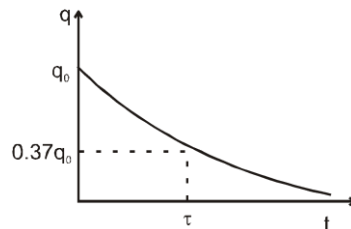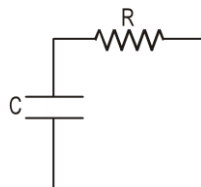

□ 63% of discharging is complete in one time constant.

### Capacitor with dielectric :

(i) Capacitance in the presence of dielectric :

## Capacitance

$$C = \frac{K \epsilon_0 A}{d} = KC_0$$

$C_0$  = Capacitance in the absence of dielectric.

- (ii) If thickness of dielectric slab is  $t$ , then its capacitance

$$C = \frac{\epsilon_0 A}{(d - t + t/k)}, \text{ where } k \text{ is the dielectric constant of slab.}$$

- ☐ It does not depend on the position of the slab.
- ☐  $k = 1$  for vacuum or air.
- ☐  $k = \infty$  for metals.

$$(iii) \quad E_{in} = E - E_{ind} = \frac{\sigma}{\epsilon_0} - \frac{\sigma_b}{\epsilon_0} = \frac{\sigma}{K \epsilon_0} = \frac{V}{d}$$

$$E = \frac{\sigma}{\epsilon_0} \quad \text{Electric field in the absence of dielectric}$$

$E_{ind}$  : Induced electric field

$$(iv) \quad \sigma_b = \sigma \left(1 - \frac{1}{K}\right). \text{ (induced charge density)}$$