<b>♦</b>				
	<b>Exercise</b> -	1		
	PAR	RT-I : ONLY ONE (	OPTION CORRECT	ТҮРЕ
SEC				
1.	The radii of two metallic spheres are shorted the (1) 25 μC from smaller t (3) 50 μC from smaller t	c spheres are 5 cm and n charge will be trans o bigger o bigger	nd 10 cm and both carry ferred– (2) 25 μC from bigge (4) 50 μC from bigge	y equal charge of $75\mu$ C. If the two er to smaller er to smaller
2.	Two isolated charged n connected to each other (1) No change in the ele (2) An increase in the el (3) Always a decrease in (4) A decrease in electri	netallic spheres of ra r, then there is: ectrical energy of the s ectrical energy of the n the electrical energy cal energy of the syst	dii R1 and R2 having ch system v of the system em until Q1 R2 = Q2 R1	arges $Q_1$ and $Q_2$ respectively are
3.	A parallel plate capacito capacitor are now move (1) The charge on the ca (2) The electrostatics en (3) The voltage between (4) The capacitance incl	or is charged and the d, farther apart. The f apacitor increases hergy stored in the cap the plates decreases reases.	e charging battery is the ollowing things happen : pacitor increases	n disconnected. The plates of the
4.	A parallel plate capacito Charge (1) remains constan (2) remains constan (3) remains constan (4) increases	r is charged and then <b>Potential</b> nt remains cons nt increases nt decreases increases	isolated. On increasing Capacitance stant decreases decreases increases decreases	the plate separation– <b>e</b>
5.	The value of one farad i	n e.s.u. is-	1	1
6.	(1) 3 × 10 <sub>10</sub> A parallel plate air capa distance between the p	(2) 9 × 1011 acitor is charged to a lates of the capacitor yeen the plates-	(3) $\frac{1}{9} \times 10_{-11}$ potential difference V. A r is increased using an	(4) $\frac{1}{3} \times 10_{-10}$ After disconnecting the battery the insulating handle. As a result the
	(1) Increases	(2) Decreases	(3) Does not change	(4) Becomes zero
7.	The capacitance of a pa between the plates is re	rallel plate capacitor is duced to 4 cm, its cap	$510 \mu\text{F}$ when distance be bacitance will be-	etween its plates is 8 cm. If distance
	(1) 5 μF	(2) 10 μF	(3) 20 µF	(4) 40 μ <del>Γ</del>
8.	Capacitance in farad of (1) 1.1 × 10 <sub>-10</sub>	a spherical conductor (2) 10 <sub>-6</sub>	with radius 1 metre is- (3) 9 × 10 <sub>-9</sub>	(4) 10–3
9.	The capacitance of spheric C = $\frac{1}{1 - \Sigma}$	erical conductor is give	en by-	
	(1) <sup>4πε</sup> <sub>0</sub> R	(2) C = 4πε <sub>0</sub> R	(3) C = 4πε <sub>0</sub> R <sub>2</sub>	(4) C = rπε <sub>0</sub> R <sub>3</sub>
10.	Eight drops of mercury of The capacitance of this	of equal radii and eacl big drop as compared	h possessing the same o I to that of each smaller of	charge combine to form a big drop. drop is-

(1) 2 times (2) 4 times (3) 8 times (4) 16 times

٠

Capacitance

11.	Capacity of a condu (1) Size of conducto (3) Material of condu	ctor depends upon- r uctor	ıpon- (2) Thickness of conductor (4) All of these			
12.	Metallic sphere of ra	adius R is charged t (2) R	o potential V. Then charge (3) Both	e q is proportional to- (4) None		
	(·) ·	(_)				

**13.** A conducting sphere of radius 10 cm is charged with 10  $\mu$ C. Another uncharged sphere of radius 20 cm is allowed to touch it for some time. After that if the sphere are separated, then surface density of charged on the spheres will be in the ratio of : (1) 1 : 4 (2) 1 : 3 (3) 2 : 1 (4) 1 : 1

- **14.**Capacitance (in F) of a spherical conductor having radius 1m, is :<br/>(1)  $1.1 \times 10_{-10}$ (2)  $10_{-6}$ (3)  $9 \times 10_{-9}$ (4)  $10_{-3}$
- **15.** The capacitance of a parallel plate capacitor is  $12\mu$ F. If the distance between its plates is reduced to half and the area of plates is doubled, then the capacitance of the capacitor will become (1)  $24\mu$ F (2)  $12\mu$ F (3)  $16\mu$ F (4)  $48\mu$ F
- 16. The radius of the circular plates of a parallel plate capacitor is R. Air is dielectric medium between the plates. If the capacitance of the capacitor is equal to the capacitance of a sphere of radius R, then the distance between the plates is

  (1) R/4
  (2) R/2
  (3) R
  (4) 2R

# SECTION (B) : CIRCUITS WITH CAPACITOR AND USE OF KCL AND KVL

1. The work done against electric forces in increasing the potential difference of a condenser from 20V to 40V is W. The work done in increasing its potential difference from 40V to 50V will be

(1) 4W (2) 
$$\frac{3\sqrt{2}}{4}$$
 (3) 2W (4)  $\frac{\sqrt{2}}{2}$ 

2. The magnitude of charge in steady state on either of the plates of condenser C in the adjoining circuit is-



**3.** The plate separation in a parallel plate condenser is d and plate area is A. If it is charged to V volt & battery is disconnected then the work done in increasing the plate separation to 2d will be–

(1) 
$$\frac{3}{2} \frac{\varepsilon_0 AV^2}{d}$$
 (2)  $\frac{\varepsilon_0 AV^2}{d}$  (3)  $\frac{2\varepsilon_0 AV^2}{d}$  (4)  $\frac{\varepsilon_0 AV^2}{2d}$ 

**4.** A capacitor of capacitance C<sub>1</sub> is charged to potential V and battery is disconnected. Now the capacitor is connected to a uncharged capacitor of capacitance C<sub>2</sub> then what will be common potential of the combination

(1) 
$$\frac{C_1V}{C_1+C_2}$$
 (2)  $\frac{C_2V}{C_1+C_2}$  (3)  $\frac{(C_1+C_2)V}{C_1+C_2}$  (4)  $\frac{C_2}{C_1+C_2}$ 

- 5. If the charge on a body is increased by  $2\mu$ C, the energy stored in it increases by 21%. The original charge on the body in micro-coulombs is (1) 10 (2) 20 (3) 30 (4) 40
- 6. What fraction of the energy drawn from the charging battery is stored in a capacitor (1) 100% (2) 75% (3) 50% (4) 25%

(2)  $d^2$ 

7. The plates of a parallel plate condenser are pulled apart with a velocity v. If at any instant mutual distance of separation is d, then the magnitude of the time of rate of change of electrostatic energy of the capacity depends on d as follows(potential difference between plates is kept constant)1

$$(1) \frac{1}{d}$$

- (3) d<sub>2</sub> (4) d
- 8. 125 water drops of equal radius and equal capacitance C, coalesce to form a single drop of capacitance C'. The relation between C and C' is-

(1) 
$$C' = 125 C$$
 (2)  $C' = C$  (3)  $C' = \frac{C}{125}$  (4)  $C' = 5C$ 

**9.** Energy per unit volume for a capacitor having area A and separation d kept at potential difference V is given by-

(1) 
$$\frac{1}{2} \varepsilon_0 \frac{V^2}{d^2}$$
 (2)  $\frac{1}{2\varepsilon_0} \frac{V^2}{d^2}$  (3)  $\frac{1}{2} CV^2$  (4)  $\frac{Q^2}{2C}$ 

**10.** The mean electric energy density between plates of a charged capacitor is- (here q = charge on the capacitor and A = area of the capacitor plate)

(1) 
$$\frac{q^2}{2\varepsilon_0 A^2}$$
 (2)  $\frac{q}{2\varepsilon_0 A^2}$  (3)  $\frac{q^2}{2\varepsilon_0 A}$  (4) None of above

- **11.** A capacitor when charged by a potential difference of 200 volt, stores a charge of 0.1 C. By discharging, energy liberated by the capacitor is-(1) -30 J (2) -15 J (3) 10 J (4) 20 J
- 12.Work done in placing a charge of  $8 \times 10_{-18}$  C on a condenser of capacity 100 microfarad is-<br/>(1)  $16 \times 10_{-32}$  J(2)  $3.1 \times 10_{-26}$  J(3)  $4 \times 10_{-10}$  J(4)  $32 \times 10_{-32}$  J
- **13.** The work done in doubling the separation between plates of a parallel plate capacitor of capacity C and having charge Q is-

$$\begin{array}{cccc} & & & & & \\ (1) & & & & \\ \hline C & & & & \\ (2) & & & \\ \hline C & & & & \\ (2) & & & \\ \hline \end{array} \begin{array}{c} & & & & & \\ Q^2 & & & & \\ \hline & & & & \\ (3) & & & \\ \hline \end{array} \begin{array}{c} & & & & \\ Q^2 & & & \\ \hline & & & \\ (4) & & \\ \hline \end{array} \begin{array}{c} & & & \\ Q^2 & & \\ \hline & & \\ (4) & & \\ \hline \end{array} \end{array}$$

14. In the adjoining diagram, (assuming the battery to be ideal) the condenser C will be charged to potential V if-



15.A capacitor 4mF charged to 50 V is connected to another capacitor of 2mF charged to 100V with plates<br/>of like charges connected together. The total energy before and after connection in multiples [10 J] is-(1)<br/>1.5 and 1.33(2) 1.33 and 1.5(3) 3.0 and 2.67(4) 2.67 and 3.0

16. A condenser of capacitance 10mF has been charged to 100 volts. It is now connected to another uncharged condenser in parallel. The common potential becomes 40 volts. The capacitance of another condenser is-

(1) 15 mF (2) 5 mF (3) 10 mF (4) 16.6 mF

17. Two capacitors of capacitances 3µF and 6µF are charged to a potential of 12V each. They are now connected to each other, with the positive plate of each joined to the negative plate of the other. The potential difference across each will be (1) 6V (2) 4V (3) 3V (4) Zero

3uF

18. In the following figure, the charge on each condenser in the steady state will be-



- Two parallel plate condensers of capacity of 20µF and 30µF are charged to the potentials of 30V and 19. 20V respectively. If likely charged plates are connected together then the common potential difference will be-
  - (1) 100 V (2) 50 V (3) 24 V (4) 10 V
- 20. The work done in placing a charge of  $8 \times 10_{-18}$  coulomb on a condenser of capacity 100 micro-farad is : (3)  $4 \times 10_{-10}$  joule (1) 16 × 10-32 joule (2) 3.1 × 10<sub>-26</sub> joule (4) 32 × 10<sub>-32</sub> joule

21. A capacitor is charged by connecting a battery across its plates. It stores energy U. Now the battery is disconnected and another identical capacitor is connected across it, then the energy stored by both capacitors of the system will be :

- $(4) \frac{3}{2} U$ (2) 2 (1) U (3) 2U
- 22. In a parallel plate capacitor, the distance between the plates is d and potential difference across plates is V. Energy stored per unit volume between the plates of capacitor is :

(1) 
$$\frac{Q^2}{2V^2}$$
 (2)  $\frac{1}{2}\varepsilon_0 \frac{V^2}{d^2}$  (3)  $\frac{\varepsilon_0^2 V^2}{d^2}$  (4)  $\frac{1}{2}\frac{\varepsilon_0^2 V^2}{d^2}$ 

23. A capacitor of capacity C1 is charged upto potential V volt and then connected in parallel to an uncharged capacitor of capacity C2. The final potential difference across each capacitor will be :

$$\begin{array}{ccc} \frac{C_2 V}{C_1 + C_2} & & \frac{C_1 V}{C_1 + C_2} & & \\ (1) & & & \\ \end{array} \end{array}$$

- 24. A parallel plate air capacitor is charged to a potential difference of V volts. After disconnecting the charging battery the distance between the plates of the capacitor is increased using an insulating handle. As a result the potential difference between the plates :
  - (1) decreases (2) does not change (3) becomes zero (4) increases

Two condensers, one of capacity C and the other of capacity 2, are connected to a V volt battery, as 25. shown.

С

1 (4) 2n CV<sub>2</sub>



The work doen in charging fully both the condensers is

(1) 
$$2CV_2$$
 (2)  $\frac{1}{4}CV_2$  (3)  $\frac{3}{2}CV_2$  (4)  $\frac{1}{2}CV_2$ 

26. The energy required to charge a parallel plate condenser of plate separation d and plate area of crosssection A such that the uniform electric field between the plates is E, is 1 1

(1) 
$$\frac{1}{2} \varepsilon_0 E_2/Ad$$
 (2)  $\varepsilon_0 E_2/Ad$  (3)  $\varepsilon_0 E_2Ad$  (4)  $\frac{1}{2} \varepsilon_0 E_2Ad$ 

- 27. A 40 µF capacitor in a defibrillator is charged to 3000 V. The energy stored in the capacitor is sent through the patient during a pulse of duration 2 ms. The power delivered to the patient is (2) 90 kW (3) 180 kW (4) 360 kW (1) 45 kW
- If there are n capacitors of capacitance C in parallel connected to V volt source, then the energy stored 28. is equal to :

(1) CV (2) 
$$\frac{1}{2}$$
 nCV<sub>2</sub> (3) CV<sub>2</sub>

- 29. A battery is used to charge a parallel plate capacitor till the potential difference between the plates becomes equal to the electromotive force of the battery. The ratio of the energy stored in the capacitor and the work done by the battery will be (3) 1/4(4) 1/2(1) 1(2) 2
- A parallel plate capacitor with air between the plates has a capacitance of 9 pF. The separation between 30. its plates is 'd'. The space between the plates is now filled with two dielectrics. One of the dielectrics has dielectric constant  $k_1 = 3$  and thickness d/3 while the other one has dielectric constant  $k_2 = 6$  and thickness 2d/3. Capacitance of the capacitor is now : (4) 1.8 pF (1) 45 pF (2) 40.5 pF (3) 20.25 pF
- 31. If the energy of a capacitor of capacitance 2µF is 0.16 joule, then its potential difference will be (1) 800 V (2) 400 V (3) 16 × 10<sub>4</sub> V (4) 16 × 10<sub>-4</sub> V
- 32. A capacitor of 6µF is charged to such an extent that the potential difference between the plates becomes 50 V. The work done in this process will be (3) 3 × 10<sub>-6</sub> J (4) 3 × 10<sub>-3</sub> J (1) 7.5 × 10<sub>-2</sub> J (2) 7.5 × 10<sub>-3</sub> J
- 33. Two identical capacitors have the same capacitance C. One of them is charged to potential V<sub>1</sub> and the other to V<sub>2</sub>. The negative ends of the capacitors are connected together. When the positive ends are also connected, the decrease in energy of the combined system is:

$$(1) \frac{1}{4} C (V_{12} - V_{22}) \qquad (2) \frac{1}{4} C (V_{12} + V_{22}) \qquad (3) \frac{1}{4} C (V_1 - V_2)_2 \qquad (4) \frac{1}{4} C (V_1 + V_2)_2$$

- 34. A capacitor is connected to a cell of emf E having some internal resistance r. The potential difference across the : (1) cell is < E(2) cell is E (3) capacitor is > E (4) capacitor is < E
- 35. A 10 µF capacitor is charged to a 1000 volt potential, then it is removed from power supplied and connected to a 6 uF uncharged capacitor. Find potential difference across each capacitor. (2) 100 V (1) 167 V (3) 625 V (4) 250 V

(1) C

(1) 3µF

**36.** The uniform electric field in the space between the plates of a parallel plate condenser of plate separation d and plate areas A is E. The energy of this charged condencer is :

$$(1) \frac{1}{2} \cdot \frac{\epsilon_0 E^2}{A.d} \qquad (2) \epsilon_0 E_2 A d \qquad (3) \frac{1}{2} \epsilon_0 E^2 A d \qquad (4) \frac{1}{2} \cdot \frac{\epsilon_0 E^2}{A d}$$

37. In the given circuit with steady current the potential drop across the capacitor must be :



# SECTION (C): COMBINATION OF CAPACITORS

1. In the adjoining circuit, the capacity between the points A and B will be -



2. The resultant capacity between the points A and B in the adjoining circuit will be -







4. The charge on the condenser of capacitance  $2\mu F$  in the following circuit will be –



**5.** Five capacitors of 10μF capacity each are connected to a d.c. potential difference of 100 volts as shown in the figure. The equivalent capacitance between the points A and B will be equal to-



6. The equivalent capacitance between the terminals X and Y in the figure shown will be-



- 7. Three capacitors of capacity 1  $\mu$ F each, are connected in such a way, that resultant capacity is 1.5  $\mu$ F, then:
  - (1) all the capacitors are joned in series
  - (2) all the capacitors are joined in parallel
  - (3) two capacitors are in parallel, while third is in series
  - (4) two capacitors are in series, while third is in parallel
- 8. n identical condenser are joined in parallel and are charged to potential V. Now they are separated and joined in series. Then the total energy and potential difference of the combination will be-
  - (1) Energy and potential difference remain same
  - (2) Energy remains same and potential difference is nV
  - (3) Energy increases n times and potentials differences is nV
  - (4) Energy increases n times and potential difference remains same
- **9.** A parallel plate capacitor of capacitance C is connected to a battery and is charged to a potential difference V. Another capacitor of capacitance 2C is connected to another battery and is charged to potential difference 2V. The charging batteries are now disconnected and the capacitors are connected in parallel to each other in such a way that the positive terminal of one is connected to the negative terminal of the other. The final energy of the configuration is-

(1) Zero (2) 
$$\frac{25CV^2}{6}$$
 (3)  $\frac{3CV^2}{2}$  (4)  $\frac{9CV^2}{2}$ 

**10.** A 3  $\mu$ F capacitor is charged to a potential of 300 V and a 2 $\mu$ F capacitor is charged to 200 V. The capacitors are then connected in parallel with plates of opposite polarity joined together. What amount of charge will flow when the plates are so connected-(1) 250 $\mu$ C (2) 600 $\mu$ C (3) 700 $\mu$ C (4) 1300 $\mu$ C

11. The equivalent capacitance of the circuit shown, between points A and B will be-



12. In the electric circuit given below, capacitance of each capacitor is 1  $\mu$ F. The effective capacitance between the points A and B is- (in  $\mu$ F)



- **13.** The equivalent capacitance of three capacitors of capacitance  $C_1$ ,  $C_2$  and  $C_3$  connected in parallel is 12 units and the product  $C_1$ .  $C_2$ .  $C_3 = 48$ . When the capacitors  $C_1$  and  $C_2$  are connected in parallel the equivalent capacitance is 6 units. Then the capacitance are-(1) 2, 4, 6 (2) 1, 5, 6 (3) 1.5, 2.5, 8 (4) 2, 3, 7
- 14. When a potential difference of  $10_3$  V is applied between A and B, a charge of 0.75 mC is stored in the system of capacitors. The value of C is ( $\mu$  F)



(4) 2

15. What is effective capacitance between points X and Y in fig.-



(1)

U

- **16.** Ten capacitors are joined in parallel and charged with a battery up to a potential V. They are then disconnected from battery and joined again in series then the potential of this combination will be-(1) V (2) 10 V (3) 5 V (4) 2 V
- **17.** The energy stored in the capacitor is U, when it is charged with a battery. After disconnecting battery another capacitor of same capacity is connected in parallel with it, then energy stored in each capacitor is-
- (1)  $\overline{6}$  (2)  $\overline{4}$  (3) 9U (4) 8U **18.** Minimum numbers of 8µF and 250V capacitors are used to make a combination of 16µF and 1000V are-
  - (1) 4 (2) 32 (3) 8 (4) 3

U

- **19.** A condenser of capacity 50  $\mu$ F is charged to 10V. The energy stored is-(1) 1.25 x 10<sub>-3</sub> J (2) 2.5 x 10<sub>-3</sub> J (3) 3.75 x 10<sub>-3</sub> J (4) 5 x 10<sub>-3</sub> J (4) 5 x 10<sub>-3</sub> J
- **20.** The capacitors A and B are connected in series with a battery as shown in the figure. When the switch S is closed and the two capacitors get charged fully, then-



- (1) The potential difference across the plates of A is 4V and across the plates of B is 6V
- (2) The potential difference across the plates of A is 6V and across the plates of B is 4V
- (3) The ratio of electric energies stored in A and B is 2 : 3 (4) The ratio of charges on A and B is 3 : 2
- 21. Potential difference across capacitance of 4.5 µF-



22. The equivalent capacitance in the circuit shown in fig. will be-



- **23.** Three condenser of capacity C each are joined first in series and then in parallel. The capacity becomes n times, where n is-
  - (1) 3 (2) 6 (3) 9 (4) 12

**24.** Two spherical conductors A and B of radius a and b (b > a) are placed in air concentrically. B is given charge +Q coulomb and A is grounded. The equivalent capacitance of these will be-

(1) 
$$4\pi\varepsilon_0 \frac{ab}{b-a}$$
 (2)  $4\pi\varepsilon_0 (a+b)$  (3)  $4\pi\varepsilon_0 b^2$  (4)  $4\pi\varepsilon_0 \frac{b^2}{b-a}$ 

**25.** Two capacitor  $C_1 = 2\mu F$ ,  $C_2 = 6\mu F$  are in series order, connected in parallel to a third capacitor of  $4\mu F$ . This combination is connected to 2 volt battery, in charging these capacitors energy consumed by the battery is-



16

(1)  $22 \times 10_{-6}$  joule (2)  $11 \times 10_{-6}$  joule (3)  $\overline{3} \times 10_{-6}$  joule (4)  $\overline{3} \times 10_{-6}$  joule

**26.** A capacitor of capacity  $C_1 = 1 \ \mu F$  can withstand maximum voltage  $V_1 = 6 \ kV$  and other capacitor  $C_2 = 3 \ \mu F$  can withstand maximum voltage  $V_2 = 4 \ kV$ . If these are connected in series, then the combined system can withstand a maximum voltage at-(1) 4 kV (2) 6 kV (3) 8 kV (4) 10 kV

27. Conducting sphere of radius R<sub>1</sub> is covered by concentric sphere of radius R<sub>2</sub>. Capacity of this combination is proportional to-

$$\begin{array}{ccc} \frac{R_2 - R_1}{R_1 R_2} & & \frac{R_2 + R_1}{R_1 R_2} & & \frac{R_1 R_2}{R_1 R_2} & & \frac{R_1 R_2}{R_1 + R_2} & & \frac{R_1 R_2}{R_2 - R_1} \end{array}$$

**28.** Two capacitors when connected in series have a capacitance of 3  $\mu$ F, and when connected in parallel have a capacitance of 16  $\mu$ F. Their individual capacities are-(1) 1  $\mu$ F, 2  $\mu$ F (2) 6  $\mu$ F, 2  $\mu$ F (3) 12  $\mu$ F, 4  $\mu$ F (4) 3  $\mu$ F, 16  $\mu$ F

**29.** A parallel plate capacitor is formed by placing n plates in alternate series one over another. If the capacity<br/>between any two consecutive plates is C, then total capacity of the capacitor is-<br/>(1) C(2) nC(3) (n - 1) C(4) (n + 1) C

**30.** Consider the situation shown in fig. The capacitor A has a charge q on it whereas B is uncharged. The charge appearing on the capacitor B a long time after the switch is closed is-



**31.** Two capacitors are joined as shown in figure. Potentials at points A and B are V<sub>1</sub> and V<sub>2</sub> respectively. The potential of point D is-



(2) 500 volt

(1) 300 volt

**33.** How the seven condensers, each of capacity 2μF, should be connected in order to obtain a resultant 10

(3) 600 volt

(4) 400 volt



**34.** Five capacitors, each of capacitance value C are connected as shown in the figure. The ratio of capacitance between P and R, and the capacitance between P and Q is –



**35.** In the given figure, the capacitors  $C_1$ ,  $C_3$ ,  $C_4$   $C_5$  have a capacitance  $4\mu$ F each. If the capacitor  $C_2$  has a capacitance 10  $\mu$ F, then effective capacitance between A and B will be :



- **36.** Three capacitors each of capacity  $4\mu$ F are to be connected in such a way that the effective capacitance is 6  $\mu$ F. This can be done by :
  - (1) connecting two in series and one in parallel(3) connecting all of them in series
- (2) connecting two in parallel and one in series
- hem in series (4) connecting all of them in parallel

**37.** A network of four capacitors of capacity equal to  $C_1 = C$ ,  $C_2 = 2C$ ,  $C_3 = 3C$  and  $C_4 = 4C$  are connected to a battery as shown in the figure. The ratio of the charges on  $C_2$  an  $C_4$  is :



- **38.** A parallel plate capacitor is made by stacking n equally spaced plates connected alternatively. If the capacitance between any two adjacent plates is 'C', then the resultant capacitance is : (1) (n-1)C (2) (n+1)CO (3) C (4) nC
- **39.** Two spheres of capacitances 3μF and 5μF are charged to 300 V and 500 V respectively and are connected together. The common potential in steady state will be (1) 400 V (2) 425 V (3) 350 V (4) 375 V
- 40. In the combination shown in the figure, the ideal voltmeter reading will be



**41.** In the given network capacitance  $C_2 = 10 \ \mu\text{F}$ ,  $C_1 = 5 \ \mu\text{F}$  and  $C_3 = 4 \ \mu\text{F}$ . The resultant capacitance between P and Q will be :



42. If the equivalent capacitance between A and B is 1µF, then the value of C will be



**43.** The equivalent capacitance between point A and B is



**44.** A combination arrangement of the capacitors is shown in the figure

(i)  $C_1 = 3 \mu F$ ,  $C_2 = 6 \mu F$  and  $C_3 = 2 \mu F$  then equivalent capacitance between 'a' and 'b' is :



- (ii) If a potential difference of 48 V is applied across points a and b, then charge on the capacitor C<sub>3</sub> at steady state condition will be : (1)  $8 \mu C$  (2)  $16 \mu C$  (3)  $32 \mu C$  (4)  $64 \mu C$
- **45.** Two spherical conductors A<sub>1</sub> and A<sub>2</sub> of radii r<sub>1</sub> and r<sub>2</sub> are placed concentrically in air. The two are connected by a copper wire as shown in figure. Then the equivalent capacitance of the system is



 $4\pi\epsilon_0 \mathbf{k} \mathbf{r}_1 \cdot \mathbf{r}_2$ 

(1) 
$$r_2 - r_1$$

(2) 4π∈₀ (r1 + r2)(3) 4π∈₀r2

no oborgo poplace te ferre

(4) 4π∈0r1

- 46. Eight drops of mercury of same radius and having same charge coalesce to form a big drop. Capacitance of big drop relative to that of small drop will be (1) 16 times (2) 8 times (3) 4 times (4) 2 times
- 47. In the figure given, the effective capacitance between A and B will be



**48.** If the shown figure combination of four capacitors and their values are given. Charge and potential difference acorss 4  $\mu$ F capacitor will be -



(3) R/C

(4) C/R

(1) +RC

(2) –RC

6. If a current, that charges a capacitor, is constant, then graph representing the change in voltage across the capacitor with time t is-



7. In the adjoining diagram, (assuming the battery to be ideal) the condenser C will be fully charged to potential V if -



8. In the following figure, the charge on each condenser in the steady state will be-

		$\begin{array}{cccccccccccccccccccccccccccccccccccc$	
(1) 3μC	(2) 6μC	(3) 9µC	(4) 12μC

- 9. The plates of a capacitor of capacitance 10  $\mu$ F, charged to 60  $\mu$ C, are joined together by a wire of resistance 10  $\Omega$  at t = 0, then (i) the charge on the capacitor in the circuit at t = 0 is : (1) 120  $\mu$ C
  (2) 60  $\mu$ C
  (3) 30  $\mu$ C
  (4) 44  $\mu$ C
  (ii) the charge on the capacitor in the circuit at t = 100  $\mu$ s is : (1) 120  $\mu$ C
  (2) 60  $\mu$ C
  (3) 22  $\mu$ C
  (4) 18  $\mu$ C
  (iii) the charge on the capacitor in the circuit at t = 1.0 ms is : (take e<sub>10</sub> = 20000)
  - (1)  $0.003 \ \mu C$  (2)  $60 \ \mu C$  (3)  $44 \ \mu C$  (4)  $18 \ \mu C$

**10.** Dotted line represents the charging of a capacitor with resistance X. If resistance is made 2X then which will be the graph of charging



11. n resistances each of resistance R are joined with capacitors of capacity C (each) and a battery of emf E as shown in the figure. In steady state condition ratio of charge stored in the first and last capacitor is



# SECTION (E): CAPACITOR WITH DIELECTRIC

1. The distance between the plates of a parallel plate condenser is d. If a copper plate of same area but d

```
thickness2is placed between the plates then the new capacitance will become-(1) half(2) double(3) one fourth(4) unchanged
```

2. On placing a dielectric slab between the plates of an isolated charged condenser its-

•	Capacitance	Charge	Potential Difference	Energy stored	Electric field
(1)	decreases	remains unchanged	decreases	increases	increases
(2)	increases	remains unchanged	increases	increases	decreases
(3)	increases	remains unchanged	decreases	decreases	decreases
(4)	decreases	remains unchanged	decreases	increases	remains unchanged

3. A parallel plate condenser is connected to a battery of e.m.f. 4 volt. If a plate of dielectric constant 8 is inserted into it, then the potential difference on the condenser will be-(1) 1/2 V (2) 2V (3) 4V (4) 32V

In the above problem if the battery is disconnected before inserting the dielectric, then potential difference will be (1) 1/2 V
 (2) 2V
 (3) 4V
 (4) 32V

5. A parallel plate condenser with plate separation d is charged with the help of a battery so that U₀ energy is stored in the system. A plate of dielectric constant K and thickness d is placed between the plates of condenser while battery remains connected. The new energy of the system will be-

		$U_0$	
(1) KU₀	(2) K <sub>2</sub> U <sub>0</sub>	(3) K	(4) K <sup>2</sup>

→				
6.	In the above problem i	f the battery is disconnec	ted before placing the pl	ate, then new energy will be-
		$\frac{U_0}{2}$	U <sub>0</sub>	
	(1) K <sub>2</sub> U <sub>0</sub>	(2) K <sup>2</sup>	(3) K	(4) KU <sub>0</sub>
7.	A parallel plate capacit introduced between the	tor is first charged and the e plates. The quantity that	en disconnected from ba at remains unchanged is	ttery and then a dielectric slab is
	(1) Charge Q	(2) Potential V	(3) Capacity C	(4) Energy U
8.	A parallel capacitor of in it is E. If a dielectric energy and capacitance	capacitance C is charge slab of dielectric constar e will become	d and disconnected fron ht 6 is ineserted betweer	n the battery. The energy stored the plates of the capacitor then
			<u>⊢</u> ,6C	
	(1) 6E, 6C	(2) E, C	(3) 6	(4) E, 6C
9.	When a dielectric mat between the plates	erial is introduced betwe	en the plates of a charg	ged condenser, the electric field
	(1) decreases	(2) increases	(3) does not change	(4) may increase or decrease
10.	A condenser is charge condenser, then correct	ed and then battery is re	emoved. A dielectric pla	te is put between the plates of
	(1) Q constant V and L (3) Q increases V decr	decrease reases U increases	(2) Q constant V increa (4) None of these	ases U decreases
11.	While a capacitor rema (1) the energy stored in (2) the electric field be (3) charges flow from t (4) the potential different	ains connected to a batte in the capacitor decreases tween the plates increase he battery to the capacito ince between the plates is	ry, a dielectric slabis slip s es or s changed	ped between the plates. Then
12.	In a parallel plate capa them. The thickness of becomes	acitor of capacitance C, a of the sheet is half of the	a metal sheet is inserted e seperation between th	d between the plates, parallel to ne plates. The capacitance now
	(1) 0/4	(2) 0/2	(3) 20	(4) 40
13.	The plates of parallel p plates. Then to mainta 1.6 mm. The dielectric	late capacitor are charge in the same potential diff constant of the plate is- (2) 1 25	ed upto 100 V. A 2 mm th ference, the distance be	ick plate is inserted between the tween the plates is increases by
	(1)0	(2) 1.20	(0) +	(+) 2.0
14.	Between the plates of In the rest of the space difference across the c	parallel plate condenser a e, there is another plate condenser will be-	a plate of thickness t1 and of thickness t2 and diel	d dielectric constant K1 is placed. ectric constant k2. The potential
	(1) $\frac{Q}{A\varepsilon_0} \left( \frac{t_1}{k_1} + \frac{t_2}{k_2} \right)$	(2) $\frac{\varepsilon_0 Q}{A} \left( \frac{t_1}{k_1} + \frac{t_2}{k_2} \right)$	(3) $\frac{Q}{A\varepsilon_0} \left(\frac{k_1}{t_1} + \frac{k_2}{t_2}\right)$	(4) $\frac{\varepsilon_0 Q}{A}$ (k <sub>1</sub> t <sub>1</sub> + k <sub>2</sub> t <sub>2</sub> )
15.	A sheet of aluminium two plates of the capace (1) Invariant for all pos (2) Maximum when the (3) Maximum when the (4) Maximum when the	is inserted in the air gap citor. The capacitance of itions of the sheet e sheet is midway betwee e sheet is just near the +v e sheet is just near the -v	of a parallel plate capac the capacitor is- en the 2 plates ve plate. ve plate.	sitor, without touching any of the
16.	The value of a capaci having a thickness of 0 length of the foil used i	tor formed by a thin met 0.015 mm. The dielectric o is-	allic foil is 2 μF. The foi constant of the paper is 2	l is folded with a layer of paper 2.5 and its breadth is 40 mm. The
	(1) 0.34 m	(2) 1.33 m	(3) 13.4 mm	(4) 33.9 m

- 17. A parallel plate air capacitor is charged by connecting its plates to a battery. Without disconnecting the battery, a dielectric is introduced between its plates. As a result-
  - (1) P.D. between the plates increases
  - (3) Capacitance of the capacitor decreases
- (2) Charge on the plates decreases
- (4) None of the above
- 18. A capacitor is charged using a battery, and battery is withdrawn later on. Now a dielectric slab is introduced between the capacitor plates then the correct statement is-
  - (1) Q increase, V decrease, U increase
  - (2) Q remains constant, V increases, U decreases
  - (3) Q remains constant, V and U both decreases
  - (4) None of these
- 19. A dielectric slab of thickness d is inserted in a parallel plate capacitor whose negative plate is at X = 0and positive plate is at X = 3d. The slab is equidistant from the plates. The capacitor is given some charge. As X goes from 0 to 3 d-
  - [a] The electric potential increases at first, then decreases and again increases.
  - [b] The electric potential increases continuously.
  - [c] The direction of the electric field remains the same
  - [d] The magnitude of the electric field remains the same
  - (4) a. b. d (1) a. b (2) b. c (3) b. d
- 20. A parallel plate condenser with oil between the plates (dielectric constant of oil K = 2) has a capacitance C. If the coil is removed, then capacitance of the capacitor becomes-

$$\frac{C}{2}$$
 (2)

(1)

- С (4) √2 C  $\sqrt{2}$ (3) 2C
- 21. Plate separation of a  $15\mu$ F capacitor is 2 mm. A dielectric slab (K = 2) of thickness 1 mm is inserted between the plates. Then new capacitance is given by-(1) 15 µF (2) 20 µF (3) 30 µF (4) 25 µF
- 22. The capacity of a parallel plate capacitor with no dielectric substance but with a separation of 0.4 cm is 2 µF. The separation is reduced to half and it is filled with a substance dielectric of value 2.8. The new capacity of the capacitor is-
  - (1) 11.2 µF (2) 15.6 µF (3) 19.2 µF (4) 22.4 µF
- 23. Effective capacitance if Cair = 10 µF-



- 24. While a capacitor remains connected to a battery, a dielectric slab is slipped between the plates-
  - (1) The electric field between the plates increases
  - (2) The energy stored in the capacitor decreases
  - (3) The potential difference between the plates is changed
  - (4) Charges flow from the battery to the capacitor.

**25.** A parallel plate condenser is filled with two dielectric as shown in fig. Area of each plate is A m<sub>2</sub> and the separation is d metre. The dielectric constants are K<sub>1</sub> and K<sub>2</sub> respectively. Its capacitance in farad will be-



**26.** Capacity of air capacitor (parallel plate) is 10µC. Now a dielectric of dielectric constant 4 is filled in the half space between the plates, then new capacity will be-



27. A parallel plate capacitor is filled by copper plate of thickness b. The new capacity will be-

(1) 
$$\frac{\varepsilon_0 A}{2d-b}$$
 (2)  $\frac{\varepsilon_0 A}{d-b}$  (3)  $\frac{\varepsilon_0 A}{d-b/2}$  (4)  $\frac{\varepsilon_0 A}{d}$ 

- **28.** Putting a dielectric substance between two plates of a condenser, the capacity, potential and potential energy respectively-
  - (1) Increases, decreases, decreases
- (2) Decreases, increases, increases
- (3) Increases, increases, increases
- (4) Decreases, decreases, decreases
- **29.** A parallel plate capacitor of plate area A, separation d is filled with dielectrics as shown in fig. The dielectric constants are K<sub>1</sub> and K<sub>2</sub>. Net capacitance is-



**30.** Two parallel plates capacitors of value C and 2C are connected in parallel and are charged to a potential difference V. If now battery is disconnected and a medium of dielectric constant K is introduced between the plates of the capacitor C, then the potential between the capacitors plates will become-

(1) 
$$3V[K+2]$$
 (2)  $\frac{[K+2]}{3V}$  (3)  $\frac{3V}{[K+2]}$  (4)  $\frac{3[K+2]}{V}$ 

**31.** As shown in the figure half the space between plates of a capacitor is filled with an insulator material of dielectric constant K, if initial capacity was C then the new capacity is-



**32.** Two materials of dielectric constant k<sub>1</sub> and k<sub>2</sub> are filled between two parallel plates of a capacitor as shown in figrue. The capacity of the capacitor is :



**33.** A parallel plate condenser with a dielectric of dielectric constant *K* between the plates has a capacity *C* and is charged to a potential *V* volts. The dielectric slab is slowly removed from between the plates and then reinserted. The net work done by the system in this process is 1

(1) 
$$\frac{1}{2}$$
 (K-1)CV<sub>2</sub> (2) CV<sub>2</sub>(K - 1)/K (3) (K - 1)CV<sub>2</sub> (4) zero

34. After charging a capacitor the battery is removed. Now by placing a dielectric slab between the plates (1) the potential difference between the plates and the energy stored will decrease but the charge on plates will remain same

(2) the charge on the plates will decrease and the potential difference between the plates will increase(3) the potential difference between the plates will increase and energy stored will decrease but the charge on the plates will remain same

(4) the potential difference, energy stored and the charge will remain unchanged

**35.** A parallel plate capacitor is filled with two dielectrics as shown in figure. If A is area of each plate, then the effective capacitance between X and Y is



36. An insulator plate is passed between the plates of a capacitor. Then current



(1) 20 V
(2) 25 V
(3) 75 V
(4) 100 V

2. In the above question, the potential difference between B and C in steady state will be

(2) 25 V

100V

**3.** Three capacitors of same capacitance are connected in parallel. When they are connected to a cell of 2 volt, total charge of  $1.8\mu$ C is accumulated on them. Now they are connected in series and then charged by the same cell. The total charge stored in them will be (1)  $1.8\mu$ C (2)  $0.9\mu$ C (3)  $0.6\mu$ C (4)  $0.2\mu$ C

(3) 50 V

(4) 75 V

(1) 20 V

Each edge of the cube contains a capacitance C. The equivalent capacitance between the points A and 4. B will be -



- 5. A capacitor of capacitance 500µF is charged at the rate of 100µC/s. The time in which the potential difference will become 20 V, is (3) 20 s (4) 10 s
  - (1) 100 s (2) 50 s
- 6. A network of uncharged capacitors and resistances is shown



Current through the battery immediately after key K is closed and after a long time interval is :

(1) 
$$\frac{E}{R_1}$$
,  $\frac{E}{R_1 + R_3}$   
(2)  $\frac{E}{R_1 + R_3}$ ,  $\frac{E}{R_1 + \frac{R_2 R_3}{R_2 + R_3}}$   
(3) zero,  $\frac{E}{R_1}$   
(4)  $\frac{E}{R_1 + \frac{R_2 R_3}{R_2 + R_3}}$ ,  $\frac{E}{R_1}$ 

7. In the given circuit, a charge of +80 µC is given to the upper plate of the 4µF capacitor. Then in the steady state, the charge on the upper plate of the  $3\mu$ F capacitor is :





(4)

h

(3)

d 🗕

- 6. A parallel plate air capacitor of capacitance C is connected to a cell of emf V and then disconnected from it. A dielectric slab of dielectric constant K, which can just fill the air gap of the capacitor, is now inserted in it. Which of the following is incorrect?
  [AIPMT-2015]
  - (1) The energy stored in the capacitor decreases K times.

$$\frac{1}{2}CV^2\left(\frac{1}{K}-1\right)$$

(3) The charge on the capacitor is not conserved.

(2) The chance in energy stored is

- (4) The potential difference between the plates decreases K times.
- A capacitor of 2μF is charged as shown in the diagram. When the switch S is turned to position 2, the percentage of its stored energy dissipated is : [AIPMT-2016]



8. A parallel- plate capacitor of area A, plate separation d and capacitance C is filled with four dielectric materials having dielectric constant k<sub>1</sub>, k<sub>2</sub>, k<sub>3</sub> and k<sub>4</sub> as shown in the figure below. If a single dielectric material is to be used to have the same capacitance C in this capacitor, then its dielectric constant k is given by [NEET 2016]



- 9. A capacitor is charged by a battery. The battery is removed and another identical uncharged capacitor is connected in parallel. The total electrostatic energy of resulting system : [NEET 2017]

   (1) increases by a factor of 4
   (2) decreases by a factor 2
   (3) remains the same
   (4) increases by a factor of 2
- 10 The electrostatic force between the metal plates of an isolated parallel plate capacitor C having a charge Q and area A, is : [NEET 2018]
  - (1) independent of the distance between the plates
  - (2) inversely proportional to the distance between the plates
  - $\left( 3\right)$  proportional to the square root of the distance the plates
  - (4) linearly proportional to the distance between the plates

(1) 75%

**11.** Two identical capacitors C<sub>1</sub> and C<sub>2</sub> of equal capacitance are connected as shown in the circuit. Terminals a and b of the key k are connected to charge capacitor C<sub>1</sub> using battery of emf V volt. Now disconnecting a and b the terminals b and c are connected. Due to this, what will be the percentage loss of energy? [NEET\_2019-II]



# PART - III : JEE (MAIN) / AIEEE PROBLEMS (PREVIOUS YEARS)

(1) 1 (2) $\overline{2}$ (3) $\overline{4}$ (4) 2		<u> </u>	<u>.</u>	
	(1) 1	(2) 2	(3) 4	(4) 2

- 2. A resistor 'R' and  $2\mu$ F capacitor in series is connected through a switch to 200 V direct supply. Across the capacitor is a neon bulb that lights up at 120 V. Calculate the value of R to make the bulb light up 5s after the switch has been closed. ( $log_{10}2.5 = 0.4$ ) [AIEEE 2011, 4/120, -1] (1)  $1.3 \times 10_4 \Omega$  (2)  $1.7 \times 10_5 \Omega$  (3)  $2.7 \times 10_6 \Omega$  (4)  $3.3 \times 10_7 \Omega$
- 3. Combination of two identical capacitors, a resistor R and a dc voltage source of voltage 6V is used in an experiment on a (C R) circuit. It is found that for a parallel combination of the capacitor the time in which the voltage of the fully charged combination reduces to half its original voltage is 10 second. For series combination the time needed for reducing the voltage of the fully charged series combination by half is : [AIEEE 2011, 11 May; 4, –1]



The figure shows an experimental plot discharging of a capacitor in an RC circuit. The time constant τ of this circuit lies between : [AIEEE 2012; 4/120, -1]

(4) 20 second



5.

- 6. A parallel plate capacitor is made of two circular plates separated by a distance of 5 mm and with a dielectric of dielectric constant 2.2 between them. When the electric field in the dielectric is  $3 \times 10_4$  V/m, the charge density of the positive plate will be close to : [JEE- Main 2014] (1)  $6 \times 10_{-7}$ C/m<sub>2</sub> (2)  $3 \times 10_{-7}$ C/m<sub>2</sub> (3)  $3 \times 10_4$ C/m<sub>2</sub> (4)  $6 \times 10_4$ C/m<sub>2</sub>
- 7. In the given circuit, charge  $Q_2$  on the  $2\mu$ F capacitor changes as C is varied from  $1\mu$ F to  $3\mu$ F.  $Q_2$  as a function of 'C' is given properly by : (figures are drawn schematically and are not to scale)



A combination of capacitors is set up as shown in the figure. The magnitude of the electric field, due to a point charge Q (having a charge equal to the sum of the charges on the 4μF and 9μF capacitors), at a point distance 30 m from it, would equal : [JEE Main 2016]



A capacitance of 2μF is required in an electrical circuit across a potential difference of 1.0 kV. A large number of 1μF capacitors are available which can withstand a potential difference of not more than 300 V.

The minimum number of	[JEE Main 2017]		
(1) 32	(2) 2	(3) 16	(4) 24

 10.
 In the given circuit diagram when the current reaches steady state in the circuit, the charge on the capacitor of capacitance C will be :

 [JEE Main 2017]



**11.** A parallel plate capacitor of capacitance 90 pF is connected to a battery of emf 20V. If a dielectric material 5

of dielectric constant  $K = \overline{3}$  is inserted between the plates, the magnitude of the induced charge will be : [JEE-Main-2018]

**12.** A parallel plate capacitor with square plates is filled with four dielectrics of dielectric constants K<sub>1</sub>, K<sub>2</sub>, K<sub>3</sub>, K<sub>4</sub> arranged as shown in the figure. The effective dielectric constant K will b :**[JEE-Main-2019]** 



**13.** A parallel plate capacitor is of area 6 cm<sup>2</sup> and a separation 3 mm. The gap is filled with three dielectric materials of equal thickness (see figure) with dielectric constants  $K_1 = 10$ ,  $K_2 = 12$  and  $K_3 = 14$ . The dielectric constant of a material which when fully inserted in above capacitor, gives same capacitance would be : **[JEE-Main-2019]** 



14. A parallel plate capacitor having capacitance 12 pF is charged by a battery to a potential difference of 10 V between its plates. The charging battery is now disconnected and a porcelain slab of dielectric constant 6.5 is slipped between the plate. The work done by the capacitor on the slab is

[JEE-Main-2019]

capacitance of  $\left(\frac{6}{13}\right)\mu$ F. Which of the combinations, shown in figures below, will achieve the desired value? [JEE-Main-2019]



16. In the figure shown below, the charge on the left plate of the 10 μF capacitor is -30 μC. The charge on the right plate of the 6 μF capacitor is : [JEE-Main-2019]



- 17. A parallel plate capacitor with pates of area 1 m<sup>2</sup> each, are at a separation of 0.1 m. If the electric field between the plates is 100 N/C, the magnitude of charge on each plate. (Take  $\epsilon_0 = 8.85 \times 10^{-12} \frac{C^2}{N-m^2}$ ) [JEE-Main-2019] (1)  $6.85 \times 10^{-10}$  C (2)  $7.85 \times 10^{-10}$  C (3)  $9.85 \times 10^{-10}$  C (4)  $8.85 \times 10^{-10}$  C
- 18. In the figure shown, after the switch 'S' is turned position 'A' to position 'B', the energy dissipated in the circuit in terms of capacitance 'C' and total charge 'Q' is: [JEE-Main-2019]



Capacitance				
(1) $\frac{3}{8} \frac{Q^2}{C}$	(2) $\frac{5}{8} \frac{Q^2}{C}$	(3) $\frac{1}{8} \frac{Q^2}{C}$	(4) $\frac{3}{4} \frac{Q^2}{C}$	·

Answers

F

EXERCISE # 1													
SECT	ION (A) :												
1.	(1)	2.	(4)	3.	(2)	4.	(2)	5.	(2)	6.	(1)	7.	(3)
8.	(1)	9.	(2)	10.	(1)	11.	(1)	12.	(3)	13.	(3)	14.	(1)
15.	(4)	16.	(1)										
SEC	TION (E	3):											
1.	(2)	2.	(3)	3.	(4)	4.	(1)	5.	(2)	6.	(3)	7.	(2)
8.	(4)	9.	(1)	10.	(1)	11.	(3)	12.	(4)	13.	(2)	14.	(3)
15.	(1)	16.	(1)	17.	(2)	18.	(4)	19.	(3)	20.	(4)	21.	(2)
22.	(2)	23.	(2)	24.	(4)	25.	(3)	26.	(3)	27.	(2)	28.	(2)
29.	(4)	30.	(2)	31.	(2)	32.	(2)	33.	(3)	34.	(2)	35.	(3)
36.	(3)	37.	(3)										
SEC	TION (C	C):											
1.	(2)	2.	(3)	3.	(4)	4.	(2)	5.	(4)	6.	(2)	7.	(4)
8.	(2)	9.	(3)	10.	(2)	11.	(3)	12.	(1)	13.	(1)	14.	(4)
15.	(1)	16.	(2)	17.	(2)	18.	(2)	19.	(2)	20.	(2)	21.	(1)
22.	(4)	23.	(3)	24.	(4)	25.	(1)	26.	(3)	27.	(4)	28.	(3)
29.	(3)	30.	(1)	31.	(3)	32.	(4)	33.	(3)	34.	(3)	35.	(2)
36.	(1)	37.	(2)	38.	(1)	39.	(2)	40.	(4)	41.	(3)	42.	(1)
43.	(4)	44.	(i)	(1)		(ii)	(4)	45.	(3)	46.	(4)	47.	(3)
48.	(4)												
SEC	TION (C	<b>)</b> ):											
1.	(i) (2)	(ii) (3)	(iii) (1)	<b>2.</b> (i) (1)	(ii) (2)	3.	(i) (3)	(ii) (2)	(iii) (3)	(iv) (4)	4.	(3)	
5.	(1)	6.	(3)	7.	(3)	8.	(4)	9.	(i) (2)	(ii) (3)	(iii) (1)	10.	(2)
11.	(4)												
SEC	TION (E	E):											
1.	(2)	2.	(3)	3.	(3)	4.	(1)	5.	(1)	6.	(3)	7.	(1)
8.	(3)	9.	(1)	10.	(1)	11.	(3)	12.	(3)	13.	(1)	14.	(1)
15.	(1)	16.	(4)	17.	(4)	18.	(3)	19.	(2)	20.	(1)	21.	(2)
22.	(1)	23.	(1)	24.	(4)	25.	(4)	26.	(1)	27.	(2)	28.	(1)
29.	(3)	30.	(3)	31.	(1)	32.	(1)	33.	(4)	34.	(1)	35.	(4)
36.	(2)	37.	(2)	38.	(1)	39.	(1)	40.	(4)				
EXERCISE # 2													
1.	(2)	2.	(4)	3.	(4)	4.	(1)	5.	(1)	6.	(1)	7.	(3)
						EXERC	CISE # 3	3					
						D۸۵	י _ דכ						
1.	(3)	2.	(4)	3.	(4)	4.	(3)	5.	(3)	6.	(3)	7.	(1)
8.	(4)	9.	(2)	10	(1)	11.	(3)						
_		_		_		PAR	RT - II	_		_		_	
1.	(3)	2.	(3)	3.	(3)	4.	(4)	5.	(2)	6.	(1)	7.	(2)
8.	(2)	9.	(1)	10.	(4)	11.	(3)	<b>12.</b> (4 d	or Bonus	s) <b>13.</b>	(4)	14.	(3)

Ca	apacita	ance						•
• 15.	(3)	16.	(4)	17.	(4)	18.	(1)	•