

Exercise-I

- | | | | | | | |
|-------|--------|--------|--------|-------|-------|-------|
| 1. B | 2. B | 3. D | 4. A | 5. A | 6. C | 7. C |
| 8. C | 9. D | 10. D | 11. D | 12. D | 13. B | 14. B |
| 15. D | 16. C | 17. A | 18. C | 19. D | 20. A | 21. A |
| 22. A | 23. B | 24. B | 25. D | 26. D | 27. C | 28. B |
| 29. A | 30. B | 31. A | 32. B | 33. C | 34. C | 35. D |
| 36. D | 37. B | 38. C | 39. B | 40. A | 41. B | 42. C |
| 43. B | 44. D | 45. C | 46. C | 47. B | 48. D | 49. D |
| 50. B | 51. B | 52. B | 53. A | 54. B | 55. B | 56. C |
| 57. B | 58. A | 59. C | 60. A | 61. B | 62. D | 63. A |
| 64. A | 65. D | 66. B | 67. A | 68. A | 69. B | 70. B |
| 71. D | 72. A | 73. D | 74. B | 75. D | 76. C | 77. C |
| 78. A | 79. D | 80. B | 81. C | 82. C | 83. D | 84. D |
| 85. B | 86. A | 87. A | 88. A | 89. A | 90. B | 91. B |
| 92. B | 93. B | 94. A | 95. D | 96. C | 97. B | 98. D |
| 99. D | 100. A | 101. D | 102. C | | | |

Exercise-II

- | | | | | | | |
|----------|-----------|---------|------------|-----------|---------|----------|
| 1. A,B,C | 2. A | 3. D | 4. A,B,C,D | 5. A,D | 6. C | 7. A,C,D |
| 8. A | 9. C | 10. A,C | 11. A,C | 12. D | 13. A,D | 14. C |
| 15. B,C | 16. A,C,D | 17. A | 18. A,B | 19. A,B,C | 20. A,C | |

Exercise-III

- | | | | |
|--|--|------------------------|---|
| 1. 1.5625×10^{19} | 2. 1.25×10^{-17} , (b) $\frac{2}{\pi} \times 10^6 \text{ A/m}^2$ | 3. 25 V/m | 4. (a) 7.5 V, (b) 24 mA(c) greater than 12 V |
| 5. zero | 6. 19 V | 7. (a) 3.7 V (b) 3.7 V | 8. 1Ω 9. 600Ω |
| 10. 1 V | 11. $\frac{3}{20} = 0.15\text{A}$, $\frac{3 \times 5.5}{20} = 0.83\text{A}$ | | 12. $I = 2.5\text{ A}$, $V = 3.5\text{ volts}$ |
| 13. $\frac{25}{9}\text{V} = 2.78\text{V}$, $\frac{5}{18}\text{A} = 0.278\text{A}$ | 14. B | 15. 1W | 16. $\frac{22}{35}\Omega$ 17. $\frac{3r}{5}$ |
| 18. (a) 12 W (b) 4W (c) 8 W (d) 4Ω (e) 4W | | | |
| 19. 90 watt. | 20. 12A, - 20 W | 21. $\sqrt{R_1 R_2}$ | |


22. (a) $\frac{50}{11} = 4.55 \text{ A}$ (b) $\frac{22 \times 11}{5} = 48.4 \Omega$ (c) 1000 W (d) 240 cal s^{-1} (e) $80/3 \text{ gm}$
23. 90%
24. (a) $E = 10 \text{ V}$ each (b) (A) act as a source and (B) act as load
(c) $V_A = 9 \text{ V}$, $V_B = 11 \text{ V}$ (d) $P_A = 9 \text{ W}$, $P_B = 11 \text{ W}$ (e) Heat rate = 1 W each
(f) 10 watt. (g) 9V, 11 V (b) -9W, 11 W
25. 4Ω 26. 20 ohm 27. $\frac{50}{73} \text{ A}$ 28. 46.67 cm
29. 4 ohm 30. $\frac{10}{3} \Omega, 5 \Omega$ 31. 7.5 m, 8.75 m, 6.25 m

Exercise-IV


1. $(3/11)\alpha$ 2. (a) $J_0 A/3$; (b) $2J_0 A/3$ 3. $\frac{R_2}{R_1} = \frac{3}{5}$ 4. (i) 10.52Ω ; (ii) 0.3125Ω
5. 7/5 times the length of any side of the square
6. (i) $\frac{(k-1)^2}{k}; \frac{k}{(k-1)}$ (ii) $\frac{((k-1)/k^2)V_0}{R^3}$ 7. 4/9 kg/sec, 450 sec 8. (i) $V_{ab} = -12 \text{ V}$, (ii) 3 amp from b to a
9. $11 + 6\sqrt{2}$ 10. $R = \frac{\rho_0 L}{A} \left(1 - \frac{1}{e}\right)$; $I = \frac{V_0 A}{\rho_0 L} \left(\frac{e}{e-1}\right)$; $V = \frac{V_0(e^{-x/L} - e^{-1})}{1 - e^{-1}}$ 11. 7.2 m 13. $-\frac{22}{9} V_n$
14. $\alpha_{\text{eff}} = \frac{5}{4}\alpha$ 15. 233.3 Ω , 144V 16. (a) 6m, (b) 1Ω 17. (a) 1.01 W, (b) 0-5A, 0-10 V, (c) 0.05 A

Exercise-V

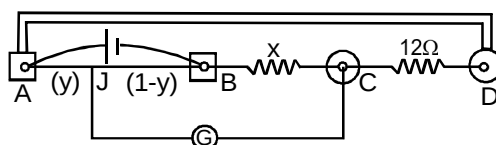1. $20/3 \text{ V}$ 2. (i) D; (ii) $M^{-1} L^{-3} T^3 A^2$; (iii) $\frac{V_1 r_2 + V_2 r_1}{r_1 + r_2}, \frac{r_1 r_2}{r_1 + r_2}$ 3. D 4. A



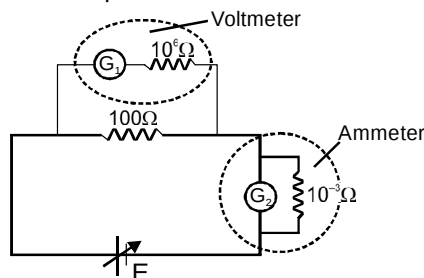5. A 6. D 7. (a) No, (b) (c) 8Ω 8. A 9. A
10. Battery should be connected across A and B. Out put can be taken across the terminals A and C or B and C



11. A 12. C 13. 14. B 15. D
16. This is true for $r_1 = r_2$; So R_2 given most accurate value 17. A 18. A 19. C
20. D 21. A, D 22. C 23. D 24. C 25. 4
26. B 27. 5 28. A, B, C, D