

CURRENT ELECTRICITY

EXERCISE – I

SINGLE CORRECT

1. B


$$\frac{\rho_1 \ell_1 (1 + \alpha_1 \Delta T)}{A} + \frac{\rho_2 \ell_2 (1 + \alpha_2 \Delta T)}{A} = R$$

Total resistance is independent of temp.

$$\Rightarrow \frac{\rho_1 \ell_1 \alpha_1 \Delta T}{A} + \frac{\rho_2 \ell_2 \alpha_2 \Delta T}{A} = 0$$

$$\Rightarrow \rho_1 \ell_1 \alpha_1 + \rho_2 \ell_2 \alpha_2 = 0$$

2. B

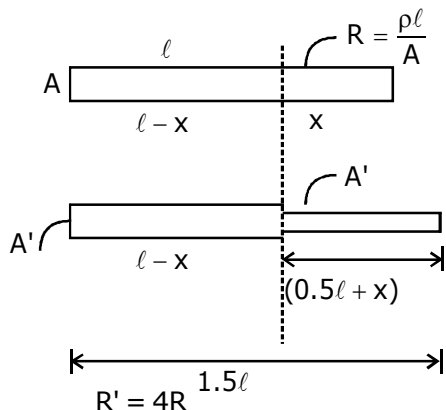

$$Ax = A'(0.5\ell + x)$$

$$A' = \frac{Ax}{0.5\ell + x}$$

$$\Rightarrow \frac{4\rho\ell}{A} = \frac{\rho(\ell - x)}{A} + \frac{\rho(0.5\ell + x)}{A'}$$

$$\Rightarrow \frac{4\rho\ell}{A} = \frac{\rho(\ell - x)}{A} + \frac{\rho(0.5\ell + x)^2}{Ax}$$

$$\Rightarrow 4\ell x = \ell x - x^2 + (0.5\ell)^2 + \ell x + x^2$$

After solving $x = (1/8)\ell$

3. D

$$\left. \begin{aligned} x &= \frac{\rho 4a}{2a^2} = \frac{2\rho}{a} \\ y &= \frac{\rho a}{8a^2} = \frac{\rho}{8a} \\ z &= \frac{\rho(2a)}{4a^2} = \frac{\rho}{2a} \end{aligned} \right\} \text{From } R = \frac{\rho \ell}{A}$$

$$x > z > y$$

4. A

$$R_1 = \frac{\rho_B \ell_B}{A} (1 + \alpha_B \Delta T)$$

$$R_2 = \frac{\rho_C \ell_C}{A} (1 + \alpha_C \Delta T)$$

$$\text{Req.} = R_1 + R_2$$

$$\text{Req.} = \frac{\rho_B \ell_B}{A} + \frac{\rho_B \ell_B}{A} \alpha_B \Delta T + \frac{\rho_C \ell_C}{A} + \frac{\rho_C \ell_C}{A} \alpha_C \Delta T$$

Net resistance is independent of temp.

$$\Rightarrow \frac{\rho_B \ell_B \alpha_B \Delta T}{A} + \frac{\rho_C \ell_C \alpha_C \Delta T}{A} = 0$$

$$\Rightarrow \frac{\ell_B}{\ell_C} = \left| \frac{\alpha_C \rho_C}{\rho_B \alpha_B} \right|$$

5. A

$$R = \frac{V}{I} \Rightarrow R = \frac{10}{2.5} = 4\Omega$$

$$dR = \frac{dV}{V} - \frac{V}{I^2} dI \Rightarrow \frac{dR}{R} = \frac{dV}{V} - \frac{dI}{I}$$

$$\frac{dR}{4} = \frac{0.1}{10} + \frac{0.05}{2.5}$$

$$dR = 0.12$$

$$\Rightarrow R = 4 \pm 0.12$$

6. C

$$i = n_1 e A V_{d1}, i = n_2 e A V_{d2}, \frac{n_1}{n_2} = \frac{V_{d2}}{V_{d1}} = \frac{4}{1}$$

7. C

$$I = neAV_d, A = \pi r^2$$

$$I' = neA'V_d'$$

$$= ne \frac{\pi r^2}{4} \cdot 2V_d$$

$$= I/2$$

8. C

$$y : \rho = \rho_0 (1 + \alpha \Delta T)$$

 α is -ve for semi conductor $z : \text{temp} \uparrow \tau \downarrow$ Hence rate of collision $\uparrow$

9. D

B'coz copper is a conductor

But germanium & Si are semi conductors.


10. D

$$i_1 = neAV, i_2 = n(2e)Av/4$$

$$i = i_1 + i_2$$

$$= \frac{3neAV}{4}$$

11. D

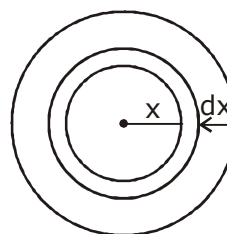

$$I = \begin{cases} J_0 \left(\frac{x}{R} - 1 \right) & \text{for } 0 \leq x < R/2 \\ J_0 \frac{x}{R} & \text{for } \frac{R}{2} \leq x \leq R \end{cases}$$

$$i = \int_0^{R/2} J_0 \left(\frac{x}{R} - 1 \right) 2\pi x dx + \int_{R/2}^R J_0 \frac{x}{R} 2\pi x dx$$

$$i = \frac{5}{12} \pi J_0 R^2$$


12. D

$$i_1 = ne \left(\frac{\pi d^2}{4} \right) V_d$$

$$i_2 = ne \frac{\pi d^2}{16} V'$$

$$\therefore i_1 = i_2$$

$$\Rightarrow V' = 4V_d$$

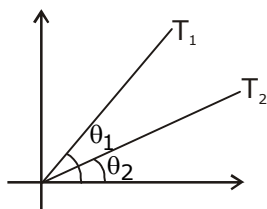13. B

$$R = \frac{V}{I} \Rightarrow \frac{I}{V} = \frac{1}{R}$$

$$\therefore \theta_1 > \theta_2$$

$$\Rightarrow R_1 < R_2$$

$$\Rightarrow T_1 < T_2$$

$$\therefore T \uparrow R \uparrow$$

14. B

$$i = neAV_d$$

$$\frac{i}{\rho s q} = V_d$$

15. D

$\vec{F} = -e \vec{E}$
So e^- moves randomly but slowly drift opposite to E .

16. C

$$i = neAV_d$$

i is same so
 $A \uparrow V_d \downarrow$

17. A

$$R = \frac{\rho \ell}{A}$$

$$R_{\text{square}} = \frac{3.5 \times 10^{-5} \times 50 \times 10^{-2}}{(10^{-2})^2}$$

$$= \frac{35}{2} \times 10^{-2} \Omega$$

$$R_{\text{rectangle}} = \frac{3.5 \times 10^{-5} \times 2[1 \times 10^{-2}]}{(50 \times 10^{-4})}$$

$$= 7 \times 10^{-5}$$

18. C

$$E + ir = 12.5 \text{ Volt}$$


$$E + (0.5 \times 1) = 12.5$$

$$E = 12 \text{ volt}$$


19. D $E - ir = 0$

$$E - ir = V \text{ (Discharging)}$$

$$E + ir = V \text{ (Charging)}$$

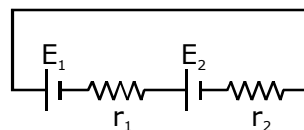
20. A

$$\frac{E_1 + E_2}{r_1 + r_2} = I_1$$

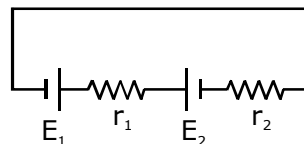

$$\frac{-(E_2 - E_1)}{r_1 + r_2} = I_2$$

$$\frac{E_1 + E_2}{E_1 - E_2} = \frac{I_1}{I_2} \Rightarrow E_1 = \frac{(I_1 + I_2)}{(I_1 - I_2)} E_2$$

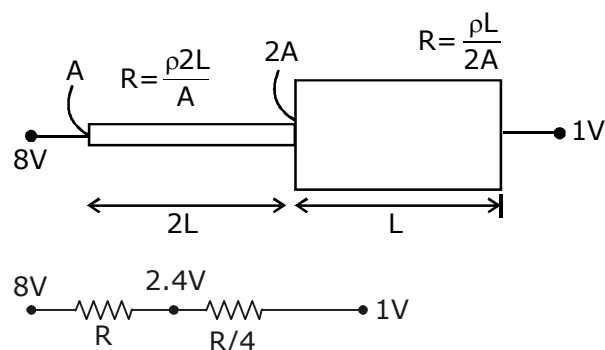
21. A**22. A**

$$i = \frac{4}{4} = 1 \text{ Amp}$$

$$V = E + ir = 2 + 1 \times 3 = 5V$$

23. B

$$\text{In b } V = E + ir$$

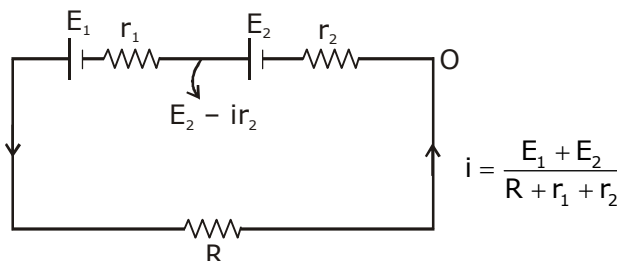24. B

So for $E_2 - ir_2 < 0$ (for increasing i)

$$E_2 - \left(\frac{E_1 + E_2}{R + r_1 + r_2} \right) r_2 < 0$$

$$\Rightarrow E_2 (R + r_1) < E_1 r_2$$

25. D

From graph $I = 0 \Rightarrow$ Open ckt.


$$V = y = E$$

When $V = 0$: $I_{\max}$

$$E = ir$$

$$y = xr$$

$$r = y/x$$

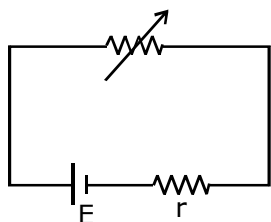
26.D

$$E - ir = V$$

$$V = E - \frac{E}{R+r} \cdot r$$

at $R = 0$

$$V = 0$$

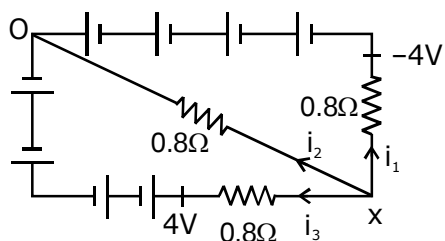27. C

$$i_1 + i_2 + i_3 = 0$$


$$\frac{x+4}{0.8} + \frac{x}{0.8} + \frac{x-4}{0.8} = 0$$

$$x = 0$$

i.e. there is no current in 0.8Ω resistor

$$i_1 = i_3 = i = \frac{4}{0.8} = 5A$$

$$\Rightarrow V = E - ir = 1 - (5)(0.2) = 0$$

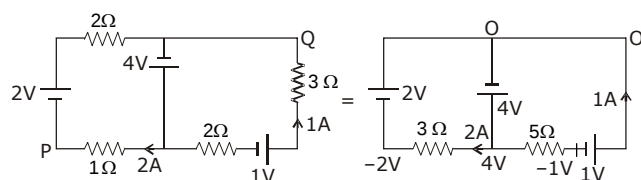28. B

$$\text{Now } V_p = +2 - 4 + V_Q$$

$$V_p - V_Q = 2V$$

29. A

From $V : IR$


$$\text{When } S_1 \text{ is closed } V_1 = \left(\frac{E}{4R} \right) 3R = \frac{3E}{4} = 0.75E$$

$$\text{When } S_2 \text{ is closed } V_2 = \frac{E}{7R} \cdot 6R = \frac{6E}{7} = 0.85E$$

When both S_1 & S_2 are closed

$$V_3 = \frac{E}{8R} \times 2R = \frac{2E}{8} = 0.25E$$

$$V_2 > V_1 > V_3$$

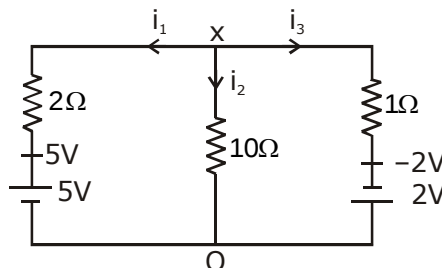
30. B

$$i_1 + i_2 + i_3 = 0$$

$$\frac{x-5}{2} + \frac{x}{10} + \frac{x+2}{1} = 0$$


$$x = \frac{5}{16}$$

$$\Rightarrow i_2 = \frac{5}{16 \times 10} = 0.03A$$

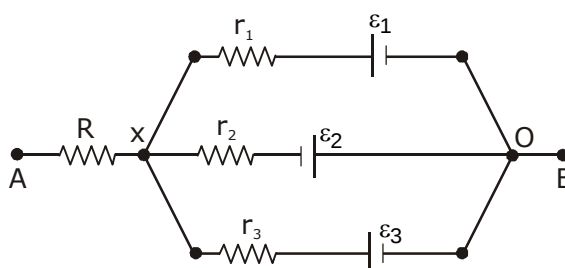31. A Theory**32. B**

$$\frac{x - \varepsilon_1}{r_1} + \frac{x - \varepsilon_2}{r_2} + \frac{x - \varepsilon_3}{r_3} = 0$$

$$x = 2 \text{ volt}$$

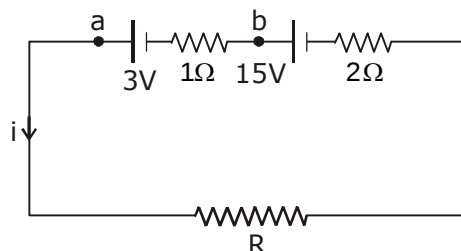33. C


$$i = \frac{18}{R+3}$$

$$V_b = -\frac{-18}{R+3} (1) + 3 + V_a$$

$$V_b - V_a = 0 = -18 + 3R + 9$$


$$\Rightarrow 3R = 9$$

$$R = 3\Omega$$

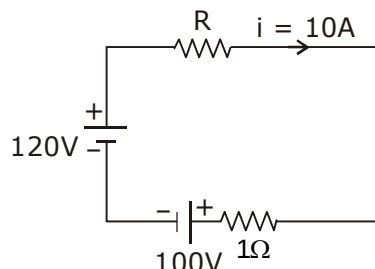34.C

$$\Rightarrow \frac{20}{R+1} = 10$$

$$R = 1\Omega$$

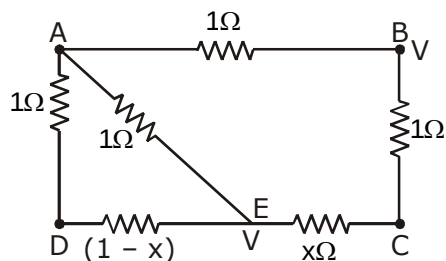35. D

$$x = \frac{(2-x)1}{3-x}, \quad x^2 - 4x + 2 = 0$$

$$x = 2 \pm \sqrt{2}$$

$$\frac{CE}{ED} = \frac{2-\sqrt{2}}{\sqrt{2}-1}$$

$$\frac{CE}{ED} = \frac{(2-\sqrt{2})(\sqrt{2}+1)}{(\sqrt{2}-1)(\sqrt{2}+1)} = \frac{2\sqrt{2}+2-2-\sqrt{2}}{1}$$

$$\frac{CE}{ED} = \sqrt{2}$$

36.D


$$V = 0.3 \times 20 = 6V$$

$$i_1 : i_1 : i_3 = \frac{1}{R_1} : \frac{1}{20} : \frac{1}{15}$$

$$= 60 : 3R_1 : 4R_1$$



$$\Rightarrow 0.3 = \frac{3R_1}{60+7R_1} \times (0.8)$$

$$\Rightarrow R_1 = 60\Omega$$

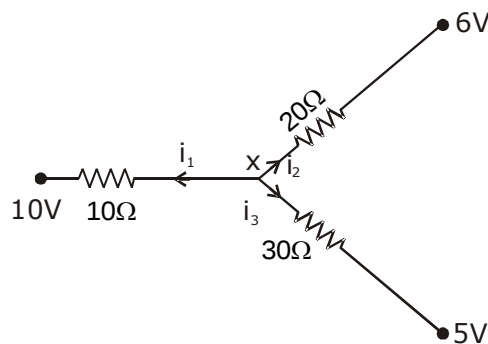37. B

$$\text{Now } \frac{x-10}{10} + \frac{x-6}{20} + \frac{x-5}{30} = 0$$

$$x = 8V, \quad i_1 = \frac{10-8}{10} = 0.2A$$

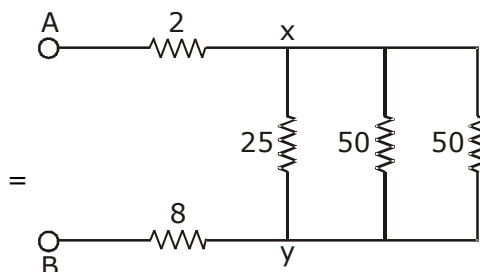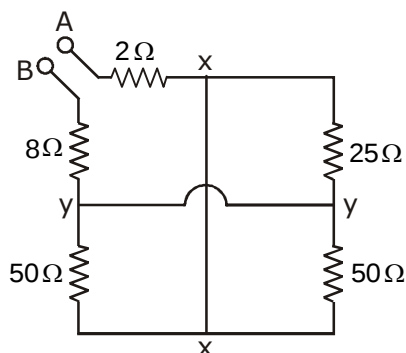
38. C**39. B**

$$R_{eq} = 2 + \frac{25}{2} + 8 = \frac{45}{2}\Omega$$

40. A $S = R + R = 2R$


$$P = \frac{R}{2}, \quad S = nP \Rightarrow 2R = \frac{nR}{2}$$

$$n = 4\Omega$$


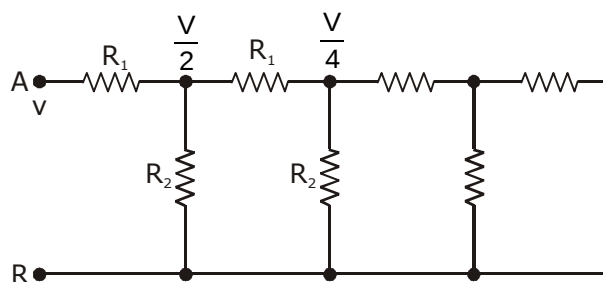
41. B

$$\frac{V}{2R_1} = \frac{V}{2R_2} + \frac{V}{4R_1}$$


$$\frac{1}{R_1} = \frac{1}{R_2} + \frac{1}{2R_1} \Rightarrow \frac{R_2}{R_1} = 2$$

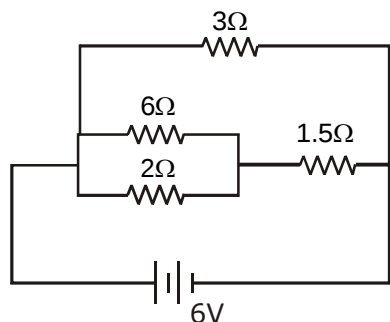42.C

$$R_{eq} = \frac{3}{2}, i = \frac{6}{\frac{3}{2}} = 4A$$

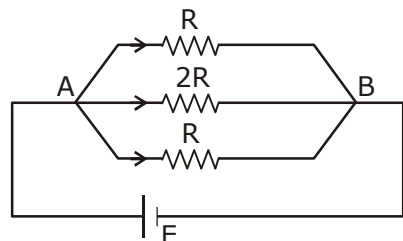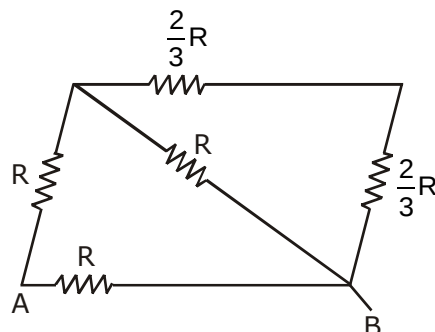43.B**44.D**

$$R_{eq} = \frac{11R}{18}$$

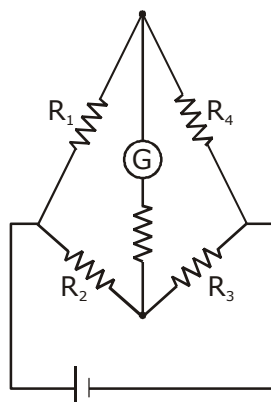45.C

For balanced condition

$$R_1 R_3 = R_4 R_2$$



(A) No effect of emf of battery

(B) $(R_1 + 10)(R_3 + 10) \neq (R_2 + 10)(R_4 + 10)$

Incorrect

(C) $(5R_1)(5R_3) = (5R_2)(5R_4)$ $R_1 R_3 = R_2 R_4$ correct.

(D)

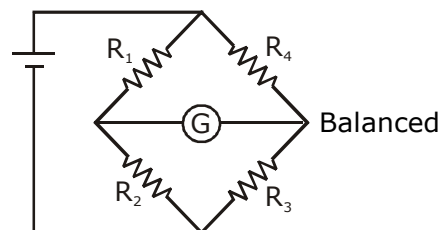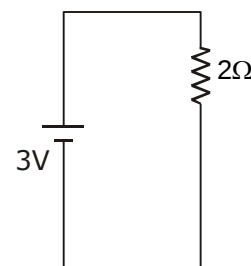**46. C**

$$i = \frac{3}{2} = 1.5A$$

47. B

625 (P) = SQ

....(1)

when P,Q is interchanged

Q(676) = PS

....(2)



From eq. (1) & (2)

$$\frac{676}{S} = \frac{S}{625}$$

$$S = 650 \Omega$$

48. D

Balanced W.S.B.

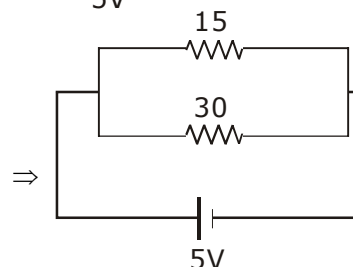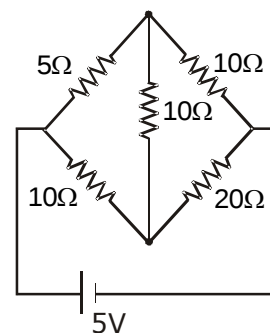


Balance W.S.B.

Req. = 10Ω


$$i = \frac{5}{10} = 0.5 \text{ A}$$

49.D

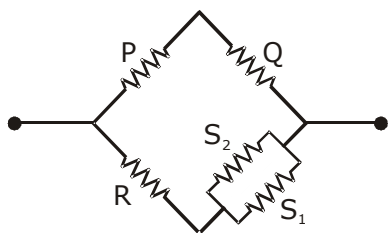

$$P \left[\frac{S_1 S_2}{S_1 + S_2} \right] = RQ$$


50. B

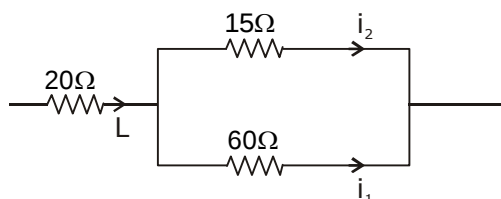

$$\text{Given } \frac{15 \times i}{75} = 0.75$$



$$\text{Now } i_2 = \frac{60 \times i}{75} = \left[\frac{60 \times 0.75 \times 75}{15} \right] = 3 \text{ A}$$

51.[B]

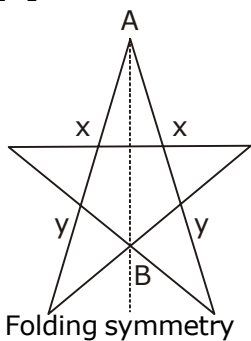


Folding symmetry

52. B

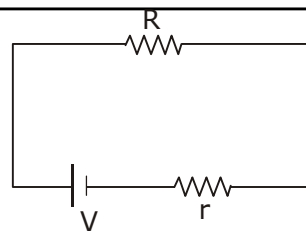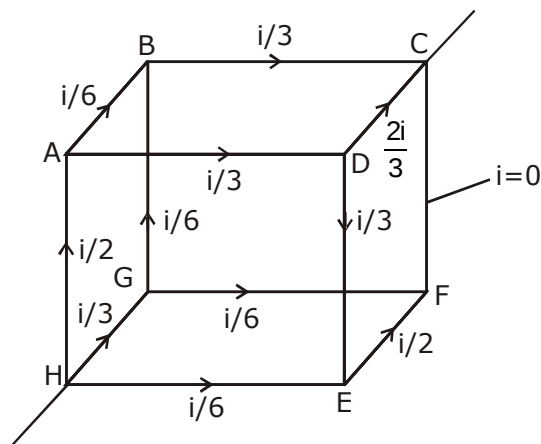


$$i = \frac{V}{R+r}$$

54.B

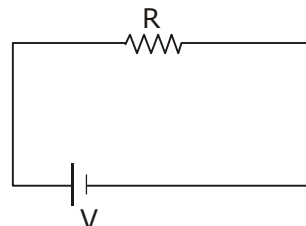

$$\text{Initially } H = \frac{V^2}{R}$$

Now after cutting

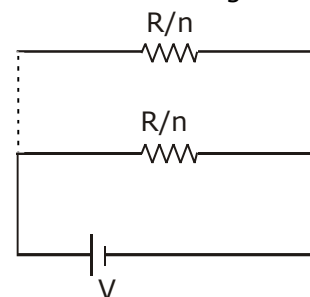

Power in one branch

$$= \frac{V^2}{R/n} = \frac{nV^2}{R}$$

$$\text{Total power} = \frac{nV^2}{R} + \frac{nV^2}{R} + \dots = \frac{n^2 V^2}{R}$$

55. B

$$H = \frac{V^2}{R} \Delta t, \text{ \& } R = \frac{\rho \ell}{A}$$

56. C

$$R = \frac{V_{\text{rated}}^2}{P_{\text{rated}}} \Rightarrow R \propto V_{\text{rated}}^2$$

 $\therefore$ In series I is same.


$$\text{Power} = I^2 R \propto V_{\text{rated}}^2$$

$$57. \text{ B } P_1 = \frac{(220)^2}{R}$$

$$P_2 = \frac{(220)^2}{R/2} + \frac{(220)^2}{R/2}$$

$$P_2 = \frac{4(220)^2}{R}$$

$$\frac{P_2}{P_1} = 4$$

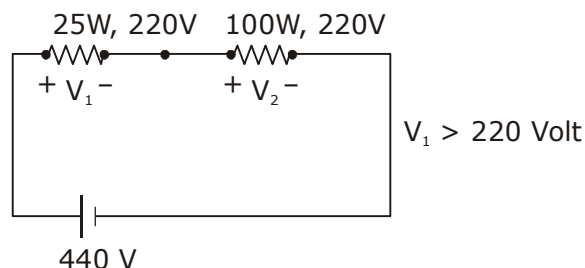58. A**59. C**

$$P = V \cdot i, P = E \cdot \ell \cdot JA$$

$$\frac{P}{\ell A} = EJ$$

60. A

$$i = \frac{dQ}{dt} = 2 - 16t$$

$$\text{Heat} = R \int_0^{1/8} (2 - 16t)^2 dt$$

$$\mathbf{61. B} \quad P = \frac{V^2}{R} \quad R = \frac{\rho \ell}{A}$$


$$P' = \frac{V^2}{0.9R} \quad R' = \frac{\rho(\ell - 0.1\ell)}{A}$$

$$P' = \frac{1.11V^2}{R} = 0.9 \frac{\rho \ell}{A}$$

$$R' = \frac{0.9\rho \ell}{A}$$

62. D

$$R_A = \frac{(200)^2}{300}$$

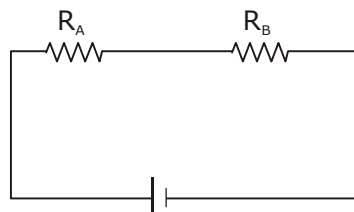


200 V D.C.

$$R_B = \frac{(200)^2}{600}$$

$$R_{eq} = R_A + R_B, P = \frac{(200)^2}{\frac{(200)^2}{300} + \frac{(200)^2}{600}}$$

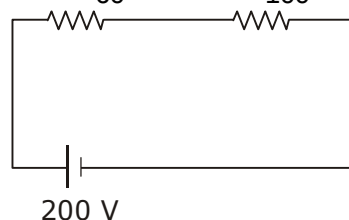63. [A]

$$R_1 = \frac{(200)^2}{60} \quad R_2 = \frac{(200)^2}{100}$$




$$P = \frac{(200)^2}{R_{eq}}$$


$$= \frac{(200)^2}{(200)^2 \left[\frac{1}{60} + \frac{1}{100} \right]} = 37.5 \text{ W}$$

64. A

$$R = (120)^2 / 60$$

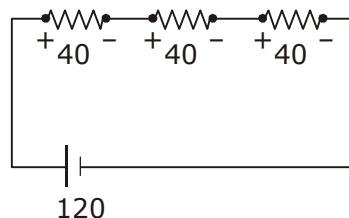


$$P = \frac{(40)^2}{(120)^2} \times 60, = 6.7 \text{ Watt}$$

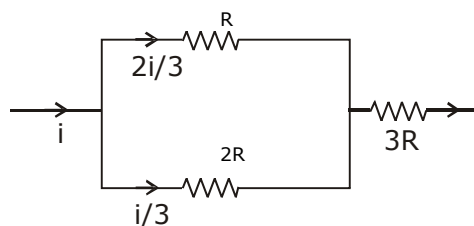65. D**66. B**

$$\text{Given } \frac{(15)^2}{R} + \frac{(15)^2}{2} = 150$$

$$\Rightarrow \frac{1}{R} + \frac{1}{2} = \frac{10}{15}, \quad \frac{1}{R} = \frac{1}{6} \Rightarrow R = 6\Omega$$

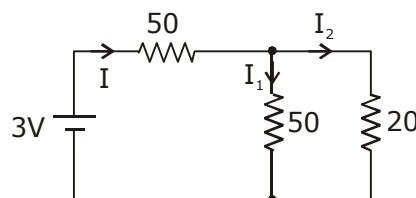67. A
 $I^2 R$ is maximum for R_1 resistance As $I > I_1$ & I_2


68. A

$$i = At + B$$

$$\text{at } t = \Delta T, i = 0$$

$$\Rightarrow 0 = A\Delta T + B$$

$$\Rightarrow A\Delta T = -B$$

$$q = \int_0^{\Delta T} dq = \int_0^{\Delta T} (At - A\Delta T) dt$$

$$\Rightarrow q = \frac{A\Delta T^2}{2} - B\Delta T$$

$$\Rightarrow q = -\frac{A\Delta T^2}{2} \Rightarrow A = \frac{-2q}{\Delta T^2}$$

$$\text{Heat} = \int_0^{\Delta T} i^2 R dt = \int_0^{\Delta T} \left(\frac{-2qt}{\Delta T^2} + \frac{2q}{\Delta T} \right)^2 R dt$$

$$= \frac{4q^2}{\Delta T^2} \int_0^{\Delta T} \left(1 - \frac{t}{\Delta T} \right)^2 R dt$$


$$= \frac{4q^2}{\Delta T^2} \left[\Delta T + \frac{(\Delta T)^3}{3(\Delta T)^2} - \frac{2(\Delta T)^2}{2\Delta T} \right] R = \frac{4q^2 R}{3\Delta T}$$

69. B

$$P = V.I \quad V \propto I^2$$

70. B


As R_{eq} decreases I_{net} increases hence current through X increases but as I_{net} will now be distributed in Y & Z, current in Y decreases.

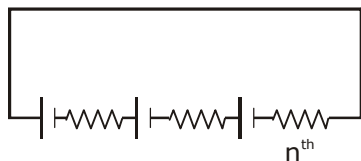71. D

$$i = \frac{nE}{nr} = \frac{E}{r}$$


Independent of n

$$\mathbf{72. A} \quad i = \frac{E}{r/n} = \frac{nE}{r}$$

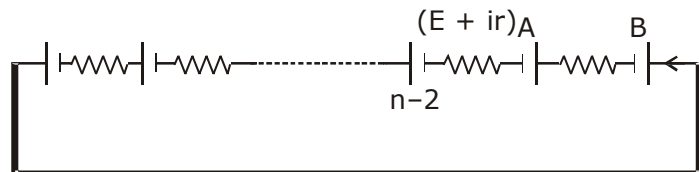73. D

$$E_{eq} = (n-4) \cdot E \quad r_{eq} = nr$$

$$i = \frac{(n-4)E}{nr} \quad \left[E + \frac{(n-4)E}{nr} \cdot r \right] = 2E \left(1 - \frac{2}{n} \right)$$

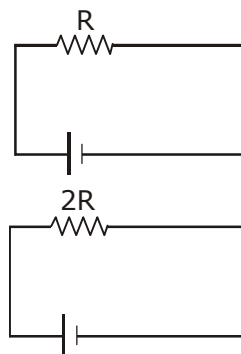74. B

$$L \rightarrow R$$

$$2L \rightarrow 2R$$

$$\Delta Q' = 2\Delta Q$$

to raise ΔT temperature in same time t.

$$I'^2 R' \Delta t = 2I^2 R \Delta T$$

$$I'^2 (2R) \Delta T = 2I^2 R \Delta T$$

$$\Rightarrow I' = I$$

$$\frac{nE}{2R} = \frac{3E}{R} \Rightarrow n = 6$$

75. D

From Maximum Power Transfer Theorem




$$Y_{max} = R + 2\Omega$$

$$\Rightarrow 5\Omega = R + 2\Omega$$

$$\Rightarrow R = 3\Omega$$

76. C

High resistance in series

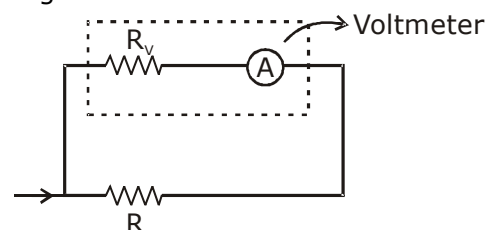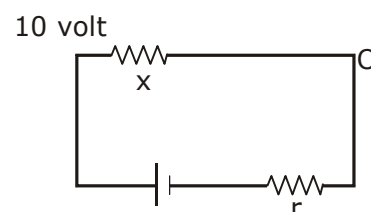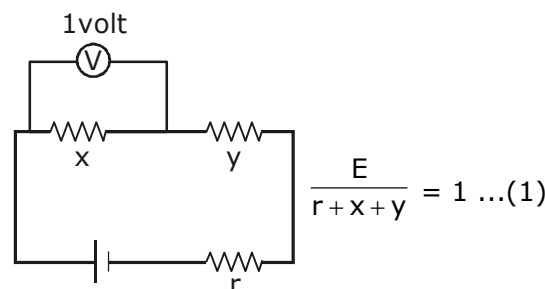**77. C**

$$E - \frac{Er}{x+r} = 10 \text{ volt}$$


$$\frac{Ex}{x+r} = 10 \text{ volt} \quad \dots(2)$$

$$\frac{Ex}{r+x+y} = 1 \text{ volt} \quad \dots(3)$$

$$\Rightarrow x = 1\Omega$$

$$\frac{12+1}{1+r} = 10$$

$$\Rightarrow r = 0.2\Omega$$

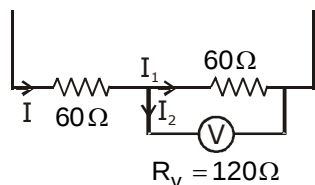78. A

Net current

$$I = \frac{120}{60+40} = 1.2\text{A}$$

$$I_1 : I_2 = \frac{1}{60} : \frac{1}{120} \\ = 2 : 1$$

$$I_1 = \frac{2}{3} \times 1.2 = 0.8 \text{ Amp.}$$


hence Reading $V = 0.8 \times 60 = 48 \text{ V}$ **79. D**

$$\frac{i}{2} R_g = \frac{i}{2} (20) \Rightarrow R_g = 20$$

80. B

$$i_g = \frac{0.2}{20} = 0.01 \text{ Ampere}$$


$$i = i_g \left(1 + \frac{r_2}{R} \right) \Rightarrow 10 = 0.01 \left(1 + \frac{20}{R} \right) \\ R \approx 0.02$$

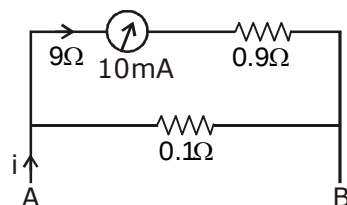81. C

$$10 \times 10^{-3} = \frac{0.1}{10} \times i \Rightarrow i = 1 \text{ Ampere}$$



82. C

$$i_g = 10 \times 10^{-3}$$

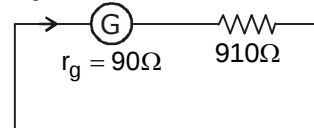


$$V = i_g (R + r_g) \\ V = 10^{-2} (1000) \\ = 10 \text{ Volt}$$


$$n = \frac{10}{0.1} = 100$$

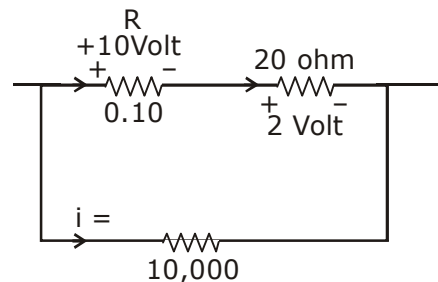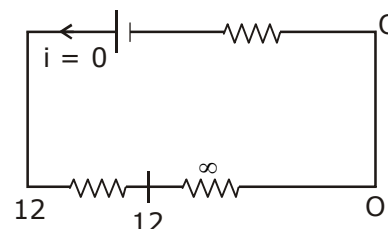83. D**84. D****85. B**


Voltmeter must be connected in parallel and Ammeter in series with the resistance in circuit.

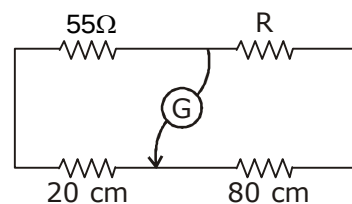86. A

$$\Rightarrow R(20) = 55(80) \\ R = 220 \Omega$$

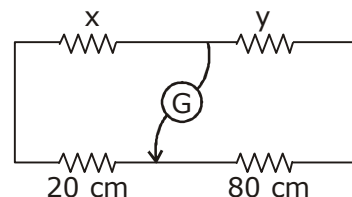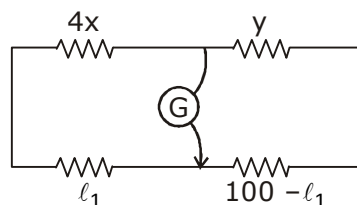87. A

$$x(80) = y(20) \\ 4x = y \\ \text{when } 4x \text{ \& } y$$



$$4x(100 - l_1) = y l_1$$

$$l_1 = \frac{100}{2} = 50 \text{ cm}$$

88. A

$$R_1 \times 60 = R_2 \times 40 \quad \dots(1)$$

$$R_1 \times 50 = \frac{R_2 \times 10}{R_2 + 10} \times 50 \quad \dots(2)$$

89. A

$$\text{Potential gradient } x = \frac{6}{1}$$

$$6l = 4 \Rightarrow l = \frac{2}{3} \text{ m}$$

90. B

$$12 \times (100 - x) = 18 + x$$

$$1200 - 12x = 18 + x$$


$$30x = 1200$$

$$x = 40 \text{ cm}$$

$$12 \times (100 - x) = 8x$$


$$1200 - 12x = 8x$$

$$\Rightarrow x = 60 \text{ cm}$$

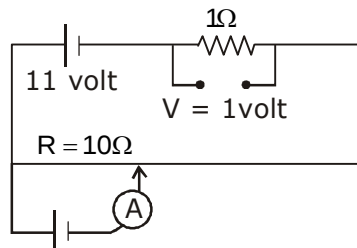91. B

$$I = \frac{11}{10+1} = 1 \text{ Amp}$$


$$x = \frac{11-1}{10} = \frac{1 \text{ volt}}{\text{m}}$$

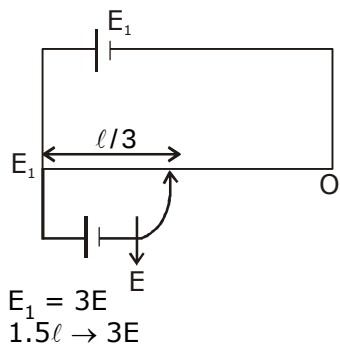92. B

$$E_1 = 3E$$

$$1.5l \rightarrow 3E$$


$$E \rightarrow \frac{l}{2}$$

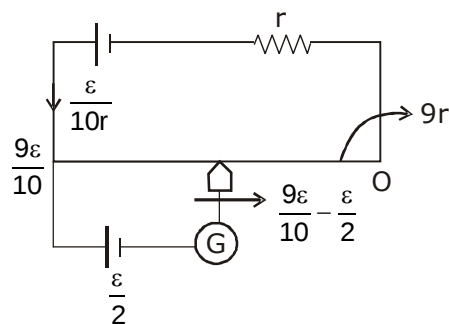93. B

$$L \rightarrow \frac{9\epsilon}{10}$$

$$I \rightarrow \frac{10L}{9\epsilon}$$


$$\Rightarrow \frac{\epsilon}{2} \rightarrow \frac{5L}{9}$$

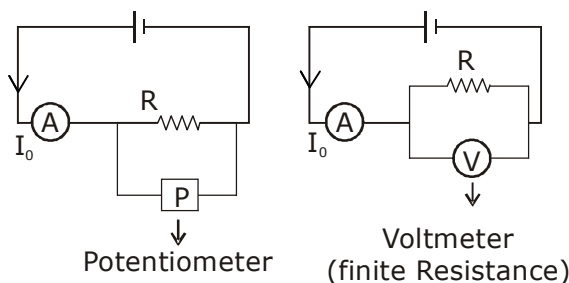94. A

In case of voltmeter $R_{eq} < R$ hence


$$I > I_0$$

As voltmeter always take some current from the circuit $V < V_0$

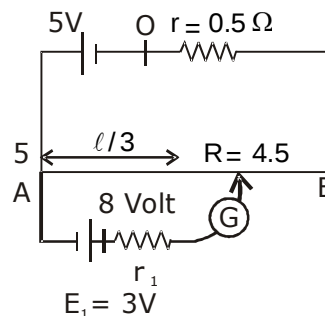95. D

As Battery is connected in reverse order E_1 will not be balanced on entire length of wire AB.

96. C

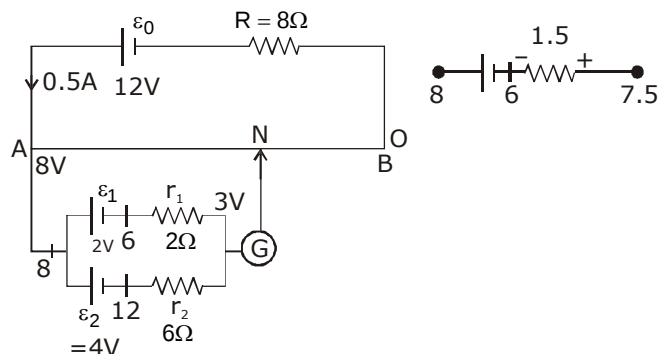


$$8 \rightarrow 4m$$

$$1m \rightarrow 2 \text{ Volt}$$

$$1 \text{ Volt} \rightarrow 0.5 m$$

$$0.5 \text{ volt} \rightarrow 25 \text{ cm}$$


97. B

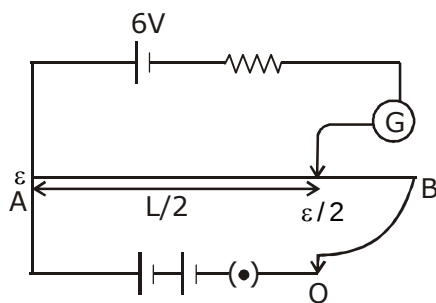S₂ is open

$$\frac{\varepsilon}{2} = 6V \quad \varepsilon = 12V$$

$$\ell \rightarrow 12V$$
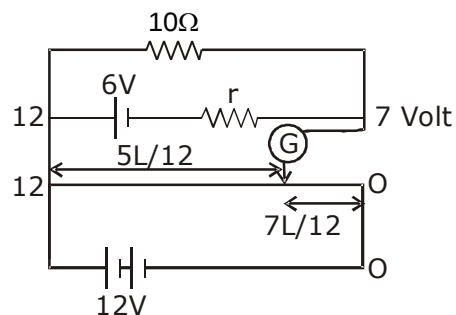
$$\frac{7\ell}{12} \rightarrow 7 \text{ volt}$$



$$6 - ir = 5$$

$$6 - \frac{6}{10+r} r = 5$$

$$\Rightarrow 6r = 10 + r \Rightarrow r = 2\Omega$$

$$98. \text{ S-1 } E = \frac{V}{\ell} = \frac{iR}{\ell}$$


$$\text{and } R = \frac{\rho \ell}{A}$$

S-2 in series, current is same.

$$99. V = E - ir \text{ discharging}$$

$$V = E + ir \text{ charging}$$
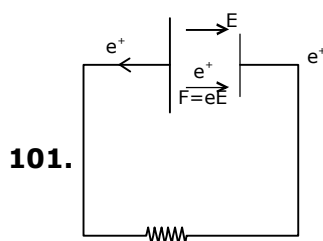
$$100. H = i^2 R t \Rightarrow T \uparrow R \uparrow$$



101.

Work done = -ve

$$102. T \uparrow \rho \uparrow$$

$$\sigma = \frac{1}{\rho} \downarrow$$