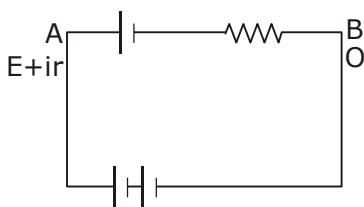
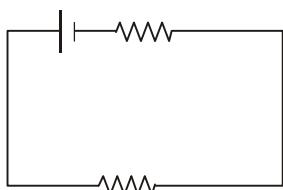
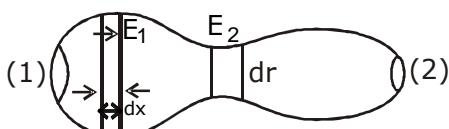


**EXERCISE – II****MULTIPLE CHOICE QUESTIONS****1. A,B,C****2. A**

$$V = E - ir$$

- r = Slope  
**3. D**  $i = neAV_d$

$$V = iR$$

**4. A,B,C,D**

$$i = neAV_d$$

$$R = \frac{\rho l}{A}$$

$$E_1 = \frac{V}{dx} \Rightarrow = \frac{iR}{dx} = \frac{i\rho dx}{A \cdot dx}$$

$$= \frac{i\rho}{A} \Rightarrow E_1 \propto \frac{1}{A}$$

$$P = i^2 R \Rightarrow i^2 \frac{\rho dx}{A}$$


**5. [A,D]**

$$i = neAV_d \Rightarrow dq = neAV_d \cdot dt$$

↓  
 is fixed.

**6. C** In parallel resistance ↓ ∴ i ↑**7. A,C,D**

In parallel resistance ↓ ∴ i ↑

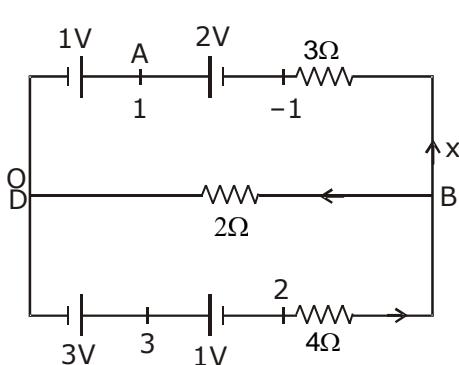


$$\frac{x}{2} + \frac{x-2}{4} + \frac{x+1}{3} = 0$$


$$\frac{6x + 3x - 6 + 4x + 4}{12} = 0$$

$$\Rightarrow 13x = 2$$

$$x = \frac{2}{13} \text{ volt}$$

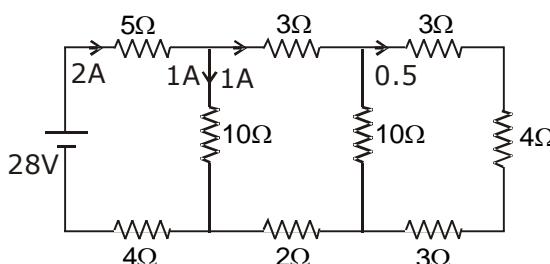**8. A**

**9. C** In parallel combination equivalent resistance  $R_{eq}$  is less than the minimum value of any of resistance  $R_1 < R$   
 In series  $R_{eq}$  is greater than maximum of resistance.  $R_2 > R$ .

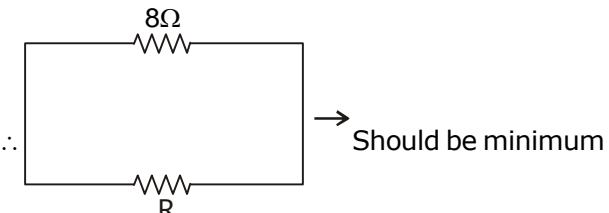**10. A,C**Current should be maximum in  $2\Omega$ 

$$\Rightarrow R = 0 \\ \text{Power} = 72 \text{ watt.}$$


**11. A,C**

$$\left. \begin{array}{l} R_1 = \frac{V}{I} = \frac{10V}{10mA} = 1k\Omega \\ R_2 = \frac{220V}{50mA} = 4.4k\Omega \end{array} \right\} \Rightarrow (\text{A}) \text{ and } (\text{C})$$

**12. D**  $r = i_g (R + r_g)$ **13. A,D**

To ensure maximum current through ammeter its resistance should be small.

To ensure minimum current through voltmeter its resistance must be very large.

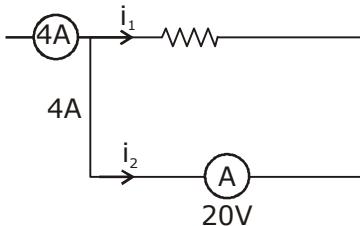**14.C**

$$R = \frac{V}{i}$$

$$i_1 < 4A$$

$$20 = i_1 R$$

$$R = \frac{20}{i_1} > 5\Omega$$

**15. B,C**

$$i = i_g \left( 1 + \frac{r_g}{R} \right)$$

$$V = i_g (r + R_g)$$

**16. A,C,D**


If devices are ideal then  $R_v = \infty$  so  $i = 0$

$$R_A = 0$$

So (A)

(C)

(D) ∵ Current through ammeter and voltmeter will be high.

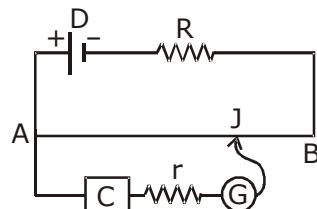**17. A**

(A) Zero deflection does not depend on  $r$

(B) If  $R > R_0$  then drop across potentiometer is negligible

∴ We will not get zero deflection


(C) Notes

(D) Notes

**18. A,B**

As emf of  $E_1$  is distributed over the wire AB. Hence A is correct  $E_2$  is balanced by fraction of length of wire  $E_1 > E_2$ .

We only balance potential difference hence B is correct.

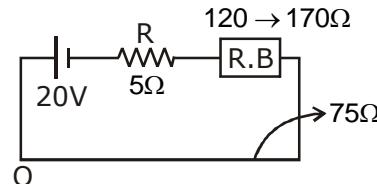**19. A,B,C**

$$V_{\max} = \frac{20 \times 75}{200} = 7.5 \text{ volt}$$

A, B, C

**20. A,C**

In parallel each will take 10A and hence combination requires  $10 + 10 = 20 \text{ A}$

In series current will be same in each fuse and that will be equal to required circuit current hence combination requires the same current 10 A