
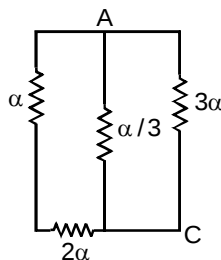


EXERCISE – IV**TOUGH SUBJECTIVE PROBLEMS**

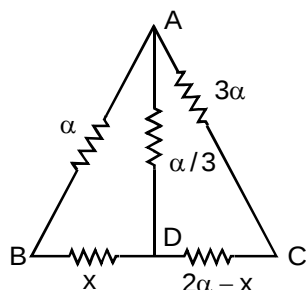1. Now

$$R_{eq} = \frac{1}{\alpha + x} + \frac{3}{\alpha} + \frac{1}{5\alpha - x}$$

$$\Rightarrow \frac{d}{dx} \left(\frac{1}{R_{eq}} \right) = 0 \text{ for } (R_{eq})_{max}$$



$$\Rightarrow \frac{1}{(5\alpha - x)^2} - \frac{1}{(\alpha - x)^2} = 0$$


$$\Rightarrow x = 2\alpha$$

$$\text{Now circuit is } R_{eq} = \left(\frac{3}{11} \right) \alpha$$

2. A
(a) from $I = JA$

$$\int_0^I dl = \int_0^R I_0 \left(1 - \frac{r}{R} \right) 2\pi r dr$$

$$I = \frac{\pi J_0 R^2}{3}$$

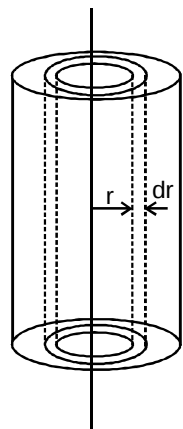


$$I = \frac{J_0 A}{3}$$

$$(b) \int_0^I dl = \int_0^R \frac{J_0 r}{R} \cdot 2\pi r dr$$


$$I = \frac{2\pi J_0}{R} \left(\frac{R^3}{3} \right) = \frac{2}{3} \pi J_0 R^2 \Rightarrow I = \frac{2J_0 A}{3}$$

3. Case - I

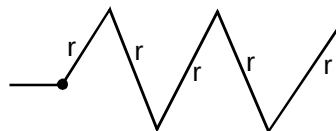

$$R_1 = 5r$$

Case - II

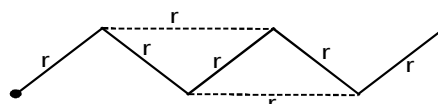

$$R_2 = r + (2r \parallel 2r) + r = 3r \text{ (with the help of W.S.B)}$$

$$\therefore \frac{R_2}{R_1} = \frac{3}{5}$$

4. (a) $0.44 = 0.2 V^{5/2}$


$$\Rightarrow V^{5/2} = 2.2$$

...(1)

$$6 - V = 0.44 R$$

...(2)

Solving (1) & (2), we get

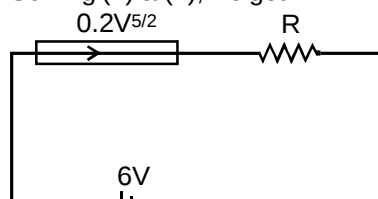

$$R = 10.52 \Omega$$

$$(b) 0.2 V^{5/2} \times V = 2 \times (0.2 V^{5/2})^2 R$$

$$0.2 V^{7/2} = 0.08 V^5 R$$

$$1 = 0.4 V^{3/2} R$$

$$6 - V = 0.2 V^{5/2} R$$

$$6 = V(1.5)$$

$$V = 4V$$

$$\Rightarrow R = \frac{1}{3.2} = 0.3125$$

5. Given circuit is


Applying KVL :


$$2r I_1 + I_3 r - I_2 r = 0$$

$$\Rightarrow 2I_1 + I_3 - I_2 = 0$$

...(1)
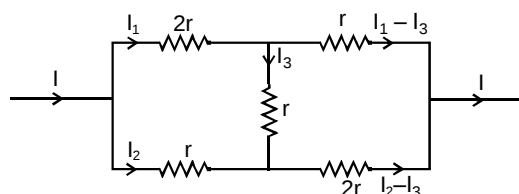
$$(I_1 - I_3) r - (I_2 + I_3) 2r - I_3 r = 0$$



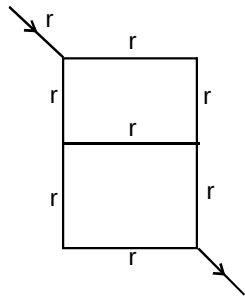

$$\Rightarrow I_1 - 2I_2 - 4I_3 = 0 \quad \dots(2)$$

Solving (1) & (2), we get

$$I_2 = -3I_3, 4I_1 = -2I_3$$


$$I = I_1 + I_2 = -5I_3 \Rightarrow \frac{I_3}{I} = \frac{1}{5}$$

6. (i)

$$\left[1 - \frac{1}{K}\right] \frac{V_0}{R_1} = \frac{V_0}{KR_2} + \frac{V_0}{KR_1} \left[1 - \frac{1}{K}\right]$$

$$\frac{K-1}{R_1} = \frac{1}{R_2} + \frac{K-1}{KR_1}$$
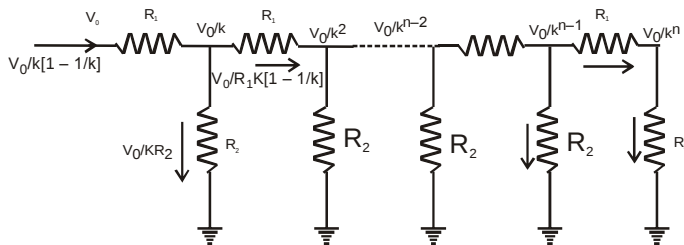
$$\frac{K-1}{R_1} \left[1 - \frac{1}{K}\right] = \frac{1}{R_2}$$



$$\frac{R_1}{R_2} = \frac{(K-1)^2}{K}$$

Now from again apply KCL

$$\left[\frac{V_0}{k^{n-2}} - \frac{V_0}{k^{n-1}} \right] \frac{1}{R_1} = \frac{V_0}{k^{n-1}R_2} + \frac{V_0}{k^n R_3}$$

$$\Rightarrow \frac{k^2 - k}{R_1} = \frac{k}{R_2} + \frac{1}{R_3}$$

$$\frac{R_2}{R_1} K(K-1) = K + \frac{R_2}{R_3} \Rightarrow \frac{R_2}{R_3} = \frac{K}{K-1}$$

$$(ii) \quad i = \frac{V_0}{KR_2} = \frac{V_0(K-1)}{K^2 R_3} = \frac{V_0}{R_3} \frac{K-1}{K^2}$$

7. Power given to turbines is x



$\Rightarrow 90\%$ of $x = 40$ W

$$x = \frac{400}{9} \text{ W}, mgh = \frac{400}{9} \Rightarrow m = \frac{4}{9} \text{ kg/sec.}$$



$$t = \frac{200}{4} \times 9 = 450 \text{ sec.}$$

8. (a) When switch is open

$$i = \frac{36}{9/2} = 8 \text{ A}$$

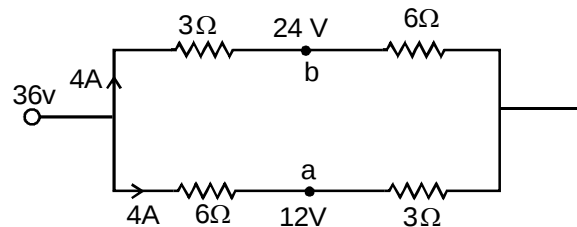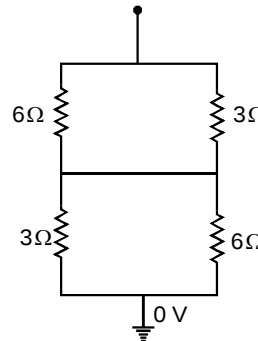

$$v_b - v_a = 12 \text{ V}$$

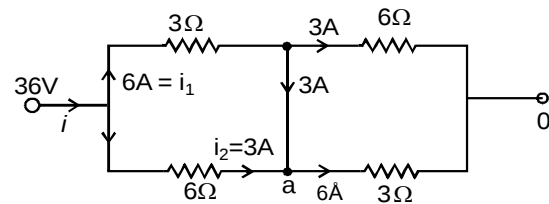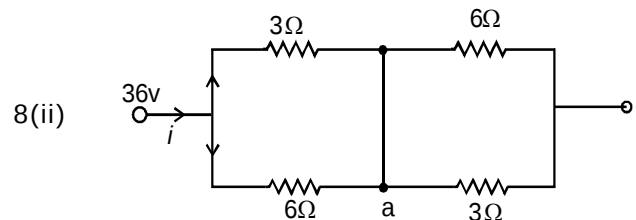


$$i = \frac{36}{4} = 9 \text{ A}$$

9. Let us assume each wire have cross sectional area is A and square of length ℓ then


$$R = \frac{\rho \ell}{A}$$

$$P_{AB} = \frac{V^2}{R}$$

for power in DC

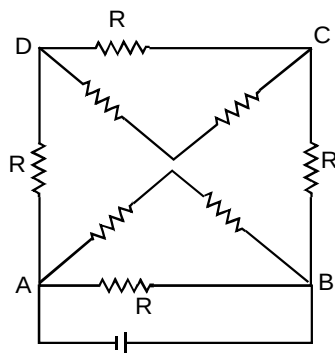
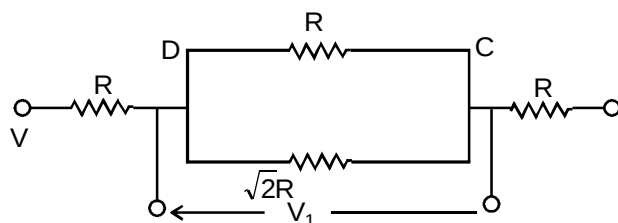
$$V_1 = \frac{V \left(\frac{R\sqrt{2}}{\sqrt{2}+1} \right)}{\frac{R\sqrt{2}}{\sqrt{2}+1} + 2R} = \frac{V\sqrt{2}}{3\sqrt{2}+2}, \quad P_{DC} = \frac{V_1^2}{R}$$




$$\frac{P_{AB}}{P_{DC}} = \frac{(3\sqrt{2}+2)^2}{2} = 11 + 6\sqrt{2}$$

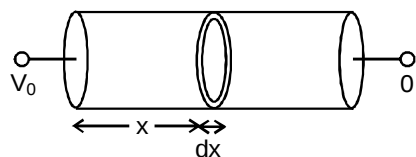10. Given $\rho = \rho_0 e^{-x/L}$

$$(a) dR = \frac{\rho_0 e^{-x/L} dx}{A}$$

$$R = \frac{1}{A} \int_0^L \rho_0 e^{-x/L} dx = \frac{-L\rho_0}{A} [e^{-x/L}]_0^L$$



$$R = \frac{\rho_0 L}{A} \left[1 - \frac{1}{e} \right] \Rightarrow i = \frac{V}{R} = \frac{V_0 A}{\rho_0 L} \left(\frac{e}{e-1} \right)$$

$$(b) V(x) = I R(x)$$

$$\int_{V_0}^{V_x} dv = \frac{V_0 A}{\rho_0 L} \left(\frac{e}{e-1} \right) \frac{\rho_0}{A} \int_0^x e^{-x/L} dx$$

$$\Rightarrow V_x - V_0 = \frac{V_0}{L} \left(\frac{e}{e-1} \right) \left(\frac{-L}{1} \right) [e^{-x/L}]_0^x$$


$$V_x - V_0 = \frac{V_0 e}{(1-e)} [e^{-x/L} - 1]$$

$$\Rightarrow V_x = V_0 \left[\frac{(e^{-x/L} - 1)}{(1-e^{-1})} + 1 \right] \Rightarrow V_x = V_0 \left[\frac{e^{-x/L} - e^{-1}}{1-e^{-1}} \right]$$

11. Resistance of potentiometer wire = $11.5 \times 10 = 115$
Current in the circuit


$$i = \frac{2}{115} \text{ A}$$

Now cell is balanced at 6.9 m

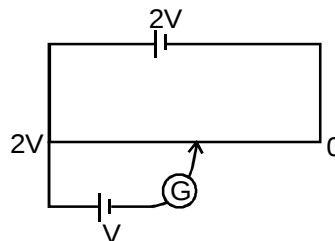

$$\text{So } (6.9 \times 11.5) = V, \quad V = 6.9 \times 11.5 \times \frac{2}{115} = 1.38 \text{ V}$$

after 5Ω is also connected then



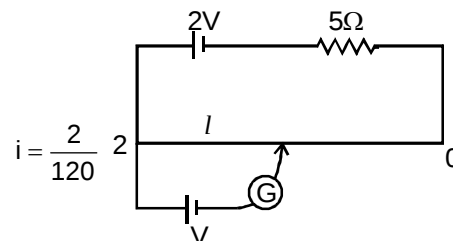


At Balanced cond.

$$i (\ell \times 11.5) = 1.38$$

$$\ell = 7.2 \text{ m}$$

- 12.

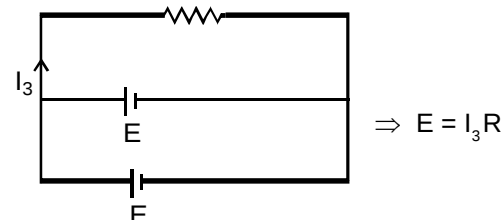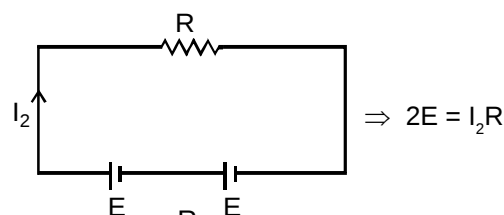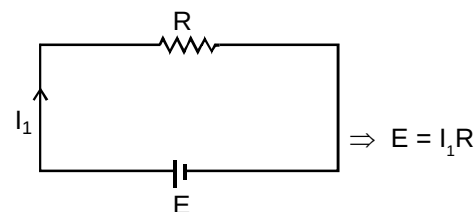


$$\text{Now } 3I_3 I_2 = \frac{6E^2}{R^2}, \quad 2I_1(I_2 + I_3) = \frac{6E^2}{R^2}$$

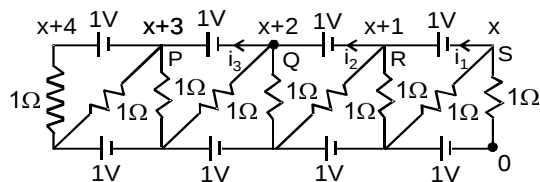13. KCL at point P, Q, R, S then find out

$$9x = 4 \Rightarrow x = \frac{4}{9}$$

$$\Rightarrow V_B - 1 - 1 - \frac{4}{9} = V_A$$



$$V_A - V_B = -\frac{22}{9} \text{ volt}$$

$$14. \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\Rightarrow \frac{1}{R_{eq}(1+\alpha_{eff})} = \frac{1}{R(1+\alpha t)} + \frac{1}{3R(1+2\alpha t)} \Rightarrow R_{eq} = \frac{3R}{4}$$

$$\frac{4}{3(1+\alpha_{eff}t)} = \frac{1}{(1+\alpha t)} + \frac{1}{3(1+2\alpha t)}$$


$$\Rightarrow \frac{4}{3}(1-\alpha_{eff}t) = (1-\alpha t) + \frac{1}{3}(1-2\alpha t)$$

$$\frac{4}{3}(1-\alpha_{eff}t) = \frac{3-3\alpha t+1-2\alpha t}{3}$$

$$\Rightarrow 4-4\alpha_{eff}t = 4-5\alpha t, \alpha_{eff} = \frac{5}{4}\alpha$$

$$15. \text{Current sensitivity} = \frac{300}{50} = 6 \text{ mA/div.}$$
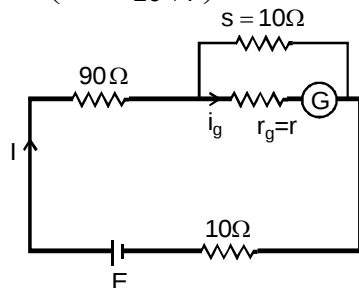
$$I = \left(\frac{E}{100 + \frac{10r}{10+r}} \right) \text{ Amp.}$$



$$i_g = \frac{10I}{(10+r)} = \frac{10}{(10+r)} \left[\frac{E}{100 + \frac{10r}{10+r}} \right]$$

$$\text{In this situation } i_g = 9 \times 6 = 54 \text{ mA}$$

$$\Rightarrow 54 \times 10^{-3} = \frac{10E}{(10+r) \left[100 + \frac{10r}{10+r} \right]} \quad \dots(1)$$

$$\text{Similarly } 30 \times 6 \times 10^{-3} = \frac{50E}{(50+r) \left[100 + \frac{50r}{50+r} \right]} \quad \dots(2)$$

from eq. (1) & (2)

$$r = 233.33 \Omega$$

$$E = 144 \text{ V}$$

$$16. (a) i = \frac{10}{10} = 1 \text{ A} \quad \text{Now}$$

$$\left(\frac{9}{12} \right) L(1) = 4.5 \Rightarrow L = 6 \text{ m}$$

$$(b) \text{ Now } i = \frac{10}{20} = 0.5 \text{ A}$$

So at balancing condn.

$$V = \frac{1}{2} \times 6 = 3 \text{ V} \Rightarrow 4.5 - \left(\frac{4.5}{2+r} \right) r = 3 \Rightarrow r = 1 \Omega$$

$$17. \text{ For ammeter } 99 I_g = (I - I_g) 1$$


$$\text{or } I = 100 I_g$$

...(i)

I_g is the full scale deflection current of the galvanometer and I the range of ammeter.

For the circuit in figure-1, given in the question
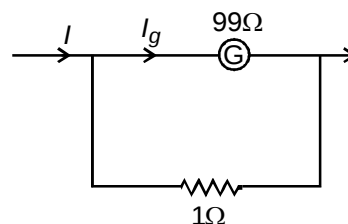
$$\frac{12 \text{ V}}{2+r + \frac{99 \times 1}{99+1}} = 3 \text{ A} \Rightarrow r = 1.01 \Omega$$



For voltmeter, range


$$V = I_g (99 + 101)$$

$$V = 200 I_g$$

Also resistance of the voltmeter = $99 + 101 = 200 \Omega$.

In figure - 2 resistance across the terminals of the battery.
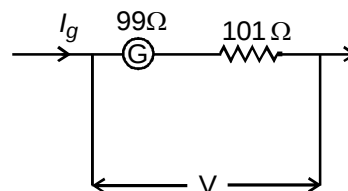
$$R_1 = r + \frac{200 \times 2}{200 + 2} = 2.99 \Omega$$



$$\therefore \text{Current drawn from the battery, } I_1 = \frac{12}{2.99} = 4.01 \text{ A}$$

$$\therefore \text{Voltmeter reading } \frac{4}{5} V = 12 - I_1 r = 12 - 4.01 \times 1.01$$

$$\Rightarrow V = 7.96 \times \frac{5}{4} = 9.95 \text{ volt}$$

$$\text{Using (ii), } I_g = \frac{9.95}{200} = 0.05 \text{ A}$$

$$\text{Using (i) range of the ammeter } I = 100 I_g = 5 \text{ A}$$