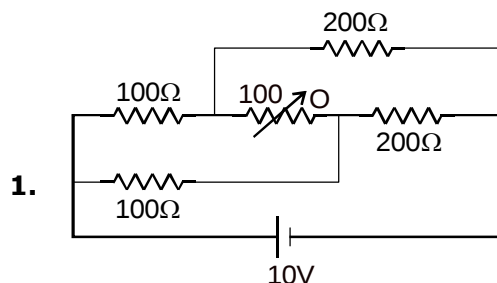


EXERCISE – V**JEE QUESTIONS**


Wheat stone bridge

2. (i) $I = \frac{\Delta Q}{\Delta t}$ remains constant.

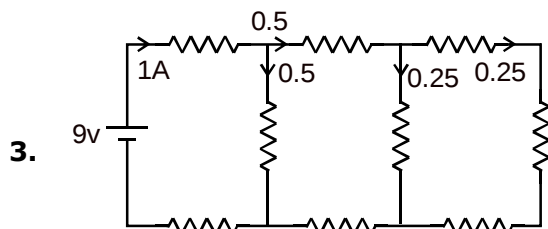
(ii) $R = \frac{\rho \ell}{A} \Rightarrow Q = \frac{RA}{\ell}$

$\sigma = \frac{1}{\rho} = \frac{\ell}{AR} = \frac{[L]}{[L^2][ML^{-2}T^{-3}A^{-2}]}$
 $= [M^{-1}L^{-3}T^3A^2]$


Notes $\frac{V_1 r_2 + V_2 r_1}{r_1 + r_2}$, $\frac{r_1 r_2}{r_1 + r_2}$



4. Wheat stone bridge is balanced.


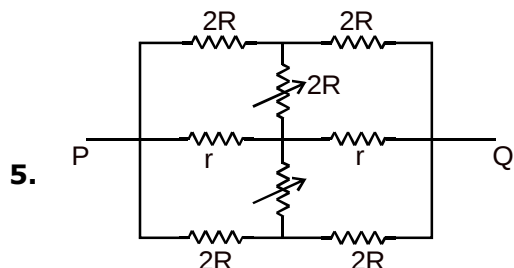


Symmetric circuit

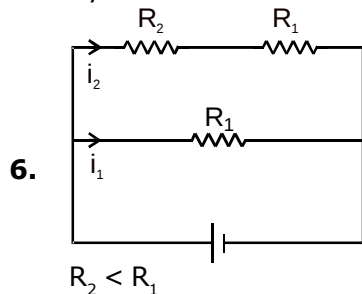

$R_2 < R_1$

7. $i_1 > i_2$
 (a) No

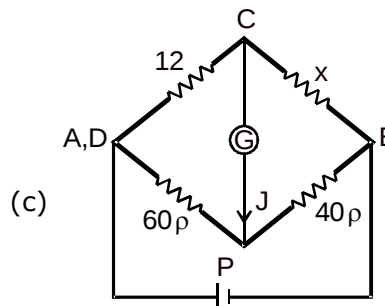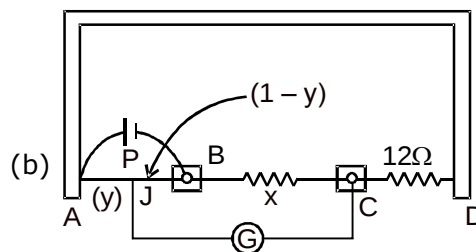

8Ω

In balance condition


$12 \times 40 \rho = x \times 60 \rho$

$x = 8\Omega$

8. For power maximum

$\Rightarrow r_{\max}$
 $P = i^2 r$

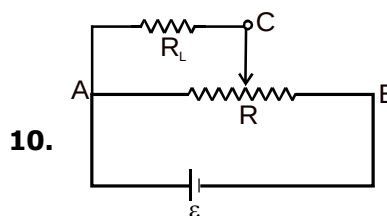
9. Potential gradient does not depend on area of cross section.





Output can be taken across the terminals A and C or B and C.

11. (A) $R_{PQ} = \frac{R \left(\frac{5R}{6} \right)}{R + \frac{5R}{6}} = \frac{5R}{11}$

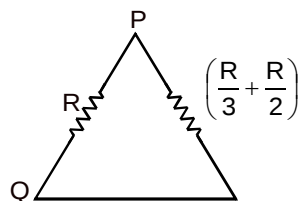
(B) $R_{QR} = \frac{\frac{4R}{3} \times \frac{R}{2}}{\frac{4R}{3} + \frac{R}{2}} = \frac{4R}{11}$


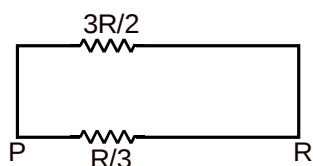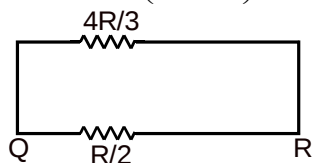
$$(C) R_{PR} = \frac{\left(\frac{3R}{2}\right)\left(\frac{R}{3}\right)}{\left(\frac{3R}{2} + \frac{R}{3}\right)} = \frac{3R}{11} = \frac{3R}{11}$$



12. C

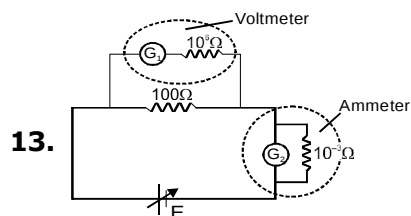

13.

14. Jayega to Ayega kahan se isliye zero hai.

$$15. i = 100 \times 10^{-6} \left(1 + \frac{100}{0.1}\right) \left\{ i = i_g \left(1 + \frac{r_g}{R}\right) \right\} = 100.1$$

mA

16. Error Ka sawal hai.

[JEE 2005]

$$x \cdot \ell_1 = R \times \ell_2$$

$$R = \frac{x\ell_1}{\ell_2} \Rightarrow x = \frac{R\ell_2}{\ell_1}$$

$$dx = \frac{R \cdot d\ell_2}{\ell_1} - \frac{R \cdot d\ell_1 \cdot \ell_2}{\ell_1^2}$$


For error

$$\frac{dx}{x} = \frac{d\ell_2}{\ell_2} + \frac{d\ell_1}{\ell_1}$$



minimum for $\ell_1 = \ell_2$

$$17. R = \frac{\rho \ell}{A}$$
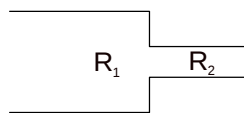
$$R_1 = \frac{\rho \ell}{2\pi(2r)^2} \quad R_2 = \frac{\rho \ell}{2\pi r^2} = \frac{R_2}{4}$$



18.

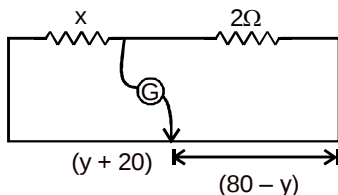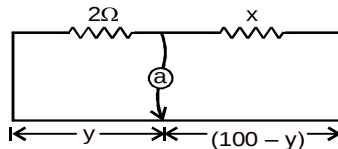

$$x > 2\Omega$$

$$2(100 - y) = xy \quad \dots(1)$$

$$x(80 - y) = 2(y + 20) \quad \dots(2)$$

19.

For R_1
Wheat stone Bridge

$$R_1 = 1\Omega$$


$$\text{for } R_2 = 0.5\Omega$$

$$\text{for } R_3 = 2\Omega$$

$$\text{Power } P = \frac{V^2}{R}$$

$$P_2 > P_1 > P_3$$

20.

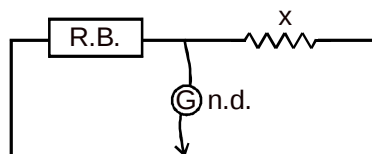If $x \uparrow$ & null deflection remains same R.B. should increase.

$$21. R_{\text{total}} = 2 + \frac{6 \times 1.5}{6 + 1.5} = 3.2 \text{ k}\Omega$$

$$(A) I = \frac{24V}{3.2k\Omega} = 7.5 \text{ mA} = I_{R_1}$$

$$I_{R_2} = \frac{R_L}{R_L + R_2} I = 1.5 \text{ mA}$$

$$I_{R_L} = 6 \text{ mA}$$

$$(B) V_{R_L} = (I_{R_L})(R_L) = 9V$$

$$(C) \frac{P_{R_1}}{P_{R_2}} = \frac{I_{R_1}^2 R_1}{I_{R_2}^2 R_2} = \frac{25}{3}$$

$$(D) \text{ When } R_1 \text{ \& } R_2 \text{ are interchanged } \frac{R_2 R_L}{R_2 + R_L} = \frac{6}{7} \text{ k}\Omega$$

Earlier it was 9V

$$P \propto V^2$$

Since Pot. difference decreases three times therefore, power dissipated will decrease 9 times.





22. $R = \frac{\rho L}{A}$

$$R = \frac{\rho L}{Lt}$$


$$R = \frac{\rho}{t}$$

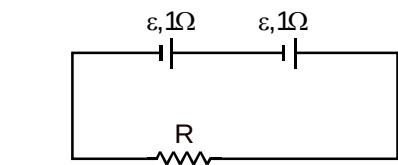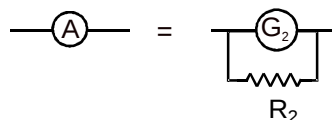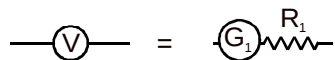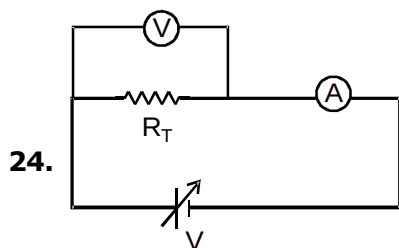23. $P = \frac{V^2}{R}$ & $100\text{ W} > 60\text{ W} > 40\text{ W}$

$$\frac{V^2}{R_{100}} > \frac{V^2}{R_{60}} > \frac{V^2}{R_{40}} \Rightarrow \frac{1}{R_{100}} > \frac{1}{R_{60}} > \frac{1}{R_{40}}$$


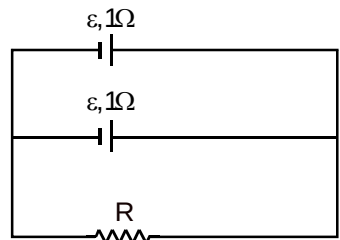
$$I_1 = \left(\frac{2\varepsilon}{R+2} \right)^2 R$$




$$I_2 = \left(\frac{\varepsilon}{R+1/2} \right)^2 R \Rightarrow \frac{I_1}{I_2} = 2.25 \Rightarrow R = 4\Omega$$

26. B


$$\ell = 52 + 1 = 53$$

$$\ell' = 48 + 2 = 50$$

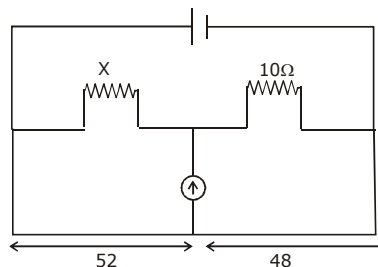

$$\frac{x}{10} + \frac{\ell}{\ell'} \Rightarrow x = \frac{530}{50} = 10.6\text{ ohm}$$


27.

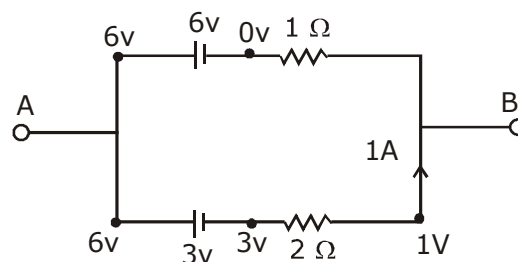

$$V_{AB} = 5\text{ V}$$

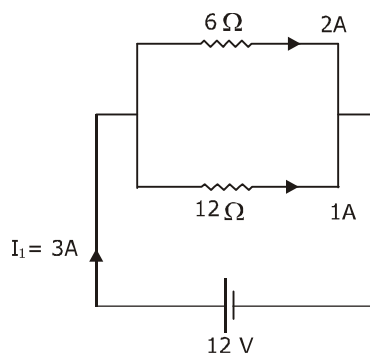28.

By symmetry the 1Ω resistances don't get any current so circuit reduces to



$$I_1 = \frac{12}{\frac{6 \times 12}{6 + 12}} = 3\text{ A}$$