

## Exercise - I

## (Objective Problems)

1. A wire of cross-section area  $A$ , length  $L_1$ , resistivity  $\rho_1$  and temperature coefficient of resistivity  $\alpha_1$  is connected to a second wire of length  $L_2$ , resistivity  $\rho_2$ , temperature coefficient of resistivity  $\alpha_2$  and the same area  $A$ , so that wire carries same current. Total resistance  $R$  is independent of temperature for small temperature change if (Thermal expansion effect is negligible)


- (A)  $\alpha_1 = -\alpha_2$  (B)  $\rho_1 L_1 \alpha_1 + \rho_2 L_2 \alpha_2 = 0$   
 (C)  $L_1 \alpha_1 + L_2 \alpha_2 = 0$  (D) None

2. In order to increase the resistance of a given wire of uniform cross section to four times its value, a fraction of its length is stretched uniformly till the full

length of the wire becomes  $\frac{3}{2}$  times the original length what is the value of this fraction ?

- (A)  $\frac{1}{4}$  (B)  $\frac{1}{8}$   
 (C)  $\frac{1}{16}$  (D)  $\frac{1}{6}$

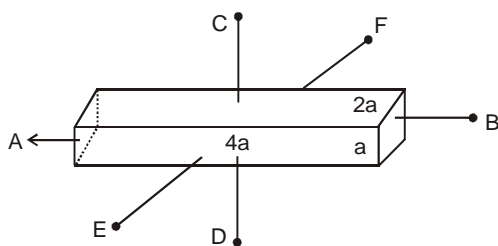3. A conductor with rectangular cross section has dimensions ( $a \times 2a \times 4a$ ) as shown in figure. Resistance across AB is  $x$ , across CD is  $y$  and across EF is  $z$ . Then



- (A)  $x = y = z$  (B)  $x > y > z$   
 (C)  $y > z > x$  (D)  $x > z > y$

4. A brass disc and a carbon disc of same radius are assembled alternatively to make a cylindrical conductor. The resistance of the cylinder is independent of the temperature. The ratio of thickness of the brass disc to that of the carbon disc is  $[\alpha$  is temperature coefficient of resistance & Neglect linear expansion]

- (A)  $\left| \frac{\alpha_C \rho_C}{\alpha_B \rho_B} \right|$  (B)  $\left| \frac{\alpha_C \rho_B}{\alpha_B \rho_C} \right|$   
 (C)  $\left| \frac{\alpha_B \rho_C}{\alpha_C \rho_B} \right|$  (D)  $\left| \frac{\alpha_B \rho_B}{\alpha_C \rho_C} \right|$

5. A current of  $(2.5 \pm 0.05)$  A flows through a wire and develops a potential difference of  $(10 \pm 0.1)$  volt. Resistance of the wire in ohm, is

- (A)  $4 \pm 0.12$  (B)  $4 \pm 0.04$   
 (C)  $4 \pm 0.08$  (D)  $4 \pm 0.02$

6. Two wires each of radius of cross section  $r$  but of different materials are connected together end to end (in series). If the densities of charge carriers in the two wires are in the ratio 1 : 4, the drift velocity of electrons in the two wires will be in the ratio.

- (A) 1 : 2 (B) 2 : 1  
 (C) 4 : 1 (D) 1 : 4

7. In a wire of cross-section radius  $r$ , free electrons travel with drift velocity  $v$  when a current  $I$  flows through the wire. What is the current in another wire of half the radius and of the same material when the drift velocity is  $2v$  ?

- (A)  $2I$  (B)  $I$   
 (C)  $I/2$  (D)  $I/4$

8. Read the following statements carefully :

Y : The resistivity of a semiconductor decreases with increases of temperature.

Z : In a conducting solid, the rate of collision between free electrons and ions increases with increase of temperature.

Select the correct statement from the following

- (A) Y is true but Z is false  
 (B) Y is false but Z is true  
 (C) Both Y and Z are true  
 (D) Y is true and Z is the correct reason for Y

9. A piece of copper and another of germanium are cooled from room temperature to 80K. The resistance of

- (A) each of them increases  
 (B) each of them decreases  
 (C) copper increases and germanium decreases  
 (D) copper decreases and germanium increases

10. An insulating pipe of cross-section area 'A' contains an electrolyte which has two types of ions  $\rightarrow$  their charges being  $-e$  and  $+2e$ . A potential difference applied between the ends of the pipe result in the drifting of the two types of ions, having drift speed =  $v$  ( $-ve$  ion) and  $v/4$  ( $+ve$  ion). Both ions have the same number per unit volume =  $n$ . The current flowing through the pipe is

- (A)  $nev A/2$  (B)  $nev A/4$   
 (C)  $5nev A/2$  (D)  $3nev A/2$

11. Current density in a cylindrical wire of radius  $R$  is

$$\text{given as } J = \begin{cases} J_0 \left( \frac{x}{R} - 1 \right) & \text{for } 0 \leq x < \frac{R}{2} \\ J_0 \frac{x}{R} & \text{for } \frac{R}{2} \leq x \leq R \end{cases} \text{ . The current}$$


flowing in the wire is

- (A)  $\frac{7}{24} \pi J_0 R^2$  (B)  $\frac{1}{6} \pi J_0 R^2$   
 (C)  $\frac{7}{12} \pi J_0 R^2$  (D)  $\frac{5}{12} \pi J_0 R^2$

**12.** A current  $I$  flows through a uniform wire of diameter  $d$  when the mean electron drift velocity is  $V$ . the same current will flow through a wire of diameter  $d/2$  made of the same material if the mean drift velocity of the electron is

- (A)  $v/4$  (B)  $v/2$   
 (C)  $2v$  (D)  $4v$

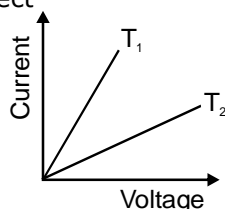**13.** The current in a metallic conductor is plotted against voltage at two different temperatures  $T_1$  and  $T_2$ . Which is correct



- (A)  $T_1 > T_2$  (B)  $T_1 < T_2$   
 (C)  $T_1 = T_2$  (D) none


**14.** A uniform copper wire carries a current  $i$  amperes and has  $p$  carriers per metre<sup>3</sup>. The length of the wire is  $\ell$  metres and its cross-section area is  $s$  metre<sup>2</sup>. If the charge on a carrier is  $q$  coulombs, the drift velocity in  $\text{ms}^{-1}$  is given by

- (A)  $i/\ell sq$  (B)  $i/psq$   
 (C)  $psq/i$  (D)  $i/ps \ell q$

**15.** In the presence of an applied electric field ( $\vec{E}$ ) in a metallic conductor.


- (A) The electrons move in the direction of  $\vec{E}$   
 (B) The electrons move in a direction opposite to  $\vec{E}$   
 (C) The electrons may move in any direction randomly, but slowly drift in the direction of  $\vec{E}$   
 (D) The electrons move randomly but slowly drift in a direction opposite to  $\vec{E}$

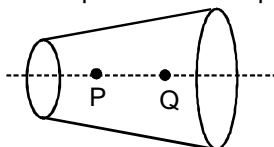**16.** A wire has a non-uniform cross-section as shown in figure. A steady current flows through it. The drift speed of electrons at points P and q is  $v_p$  and  $v_q$ .



- (A)  $v_p = v_q$  (B)  $v_p < v_q$   
 (C)  $v_p > v_q$  (D) Data insufficient

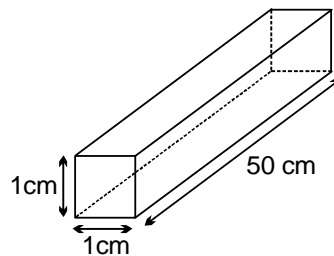**17.** A rectangular carbon block has dimensions  $1.0 \text{ cm} \times 1.0 \text{ cm} \times 50 \text{ cm}$ . Resistances are measured, first across two square ends and then across two rectangular ends, respectively. If resistivity of carbon is  $3.5 \times 10^{-5} \Omega\text{-m}$ , then values of measured resistances respectively are :



- (A)  $\frac{35}{2} \times 10^{-2} \Omega, 7 \times 10^{-5} \Omega$   
 (B)  $7 \times 10^{-5} \Omega, \frac{15}{2} \times 10^{-2} \Omega$   
 (C)  $\frac{35}{2} \times 10^{-4} \Omega, 7 \times 10^{-7} \Omega$   
 (D)  $\frac{15}{2} \Omega, 7 \times 10^{-2} \Omega$

**18.** A storage battery is connected to a charger for charging with a voltage of 12.5 Volts. The internal resistance of the storage battery is  $1 \Omega$ . When the charging current is 0.5 A, the emf of the storage battery is :

- (A) 13 Volts (B) 12.5 Volts  
 (C) 12 Volts (D) 11.5 Volts

**19.** The terminal voltage across a battery of emf  $E$  can be

- (A) 0 (B)  $> E$   
 (C)  $< E$  (D) all of above

**20.** In order to determine the e.m.f of a storage battery it was connected in series with a standard cell in a certain circuit and a current  $I_1$  was obtained. When the battery is connected to the same circuit opposite to the standard cell a current  $I_2$  flow in the external circuit from the positive pole of the storage battery was obtained. What is the e.m.f  $\epsilon_1$  of the storage battery? The e.m.f of the standard cell is  $\epsilon_2$ .


- (A)  $\epsilon_1 = \frac{l_1 + l_2}{l_1 - l_2} \epsilon_2$  (B)  $\epsilon_1 = \frac{l_1 + l_2}{l_2 - l_1} \epsilon_2$   
 (C)  $\epsilon_1 = \frac{l_1 - l_2}{l_1 + l_2} \epsilon_2$  (D)  $\epsilon_1 = \frac{l_2 - l_1}{l_1 + l_2} \epsilon_2$

**21.** One end of a Nichrome wire of length  $2L$  and cross-sectional area  $A$  is attached to an end of another Nichrome wire of length  $L$  and cross-sectional area  $2A$ . If the free end of the longer wire is at an

electric potential of 8.0 volts, and the free end of the shorter wire is at an electric potential of 1.0 volt, the potential at the junction of the two wires is equal to

- (A) 2.4 V (B) 3.2 V  
(C) 4.5 V (D) 5.6 V

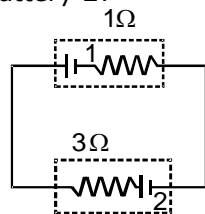
**22.** In the figure shown, battery 1 has emf = 6V and internal resistance =  $1\Omega$ . Battery 2 has emf = 2V and internal resistance =  $3\Omega$ . The wires have negligible resistance. What is the potential difference across the terminals of battery 2?




- (A) 4V  
(C) 5 V

- (B) 1.5V  
(D) 0.5V


**23.**

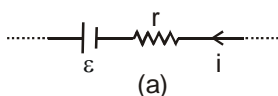


(a)

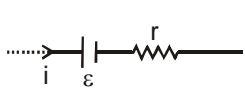

(b)

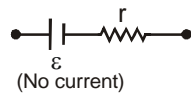

(c)

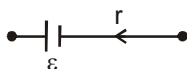


(d)

In which of the above cells, the potential difference between the terminals of a cell exceeds its emf.

- (A) a (B) b  
(C) c (D) d

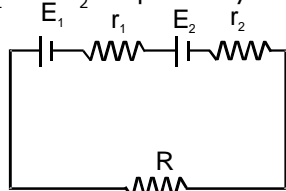
**24.** Under what condition current passing through the resistance  $R$  can be increased by short circuiting the battery of emf  $E_2$ . The internal resistances of the two batteries are  $r_1$  and  $r_2$  respectively.



- (A)  $E_2 r_1 > E_1 (R + r_2)$  (B)  $E_1 r_2 > E_2 (R + r_1)$   
(C)  $E_2 r_2 > E_1 (R + r_2)$  (D)  $E_1 r_1 > E_2 (R + r_1)$

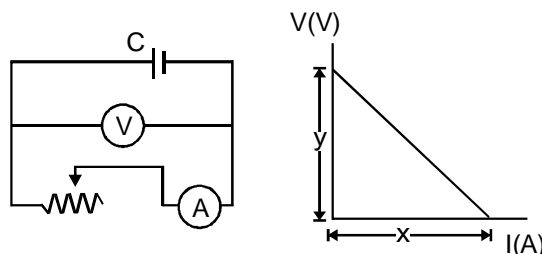
**25.** The diagram besides shows a circuit used in an experiment to determine the emf and internal resistance of the cell C. A graph was plotted of the potential difference  $V$  between the terminals of the cell against the current  $I$ , which was varied by adjusting the rheostat. The graph is shown on the right;  $x$  and  $y$  are the intercepts of the graph with the axes as

shown. What is the internal resistance of the cell ?




- (A)  $x$  (B)  $y$   
(C)  $x/y$  (D)  $y/x$

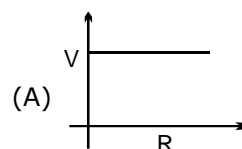
**26.** A cell of emf  $E$  has an internal resistance  $r$  & is connected to rheostat. When resistance  $R$  of rheostat is changed correct graph of potential difference across it is




(A)

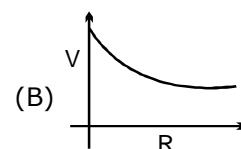

(B)

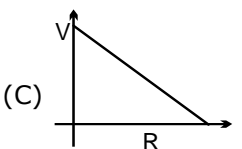


(C)

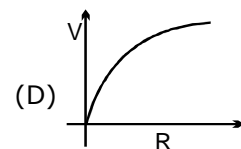


(D)

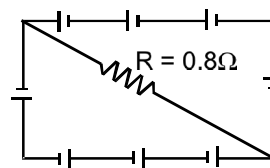**27.** A circuit is comprised of eight identical batteries and a resistor  $R = 0.8\Omega$ . Each battery has an emf of 1.0 V and internal resistance of  $0.2\Omega$ . The voltage difference across any of the battery is




- (A) 0.5 V (B) 1.0 V  
(C) 0 V (D) 2 V

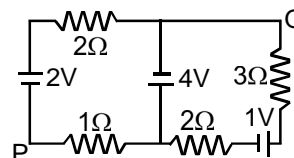**28.** In the circuit shown, what is the potential difference  $V_{PQ}$  ?




- (A) + 3V (B) + 2V  
(C) - 2V (D) none

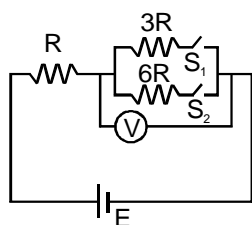**29.** In the circuit shown in figure reading of voltmeter is  $V_1$  when only  $S_1$  is closed, reading of voltmeter is  $V_2$  when only  $S_2$  is closed. The reading of voltmeter is  $V_3$  when both  $S_1$  and  $S_2$  are closed then



- (A)  $V_2 > V_1 > V_3$  (B)  $V_3 > V_2 > V_1$   
 (C)  $V_3 > V_1 > V_2$  (D)  $V_1 > V_2 > V_3$

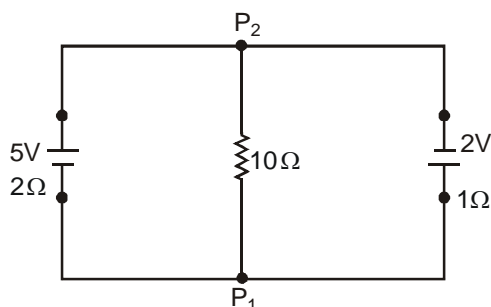**30.** A 5 V battery with internal resistance  $2\ \Omega$  and a 2V battery with internal resistance  $1\ \Omega$  are connected to a  $10\ \Omega$  resistor as shown in the figure.




The current in the  $10\ \Omega$  resistor is :

- (A) 0.03 A  $P_1$  to  $P_2$  (B) 0.03 A  $P_2$  to  $P_1$   
 (C) 0.27 A  $P_1$  to  $P_2$  (D) 0.27 A  $P_2$  to  $P_1$

**31.** The Kirchhoff's first law ( $\sum i = 0$ ) and second law ( $\sum iR = 0 = \sum E$ ), where the symbols have their usual meanings, are respectively based on


- (A) conservation of charge, conservation of energy  
 (B) conservation of charge, conservation of momentum  
 (C) conservation of energy, conservation of charge  
 (D) conservation of momentum, conservation of charge

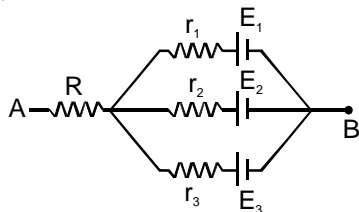**32.** In the network shown the potential difference between A and B is ( $R = r_1 = r_2 = r_3 = 1\ \Omega$ ,  $E_1 = 3\text{ V}$ ,  $E_2 = 2\text{ V}$ ,  $E_3 = 1\text{ V}$ )




- (A) 1 V (B) 2 V  
 (C) 3 V (D) 4 V

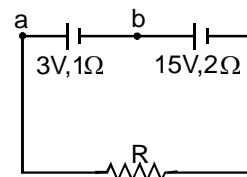**33.** Two batteries one of the emf 3V, internal resistance  $1\ \Omega$  and the other of emf 15 V, internal resistance  $2\ \Omega$  are connected in series with a resistance R as shown. If the potential difference between a and b is zero the resistance of R in ohm is




- (A) 5 (B) 7  
 (C) 3 (D) 1

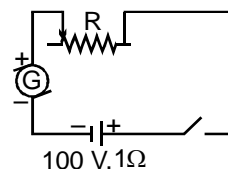**34.** The battery in the diagram is to be charged by the generator G. The generator has a terminal voltage of 120 volts when the charging current is 10 amperes. The battery has an emf of 100 volts and an internal resistance of  $1\ \Omega$ . In order to charge the battery at 10 amperes charging current, the resistance R should be set at




- (A) 0.1  $\Omega$  (B) 0.5  $\Omega$   
 (C) 1.0  $\Omega$  (D) 5.0  $\Omega$

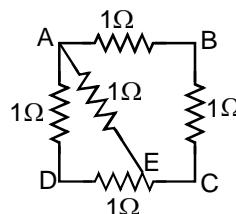**35.** ABCD is a square where each side is a uniform wire of resistance  $1\ \Omega$ . A point E lies on CD such that if a uniform wire of resistance  $1\ \Omega$  is connected across AE and constant potential difference is applied across A and C then B and E are equipotential.




- (A)  $\frac{CE}{ED} = 1$  (B)  $\frac{CE}{ED} = 2$   
 (C)  $\frac{CE}{ED} = \frac{1}{\sqrt{2}}$  (D)  $\frac{CE}{ED} = \sqrt{2}$

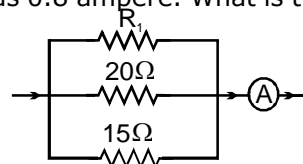**36.** In the given circuit the current flowing through the resistance  $20\ \Omega$  is 0.3 ampere while the ammeter reads 0.8 ampere. What is the value of  $R_1$ ?





- (A) 30 ohms (B) 40 ohms  
 (C) 50 ohms (D) 60 ohms

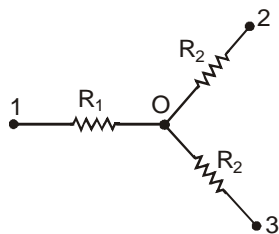**37.** Find the current flowing through the resistance  $R_1$  of the circuit shown in figure if the resistance are equal to  $R_1 = 10\ \Omega$ ,  $R_2 = 20\ \Omega$ , and  $R_3 = 30\ \Omega$ , and the potential of points 1, 2 and 3 are equal to  $\phi_1 = 10\text{V}$ ,  $\phi_2 = 6\text{V}$  and  $\phi_3 = 5\text{V}$ .








- (A) 0.1 A (B) 0.2 A  
(C) 0.3 A (D) 0.4 A

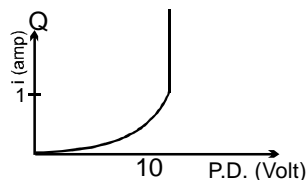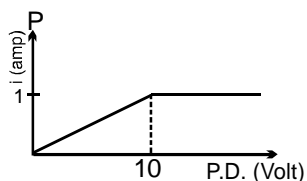
**38.** Two current elements P and Q have current voltage characteristics as shown below :



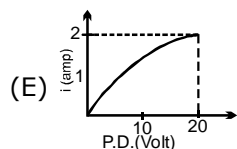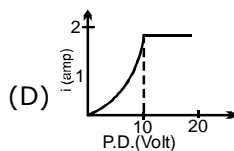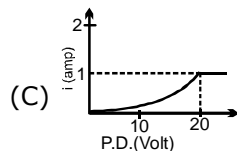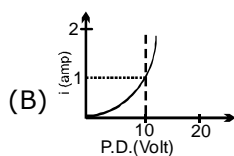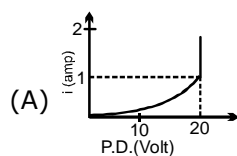Which of the graphs given below represents current voltage characteristics when P and Q are in series.



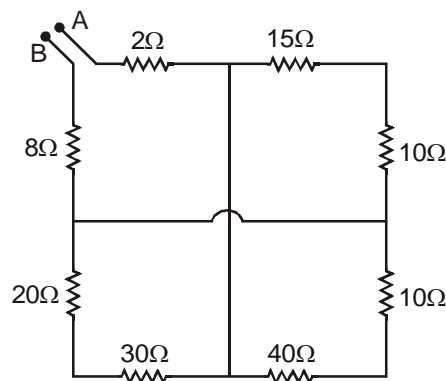**39.** The equivalent resistance between points A and B is :




- (A)  $\frac{65}{2}\ \Omega$  (B)  $\frac{45}{2}\ \Omega$   
(C)  $\frac{5}{2}\ \Omega$  (D)  $\frac{91}{2}\ \Omega$

**40.** The resistance of the series combination of two resistances is S. When they are joined in a parallel, the total resistance is P. If  $S = nP$ , then the minimum possible value of n is :


- (A) 4 (B) 3  
(C) 2 (D) 1

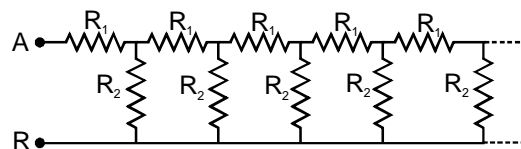**41.** Consider an infinite ladder network shown in figure. A voltage V is applied between the points A and B. This applied value of voltage is halved after each section.




- (A)  $R_1/R_2 = 1$  (B)  $R_1/R_2 = 1/2$   
(C)  $R_1/R_2 = 2$  (D)  $R_1/R_2 = 3$

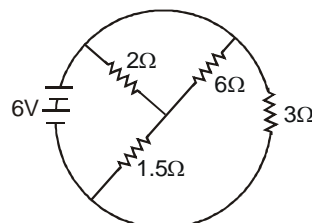**42.** The total current supplied to the circuit by the battery is :




- (A) 1 A (B) 2 A (C) 4 A (D) 6 A

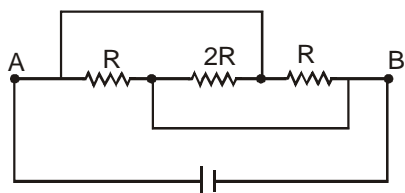43. In the figure shown the current flowing through 2 R is :



- (A) from left to right (B) from right to left  
(C) no current (D) None of these

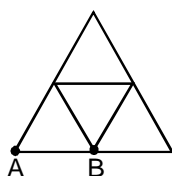44. In the diagram resistance between any two junctions is R. Equivalent resistance across terminals A and B is




- (A)  $\frac{11R}{7}$  (B)  $\frac{18R}{11}$   
(C)  $\frac{7R}{11}$  (D)  $\frac{11R}{18}$

45. In a balanced wheat stone bridge, current in the galvanometer is zero. It remains zero when

- (1) battery emf is increased  
(2) all resistances are increased by 10 ohms  
(3) all resistances are made five times  
(4) the battery and the galvanometer are interchanged  
(A) only (1) is correct  
(B) (1), (2) and (3) are correct  
(C) (1), (3) and (4) are correct  
(D) (1) and (3) are correct

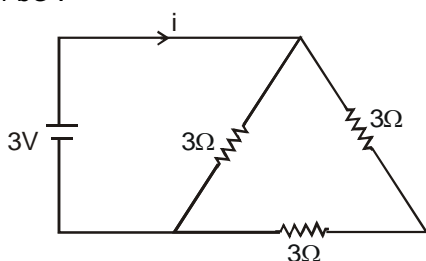
46. A 3 volt battery with negligible internal resistance is connected in a circuit as shown in the figure. Current i will be :



- (A)  $\frac{1}{3}$  A (B) 1 A  
(C) 1.5 A (D) 2 A

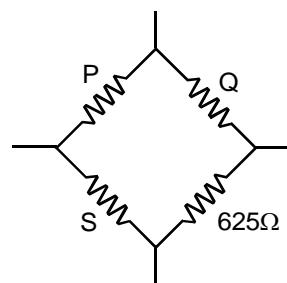
47. A Wheatstone's bridge is balanced with a resistance of  $625 \Omega$  in the third arm, where P, Q and S are in the 1<sup>st</sup>, 2<sup>nd</sup> and 4<sup>th</sup> arm respectively. If P and Q are interchanged, the resistance in the third arm has to

be increased by  $51 \Omega$  to secure balance. The unknown resistance in the fourth arm is



- (A)  $625 \Omega$  (B)  $650 \Omega$   
(C)  $676 \Omega$  (D)  $600 \Omega$

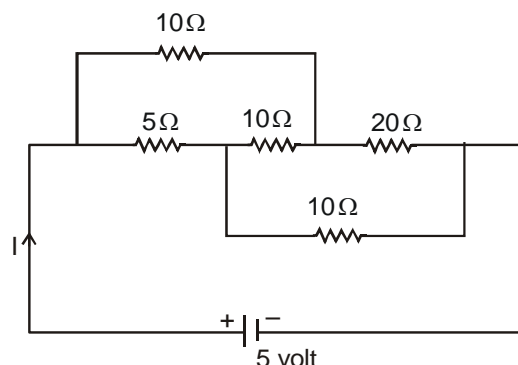48. The current I drawn from the 5 volt source will be :




- (A) 0.67 A (B) 0.17 A  
(C) 0.33 A (D) 0.5 A

49. In a Wheat stone's bridge, three resistances P, Q and R are connected in the three arms and the fourth arm is foremd by two resistances  $S_1$  and  $S_2$  connected in parallel. The condition for the bridge to be balanced will be


- (A)  $\frac{P}{Q} = \frac{R(S_1 + S_2)}{2S_1S_2}$  (B)  $\frac{P}{Q} = \frac{R}{S_1 + S_2}$   
(C)  $\frac{P}{Q} = \frac{2R}{S_1 + S_2}$  (D)  $\frac{P}{Q} = \frac{R(S_1 + S_2)}{S_1S_2}$

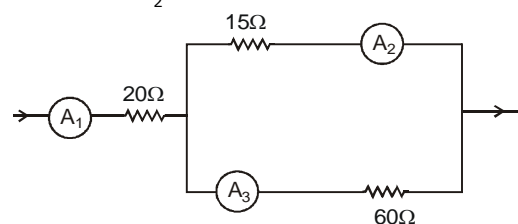50. If the reading of ammeter  $A_3$  in figure is 0.75 A. Neglecting the resistance of the ammeters, the reading of ammeter  $A_2$  will be :



- (A) 1.5 A (B) 3 A  
(C) 4.5 A (D) 6 A

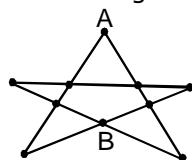
**51.** The resistance of all the wires between any two adjacent dots is  $R$ . Then equivalent resistance between A and B as shown in figure is :



- (A)  $\frac{7}{3}R$  (B)  $\frac{7}{6}R$   
(C)  $\frac{14}{8}R$  (D) None of these

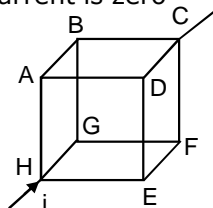**52.** In the box shown current  $i$  enters at H and leaves at C.

If  $i_{AB} = \frac{i}{6}$ ,  $i_{DC} = \frac{2i}{3}$ ,  $i_{HA} = \frac{i}{2}$ ,  $i_{GF} = \frac{i}{6}$ ,  $i_{HE} = \frac{i}{6}$ , choose the branch in which current is zero



- (A) BG (B) FC (C) ED (D) none

**53.** A resistor of resistance  $R$  is connected to a cell of internal resistance  $5\Omega$ . The value of  $R$  is varied from  $1\Omega$  to  $5\Omega$ . The power consumed by  $R$  :

- (A) increases continuously  
(B) decreases continuously  
(C) first decreases then increases  
(D) first increases then decreases.

**54.** Power generated across a uniform wire connected across a supply is  $H$ . If the wire is cut into  $n$  equal parts and all the parts are connected in parallel across the same supply, the total power generated in the wire is

- (A)  $\frac{H}{n^2}$  (B)  $n^2H$   
(C)  $nH$  (D)  $\frac{H}{n}$

**55.** A constant voltage is applied between the two ends of a uniform metallic wire. Some heat is developed in it. The heat developed is doubled if

- (A) both the length and the radius of the wire are halved  
(B) both the length and the radius of the wire are doubled  
(C) the radius of the wire is doubled  
(D) the length of the wire is doubled

**56.** When electric bulbs of same power, but different marked voltage are connected in series across the power line, their brightness will be

- (A) proportional to their marked voltage  
(B) inversely proportional to their marked voltage  
(C) proportional to the square of their marked voltage  
(D) inversely proportional to the square of their marked voltage  
(E) the same for all of them

**57.** A wire when connected to 220 V mains supply has power dissipation  $P_1$ . Now the wire is cut into two equal pieces which are connected in parallel to the same supply. Power dissipation in this case is  $P_2$ . Then  $P_2 : P_1$  is :

- (A) 1 (B) 4 (C) 2 (D) 3

**58.** Two bulbs rated (25 W – 220 V) and (100 W – 220 V) are connected in series to a 440 V line. Which one is likely to fuse ?

- (A) 25 W bulb (B) 100 W bulb  
(C) both bulbs (D) none

**59.** Rate of dissipation of Joule's heat in resistance per unit volume is (symbols have usual meaning)

- (A)  $\sigma E$  (B)  $\sigma J$  (C)  $JE$  (D) None

**60.** The charge flowing through a resistance  $R$  varies with time as  $Q = 2t - 8t^2$ . The total heat produced in

the resistance is (for  $0 \leq t \leq \frac{1}{8}$ )

- (A)  $\frac{R}{6}$  joules (B)  $\frac{R}{3}$  joules  
(C)  $\frac{R}{2}$  joules (D)  $R$  joules

**61.** If the length of the filament of a heater is reduced by 10%, the power of the heater will

- (A) increase by about 9%  
(B) increase by about 11%  
(C) increase by about 19%  
(D) decrease by about 10%

**62.** A heater A gives out 300 W of heat when connected to a 200 V d.c. supply. A second heater B gives out 600 W when connected to a 200 V d.c. supply. If a series combination of the two heaters is connected to a 200 V d.c. supply the heat output will be

- (A) 100 W (B) 450 W  
(C) 300 W (D) 200 W


**63.** Two bulbs one of 200 volts, 60 watts & the other of 200 volts, 100 watts are connected in series to a 200 volt supply. The power consumed will be

- (A) 37.5 watt (B) 160 watt  
(C) 62.5 watt (D) 110 watt

**64.** Three 60 W light bulbs are mistakenly wired in series and connected to a 120 V power supply. Assume the light bulbs are rated for single connection to 120 V. With the mistaken connection, the power dissipated by each bulb is


- (A) 6.7 W (B) 13.3 W  
(C) 20 W (D) 40 W

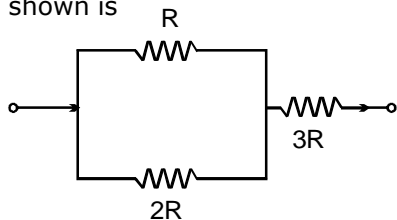65. The ratio of powers dissipated respectively in R and  $3R$ , as shown is




- (A) 9  
(C)  $4/9$   
(B)  $27/4$   
(D)  $4/27$

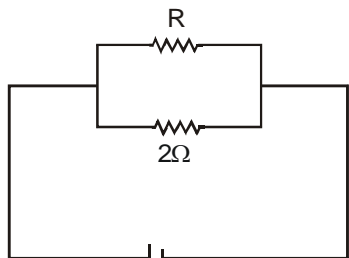66. If in the circuit, power dissipation is 150 W then R is



- (A)  $2\ \Omega$   
(C)  $5\ \Omega$   
(B)  $6\ \Omega$   
(D)  $4\ \Omega$

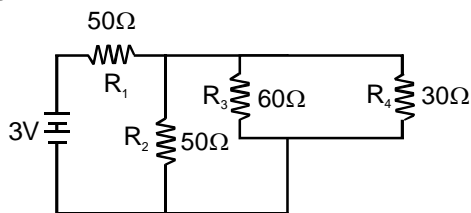67. In the circuit shown, the resistances are given in ohms and the battery is assumed ideal with emf equal to 3.0 volts. The resistor that dissipates the most power is








- (A)  $R_1$   
(C)  $R_3$   
(B)  $R_2$   
(D)  $R_4$


68. What amount of heat will be generated in a coil of resistance R due to a charge q passing through it if the current in the coil decreases to zero uniformly during a time interval  $\Delta t$

- (A)  $\frac{4}{3} \frac{q^2 R}{\Delta t}$   
(C)  $\frac{2q^2 R}{3\Delta t}$   
(B)  $\ln \frac{q^2 R}{2\Delta t}$   
(D)  $\ln \frac{(2\Delta t)}{q^2 R}$

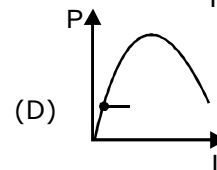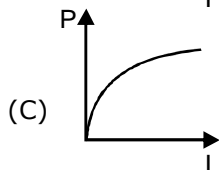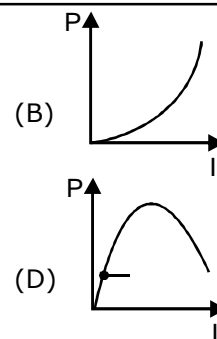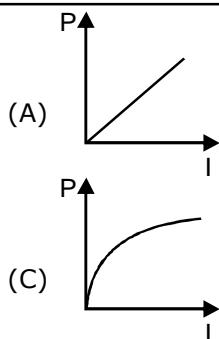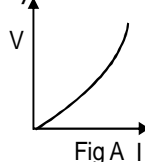69. The variation of current (I) and voltage (V) is as shown in figure A. The variation of power P with current I is best shown by which of the following graph







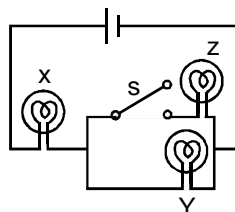
70. If X, Y and Z in figure are identical lamps, which of the following changes to the brightnesses of the lamps occur when switch S is closed?



- (A) X stays the same, Y decreases  
(B) X increases, Y decreases  
(C) X increases, Y stays the same  
(D) X decreases, Y increases

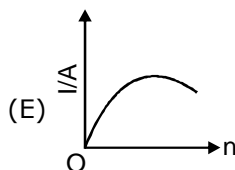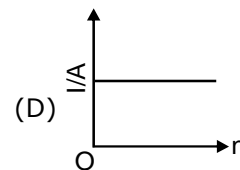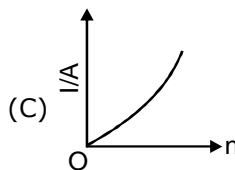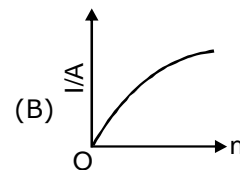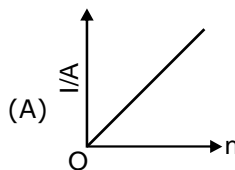
71. A battery consists of a variable number n of identical cells having internal resistance connected in series. The terminals of the battery are short circuited and the current I measured.

Which one of the graph below shows the relationship between I and n?



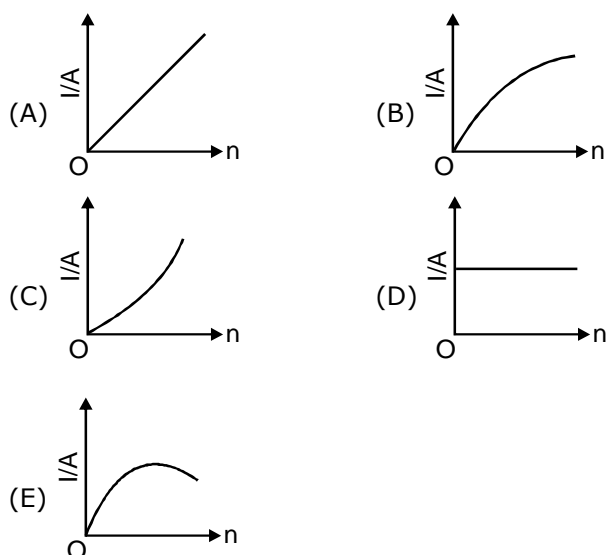72. In previous problem, if the cell had been connected in parallel (instead of in series) which of the above graphs would have shown the relationship between total current I and n?






**73.**  $n$  identical cells are joined in series with its two cells A and B in the loop with reversed polarities. EMF of each shell is  $E$  and internal resistance  $r$ . Potential difference across cell A or B is (here  $n > 4$ )

- (A)  $\frac{2E}{n}$  (B)  $2E\left(1 - \frac{1}{n}\right)$   
 (C)  $\frac{4E}{n}$  (D)  $2E\left(1 - \frac{2}{n}\right)$

**74.** A wire of length  $L$  and 3 identical cells of negligible internal resistances are connected in series. Due to the current, the temperature of the wire is raised by  $\Delta T$  in time  $t$ .  $N$  number of similar cells is now connected in series with a wire of the same material and cross section but of length  $2L$ . The temperature of the wire is raised by the same amount  $\Delta T$  in the same time  $t$ . The value of  $N$  is :

- (A) 4 (B) 6 (C) 8 (D) 9

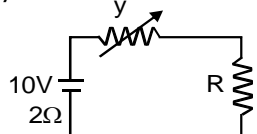**75.** In the figure shown the power generated in  $y$  is maximum when  $y = 5\Omega$ . Then  $R$  is




- (A)  $2\Omega$  (B)  $6\Omega$   
 (C)  $5\Omega$  (D)  $3\Omega$

**76.** If an ammeter is to be used in place of a voltmeter then we must connect with the ammeter a


- (A) Low resistance in parallel  
 (B) High resistance in parallel  
 (C) High resistance in series  
 (D) Low resistance in series

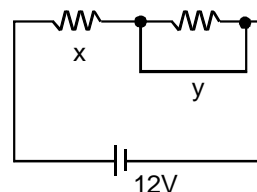**77.** When an ammeter of negligible internal resistance is inserted in series with circuit it reads 1A. When the voltmeter of very large resistance is connected across X it reads 1V. When the point A and B are shorted by a conducting wire, the voltmeter measures 10 V across the battery. The internal resistance of the battery is equal to




- (A) zero (B)  $0.5\Omega$   
 (C)  $0.2\Omega$  (D)  $0.1\Omega$

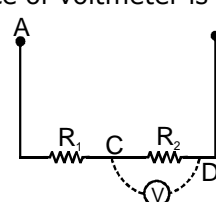**78.** Resistances  $R_1$  and  $R_2$  each  $60\Omega$  are connected in series as shown in figure. The Potential difference between A and B is kept 120 volt. Then what will be the reading of voltmeter connected between the point C & D if resistance of voltmeter is  $120\Omega$ .



- (A) 48 V (B) 24 V  
 (C) 40 V (D) None

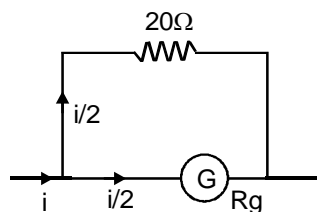**79.** In a galvanometer, the deflection becomes one half when the galvanometer is shunted by a  $20\Omega$  resistor. The galvanometer resistance is




- (A)  $5\Omega$  (B)  $10\Omega$   
 (C)  $40\Omega$  (D)  $20\Omega$

**80.** A galvanometer has a resistance of  $20\Omega$  and reads full-scale when 0.2 V is applied across it. To convert it into a 10 A ammeter, the galvanometer coil should have a

- (A)  $0.01\Omega$  resistor connected across it  
 (B)  $0.02\Omega$  resistor connected across it  
 (C)  $200\Omega$  resistor connected in series with it  
 (D)  $2000\Omega$  resistor connected in series with it

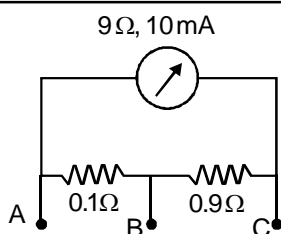**81.** A milliammeter of range 10mA and resistance  $9\Omega$  is joined in a circuit as shown. The metre gives full-scale deflection for current  $I$  when A and B are used as its terminals, i.e., current enters at A and leaves at B (C is left isolated). The value of  $I$  is




- (A) 100 mA (B) 900 mA  
(C) 1 A (D) 1.1 A

**82.** A galvanometer coil has a resistance  $90\Omega$  and full scale deflection current  $10\text{ mA}$ . A  $910\Omega$  resistance is connected in series with the galvanometer to make a voltmeter. If the least count of the voltmeter is  $0.1\text{ V}$ , the number of divisions on its scale is


- (A) 90 (B) 91  
(C) 100 (D) none

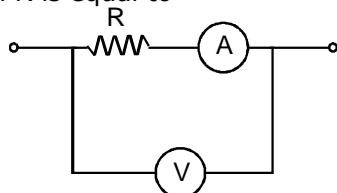**83.** In the circuit shown the resistance of voltmeter is  $10,000\text{ ohm}$  and that of ammeter is  $20\text{ ohm}$ . The ammeter reading is  $0.10\text{ Amp}$  and voltmeter reading is  $12\text{ volt}$ . Then  $R$  is equal to





- (A)  $122\Omega$  (B)  $140\Omega$  (C)  $116\Omega$  (D)  $100\Omega$

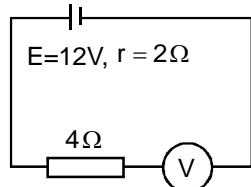**84.** By error, a student places moving-coil voltmeter  $V$  (nearly ideal) in series with the resistance in a circuit in order to read the current, as shown. The voltmeter reading will be




- (A) 0 (B) 4V (C) 6V (D) 12V

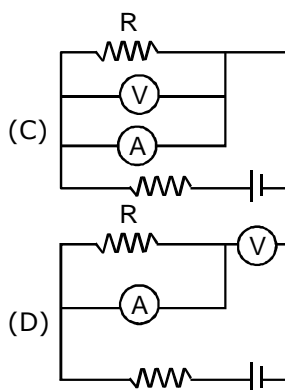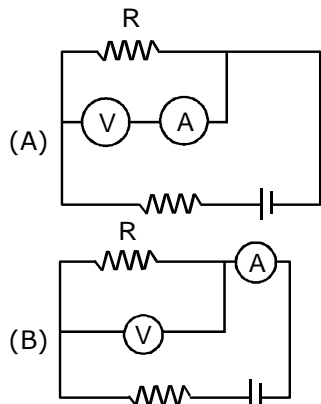**85.** Which of the following wiring diagrams could be used to experimentally determine  $R$  using ohm's law? Assume an ideal voltmeter and an ideal ammeter.



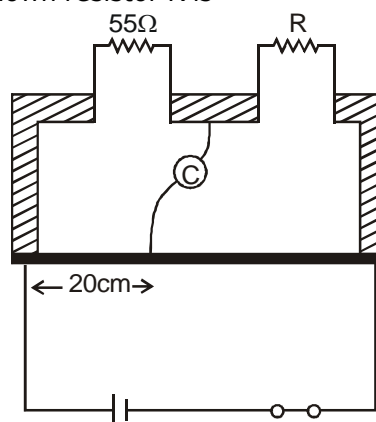**86.** Shown in the figure below is a meter-bridge set up with null deflection in the galvanometer. The value of the unknown resistor  $R$  is




- (A)  $220\Omega$  (B)  $110\Omega$   
(C)  $55\Omega$  (D)  $13.75\Omega$

**87.** In a metre bridge experiment, null point is obtained at  $20\text{ cm}$  from one end of the wire when resistance  $X$  is balanced against another resistance  $Y$ . If  $X < Y$ , then where will be the new position of the null point from the same end, if one decides to balance a resistance of  $4X$  against  $Y$ ?


- (A)  $50\text{ cm}$  (B)  $80\text{ cm}$   
(C)  $40\text{ cm}$  (D)  $70\text{ cm}$

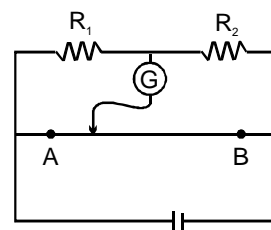**88.** In the figure shown for gives values of  $R_1$  and  $R_2$  the balance point for Jockey is at  $40\text{ cm}$  from  $A$ . When  $R_2$  is shunted by a resistance of  $10\Omega$ , balance shifts to  $50\text{ cm}$ .  $R_1$  and  $R_2$  are ( $AB = 1\text{ m}$ )




- (A)  $\frac{10}{3}\Omega, 5\Omega$  (B)  $20\Omega, 30\Omega$   
(C)  $10\Omega, 15\Omega$  (D)  $5\Omega, \frac{15}{2}\Omega$

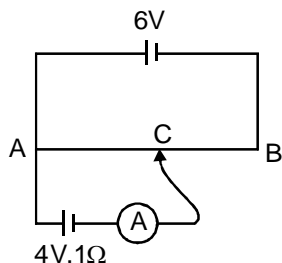**89.** A 6V battery of negligible internal resistance is connected across a uniform wire of length 1m. The positive terminal of another battery of emf 4V and internal resistance  $1\Omega$  is joined to the point A as shown in figure. The ammeter shows zero deflection when the jockey touches the wire at the point C. The AC is equal to



- (A)  $2/3$  m (B)  $1/3$  m  
(C)  $3/5$  m (D)  $1/2$  m

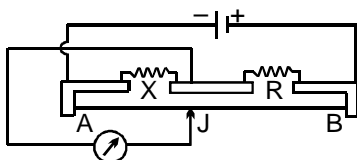**90.** The figure shows a metre- bridge circuit, with  $AB = 100$  cm,  $X = 12\Omega$  and  $R = 18\Omega$ , and the jockey J in the position of balance. If  $R$  is now made  $8\Omega$ , through what distance will J have to be moved to obtain balance ?



- (A) 10 cm (B) 20 cm  
(C) 30 cm (D) 40 cm

**91.** A potentiometer wire has length 10 m and resistance  $10\Omega$ . It is connected to a battery of EMF 11 volt and internal resistance  $1\Omega$ , then the potential gradient in the wire is


- (A) 10 V/m (B) 1 V/m  
(C) 0.1 V/m (D) none

**92.** The length of a potentiometer wire is  $l$ . A cell of emf  $E$  is balanced at a length  $l/3$  from the positive end of the wire. if the length of the wire is increased by  $l/2$ . At what distance will the same cell give a balance point.

- (A)  $\frac{2l}{3}$  (B)  $\frac{l}{2}$   
(C)  $\frac{l}{6}$  (D)  $\frac{4l}{3}$

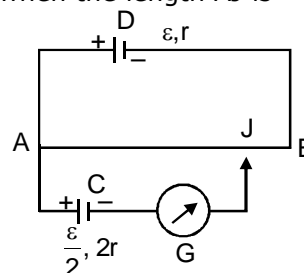
**93.** In the figure, the potentiometer wire AB of length  $L$  and resistance  $9r$  is joined to the cell D of emf  $\varepsilon$  and internal resistance  $r$ . The cell C's emf is  $\varepsilon/2$  and its

internal resistance is  $2r$ . The galvanometer G will show no deflection when the length AJ is




- (A)  $\frac{4L}{9}$  (B)  $\frac{5L}{9}$   
(C)  $\frac{7L}{18}$  (D)  $\frac{11L}{18}$

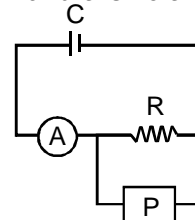**94.** An ammeter A of finite resistance, and a resistor R are joined in series to an ideal cell C. A potentiometer P is joined in parallel to R. The ammeter reading is  $I_0$  and the potentiometer reading is  $V_0$ . P is now replaced by a voltmeter of finite resistance. The ammeter reading now is  $I$  and the voltmeter reading is  $V$ .



- (A)  $I > I_0, V < V_0$  (B)  $I > I_0, V = V_0$   
(C)  $I = I_0, V < V_0$  (D)  $I < I_0, V = V_0$

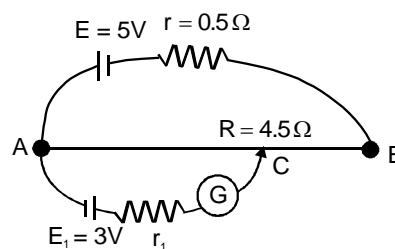
**95.** In the given potentiometer circuit length of the wire AB is 3m and resistance is  $R = 4.5\Omega$ . The length AC for no deflection in galvanometer is



- (A) 2 m (B) 1.8 m  
(C) dependent on  $r_1$  (D) none of these

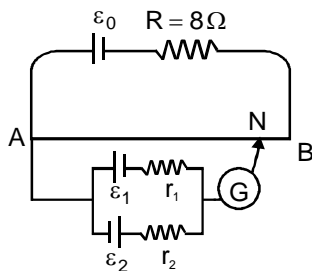
**96.** A battery of emf  $E_0 = 12$  V is connected across a 4m long uniform wire having resistance  $4\Omega/\text{m}$ . The cells of small emfs  $\varepsilon_1 = 2$  V and  $\varepsilon_2 = 4$  V having internal resistance  $2\Omega$  and  $6\Omega$  respectively, are connected as shown in the figure. If galvanometer shows no deflec-

tion at the point N, the distance of point N from the point A is equal to



- (A)  $\frac{1}{6}$  m (B)  $\frac{1}{3}$  m  
(C) 25 cm (D) 50 cm

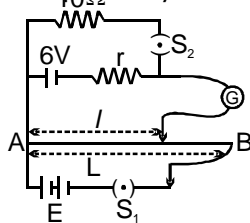97. In the arrangement shown in figure when the switch  $S_2$  is open, the galvanometer shows no deflection for  $l = L/2$ . When the switch  $S_2$  is closed, the galvanometer shows no deflection for  $l = 5L/12$ . The internal resistance ( $r$ ) of 6 V cell, and the emf  $E$  of the other battery are respectively.



- (A) 3Ω, 8V (B) 2Ω, 12V  
(C) 2Ω, 24V (D) 3Ω, 12V

98. Statement-1 : When two conducting wires of different resistivity having same cross section area are joined in series, the electric field in them would be equal when they carry current.

Statement-2 : When wires are in series they carry equal current.

- (A) STATEMENT-1 is True, STATEMENT-2 is True; STATEMENT-2 **is** a correct explanation for STATEMENT-1  
(B) STATEMENT-1 is True, STATEMENT-2 is True; STATEMENT-2 **is NOT** a correct explanation for STATEMENT-1  
(C) STATEMENT-1 is True, STATEMENT-2 is False  
(D) STATEMENT-1 is False, STATEMENT-2 is True

99. Statement-1 : Potential difference across the terminals of a battery is always less than its emf.

Statement-2 : A battery always has some internal resistance.

- (A) STATEMENT-1 is True, STATEMENT-2 is True;

STATEMENT-2 **is** a correct explanation for STATEMENT-1

(B) STATEMENT-1 is True, STATEMENT-2 is True; STATEMENT-2 **is NOT** a correct explanation for STATEMENT-1

(C) STATEMENT-1 is True, STATEMENT-2 is False

(D) STATEMENT-1 is False, STATEMENT-2 is True

100. Statement-1 : Knowing that rating is done at steady state of the filament, an electric bulb connected to a source having rated voltage consumes more than rated power just after it is switched on.

Statement-2 : When filament is at room temperature its resistance is less than its resistance when the bulb is fully illuminated

(A) STATEMENT-1 is True, STATEMENT-2 is True; STATEMENT-2 **is** a correct explanation for STATEMENT-1

(B) STATEMENT-1 is True, STATEMENT-2 is True; STATEMENT-2 **is NOT** a correct explanation for STATEMENT-1

(C) STATEMENT-1 is True, STATEMENT-2 is False

(D) STATEMENT-1 is False, STATEMENT-2 is True

101. Statement-1 : When a battery is supplying power to a circuit, work done by electrostatic forces on electrolyte ions inside the battery is positive  
Statement-2 : Electric field is directed from positive to negative electrode inside a battery

(A) STATEMENT-1 is True, STATEMENT-2 is True; STATEMENT-2 **is** a correct explanation for STATEMENT-1

(B) STATEMENT-1 is True, STATEMENT-2 is True; STATEMENT-2 **is NOT** a correct explanation for STATEMENT-1

(C) STATEMENT-1 is True, STATEMENT-2 is False

(D) STATEMENT-1 is False, STATEMENT-2 is True

102. Statement-1 : Conductivity of a metallic conductor decreases with increase in temperature.

Statement-2 : On increasing temperature the number of free electrons in the metallic conductor decreases.

(A) STATEMENT-1 is True, STATEMENT-2 is True; STATEMENT-2 **is** a correct explanation for STATEMENT-1

(B) STATEMENT-1 is True, STATEMENT-2 is True; STATEMENT-2 **is NOT** a correct explanation for STATEMENT-1

(C) STATEMENT-1 is True, STATEMENT-2 is False

(D) STATEMENT-1 is False, STATEMENT-2 is True